

COMP 160 Lab 2, Designing a Decoder

The goals of this lab are to do a little more Verilog design and to write a simple Verilog testbench.

You will design a Hex-to-Seven-Segment decoder. There is a good explanation of a similar decoder in your book, *Logic and Computer Design Fundamentals* 3rd edition, on page 107. The only difference between the decoder in your book and the one you are going to design is that you are not stopping at 9 as an output value, but rather at hexadecimal F. You will be able to use this decoder to debug circuits you design later. For more on simple Verilog and a decoder design, refer to page 184 in the book.

Connect the inputs of the decoder to the DIP switches.

Test by writing a Verilog test program (to try all possible inputs) and simulating. Then assign pins and download to the Xess board to make a final test/

Useful pinout information (from the XSA manual)

Seven-Segment Display

Top, s[6]	P49
Upper Left, s[5]	P57
Upper Right, s[4]	P46
Middle, s[3]	P60
Lower Left, s[2]	P62
Lower Right, s[1]	P39
Bottom, s[0]	P67

DIP switches (normally high)

1	P54
2	P64
3	P63
4	P56

Mail the instructor and TA copies of your decoder Verilog and of your test program.