

22 October


- 3 classes before 2nd exam!
- Control

10/22/2001

Comp 120 Fall 2001

1

Synchronous Systems

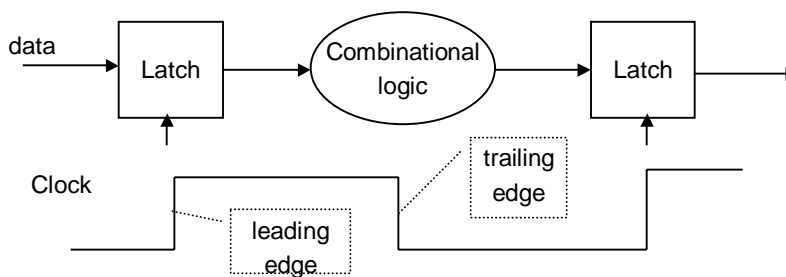

On the leading edge of the clock, the input of a latch is transferred to the output and held.


We must be sure the combinational logic has *settled* before the next leading clock edge.

10/22/2001

Comp 120 Fall 2001

2

Asynchronous Systems

 

No clock!
The data carries a "valid" signal along with it
System goes at greatest possible speed.
Only "computes" when necessary.


Everything we look at will be synchronous

10/22/2001

Comp 120 Fall 2001

3

Fetching Sequential Instructions

 


How about branch?

10/22/2001

Comp 120 Fall 2001

4

Datapath for R-type Instructions

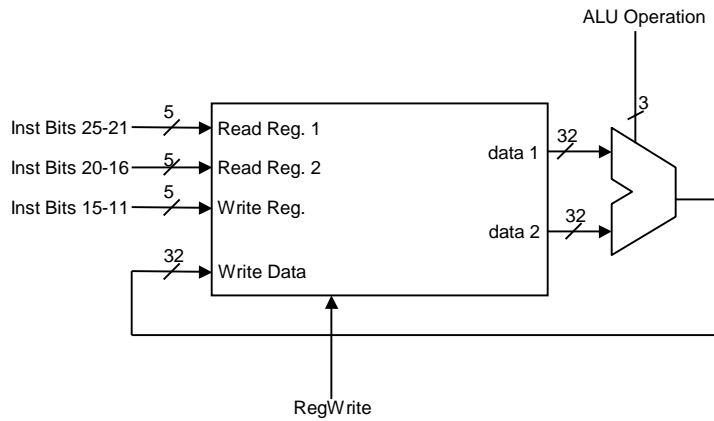


10/22/2001

Comp 120 Fall 2001

5

Fun with MUXes

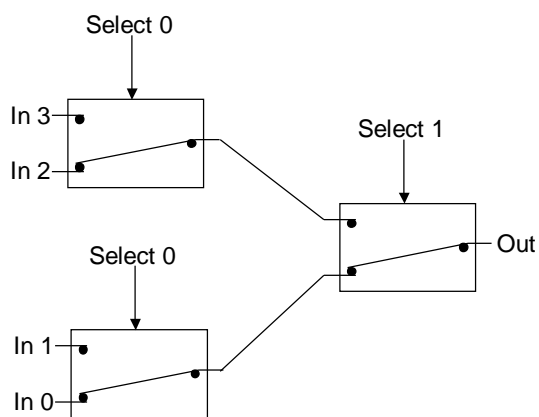

Remember the MUX?


This will route 1 of 4 different 1 bit values to the output.

10/22/2001

Comp 120 Fall 2001

6

MUX Blocks

 


The select signal determines which of the inputs is connected to the output

10/22/2001

Comp 120 Fall 2001

7

Inside there is a 32 way MUX per bit

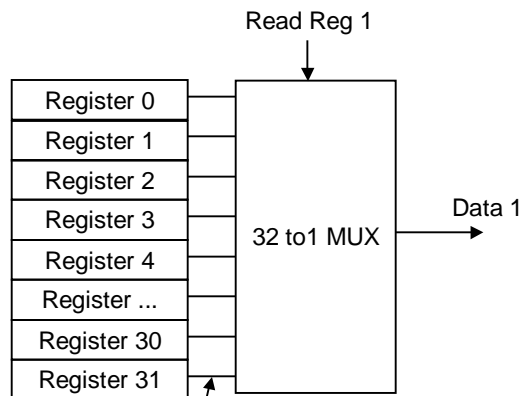

For EACH bit in the 32 bit register

LOT'S OF CONNECTIONS!


And this is just one port!

10/22/2001

Comp 120 Fall 2001

8

Our Register File has 3 ports

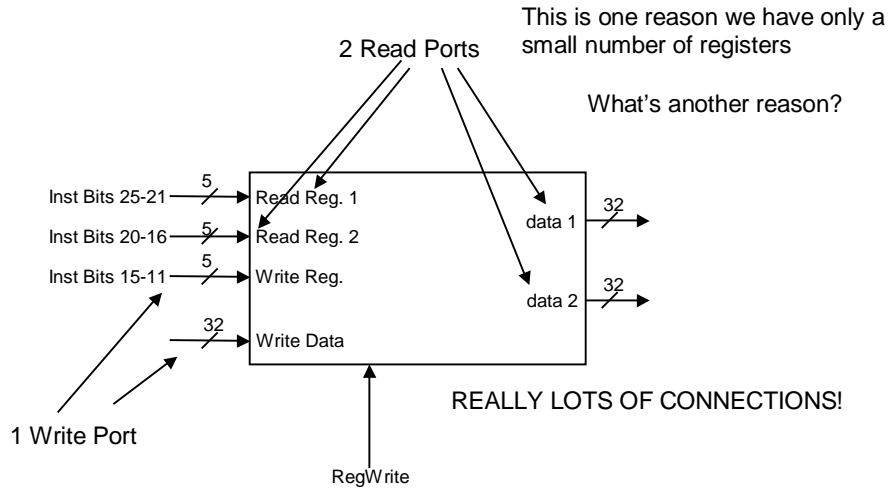

10/22/2001


Comp 120 Fall 2001

9

Implementing Logical Functions

Suppose we want to map M input bits to N output bits

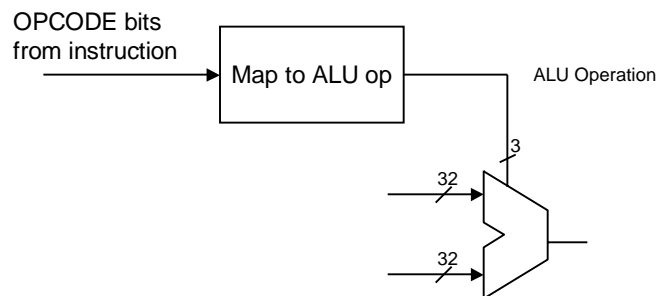For example, we need to take the OPCODE field from the instruction and determine what OPERATION to send to the ALU.




10/22/2001

Comp 120 Fall 2001

10

We can get 1 bit out with a MUX

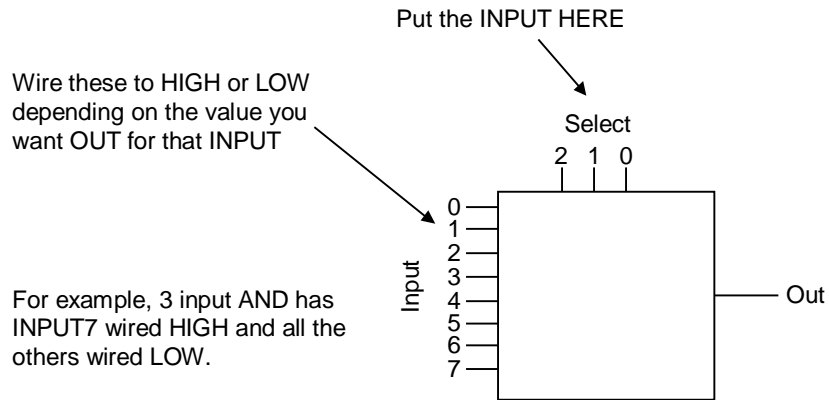


10/22/2001

Comp 120 Fall 2001

11

Or use a ROM

 


10/22/2001

Comp 120 Fall 2001

12

Or use a PLA

Programmable Logic Array

 

Think of the SUM of PRODUCTS form.

The AND Array generates the products of various input bits

The OR Array combines the products into various outputs

10/22/2001

Comp 120 Fall 2001

13

Finite State Machines

- A set of STATES
- A set of INPUTS
- A set of OUTPUTS
- A function to map the STATE and the INPUT into the next STATE and an OUTPUT


Remember "Shoots and Ladders"?

10/22/2001

Comp 120 Fall 2001

14

Traffic Light Controller

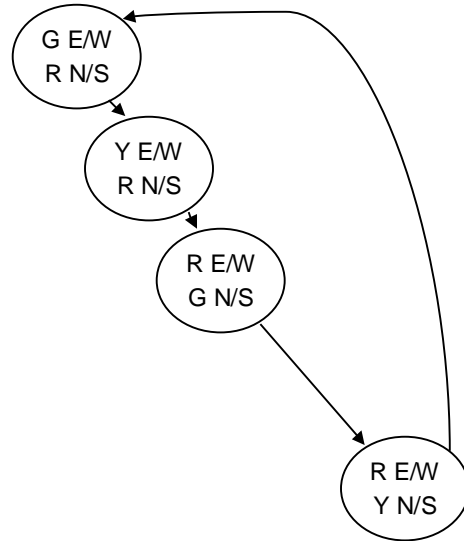


10/22/2001

Comp 120 Fall 2001

15

Implementing a FSM

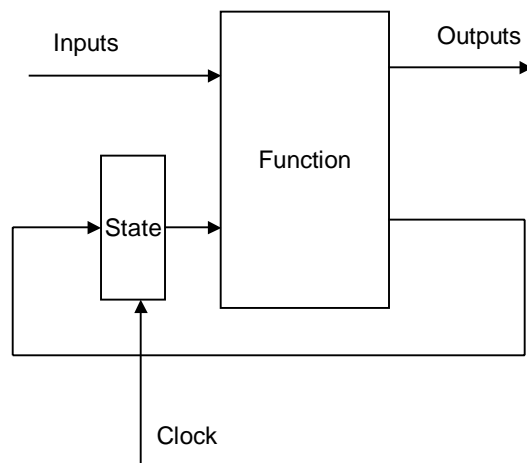

10/22/2001

Comp 120 Fall 2001

16

Recognizing Numbers

Recognize the regular expression for floating point numbers

$[\backslash t]^* [-+]? [0-9]^* (\cdot [0-9]^*)? (e[-+]? [0-9]^+)?$

Examples:

+123.456e23

.456

1.5e-10

-123

"a" matches itself

"[abc]" matches one of a, b, or c

"[a-z]" matches one of a, b, c, d, ..., x, y, or z

"0*" matches zero or more 0's ("", "0", "00", "0000")


"Z?" matches zero or 1 Z's

10/22/2001

Comp 120 Fall 2001

17

FSM Diagram

 

10/22/2001

Comp 120 Fall 2001

18

FSM Table


<p>IN : STATE → NEW STATE</p> <p>' ': start → start</p> <p>'0' '1' ... '9' : start → whole</p> <p>'+' '-' : start → sign</p> <p>'.' : start → frac</p> <p>'0' '1' ... '9' : sign → whole</p> <p>'.' : sign → frac</p> <p>'0' '1' ... '9' : whole → whole</p> <p>'.' : whole → frac</p> <p>'.' : whole → done</p> <p>'e' : whole → exp</p>	<p>'e' : frac → exp</p> <p>'0' '1' ... '9' : frac → frac</p> <p>'.' : frac → done</p> <p>'0' '1' ... '9' : exp → exp</p> <p>'.' : exp → done</p> <p>STATE ASSIGNMENTS</p> <p>start = 0 = 000</p> <p>sign = 1 = 001</p> <p>whole = 2 = 010</p> <p>frac = 3 = 011</p> <p>exp = 4 = 100</p> <p>done = 5 = 101</p> <p>error = 6 = 110</p>
---	---

10/22/2001

Comp 120 Fall 2001

19

FSM Implementation

 

Our PLA has:

- 11 inputs
- 5 outputs

10/22/2001

Comp 120 Fall 2001

20

FSM Take Home

- With **JUST** a register and some logic, we can implement complicated sequential functions like recognizing a FP number.
- This is useful in its own right for compilers, input routines, etc.
- The reason we're looking at it here is to see how designers implement the complicated sequences of events required to implement instructions
- Think of the OP-CODE as playing the role of the input character in the recognizer. The character AND the state determine the next state (and action).