


# April 3

---

- Fun with Muxes
- Implementing arbitrary logical functions
- Finite State Machines

# Fun with MUXes

---

 


Remember the MUX?

This will route 1 of 4 different 1 bit values to the output.

# MUX Blocks


---

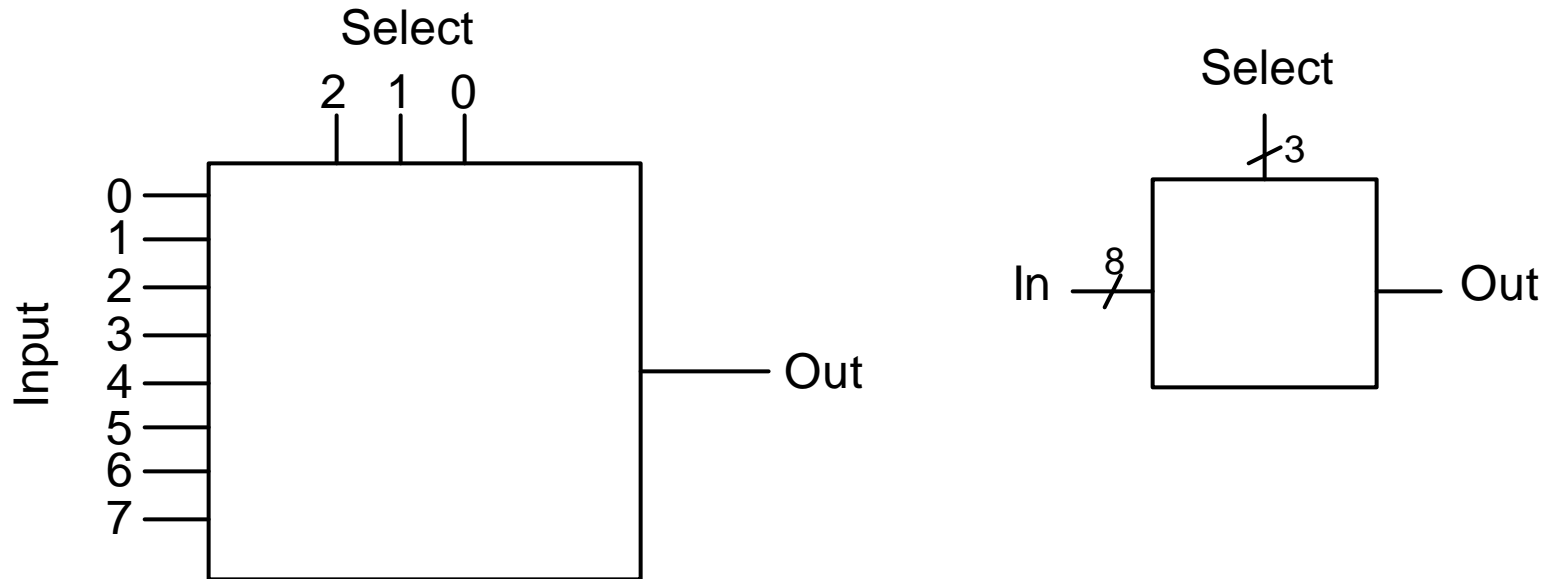

The select signal determines which of the inputs is connected to the output


# Remember the Register File?

---

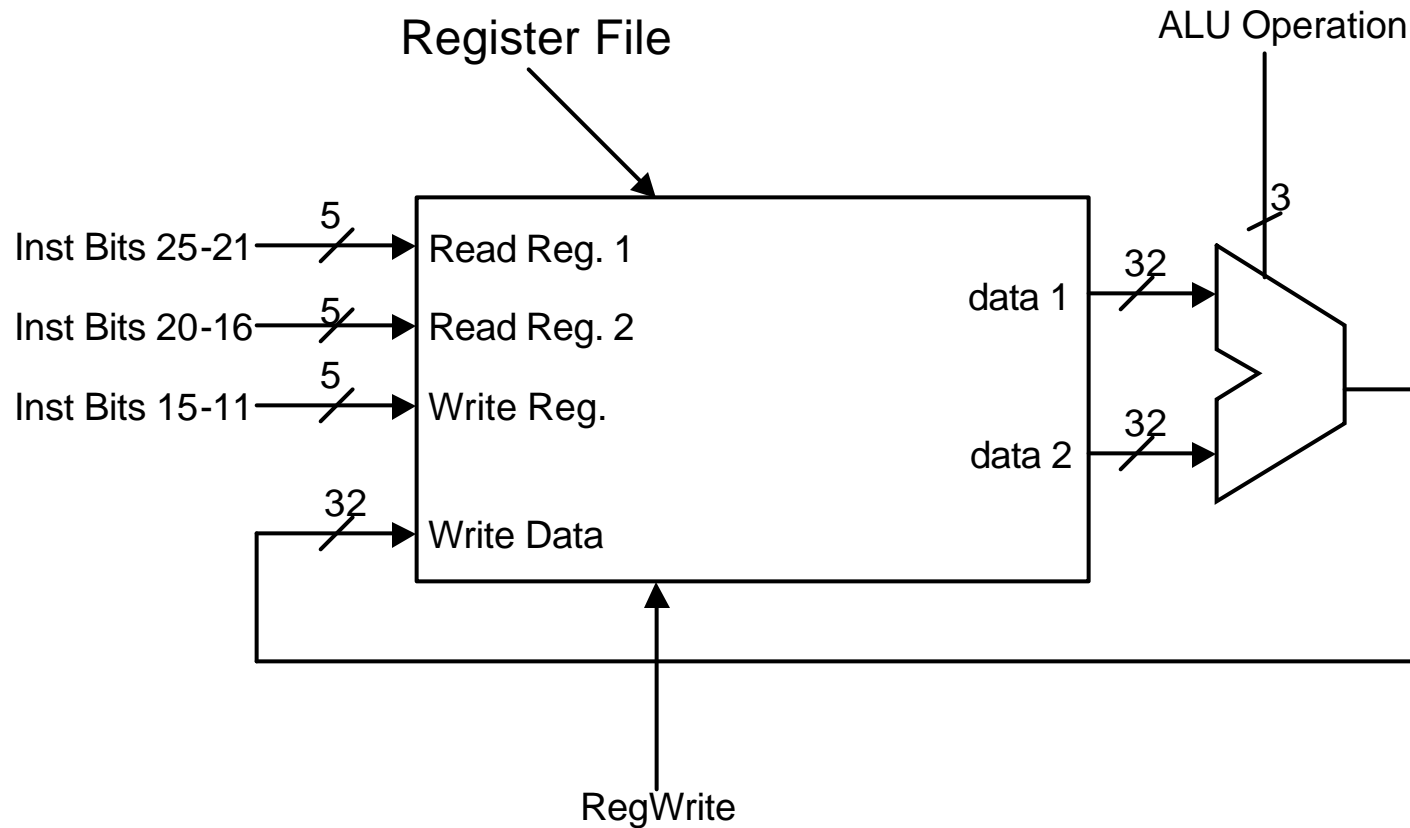

# Inside there is a 32 way MUX per bit

---

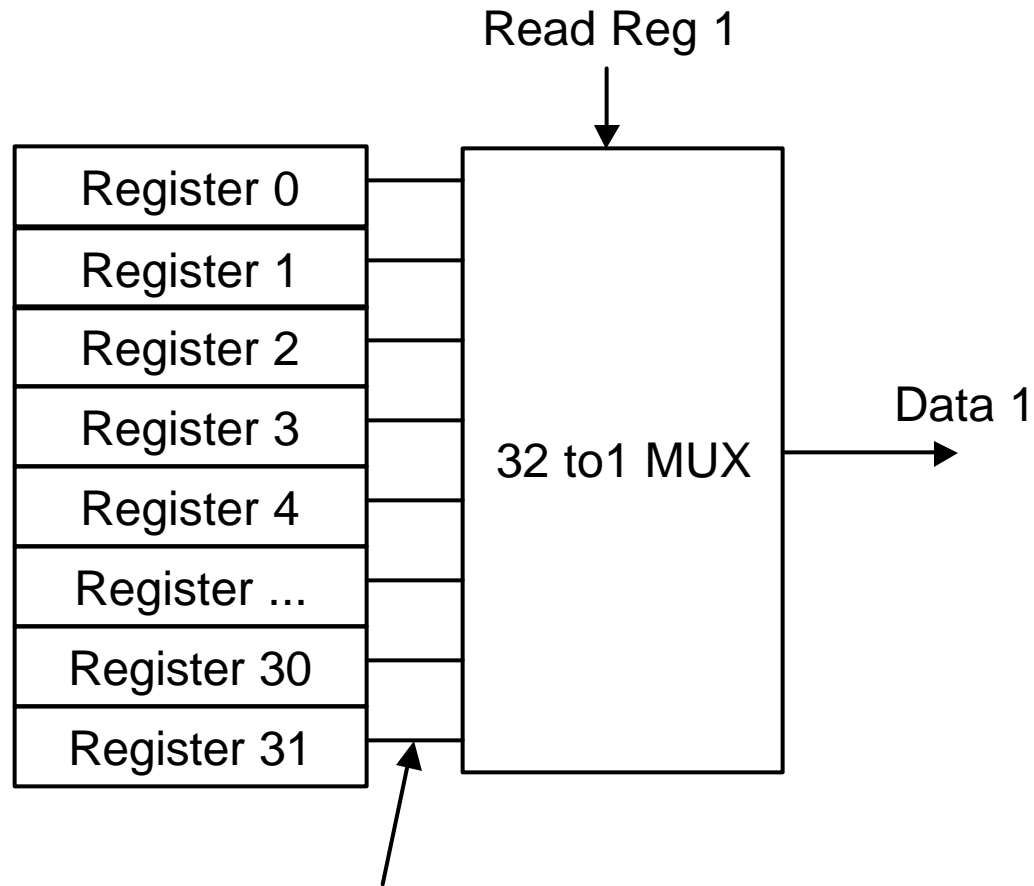


For EACH bit in the 32 bit register

LOT'S OF  
CONNECTIONS!

And this is just one port!

# Our Register File has 3 ports

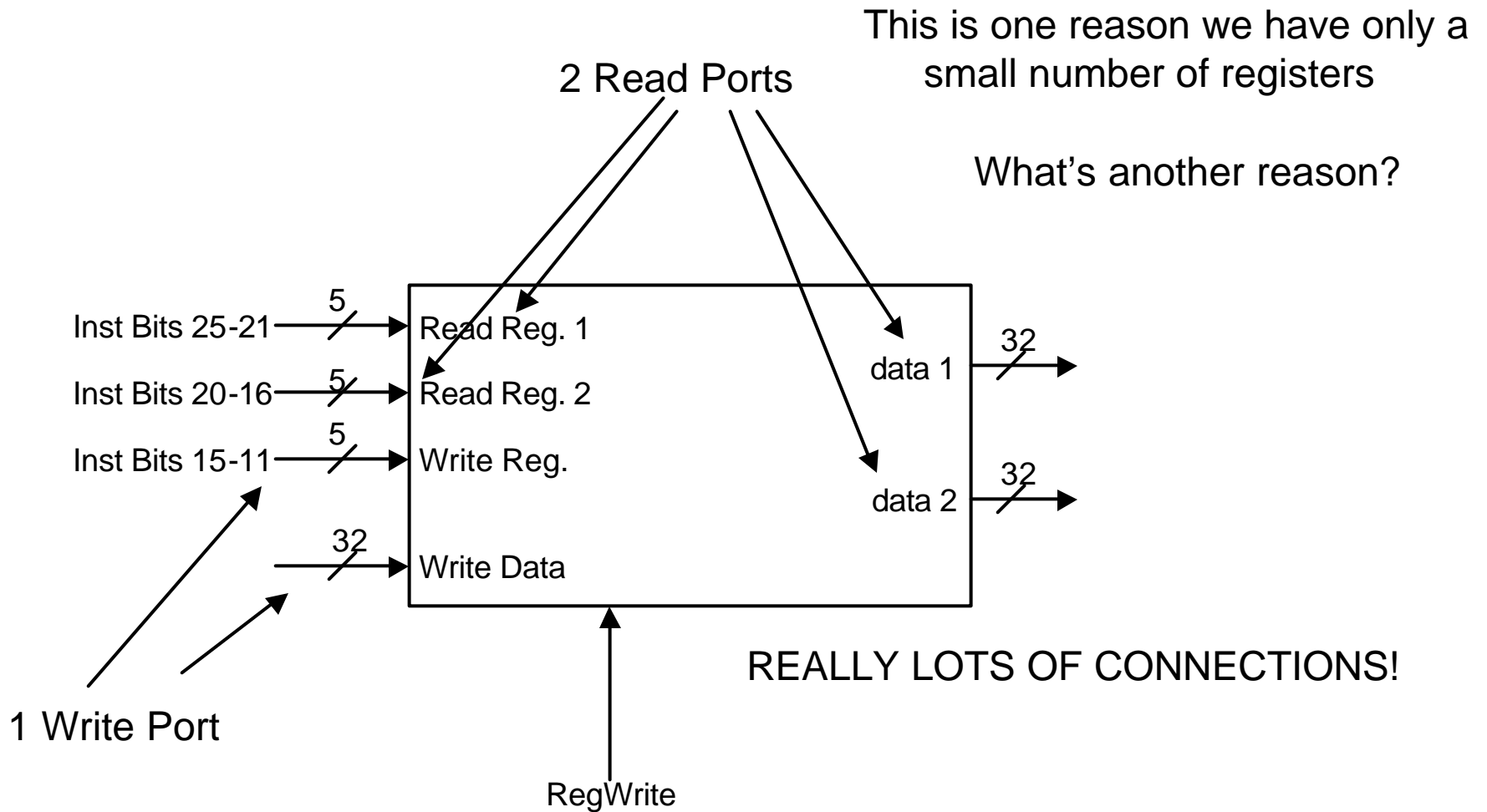


# Implementing Logical Functions

---


Suppose we want to map M input bits to N output bits

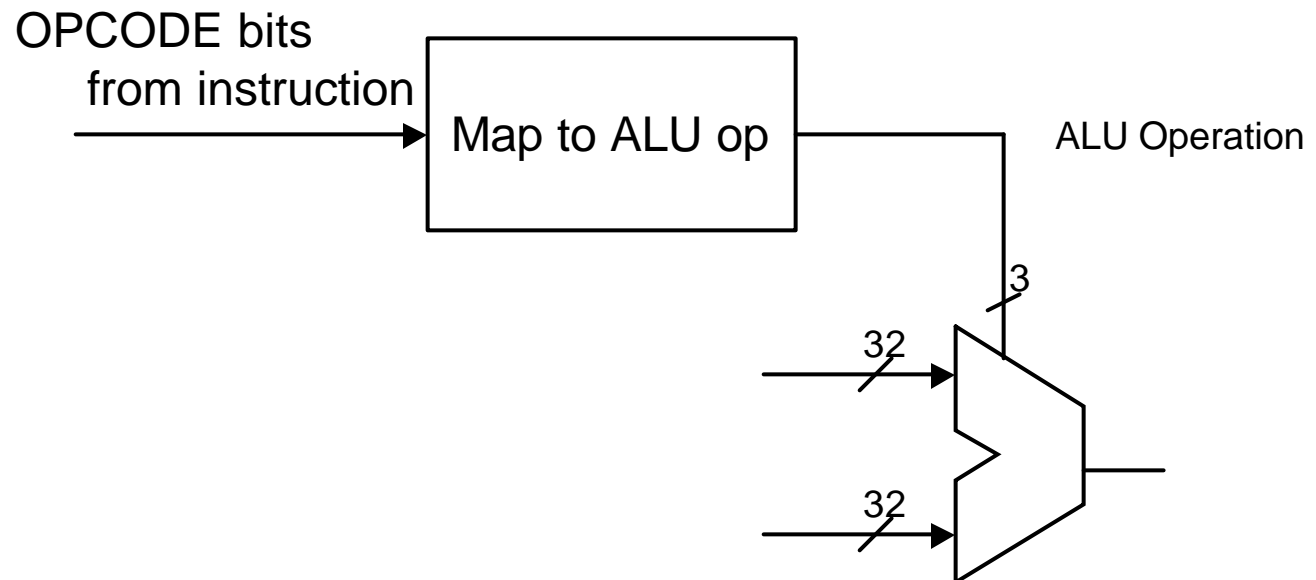For example, we need to take the OPCODE field from the instruction and determine what OPERATION to send to the ALU.




# We can get 1 bit out with a MUX

---

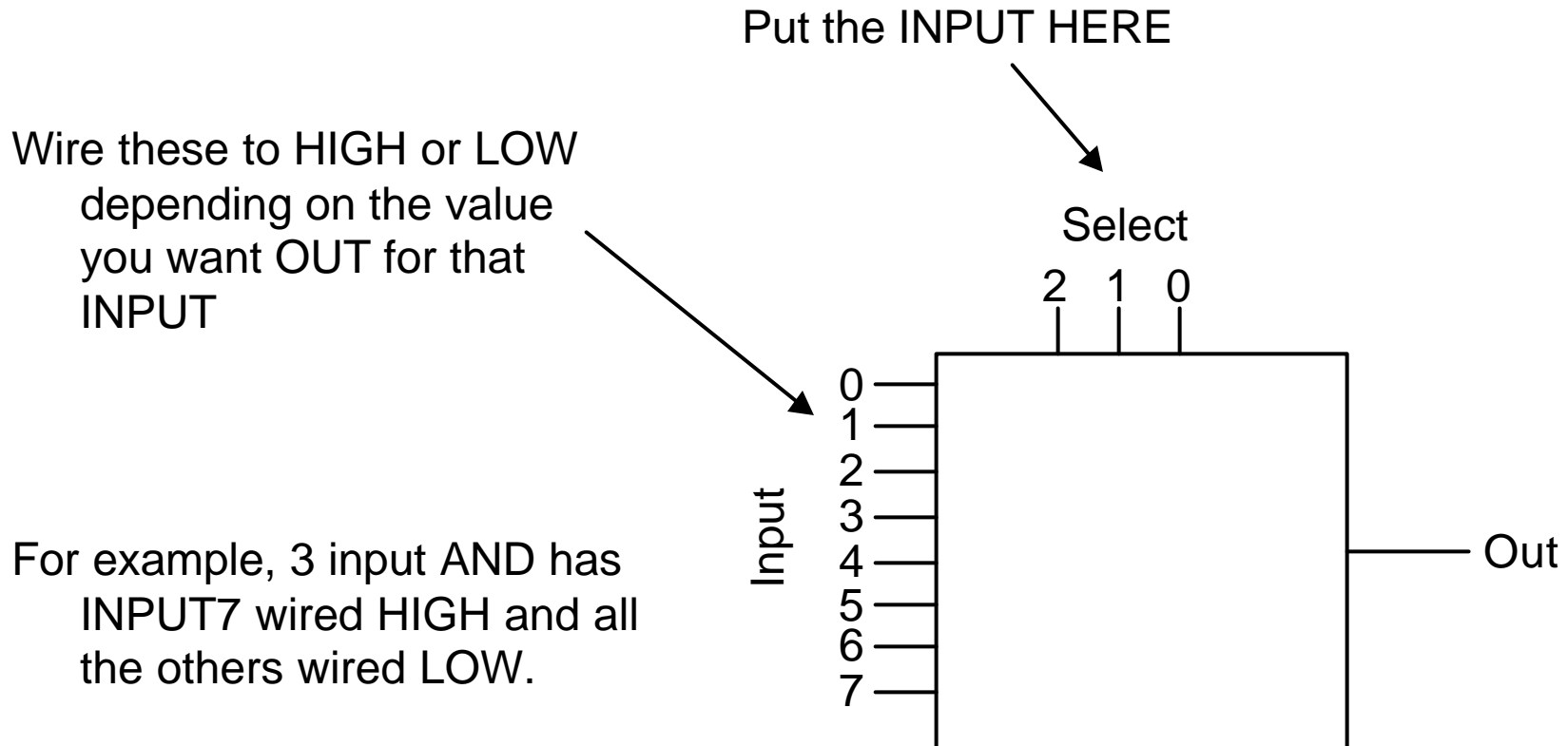


# Or use a ROM

---

 

# Or use a PLA

---

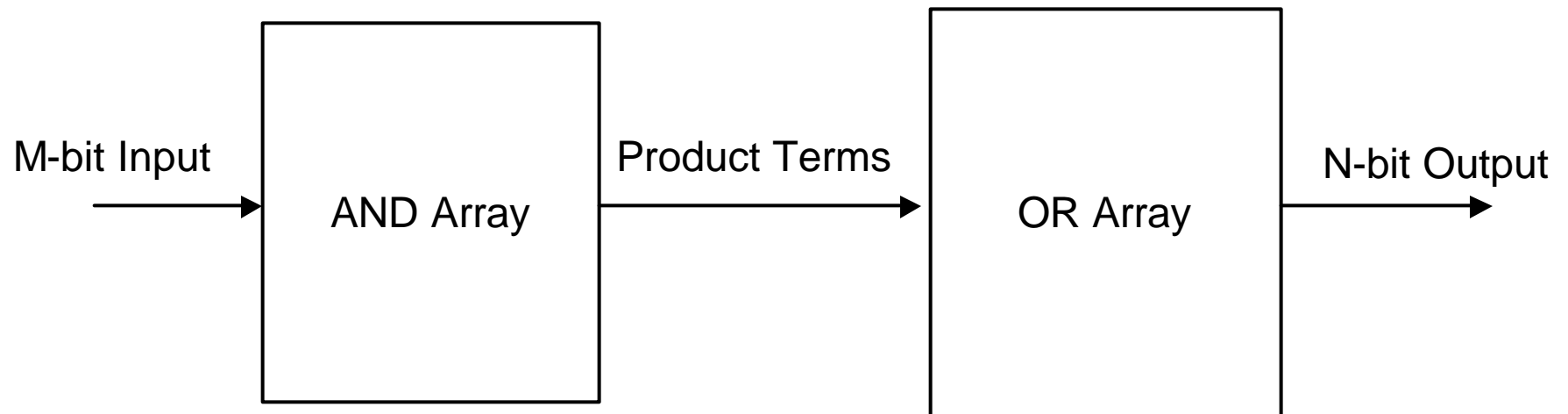

Think of the SUM of PRODUCTS form.

The AND Array generates the products of various input bits

The OR Array combines the products into various outputs

# Finite State Machines


---

- A set of STATES
- A set of INPUTS
- A set of OUTPUTS
- A function to map the STATE and the INPUT into the next STATE and an OUTPUT

Remember “Shoots and Ladders”?

# Traffic Light Controller

---

 

# Implementing a FSM

---

