 


February 27

- Chapter 4 – Arithmetic and its implementation
- Four (4) class meetings before our second test (20%) on **MARCH 20th** the **first class** after spring break.

Arithmetic

- Where we've been:
 - Performance (seconds, cycles, instructions)
 - Abstractions:
 - Instruction Set Architecture
 - Assembly Language and Machine Language
- What's up ahead:
 - Implementing the Architecture



Numbers

- Bits are just bits (no inherent meaning)
 - conventions define relationship between bits and numbers
- Binary numbers (base 2)
 - 0000 0001 0010 0011 0100 0101 0110 0111 1000 1001...
 - decimal: $0 \dots 2^n - 1$
- Of course it gets more complicated:
 - numbers are finite (overflow)
 - fractions and real numbers
 - negative numbers
 - e.g., no MIPS subi instruction; addi can add a negative number)
- How do we represent negative numbers?
 - i.e., which bit patterns will represent which numbers?

Possible Representations

- | Sign Magnitude: | One's Complement | Two's Complement |
|-----------------|------------------|------------------|
| 000 = +0 | 000 = +0 | 000 = +0 |
| 001 = +1 | 001 = +1 | 001 = +1 |
| 010 = +2 | 010 = +2 | 010 = +2 |
| 011 = +3 | 011 = +3 | 011 = +3 |
| 100 = -0 | 100 = -3 | 100 = -4 |
| 101 = -1 | 101 = -2 | 101 = -3 |
| 110 = -2 | 110 = -1 | 110 = -2 |
| 111 = -3 | 111 = -0 | 111 = -1 |
- Issues: balance, number of zeros, ease of operations
- Which one is best? Why?

MIPS uses 2's Complement

- 32 bit signed numbers:

0000	0000	0000	0000	0000	0000	0000	0000	$_{two}$	=	0_{ten}	
0000	0000	0000	0000	0000	0000	0000	0001	$_{two}$	=	$+ 1_{ten}$	
0000	0000	0000	0000	0000	0000	0000	0010	$_{two}$	=	$+ 2_{ten}$	
...											
0111	1111	1111	1111	1111	1111	1111	1110	$_{two}$	=	$+ 2,147,483,646_{ten}$	<i>maxint</i>
0111	1111	1111	1111	1111	1111	1111	1111	$_{two}$	=	$+ 2,147,483,647_{ten}$	
1000	0000	0000	0000	0000	0000	0000	0000	$_{two}$	=	$- 2,147,483,648_{ten}$	
1000	0000	0000	0000	0000	0000	0000	0001	$_{two}$	=	$- 2,147,483,647_{ten}$	<i>minint</i>
1000	0000	0000	0000	0000	0000	0000	0010	$_{two}$	=	$- 2,147,483,646_{ten}$	
...											
1111	1111	1111	1111	1111	1111	1111	1101	$_{two}$	=	$- 3_{ten}$	
1111	1111	1111	1111	1111	1111	1111	1110	$_{two}$	=	$- 2_{ten}$	
1111	1111	1111	1111	1111	1111	1111	1111	$_{two}$	=	$- 1_{ten}$	

Two's Complement Operations

- Negating a two's complement number: invert all bits and add 1
 - remember: “negate” and “invert” are quite different!
 - $-3 == -(0011) == \sim 0011 + 1 == 1100 + 1 == 1101$
- Converting n bit numbers into numbers with more than n bits:
 - MIPS 16 bit immediate gets converted to 32 bits for arithmetic
 - copy the most significant bit (the sign bit) into the other bits
 - 0010 -> 0000 0010
 - 1010 -> 1111 1010
 - “sign extension” (lbu vs. lb)

Addition & Subtraction

- Just like in grade school (carry/borrow 1s)

$$\begin{array}{r} 00111 \\ + 00110 \\ \hline 01101 \end{array} \qquad \begin{array}{r} 00111 \\ - 00110 \\ \hline 00001 \end{array} \qquad \begin{array}{r} 00110 \\ - 00101 \\ \hline 00001 \end{array}$$

- Two's complement operations easy
 - subtraction using addition of negative numbers

$$\begin{array}{r} 00000111 \\ - 00000110 \\ \hline 00000001 \end{array} \qquad \begin{array}{r} 00000111 \\ + 11111010 \\ \hline 00000001 \end{array}$$

- Overflow (result too large for finite computer word):
 - e.g., adding two n-bit numbers does not yield an n-bit number

$$\begin{array}{r} 01110000 \\ + 00010000 \\ \hline 10000000 \end{array} \quad \textit{note that overflow term is somewhat misleading, it does not mean a carry "overflowed"}$$

Detecting Overflow

- No overflow when adding a positive and a negative number
- No overflow when signs are the same for subtraction
- Overflow occurs when the value affects the sign:
 - overflow when adding two positives yields a negative
 - or, adding two negatives gives a positive
 - or, subtract a negative from a positive and get a negative
 - or, subtract a positive from a negative and get a positive
- Consider the operations $A + B$, and $A - B$
 - Can overflow occur if B is 0 ?
 - Can overflow occur if A is 0 ?

Effects of Overflow



- An exception (interrupt) occurs
 - Control jumps to predefined address for exception
 - Interrupted address is saved for possible resumption
- Details based on software system / language
 - example: flight control vs. homework assignment
- Don't always want to detect overflow
 - new MIPS instructions: `addu`, `addiu`, `subu`

note: addiu still sign-extends the operand

note: sltu, sltiu for unsigned comparisons

Logic Functions

A	B	A&B	A B
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

  

When we're doing Boolean algebra it is useful to think of AND as multiplication and OR as addition

Boolean Algebra & Gates

- Problem: Consider a logic function with three inputs: A, B, and C.

Output D is true if at least one input is true

Output E is true if exactly two inputs are true

Output F is true only if all three inputs are true

- Show the truth table for these three functions.
- Show the Boolean equations for these three functions.

A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1


$$D=A|B|C$$

$$E=(\sim A\&B\&C)|(A\&\sim B\&C)|(A\&B\&\sim C)$$

$$F=A\&B\&C$$

An ALU (arithmetic logic unit)

 - Let's build an ALU to support the `andi` and `ori` instructions
 - we'll just build a 1 bit ALU, and use 32 of them




op	a	b	res
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

- Possible Implementation (sum-of-products):

$$\sim op \ \& \ (a|b) \ | \ op \ \& \ a \ \& \ b \ == \ \sim op \ \& \ a \ | \ \sim op \ \& \ b \ | \ op \ \& \ a \ \& \ b$$

Multiplexor

 - Selects one of the inputs to be the output, based on a control input




*note: we call this a 2-input mux
even though it has 3 inputs!*

- Lets build our ALU using a MUX:

1-bit ALU for Addition


 
- Not easy to decide the “best” way to build something
 - Don't want too many inputs to a single gate
 - Don't want to have to go through too many gates
 - for our purposes, ease of comprehension is important
- Let's look at a 1-bit ALU for addition:



$$\begin{aligned} c_{out} &= a \& b \mid a \& c_{in} \mid b \& c_{in} \\ sum &= a \& \sim b \& \sim c_{in} \mid \sim a \& b \& \sim c_{in} \\ &\mid \sim a \& \sim b \& c_{in} \mid a \& b \& c_{in} \end{aligned}$$

a	b	cin	sum	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Building a 32 bit ALU

 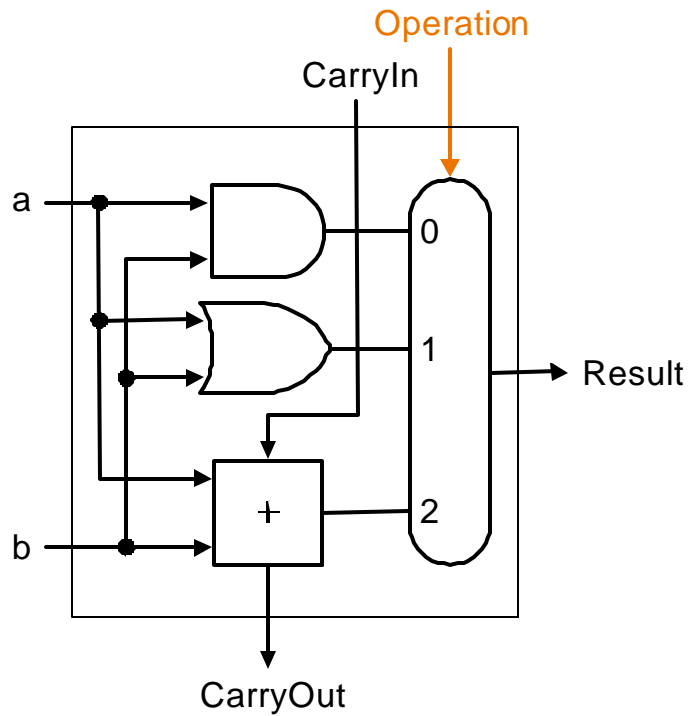

What about subtraction $(a - b)$?

- Two's complement approach: just negate b and add.
- How do we negate?

- A very clever solution:


 


Tailoring the ALU to the MIPS


- Need to support the set-on-less-than instruction (slt)
 - remember: slt is an arithmetic instruction
 - produces a 1 if $rs < rt$ and 0 otherwise
 - use subtraction: $(a-b) < 0$ implies $a < b$
- Need to support test for equality (beq \$t5, \$t6, \$t7)
 - use subtraction: $(a-b) = 0$ implies $a = b$

Supporting slt


- Can we figure out the idea?

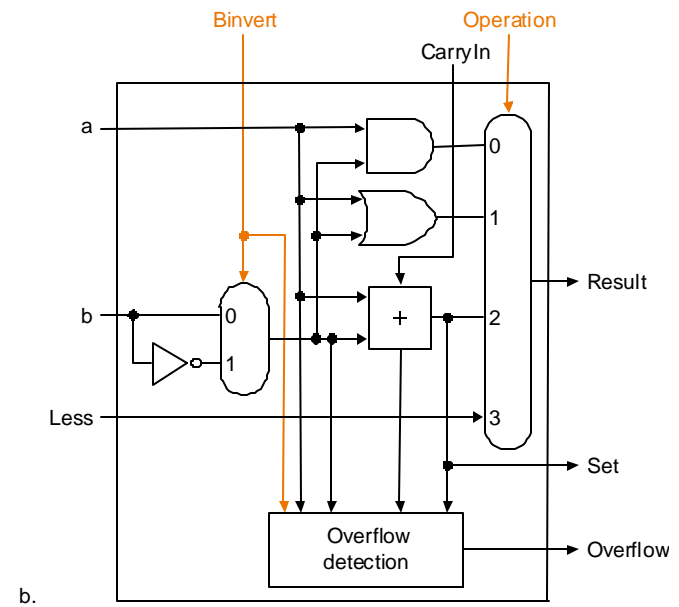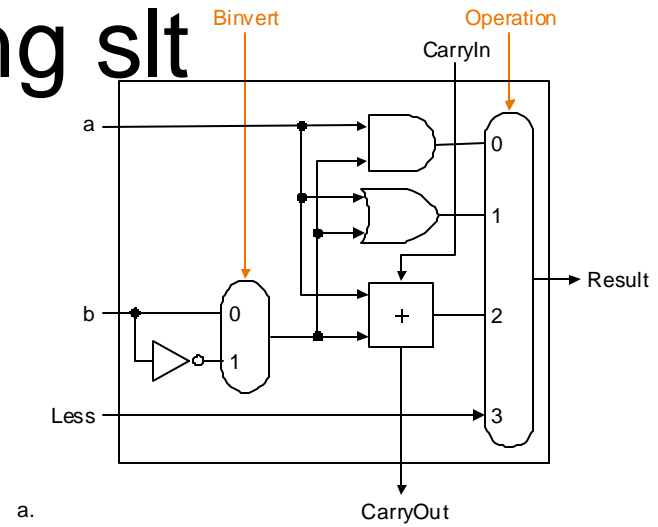


Implement SLT

 

a.

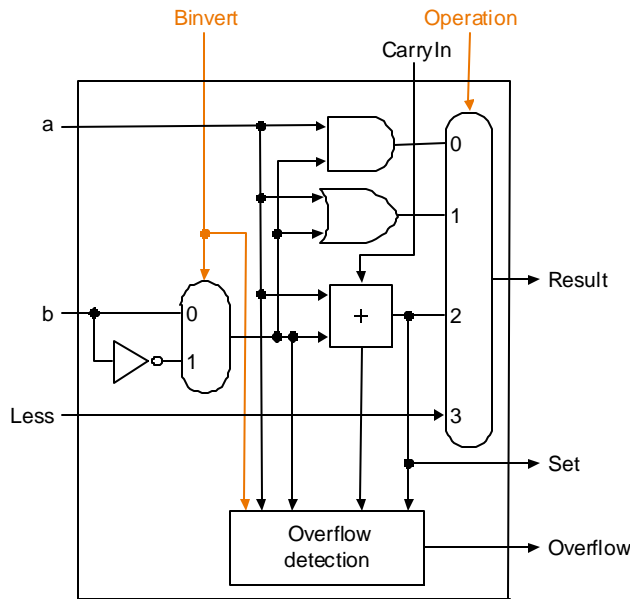

b.

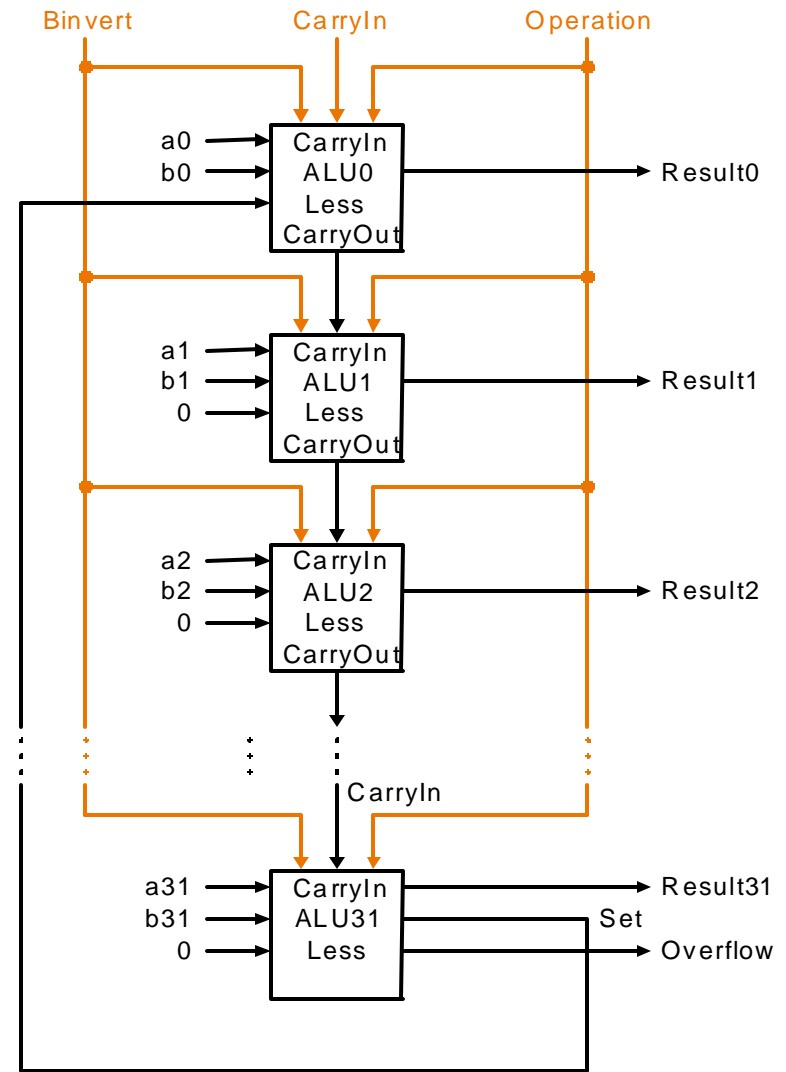


Test for equality

- Notice control lines:

000 = and
001 = or
010 = add
110 = subtract
111 = slt

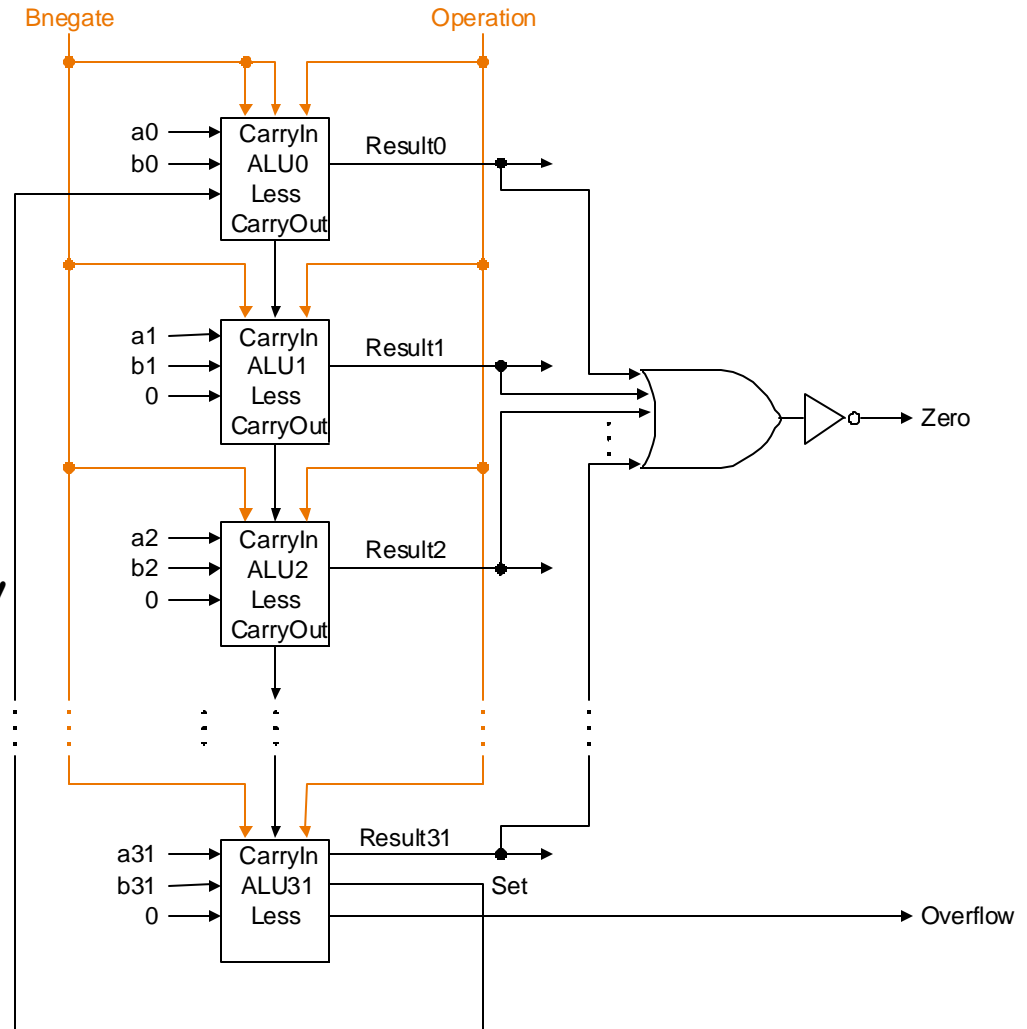•Note: zero is a 1 when the result is zero!



Conclusion

- We can build an ALU to support the MIPS instruction set
 - key idea: use multiplexor to select the output we want
 - we can efficiently perform subtraction using two's complement
 - we can replicate a 1-bit ALU to produce a 32-bit ALU
- Important points about hardware
 - all of the gates are always working
 - the speed of a gate is affected by the number of inputs to the gate
 - the speed of a circuit is affected by the number of gates in series (on the “critical path” or the “deepest level of logic”)
- Our primary focus: comprehension, however,
 - Clever changes to organization can improve performance (similar to using better algorithms in software)