
 


Memory, Latches, & Registers

 

- 1) Structured Logic Arrays
- 2) Memory Arrays
- 3) Transparent Latches
- 4) How to save
a few bucks
at toll booths**
- 5) Edge-triggered Registers

General Table Lookup Synthesis




Generalizing:

Remember from a few lectures ago that, in theory, we can build any 1-output combinational logic block with multiplexers.

For an N-input function we need a _____ input multiplexer.

BIG Multiplexers? How about 10-input function? 20-input?

General Table Lookup Synthesis

 

Generalizing:


Remember from a few lectures ago that, in theory, we can build any 1-output combinational logic block with multiplexers.

For an N-input function we need a 2^N input multiplexer.

BIG Multiplexers? How about 10-input function? 20-input?

A Mux's Guts

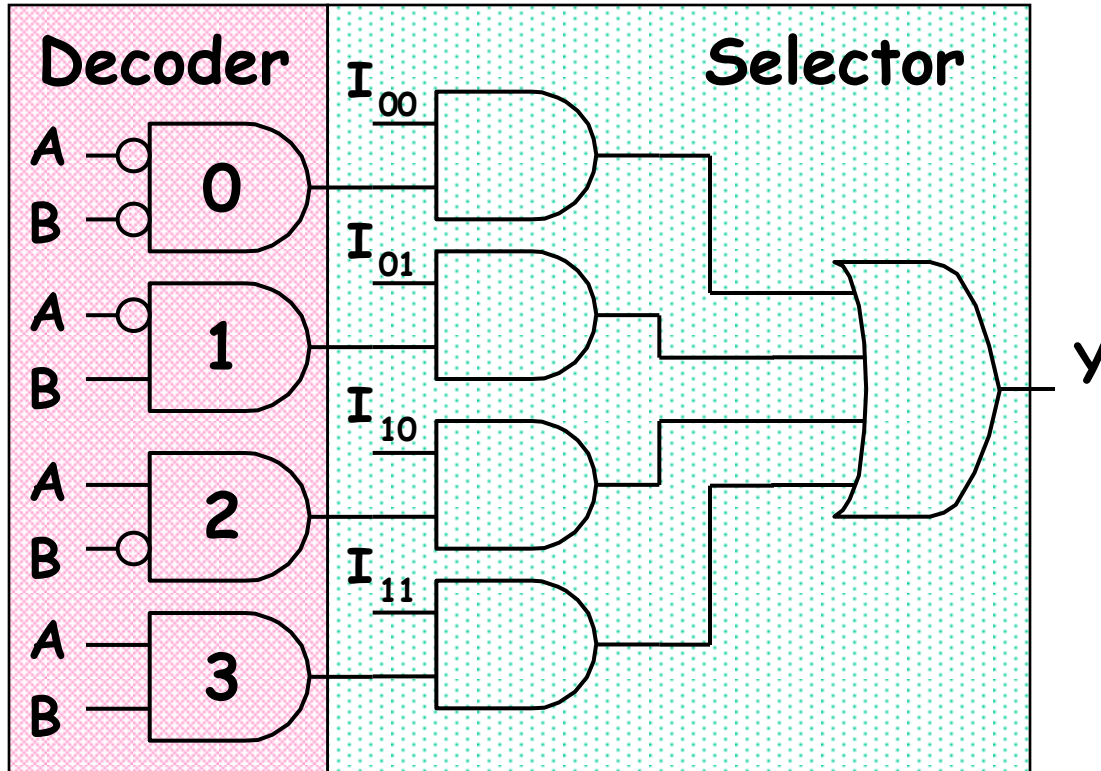A decoder generates all possible product terms for a set of inputs




Multiplexers can be partitioned into two sections.

A DECODER that identifies the desired input, and

a SELECTOR that enables that input onto the output.

Hmmm, by sharing the decoder part of the logic MUXs could be adapted to make lookup tables with any number of outputs

A New Combinational Device

 

DECODER:

k SELECT inputs,

$N = 2^k$ DATA OUTPUTS.

Selected D_j HIGH;
all others LOW.


NOW, we are well on our way to building a general purpose table-lookup device.

We can build a 2-dimensional ARRAY of decoders and selectors as follows ...

Have I mentioned that HIGH is a synonym for '1' and LOW means the same as '0'?




Shared Decoding Logic

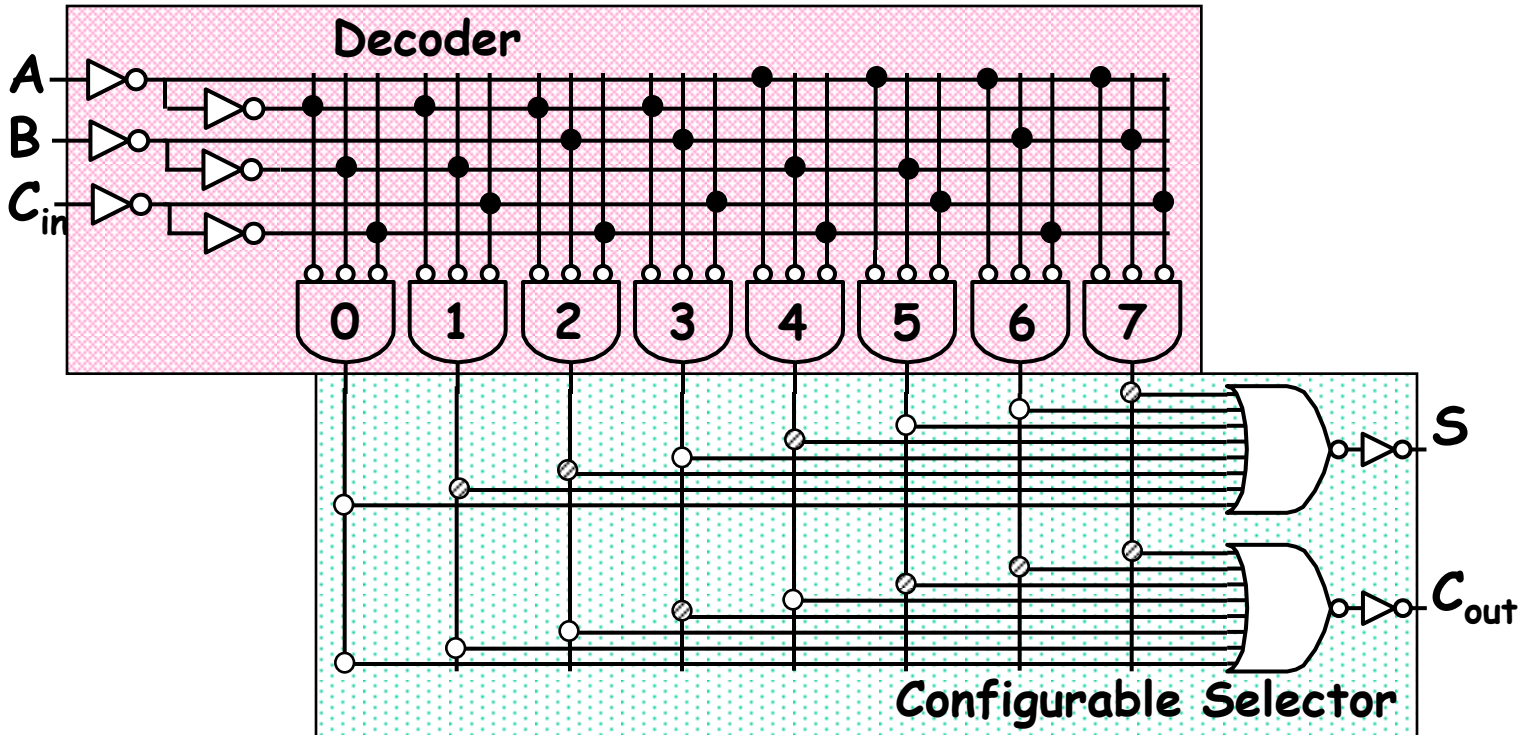

We can build a general purpose “table-lookup” device called a Read-Only Memory (ROM), from which we can implement any truth table and, thus, any combinational device

Made from PREWIRED connections ●, and CONFIGURABLE connections that can be either connected ◐ or not connected ○


Shared Decoding Logic

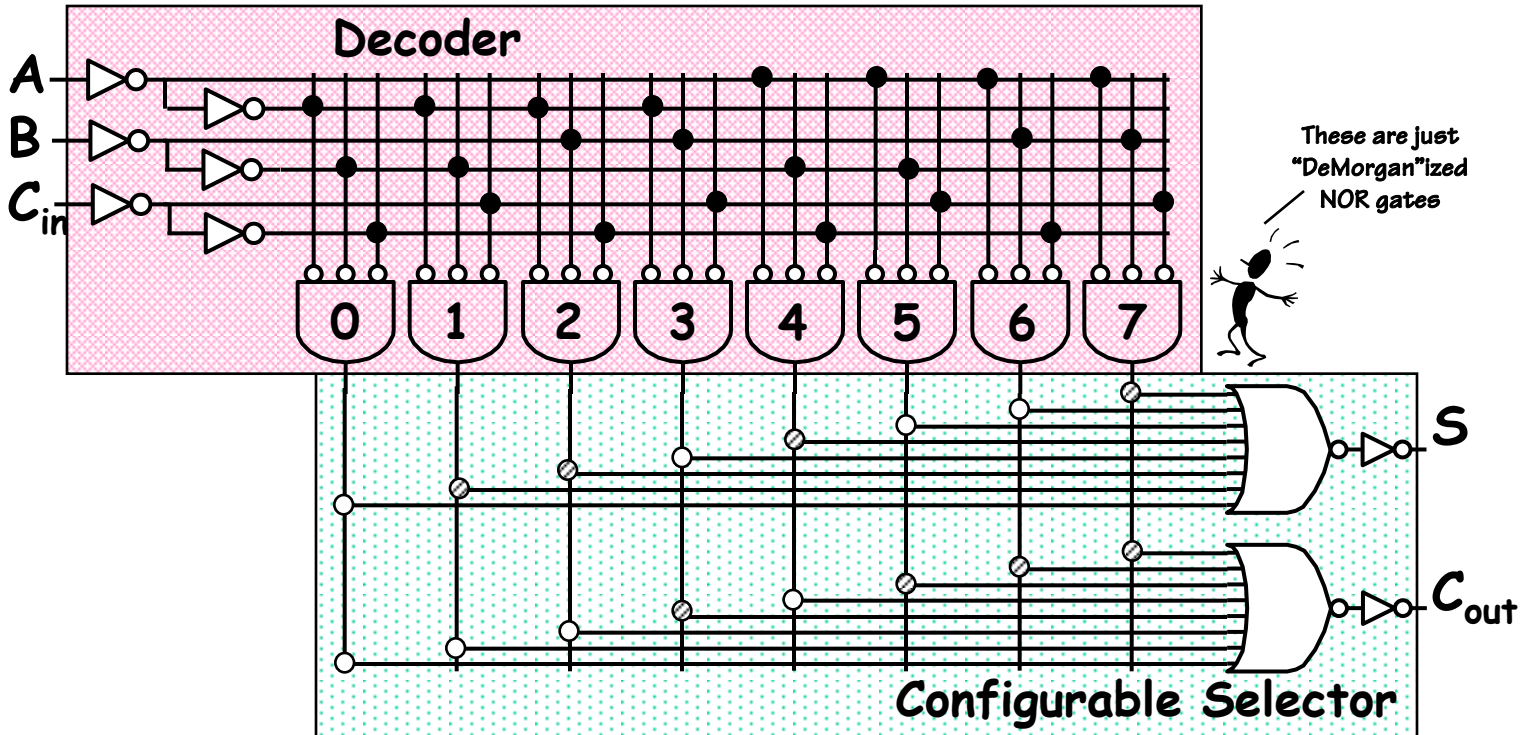

We can build a general purpose “table-lookup” device called a Read-Only Memory (ROM), from which we can implement any truth table and, thus, any combinational device

Made from PREWIRED connections ●, and CONFIGURABLE connections that can be either connected ⊙ or not connected ○


Shared Decoding Logic

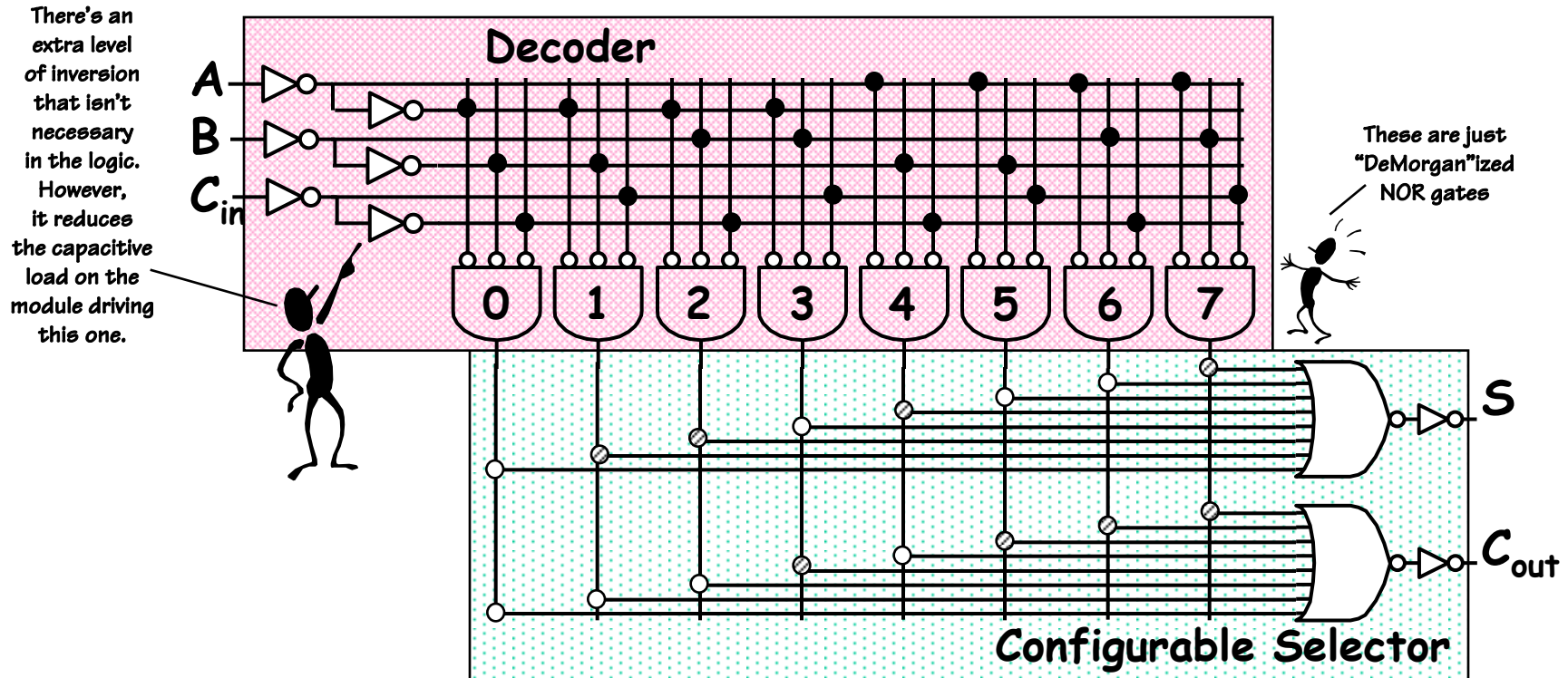

We can build a general purpose "table-lookup" device called a Read-Only Memory (ROM), from which we can implement any truth table and, thus, any combinational device

Made from PREWIRED connections ●, and CONFIGURABLE connections that can be either connected ◐ or not connected ○

Shared Decoding Logic

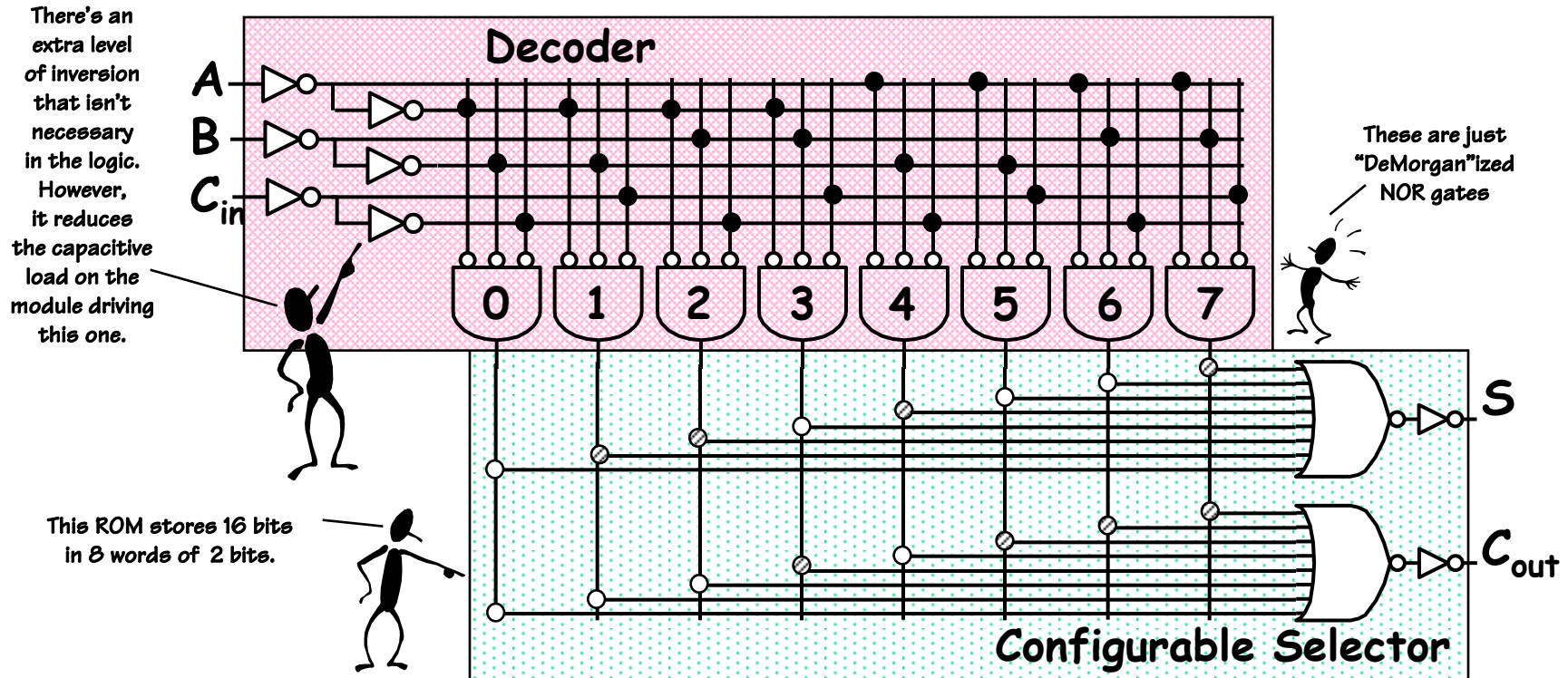

We can build a general purpose "table-lookup" device called a Read-Only Memory (ROM), from which we can implement any truth table and, thus, any combinational device

Made from PREWIRED connections ●, and CONFIGURABLE connections that can be either connected ◐ or not connected ○

Logic According to ROMs

ROMs *ignore* the structure of combinational functions ...

- Size, layout, and design are independent of function
- Any Truth table can be “programmed” by minor reconfiguration:

- Metal layer (masked ROMs)
- Fuses (Field-programmable PROMs)
- Charge on floating gates (EPROMs)
- ... etc.

Model: LOOK UP value of function in truth table...

Inputs: “ADDRESS” of a T.T. entry

ROM SIZE = # TT entries...

... for an N-input boolean function, size = _____

Logic According to ROMs

ROMs *ignore* the structure of combinational functions ...

- Size, layout, and design are independent of function
- Any Truth table can be “programmed” by minor reconfiguration:

- Metal layer (masked ROMs)
- Fuses (Field-programmable PROMs)
- Charge on floating gates (EPROMs)
- ... etc.

Model: LOOK UP value of function in truth table...


Inputs: “ADDRESS” of a T.T. entry

ROM SIZE = # TT entries...

... for an N-input boolean function, size = $2^N \times \text{\#outputs}$

Analog Storage: Using Capacitors

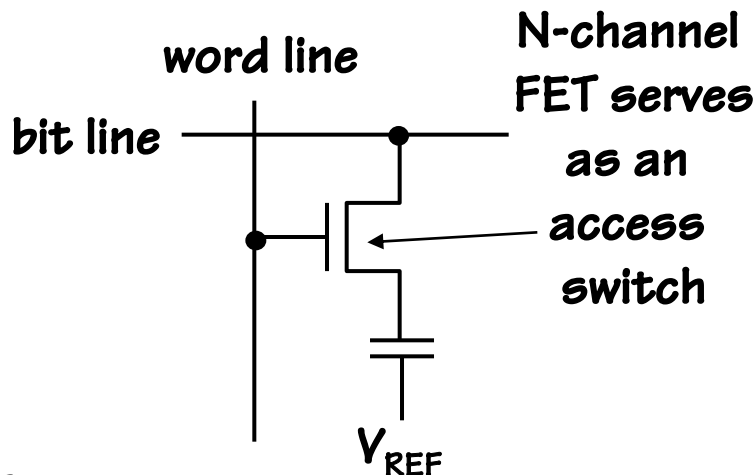We've chosen to encode information using voltages and we know from physics that we can "store" a voltage as "charge" on a capacitor:



To write:

Drive bit line, turn on access fet,
force storage cap to new voltage

To read:

precharge bit line, turn on access fet,
detect (small) change in bit line voltage

Pros:

- ◆ compact!

Cons:

- ◆ it leaks! \Rightarrow refresh


- ◆ complex interface

- ◆ reading a bit, destroys it
(you have to rewrite the value after each read)

- ◆ it's NOT a digital circuit


**This storage circuit is the
basis for commodity DRAMs**

DRAM Organization

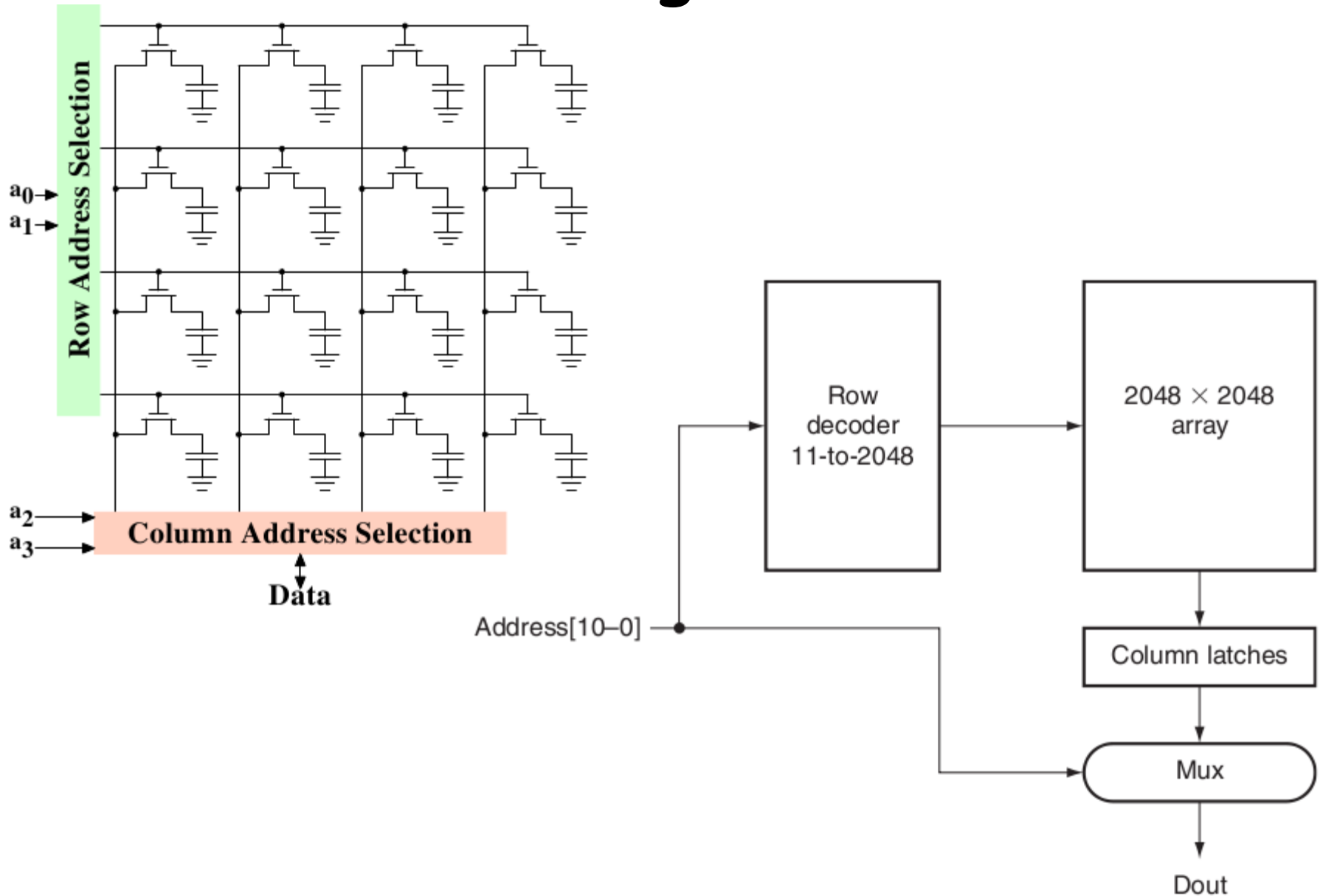

DRAM Errors

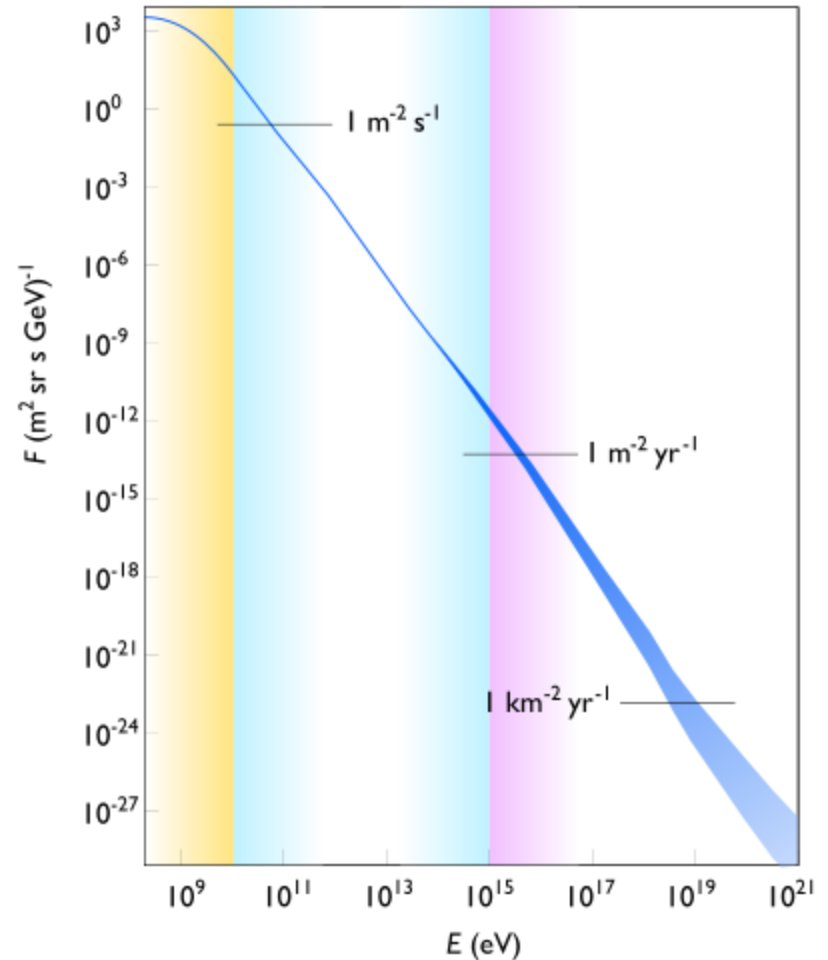
- Typical RAM cell stores about 75 fC (femtocoulombs) of charge.
- That's about $\frac{1}{2}$ million electrons
- Or at 3 Volts about 1.5 MeV (megaelectron volts)
- Sounds like a lot!
- Until you consider other sources.
- Google reports that error rates are 100's to 1000's of times higher than thought. Over 3700 errors per DIMM per year.



Cosmic Ray Flux vs Particle Energy ([link](#))


A "Digital" Storage Element

 It's also easy to build a *settable* DIGITAL storage element (called a **latch**) using a MUX and FEEDBACK:




A "Digital" Storage Element

 It's also easy to build a *settable* DIGITAL storage element (called a **latch**) using a MUX and FEEDBACK:




A "Digital" Storage Element

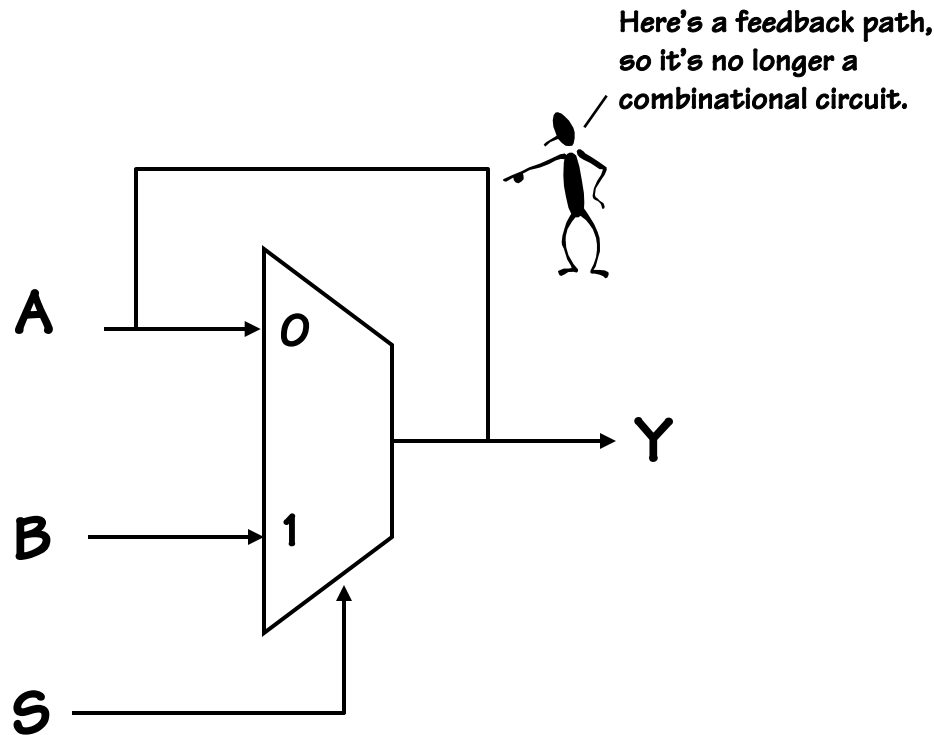It's also easy to build a settable DIGITAL storage element (called a **latch**) using a MUX and FEEDBACK:




A "Digital" Storage Element

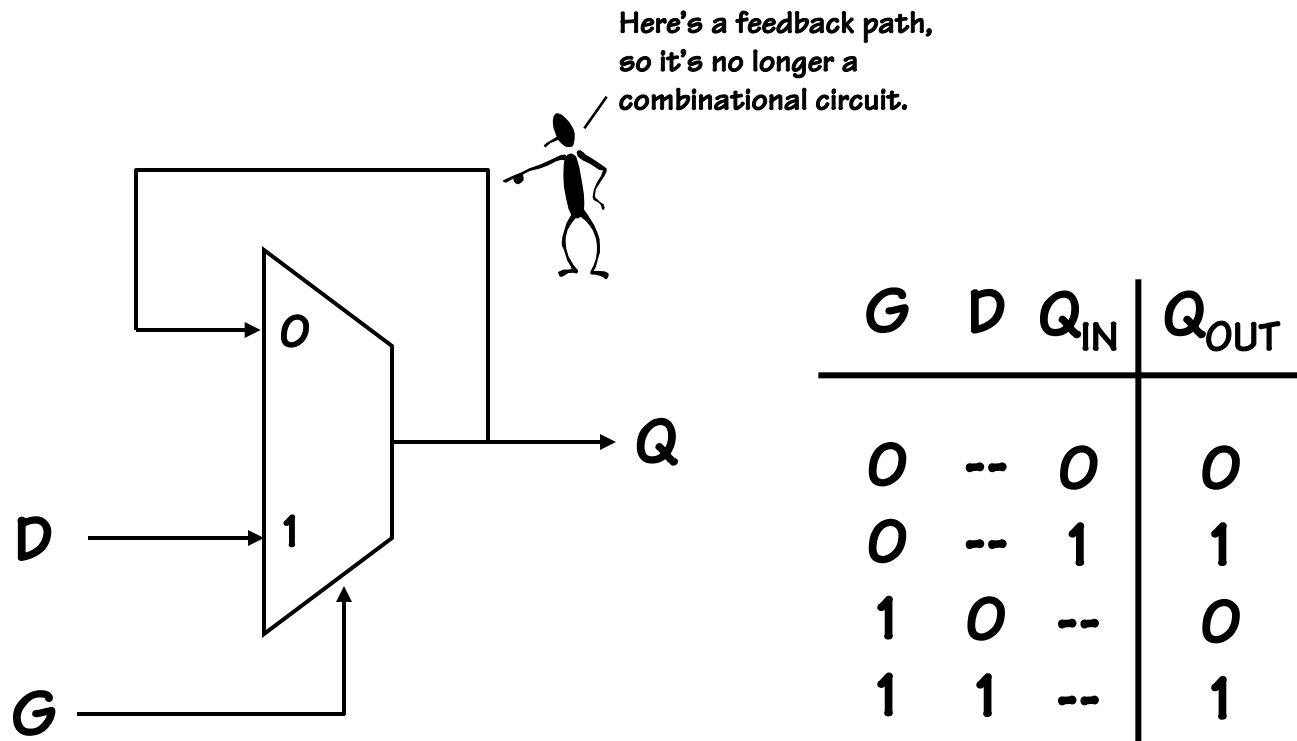It's also easy to build a *settable* DIGITAL storage element (called a **latch**) using a MUX and FEEDBACK:



A "Digital" Storage Element

 It's also easy to build a settable DIGITAL storage element (called a **latch**) using a MUX and FEEDBACK:




Here's a feedback path, so it's no longer a combinational circuit.

"state" signal appears as both input and output

G	D	Q _{IN}	Q _{OUT}
0	--	0	0
0	--	1	1
1	0	--	0
1	1	--	1

A "Digital" Storage Element

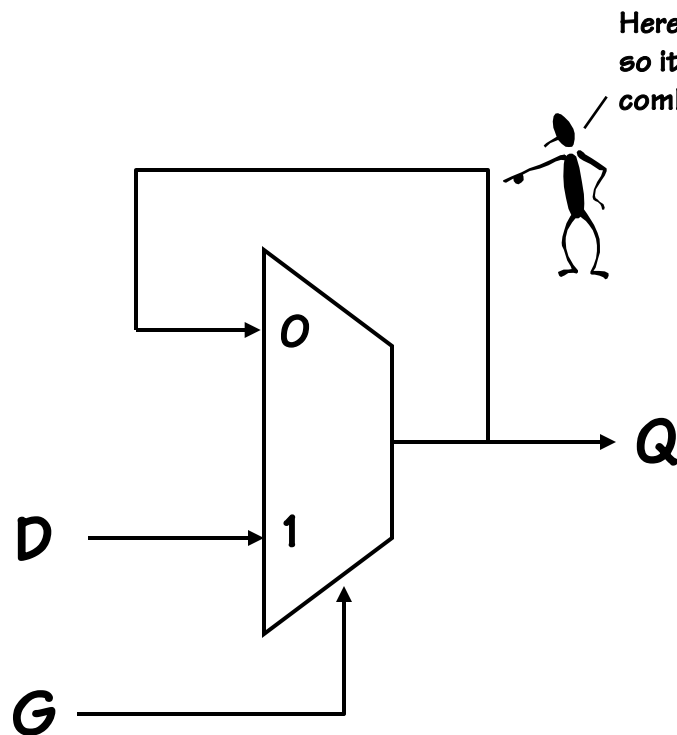It's also easy to build a settable DIGITAL storage element (called a **latch**) using a MUX and FEEDBACK:




"state" signal appears as both input and output

G	D	Q _{IN}	Q _{OUT}	
0	--	0	0	} Q stable
0	--	1	1	
1	0	--	0	} Q follows D
1	1	--	1	

Looking Under the Covers

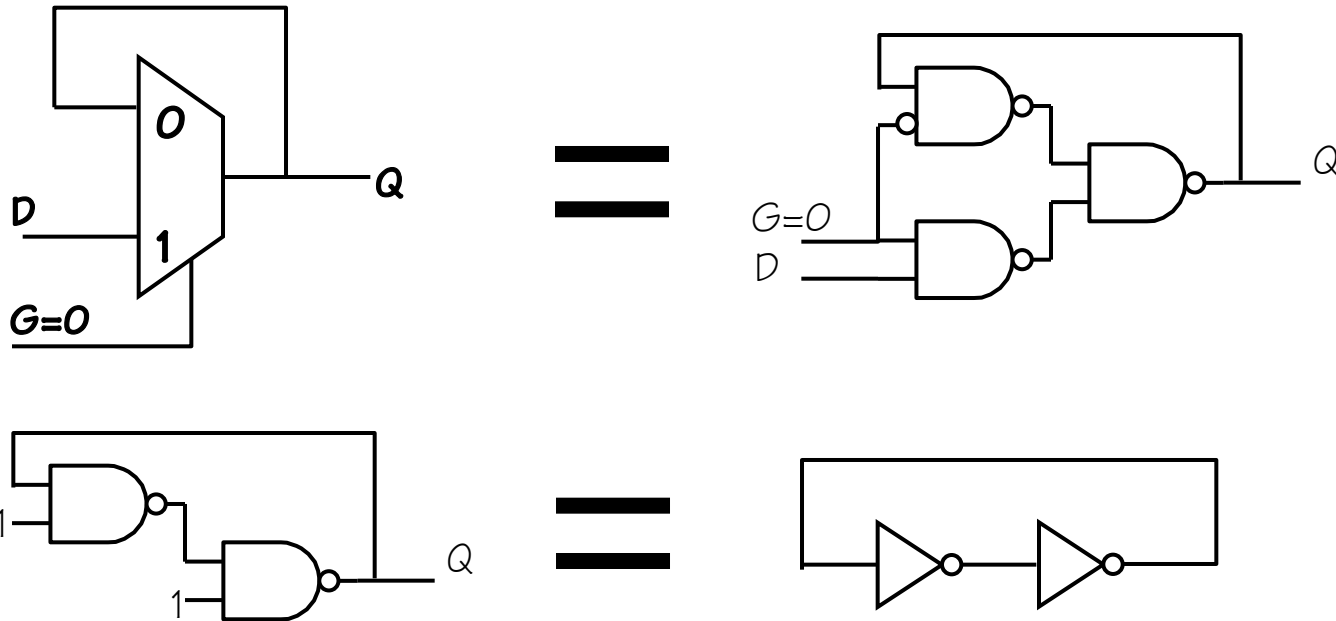Let's take a quick look at the equivalent circuit for our MUX when the gate is LOW (the feedback path is active)



This storage circuit is the basis for commodity SRAMs

Advantages:


- 1) Maintains remembered state for as long as power is applied.
- 2) State is DIGITAL

Disadvantage:

 - 1) Requires more transistors

Why Does Feedback = Storage?


BIG IDEA: use **positive feedback** to maintain storage indefinitely. Our logic gates are built to restore marginal signal levels, so noise shouldn't be a problem!




Result: a **bistable storage element**

Why Does Feedback = Storage?

 BIG IDEA: use **positive feedback** to maintain storage indefinitely. Our logic gates are built to restore marginal signal levels, so noise shouldn't be a problem!




Result: a **bistable storage element**

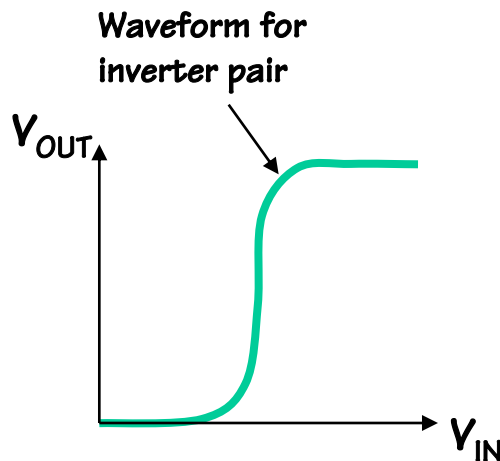


Why Does Feedback = Storage?

 BIG IDEA: use **positive feedback** to maintain storage indefinitely. Our logic gates are built to restore marginal signal levels, so noise shouldn't be a problem!




Result: a **bistable storage element**

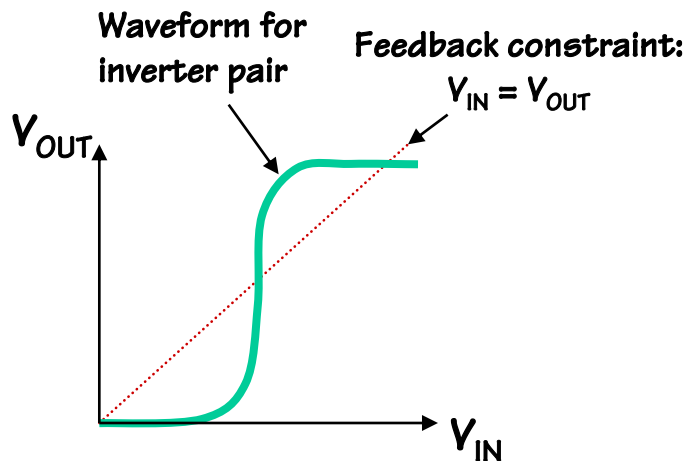


Why Does Feedback = Storage?

 BIG IDEA: use **positive feedback** to maintain storage indefinitely. Our logic gates are built to restore marginal signal levels, so noise shouldn't be a problem!



Result: a **bistable storage element**

 


Not affected by noise

Three solutions:


- ◆ two end-points are **stable**
- ◆ middle point is **unstable**

We'll get back to this!



Static D Latch

 

Positive latch

 


Negative latch

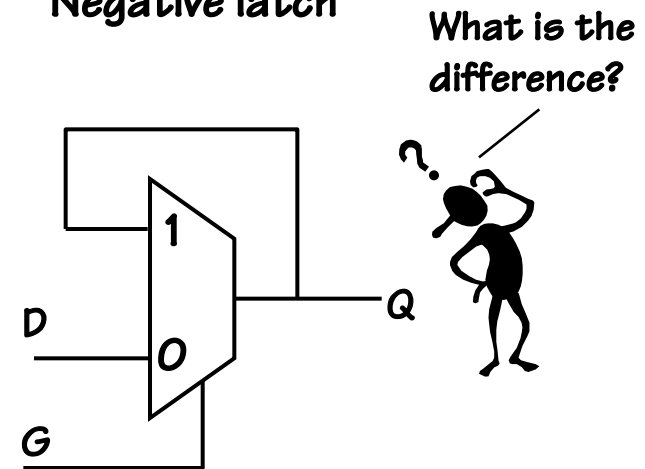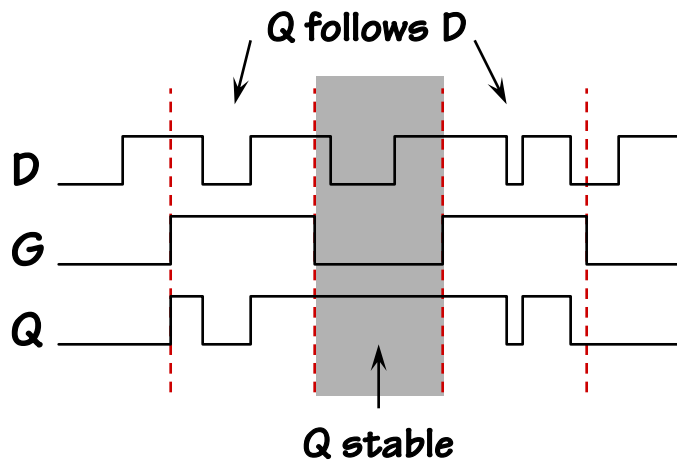

“static” means latch will hold data (i.e., value of Q) while G is inactive, however long that may be.


A DYNAMIC Discipline

 Design of sequential circuits **MUST** guarantee that inputs to sequential devices are valid and stable during periods when they may influence state changes. **This is assured with additional timing specifications.**



A DYNAMIC Discipline

 Design of sequential circuits **MUST** guarantee that inputs to sequential devices are valid and stable during periods when they may influence state changes. **This is assured with additional timing specifications.**




t_{PULSE} : minimum pulse width

guarantee G is active for long enough for latch to capture data

A DYNAMIC Discipline

 Design of sequential circuits **MUST** guarantee that inputs to sequential devices are valid and stable during periods when they may influence state changes. **This is assured with additional timing specifications.**



t_{PULSE} : minimum pulse width


guarantee G is active for long enough for latch to capture data

t_{SETUP} : setup time

guarantee that D value has propagated through feedback path before latch closes

A DYNAMIC Discipline

 Design of sequential circuits **MUST** guarantee that inputs to sequential devices are valid and stable during periods when they may influence state changes. **This is assured with additional timing specifications.**



t_{PULSE} : minimum pulse width

guarantee G is active for long enough for latch to capture data

t_{SETUP} : setup time


guarantee that D value has propagated through feedback path before latch closes

t_{HOLD} : hold time

guarantee latch is closed and Q is stable before allowing D to change


Flakey Control Systems

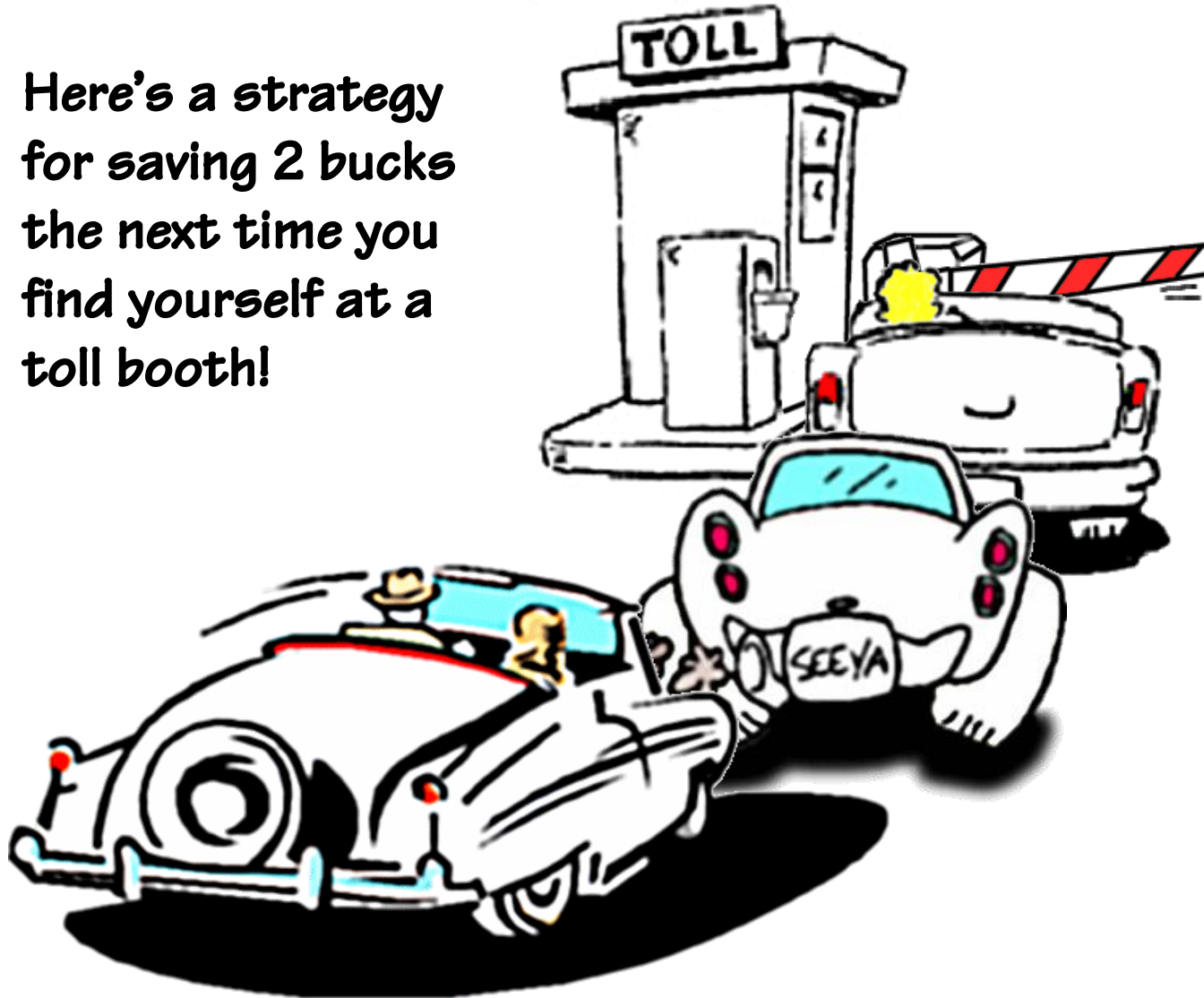Here's a strategy for saving 2 bucks the next time you find yourself at a toll booth!



Flakey Control Systems

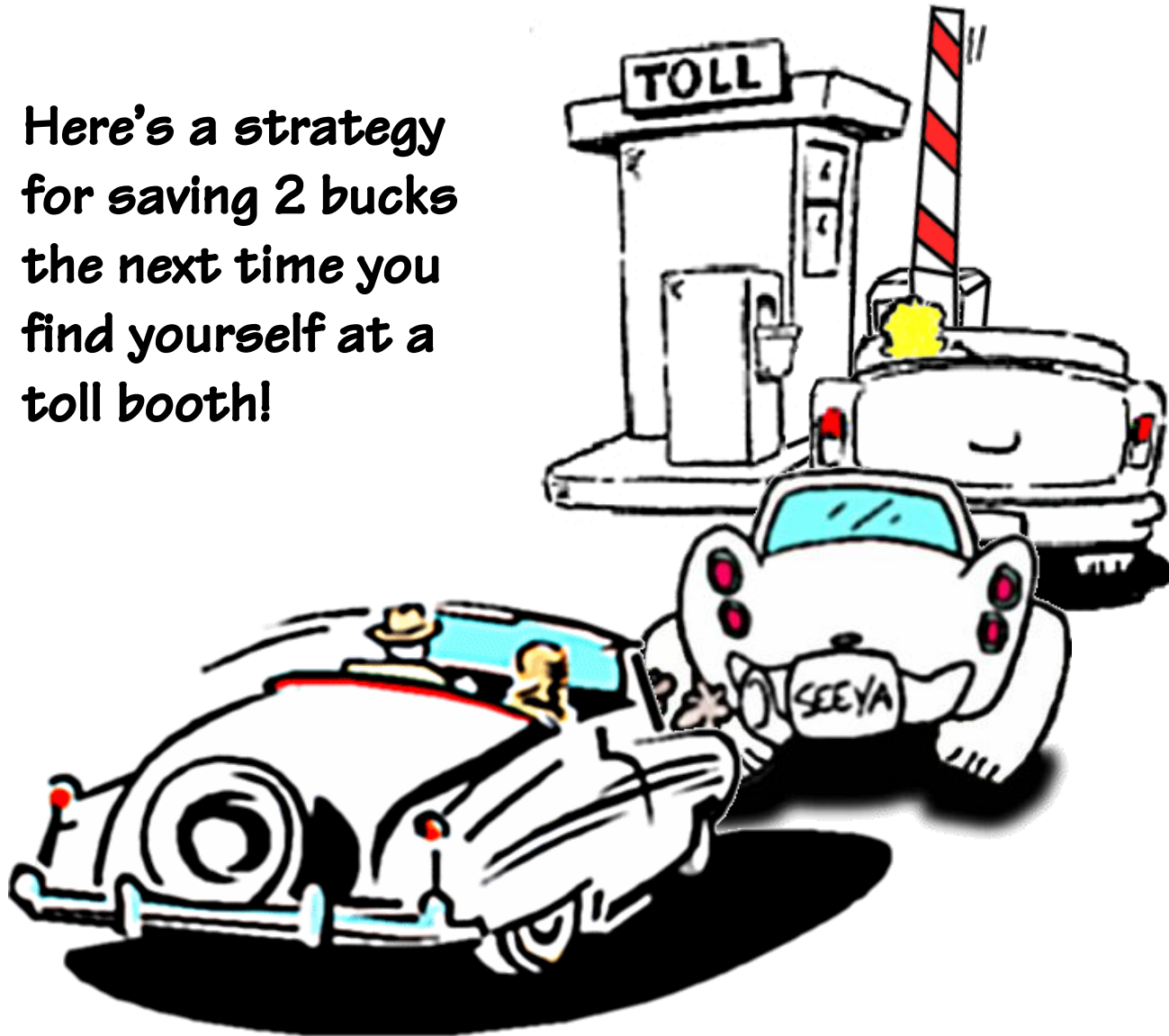Here's a strategy for saving 2 bucks the next time you find yourself at a toll booth!



Flakey Control Systems

**Here's a strategy
for saving 2 bucks
the next time you
find yourself at a
toll booth!**



Flakey Control Systems


Here's a strategy
for saving 2 bucks
the next time you
find yourself at a
toll booth!



WARNING:
Professional Drivers Used!
DON'T try this
At home!


Escapement Strategy

 The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

 The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

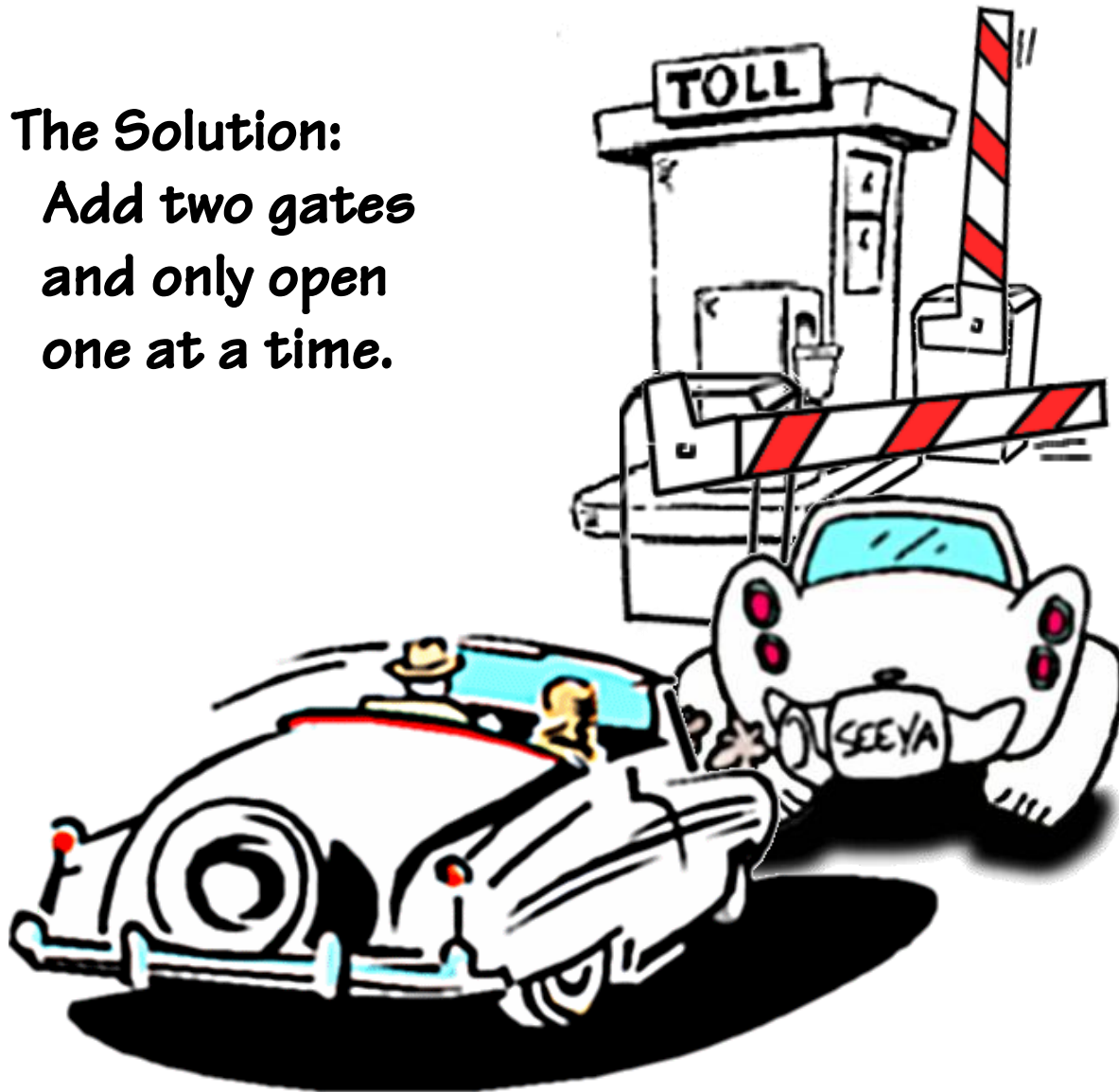The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

 The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

 The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

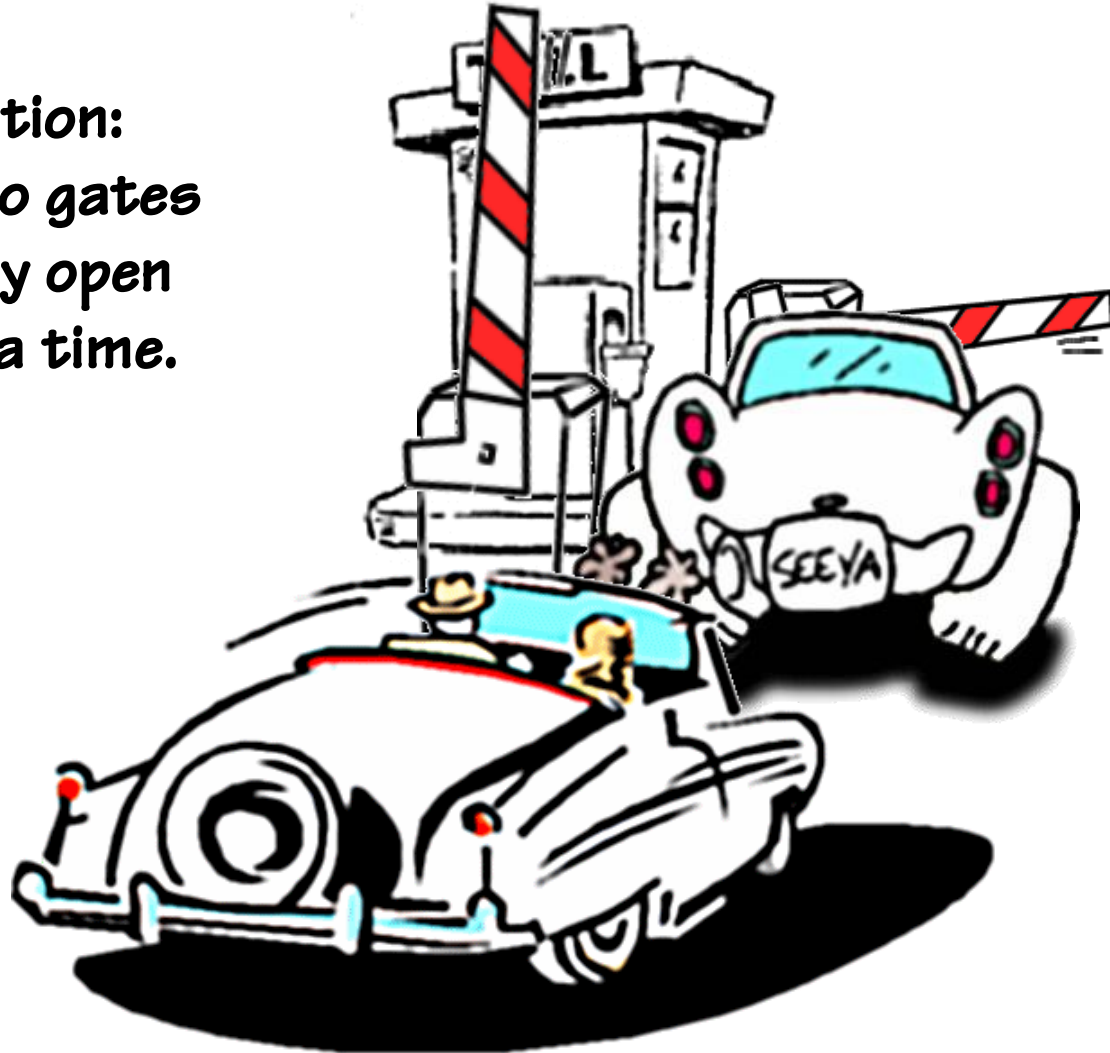The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

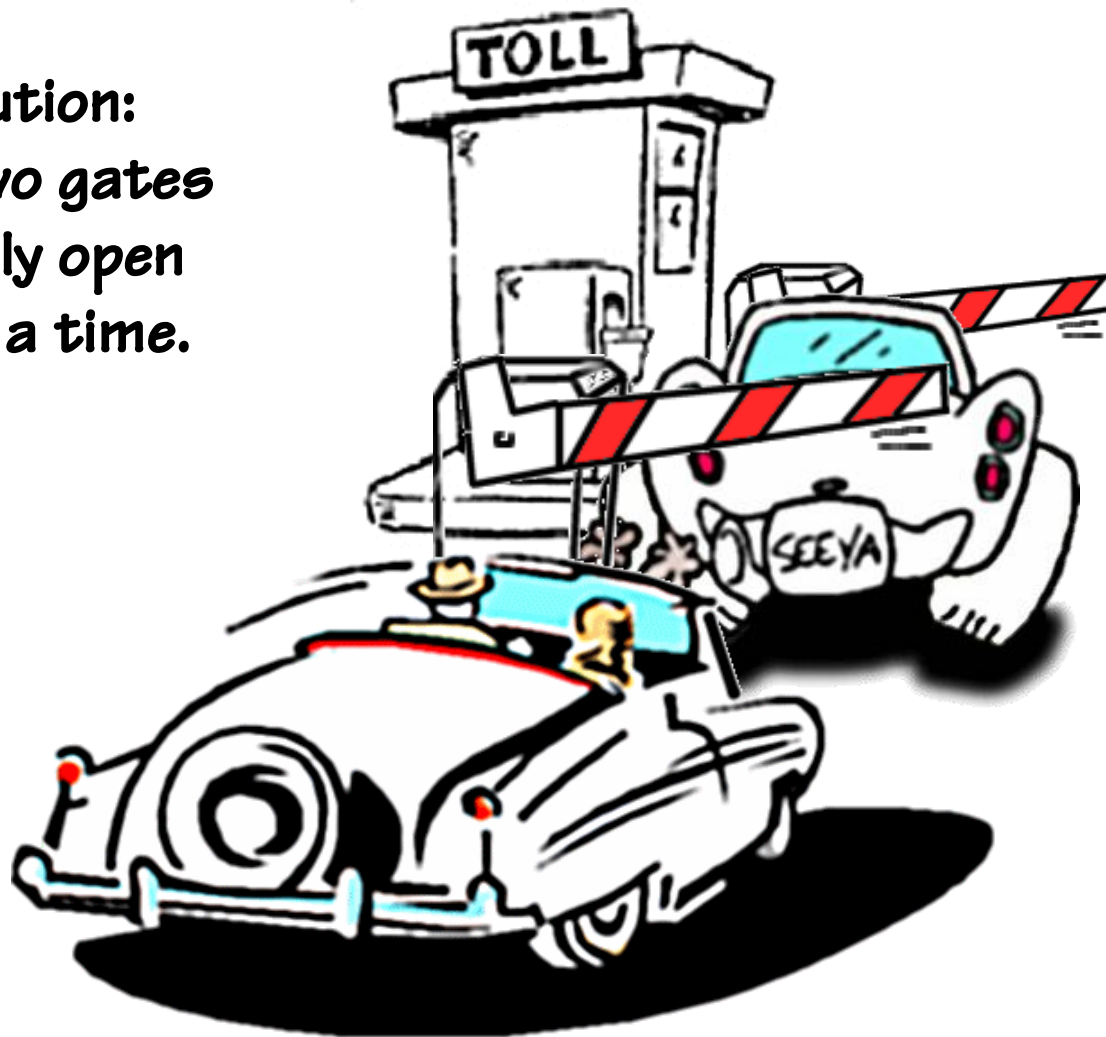The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

 The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

 The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

 The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

 The Solution:
Add two gates
and only open
one at a time.




Escapement Strategy

 The Solution:
*Add two gates
and only open
one at a time.*




Escapement Strategy

 The Solution:
*Add two gates
and only open
one at a time.*



Escapement Strategy

 The Solution:
Add two gates
and only open
one at a time.



Escapement Strategy

The Solution:
Add two gates
and only open
one at a time.



Escapement Strategy


The Solution:
Add two gates
and only open
one at a time.



KEY: At no time is there an open
path through both gates...

Edge-triggered Flip Flop

logical "escapement"

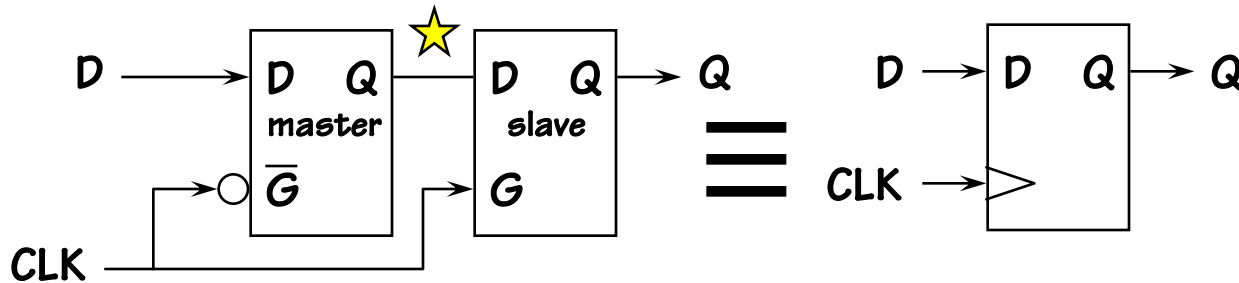



Observations:

- ♦ only one latch "transparent" at any time:
 - ♦ master closed when slave is open (CLK is high)
 - ♦ slave closed when master is open (CLK is low)→ no combinational path through flip flop
- ♦ Q only changes shortly after 0 → 1 transition of CLK, so flip flop appears to be "triggered" by rising edge of CLK


Transitions mark
instants, not
intervals



Flip Flop Waveforms

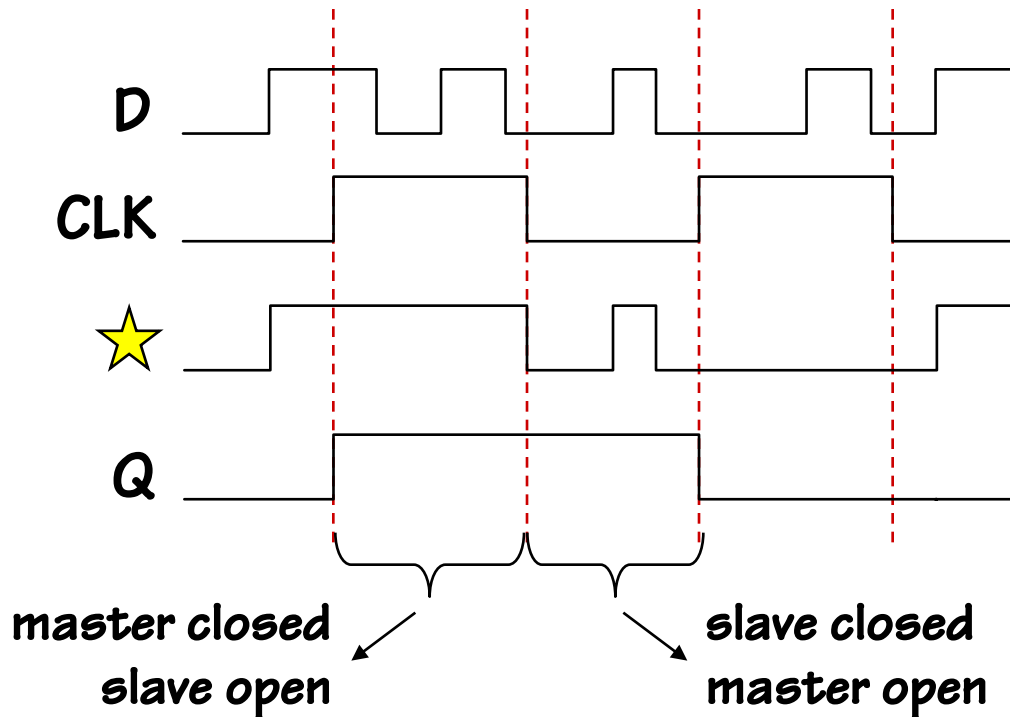
 


Two Issues


 


- Must allow time for the input's value to propagate to the Master's output while CLK is LOW.
 - This is called "SET-UP" time
- Must keep the input stable, just after CLK transitions to HIGH. This is insurance in case the SLAVE's gate opens just before the MASTER's gate closes.
 - This is called "HOLD-TIME"
 - Can be zero (or even negative!)
- Assuring "set-up" and "hold" times is what limits a computer's performance

Flip-Flop Timing Specs

 
 


Flip-Flop Timing Specs

  



t_{PD} : maximum propagation delay, CLK \rightarrow Q

Flip-Flop Timing Specs

  

t_{PD} : maximum propagation delay, CLK \rightarrow Q

Flip-Flop Timing Specs

 
 


t_{PD} : maximum propagation delay, CLK \rightarrow Q

t_{SETUP} : setup time

guarantee that D has propagated through feedback path before master closes

Flip-Flop Timing Specs

  

t_{PD} : maximum propagation delay, CLK \rightarrow Q

t_{SETUP} : setup time

guarantee that D has propagated through feedback path before master closes

t_{HOLD} : hold time

guarantee master is closed and data is stable before allowing D to change

Summary

- **Regular Arrays can be used to implement arbitrary logic functions**
 - **ROMs decode every input combination (fixed-AND array) and compute the output for it (customized-OR array)**
 - **PLAs decode an minimal set of input combinations (both AND and OR arrays customized)**
- **Memories**
 - **ROMs are HARDWIRED memories**
 - **RAMs include storage elements at each WORD-line and BIT-line intersection**
 - **dynamic memory: compact, only reliable short-term**
 - **static memory: controlled use of positive feedback**
- **Level-sensitive D-latches for static storage**
- **Dynamic discipline (setup and hold times)**