

 





Transistors, Logic, and Math

 

 - 1) The digital contract
- 2) Encoding bits with voltages
- 3) Processing bits with transistors
- 4) Gates
- 5) Truth-tables
- 6) Multiplexer Logic




CMOS Inverter

  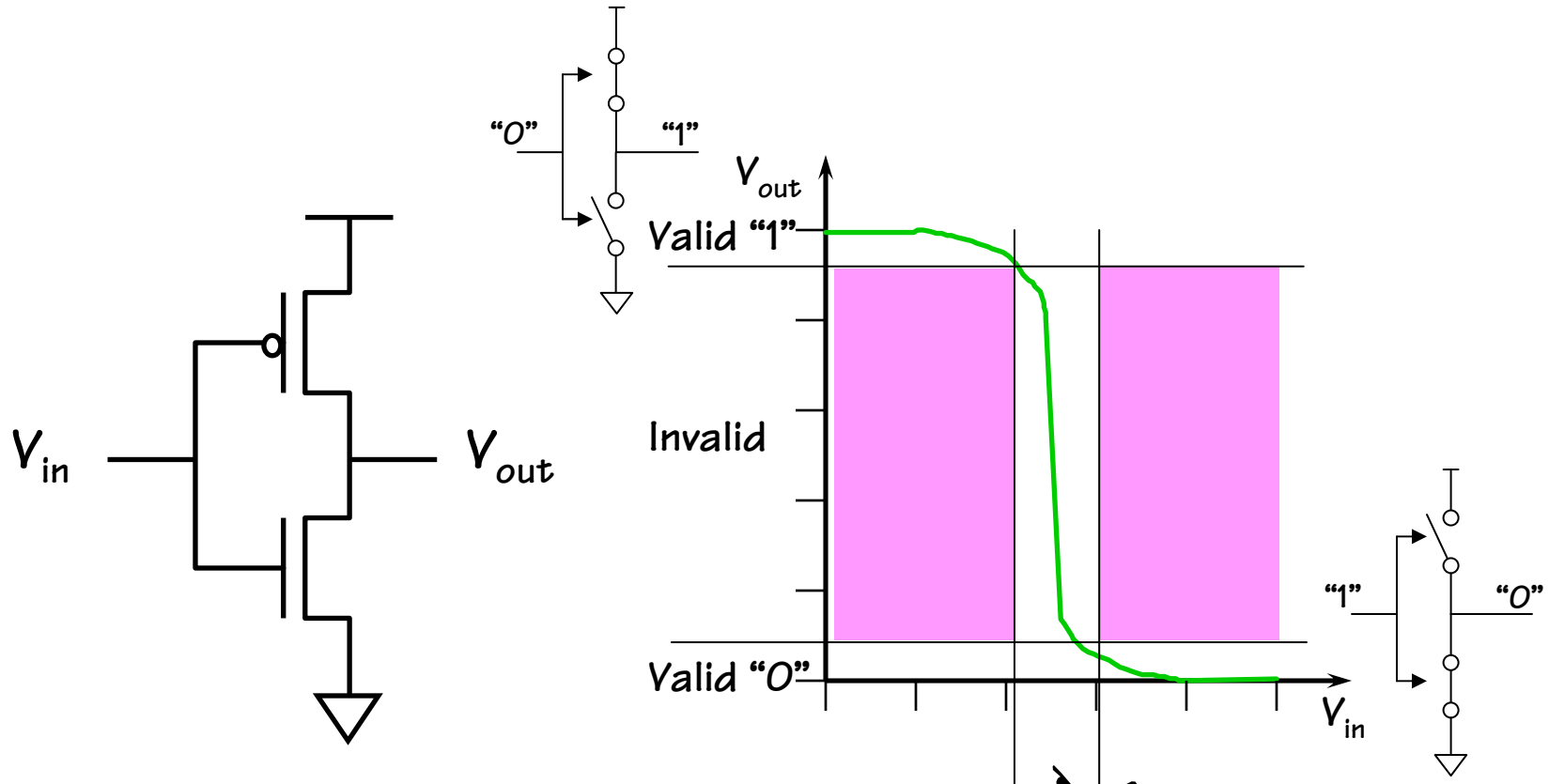

only a narrow range of input voltages result in "invalid" output values. (this diagram is greatly exaggerated)


A Two Input Logic Gate

 

What function does this gate compute?

A	B	C
0	0	
0	1	
1	0	
1	1	

Here's Another...

 


What function does this gate compute?

A	B	C
0	0	
0	1	
1	0	
1	1	

CMOS Gates Like to Invert


OBSERVATION: CMOS gates tend to be inverting!

 Precisely, one or more “0” inputs are necessary to generate a “1” output, and one or more “1” inputs are necessary to generate a “0” output. Why?



Now We're Ready to Design Stuff!

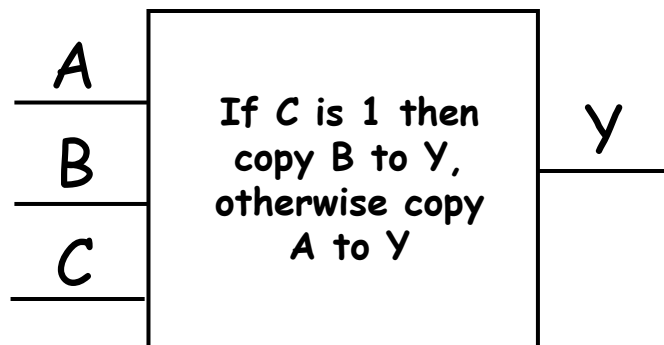We need to start somewhere -- usually it's the functional specification



Argh... I'm tired of word games



Truth Table


C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

If you are like most engineers you'd rather see a table, or formula than parse a logic puzzle. The fact is, **any combinational function can be expressed as a table.**

These "truth tables" are a concise description of the combinational system's function. Conversely, **any computation performed by a combinational system can be expressed as a truth table.**

Where Do We Start?

We have a bag of gates.

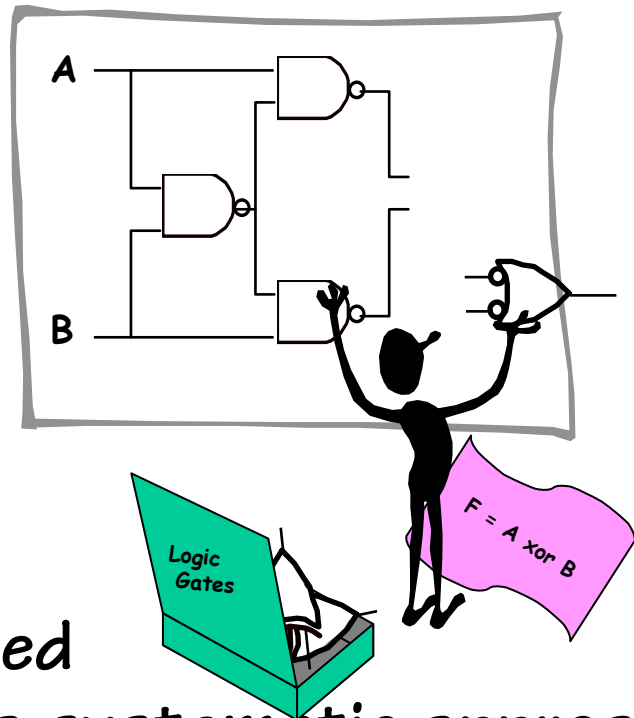

We want to
build a computer.
What do we do?

We need

... a systematic approach for designing logic

A Slight Diversion

Are we sure we have all the gates we need?

How many two-input gates are there?

AND		OR		NAND		NOR	
AB	Y	AB	Y	AB	Y	AB	Y
00	0	00	0	00	1	00	1
01	0	01	1	01	1	01	0
10	0	10	1	10	1	10	0
11	1	11	1	11	0	11	0



Hum... all of these have 2-inputs (no surprise)

... 2 inputs have 4 permutations, giving 2^2 output cases

How many permutations of 4 outputs are there? 2^4

Generalizing, there are 2^{2^N} , N-input gates!

There Are Only So Many Gates

There are only 16 possible 2-input gates

... some we know already, others are just silly

How many of these gates can be implemented using a single CMOS gate?



I N P U T A B									N O T	X O R	N O T	A N D	N O T	B O O L E A N	O R
	Z E R O	A N D	A >	B >	X O R	O R	N O T	X O R							
00	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1




Do we need all of these gates?

Nope. After all, we describe them all using AND, OR, and NOT.

We Can Make Most Gates Out of Others

B > A	
AB	Y
00	0
01	1
10	0
11	0


XOR	
AB	Y
00	0
01	1
10	1
11	0

   

How many different gates do we really need?


One Will Do!

NANDs and NORs are universal

 

Ah!, but what if we want more than 2-inputs

 I Think That I Shall Never See a Gate Lovely as a ...



N-input TREE has $O(\underline{\log N})$ levels...

Signal propagation takes $O(\underline{\log N})$ gate delays.

Here's a Design Approach

Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

1) Write out our functional spec as a truth table

2) Write down a Boolean expression for every '1' in the output

$$Y = \overline{C}BA + \overline{C}B\overline{A} + C\overline{B}\overline{A} + CBA$$

3) Wire up the gates, call it a day, and go home!

This approach will always give us logic expressions in a particular form:

SUM-OF-PRODUCTS

- it's systematic!
- it works!
- it's easy!
- we get to go home!




Straightforward Synthesis

We can implement

SUM-OF-PRODUCTS

with just three levels of
logic.


INVERTERS/AND/OR

 


Useful Gate Structures

NAND-NAND
 
$$\overline{AB} = \overline{A} + \overline{B}$$




"Pushing Bubbles"

 


DeMorgan's Laws

$$\overline{\overline{A} \overline{B}} = \overline{\overline{A+B}}$$

NOR-NOR

 
 
$$\overline{xyz} = \overline{x} + \overline{y} + \overline{z}$$




$$\overline{x+y} = \overline{xy}$$

An Interesting 3-Input Gate


Based on C, select the A or B input to be copied to the output Y.

Truth Table

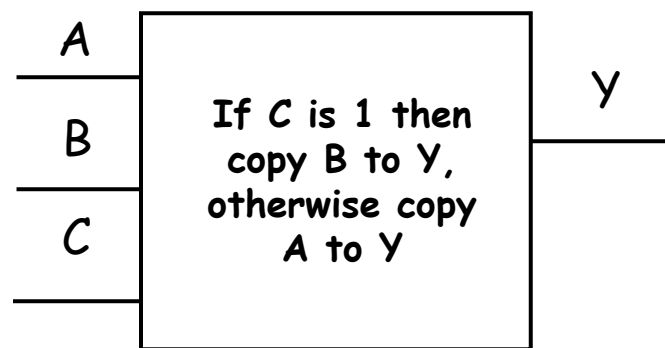


C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

2-input Multiplexer


 


schematic


 


MUX Shortcuts

A 4-input Mux
(implemented as
a tree)

  

A 4-bit wide Mux

  


Mux Logic Synthesis

Consider implementation of some arbitrary Boolean function, $F(A,B)$

... using a MULTIPLEXER as the only circuit element:

A	B	C_{in}	C_{out}
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


Full-Adder
Carry Out Logic

 

Arithmetic Circuits

Didn't I learn how to do addition in the second grade? UNC courses aren't what they used to be...
 
$$\begin{array}{r} 01011 \\ +00101 \\ \hline 10000 \end{array}$$




Finally; time to build some serious functional blocks



We'll need a lot of boxes



Review: 2's Complement

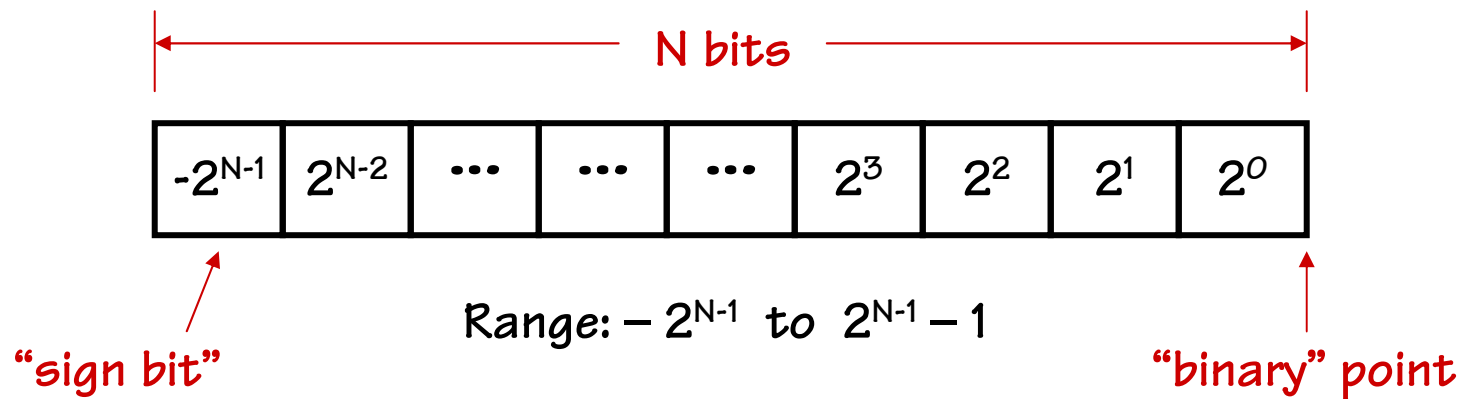

8-bit 2's complement example:

$$11010110 = -2^7 + 2^6 + 2^4 + 2^2 + 2^1 = -128 + 64 + 16 + 4 + 2 = -42$$



If we use a two's-complement representation for signed integers, the same binary addition procedure will work for adding both signed and unsigned numbers.

By moving the implicit "binary" point, we can represent fractions too:

$$1101.0110 = -2^3 + 2^2 + 2^0 + 2^{-2} + 2^{-3} = -8 + 4 + 1 + 0.25 + 0.125 = -2.625$$


Binary Addition

  Here's an example of binary addition as one might do it by "hand":



Let's start by building a block that adds one column:

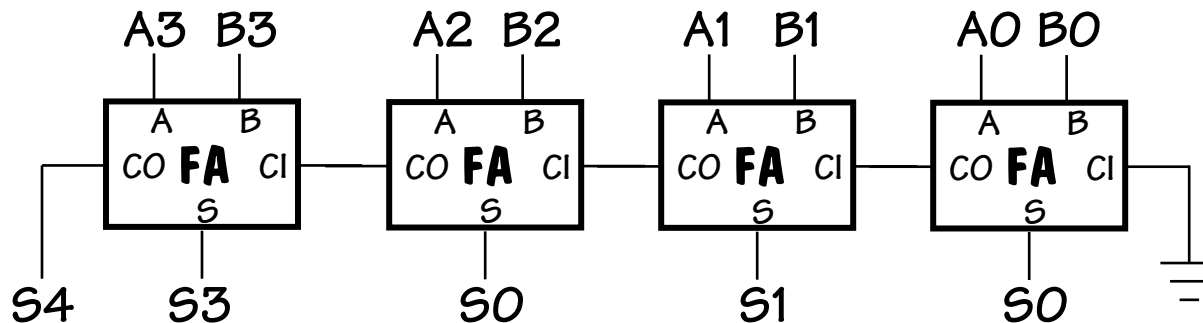Then we can cascade them to add two numbers of any size...



Designing a Full Adder: From Last Time

1) Start with a truth table:

2) Write down eqns for the "1" outputs

$$C_o = \bar{C}_i AB + C_i \bar{A} B + C_i A \bar{B} + C_i AB$$

$$S = \bar{C}_i \bar{A} B + \bar{C}_i A \bar{B} + C_i \bar{A} \bar{B} + C_i AB$$

C_i	A	B	C_o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

3) Simplifying a bit

$$C_o = C_i(A + B) + AB$$

$$S = C_i \oplus A \oplus B$$

$$C_o = C_i(A \oplus B) + AB$$


$$S = C_i \oplus (A \oplus B)$$

For Those Who Prefer Logic Diagrams ...

$$C_o = C_i(A \oplus B) + AB$$

$$S = C_i \oplus (A \oplus B)$$

- A little tricky, but only 5 gates/bit

 


Subtraction: $A - B = A + (-B)$

Using 2's complement representation: $-B = \sim B + 1$

\sim = bit-wise complement



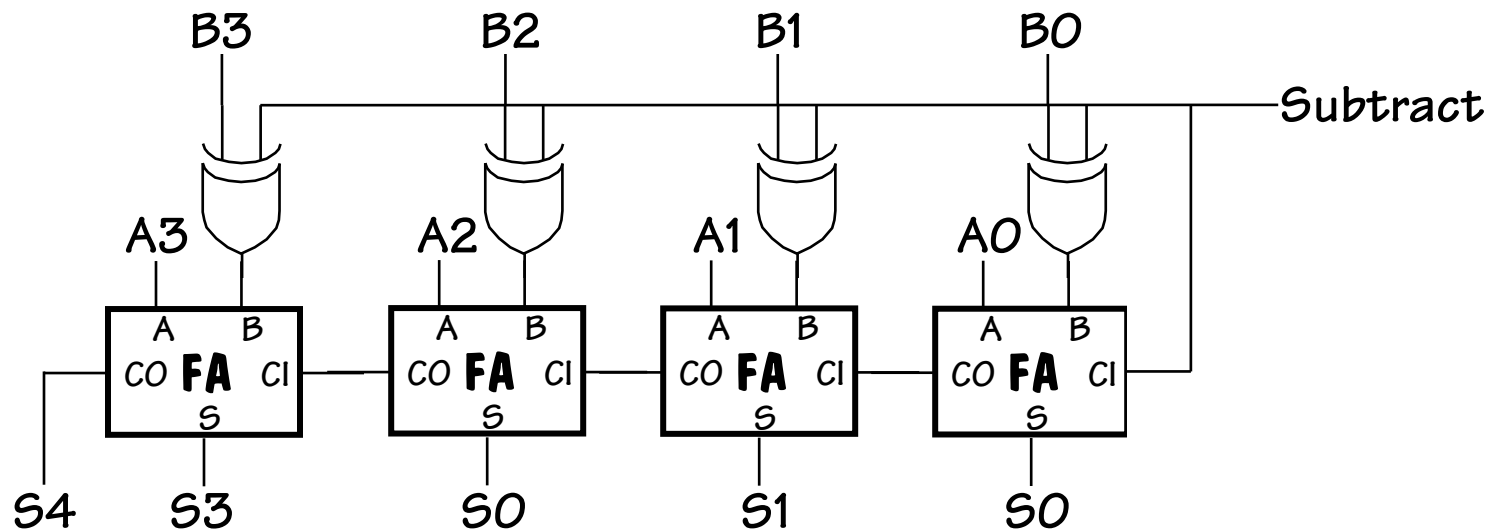So let's build an arithmetic unit that does both addition and subtraction.
Operation selected by control input:



Condition Codes

Besides the sum, one often wants four other bits of information from an arithmetic unit:

Z (zero): result is = 0 *big NOR gate*

N (negative): result is < 0 S_{N-1}

C (carry): indicates that add in the most significant position produced a carry, e.g., “1 + (-1)” *from last FA*

V (overflow): indicates that the answer has too many bits to be represented correctly by the result width, e.g., “(2ⁱ⁻¹ - 1) + (2ⁱ⁻¹ - 1)”

$$V = A_{i-1} B_{i-1} \overline{N} + \overline{A}_{i-1} \overline{B}_{i-1} N$$

-or-

$$V = C_{i-1} \oplus Q_{i-1}$$

To compare A and B, perform A-B and use condition codes:


Signed comparison:

LT	$N \oplus V$
LE	$Z + (N \oplus V)$
EQ	Z
NE	$\sim Z$
GE	$\sim (N \oplus V)$
GT	$\sim (Z + (N \oplus V))$

Unsigned comparison:


LTU	C
LEU	$C + Z$
GEU	$\sim C$
GTU	$\sim (C + Z)$

T_{PD} of Ripple-Carry Adder

 

Worse-case path: carry propagation from LSB to MSB, e.g., when adding 11...111 to 00...001.

 
$$t_{PD} = \underbrace{(t_{PD,XOR} + t_{PD,AND} + t_{PD,OR})}_{A,B \text{ to } CO} + \underbrace{(N-2) \cdot (t_{PD,OR} + t_{PD,AND})}_{CI \text{ to } CO} + \underbrace{t_{PD,XOR}}_{CI_{N-1} \text{ to } S_{N-1}} \approx \Theta(N)$$




$\Theta(N)$ is read “order N” and tells us that the latency of our adder grows in proportion to the number of bits in the operands.

Adder Summary

 Adding is not only a common, but it also tends to be one of the most time-critical of operations. As a result, a wide range of adder architectures have been developed that allow a designer to tradeoff complexity (in terms of the number of gates) for performance.



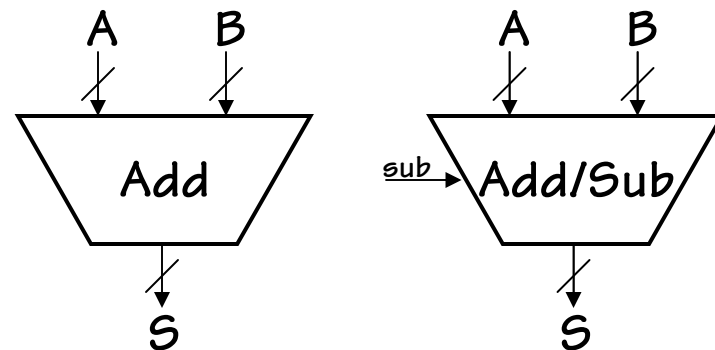At this point we'll define a high-level functional unit for an adder, and specify the details of the implementation as necessary.



Shifting Logic

Shifting is a common operation that is applied to groups of bits. Shifting can be used for alignment, as well as for arithmetic operations.

$X \ll 1$ is approx the same as $2 * X$

$X \gg 1$ can be the same as $X / 2$

For example:

$$X = 20_{10} = 00010100_2$$

Left Shift:


$$(X \ll 1) = 00101000_2 = 40_{10}$$

Right Shift:

$$(X \gg 1) = 00001010_2 = 10_{10}$$

Signed or "Arithmetic" Right Shift:
 
$$(-X \gg 1) = (11101100_2 \gg 1) = 11110110_2 = -10_{10}$$



Boolean Operations

It will also be useful to perform logical operations on groups of bits.
Which ones?

ANDing is useful for “masking” off groups of bits.

ex. $10101110 \& 00001111 = 00001110$ (mask selects last 4 bits)

ANDing is also useful for “clearing” groups of bits.

ex. $10101110 \& 00001111 = 00001110$ (0's clear first 4 bits)

ORing is useful for “setting” groups of bits.

ex. $10101110 | 00001111 = 10101111$ (1's set last 4 bits)

XORing is useful for “complementing” groups of bits.

ex. $10101110 \wedge 00001111 = 10100001$ (1's complement last 4 bits)


NORing is useful.. Uhm, because John Hennessy says it is!

ex. $10101110 \# 00001111 = 01010000$ (0's complement, 1's clear)

Boolean Unit

It is simple to build up a Boolean unit using primitive gates and a mux to select the function.

 Since there is no interconnection between bits, this unit can be simply replicated at each position. The cost is about 7 gates per bit. One for each primitive function, and approx 3 for the 4-input mux.



This is a straightforward, but not too elegant of a design.

An ALU, at Last

Now we're ready for a big one! An Arithmetic Logic Unit.

