

# Triangle Technology Executive Panel

*Learn what companies  
are looking for in  
employees*

Friday, 2 March  
3:30 p.m.

*Network*

Sitterson 014

For more info, see

*Find out  
about local  
businesses*

*Ask questions  
about the  
industry*

<http://www.cs.unc.edu/~pozefsky/TTECPanel.html>



Capital Analytics



# Help with Pete's user study

Interested in mobile audio?

Help us evaluate an auditory computer interface!

All participants will be paid \$20.00 upon completion of the study.

<http://www.cs.unc.edu/~parente/cliq/eval.html>


Contact: Peter Parente <parente@cs.unc.edu>

# Binary Multipliers

The key trick of multiplication is memorizing a digit-to-digit table...  
Everything else was just adding

x	0	1	2	3	4	5	6	7	8	9
0	0	0	0	0	0	0	0	0	0	0
1	0	1	2	3	4	5	6	7	8	9
2	0	2	4	6	8	10	12	14	16	18
3	0	3	6	9	12	15	18	21	24	27
4	0	4	8	12	16	20	24	28	32	36
5	0	5	10	15	20	25	30	35	40	45
6	0	6	12	18	24	30	36	42	48	54
7	0	7	14	21	28	35	42	49	56	63
8	0	8	16	24	32	40	48	56	64	72
9	0	9	18	27	36	45	54	63	72	81

x	0	1
0	0	0
1	0	1

 

You've got to be kidding... It can't be that easy

Reading: Study Chapter 3.

# Binary Multiplication

The "Binary" Multiplication Table

X	0	1
0	0	0
1	0	1

Hey, that looks like an AND gate



Binary multiplication is implemented using the same basic longhand algorithm that you learned in grade school.

$$\begin{array}{r} A_3 \quad A_2 \quad A_1 \quad A_0 \\ \times B_3 \quad B_2 \quad B_1 \quad B_0 \\ \hline \end{array}$$



$A_j B_i$  is a "partial product"  $\longrightarrow$

$$\begin{array}{r} A_3 B_0 \quad A_2 B_0 \quad A_1 B_0 \quad A_0 B_0 \\ A_3 B_1 \quad A_2 B_1 \quad A_1 B_1 \quad A_0 B_1 \\ A_3 B_2 \quad A_2 B_2 \quad A_1 B_2 \quad A_0 B_2 \\ + A_3 B_3 \quad A_2 B_3 \quad A_1 B_3 \quad A_0 B_3 \\ \hline \end{array}$$



Multiplying N-digit number by M-digit number gives (N+M)-digit result

Easy part: forming partial products (just an AND gate since  $B_i$  is either 0 or 1)  
 Hard part: adding M, N-bit partial products

# Multiplication: Implementation

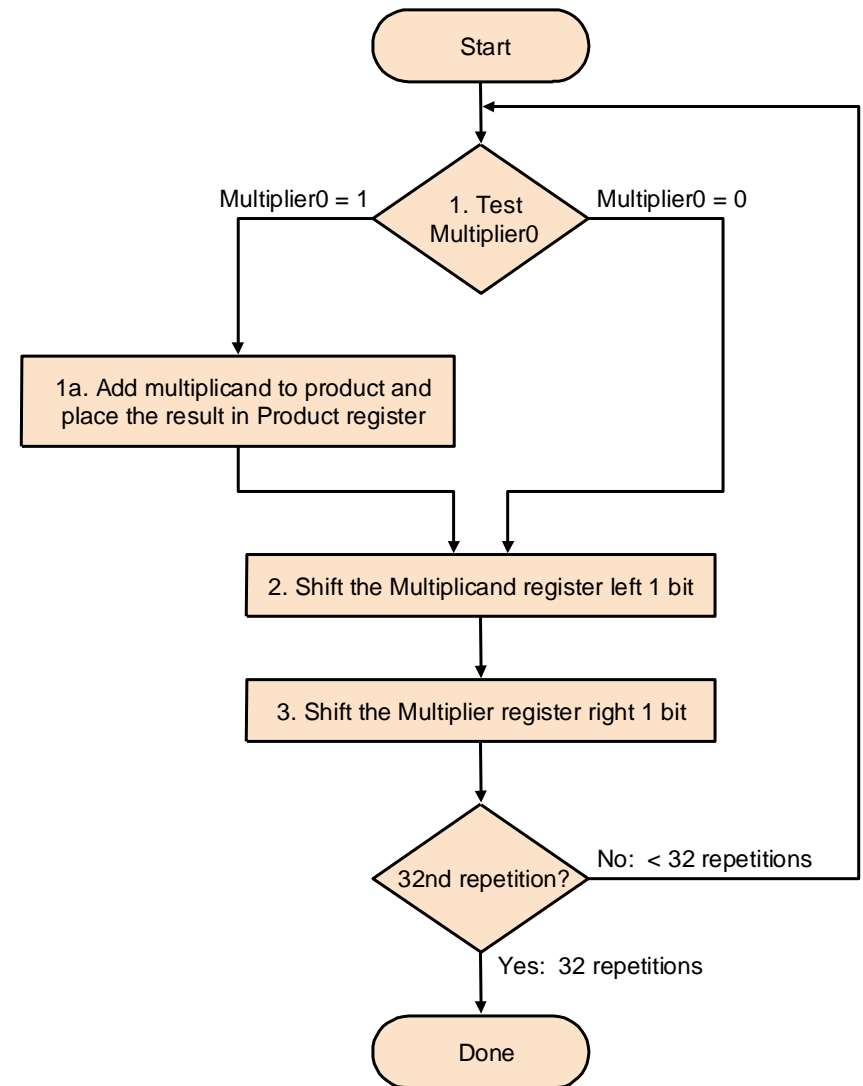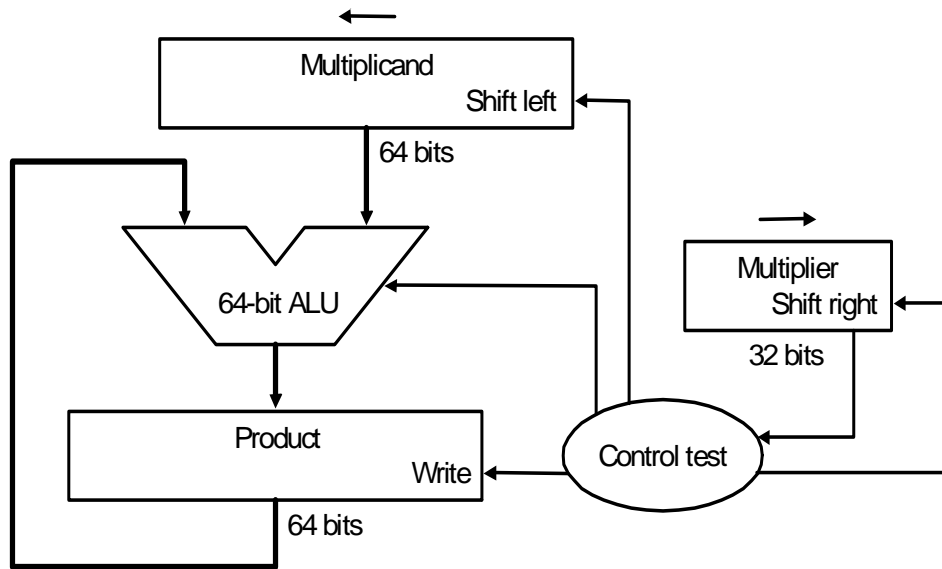


# Second Version

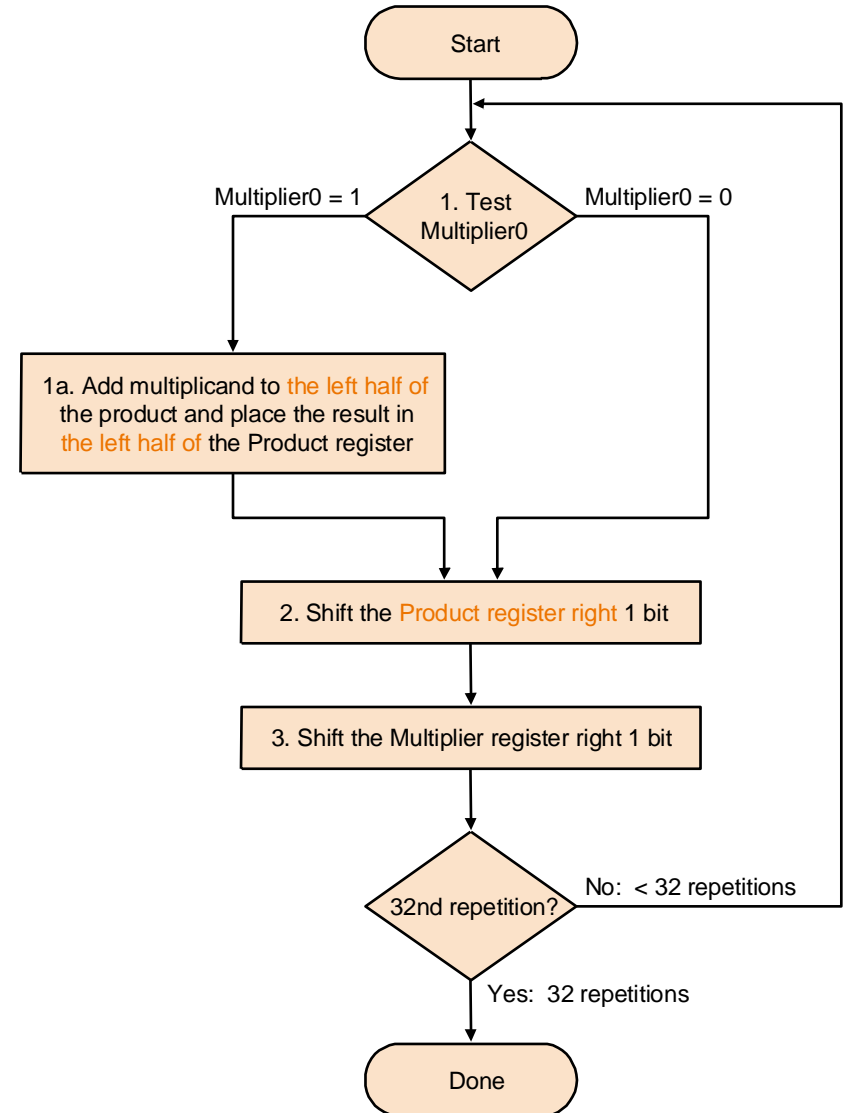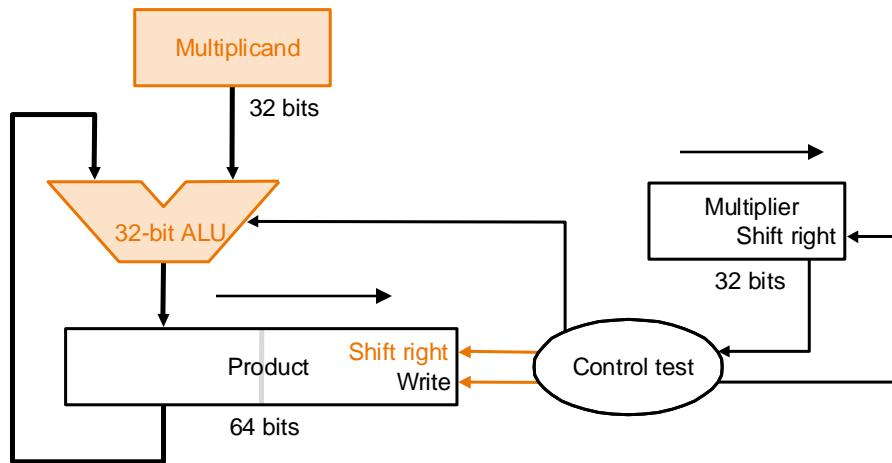


# Example for second version

Iteration	Step	Multiplier	Multiplicand	Product
0	Initial	1011	0010	0000 0000
1	Test true shift right	1011 0101	0010	0010 0000 0001 0000
2	Test true shift right	0101 0010	0010	0011 0000 0001 1000
3	Test false shift right	0010 0001	0010	0001 1000 0000 1100
4	Test true shift right	0001 0000	0010	0010 1100 0001 0110

# Final Version

 

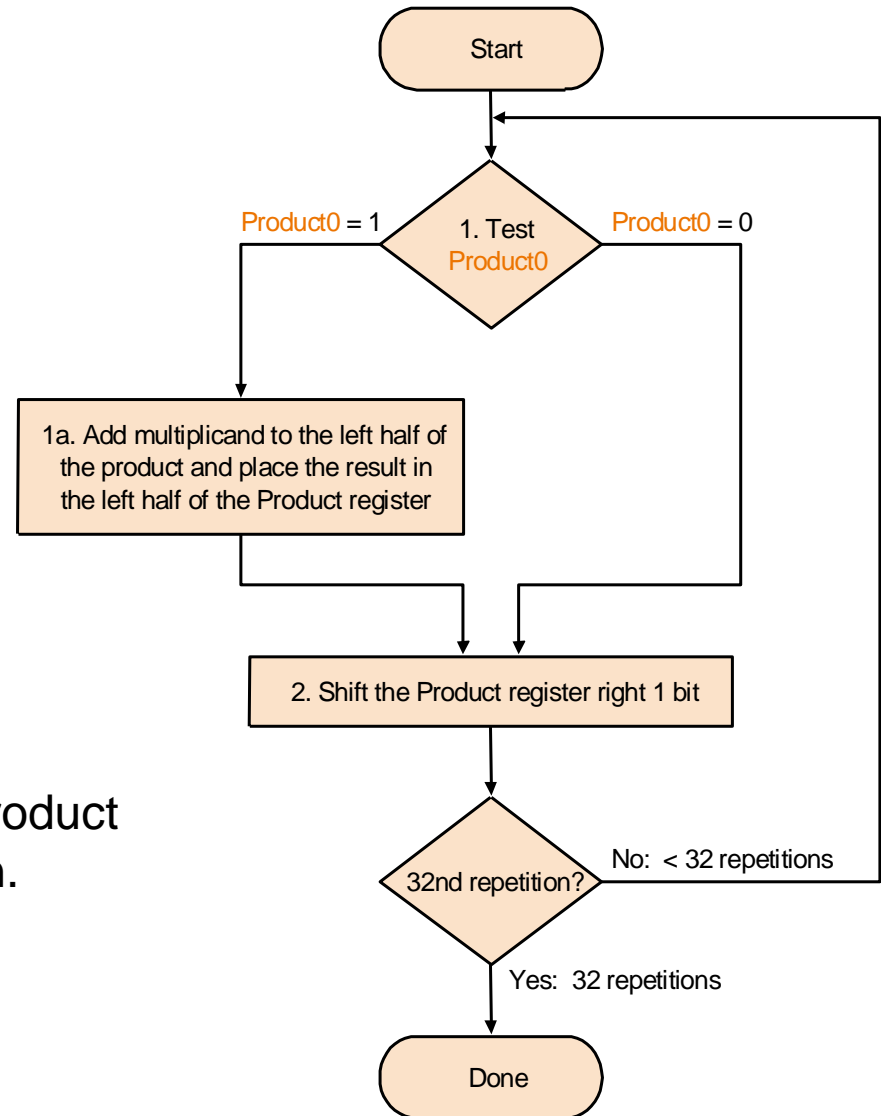The trick is to use the lower half of the product to hold the multiplier during the operation.






# What about the sign?

Positive numbers are *easy*.

How about negative numbers?

# Faster Multiply

See Booth coding in the book.

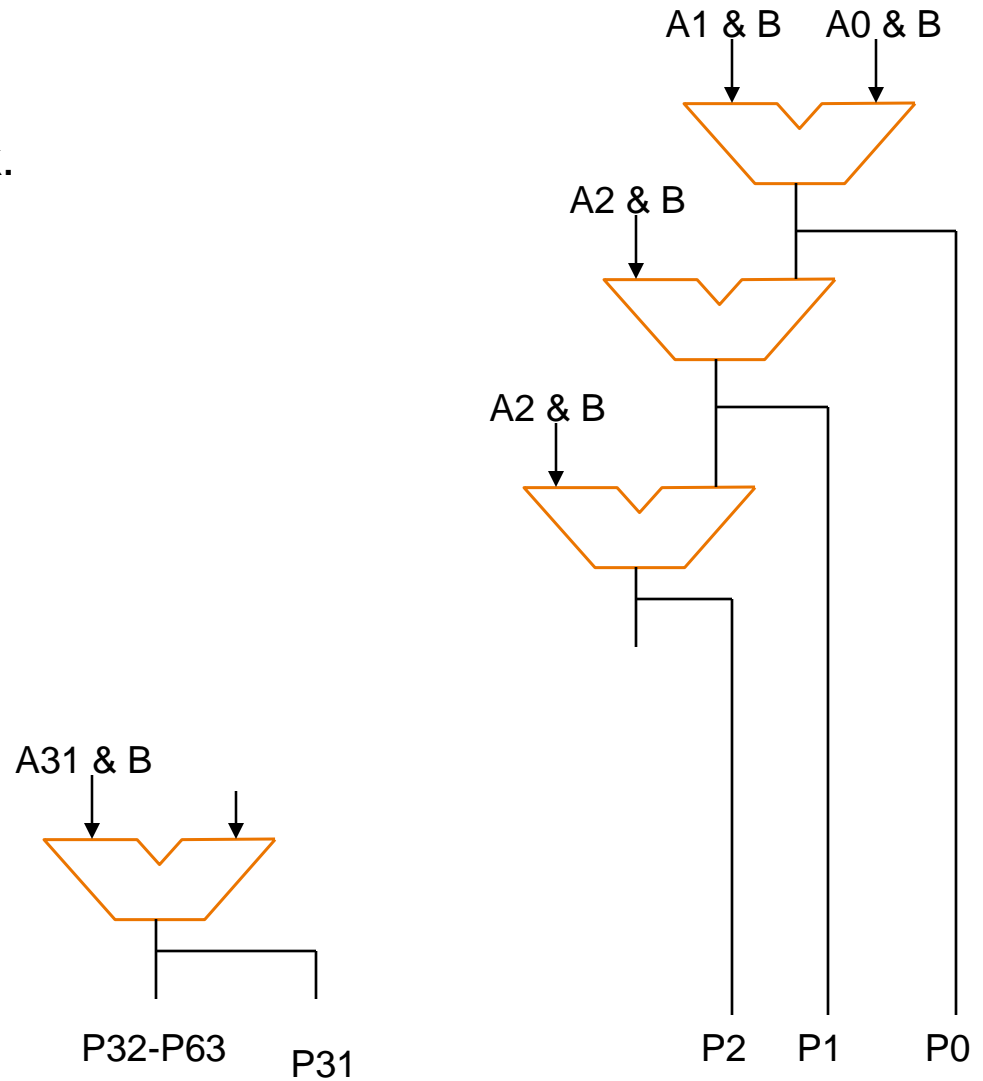

# Division

