

Control

Only 12 classes to go!

John Backus dead at 82


Phase-change Flash memory

Today Control

Next-time Quiz review


John Backus

3 December 1924 – 17 March 2007

 


As project leader with IBM John Backus developed in the early 1950's with his team: Fortran - Formula Translator. The first high level programming language. This language is most widely used in physics and engineering.

Phase-Change Flash Memory

 


Synchronous Systems

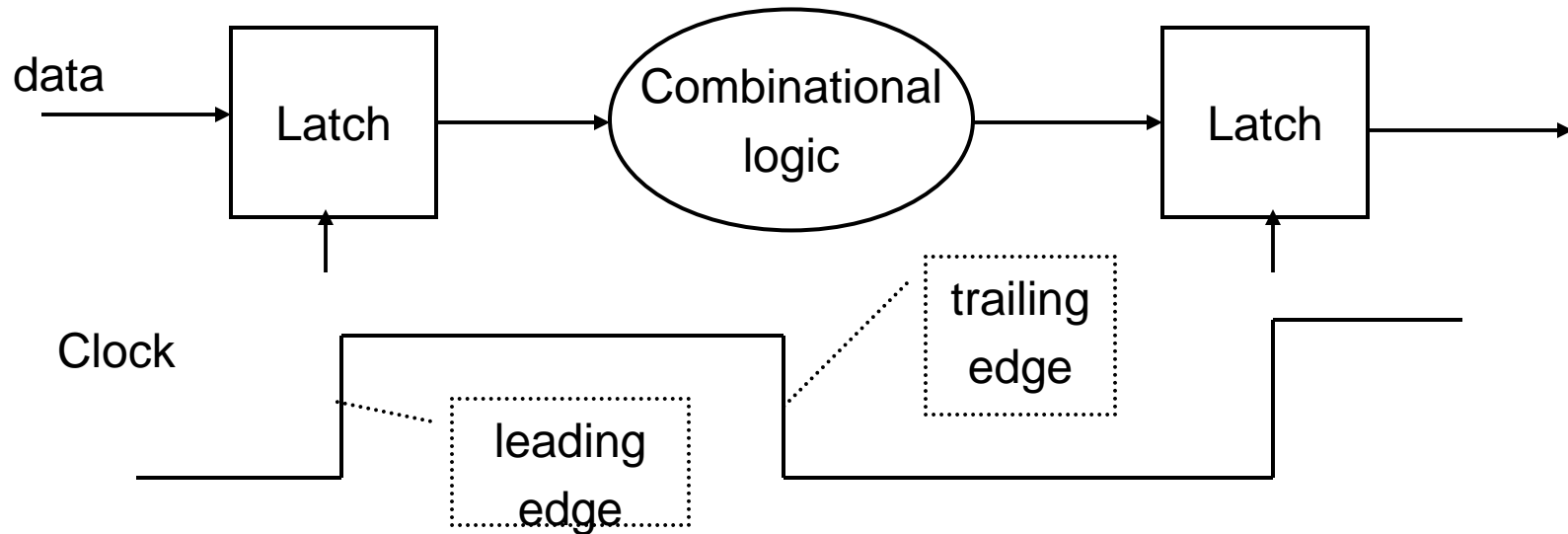

On the leading edge of the clock, the input of a latch is transferred to the output and held.

We must be sure the combinational logic has *settled* before the next leading clock edge.

Asynchronous Systems

 

No clock!


The data carries a “valid” signal along with it

System goes at greatest possible speed.

Only “computes” when necessary.


Everything we look at will be synchronous

Fetching Sequential Instructions

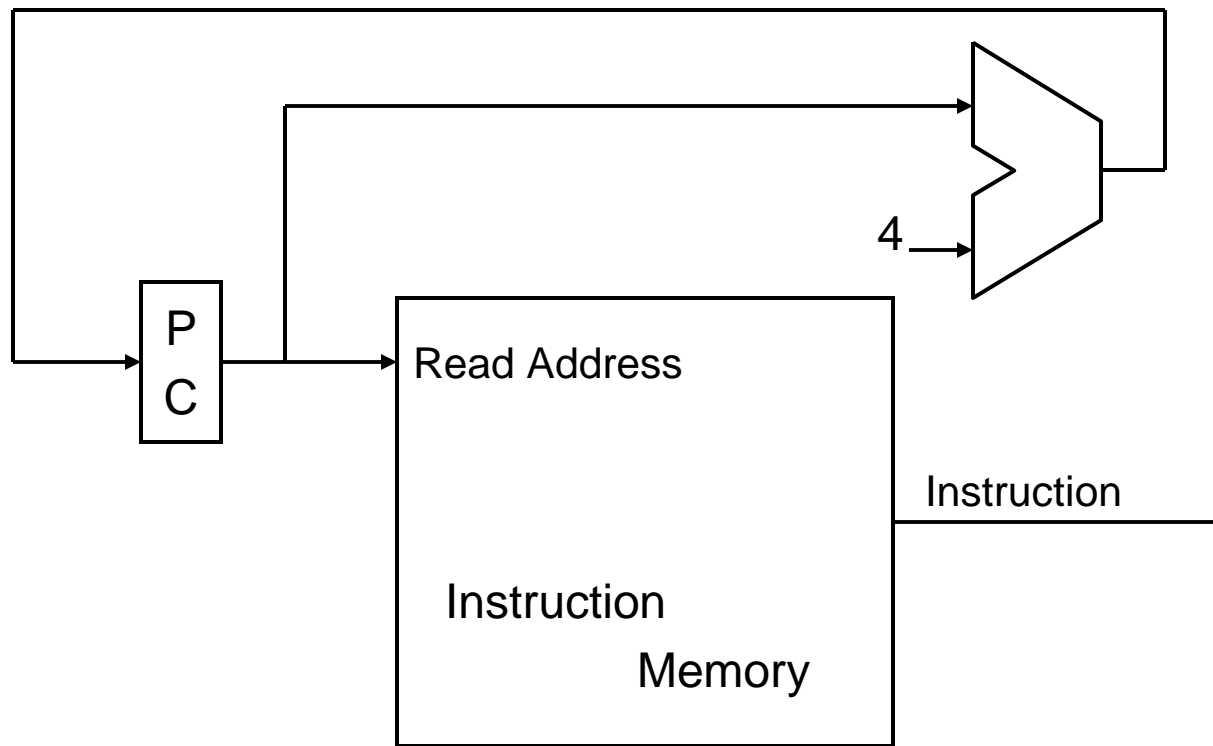


How about branch?

Datapath for R-type Instructions

 


Fun with MUXes

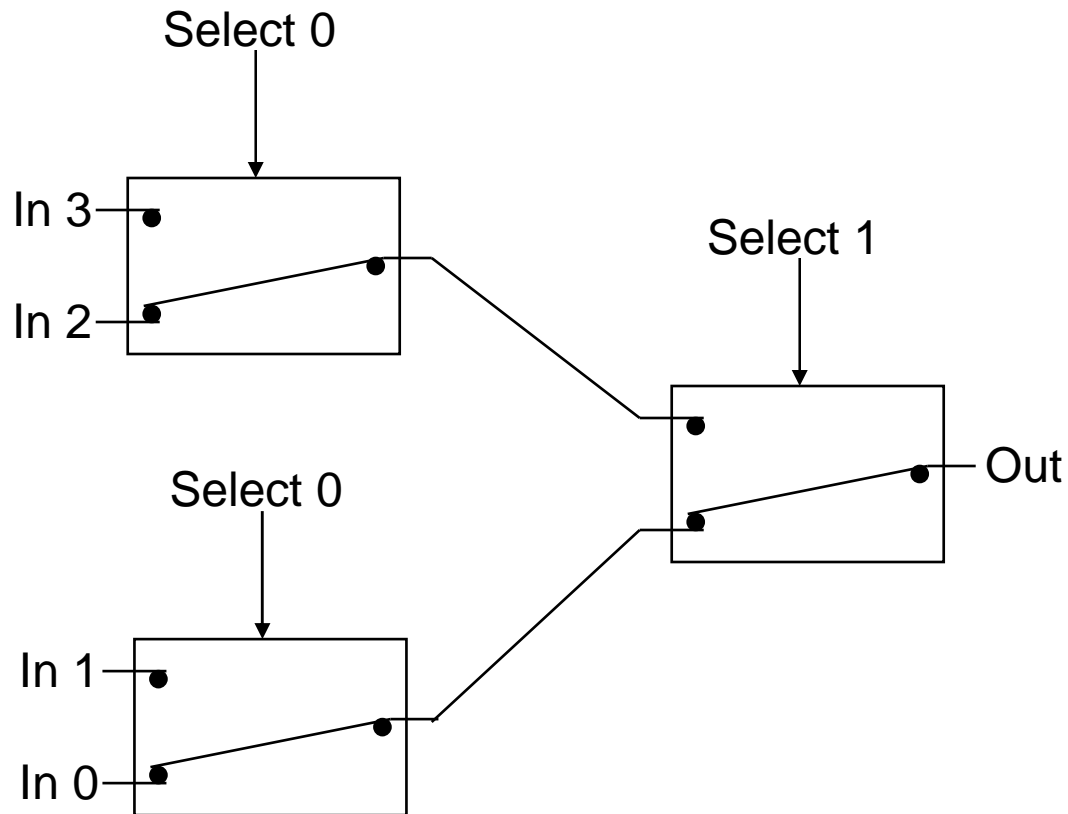

Remember the MUX?


This will route 1 of 4 different 1 bit values to the output.

MUX Blocks

 

The select signal determines which of the inputs is connected to the output

Inside there is a 32 way MUX per bit

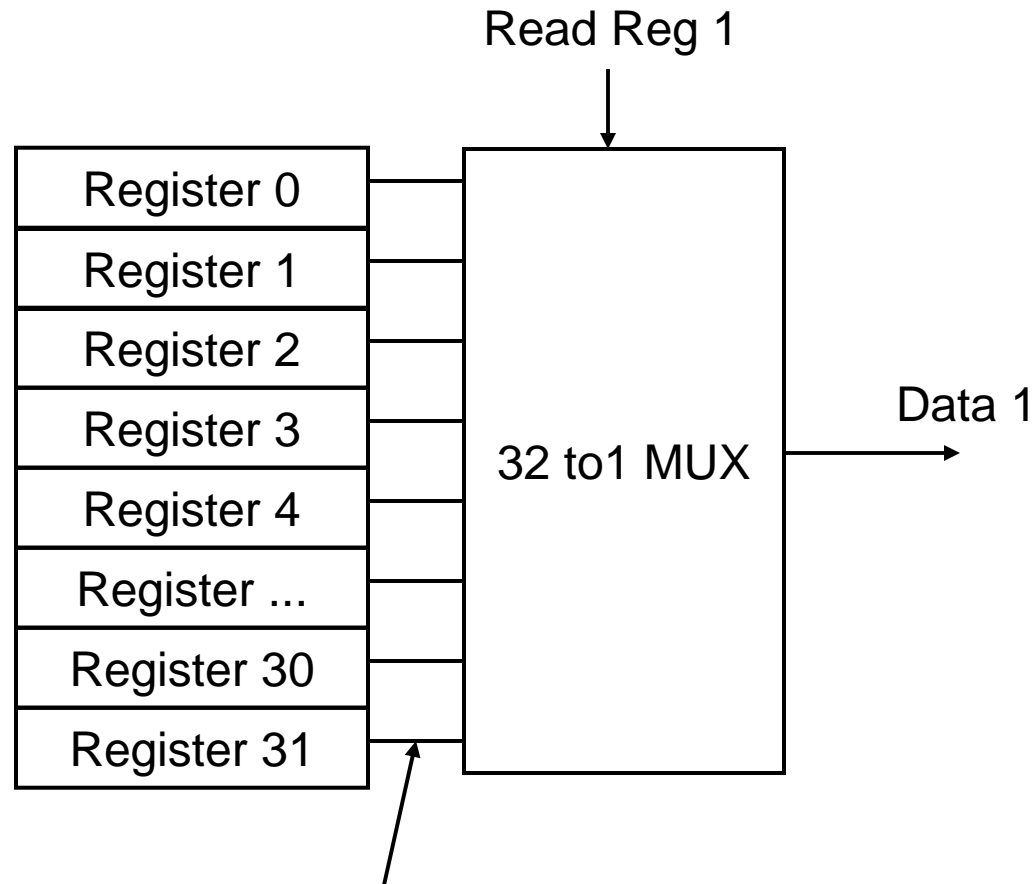


For EACH bit in the 32 bit register

LOT'S OF
CONNECTIONS!

And this is just one port!


Our Register File has 3 ports

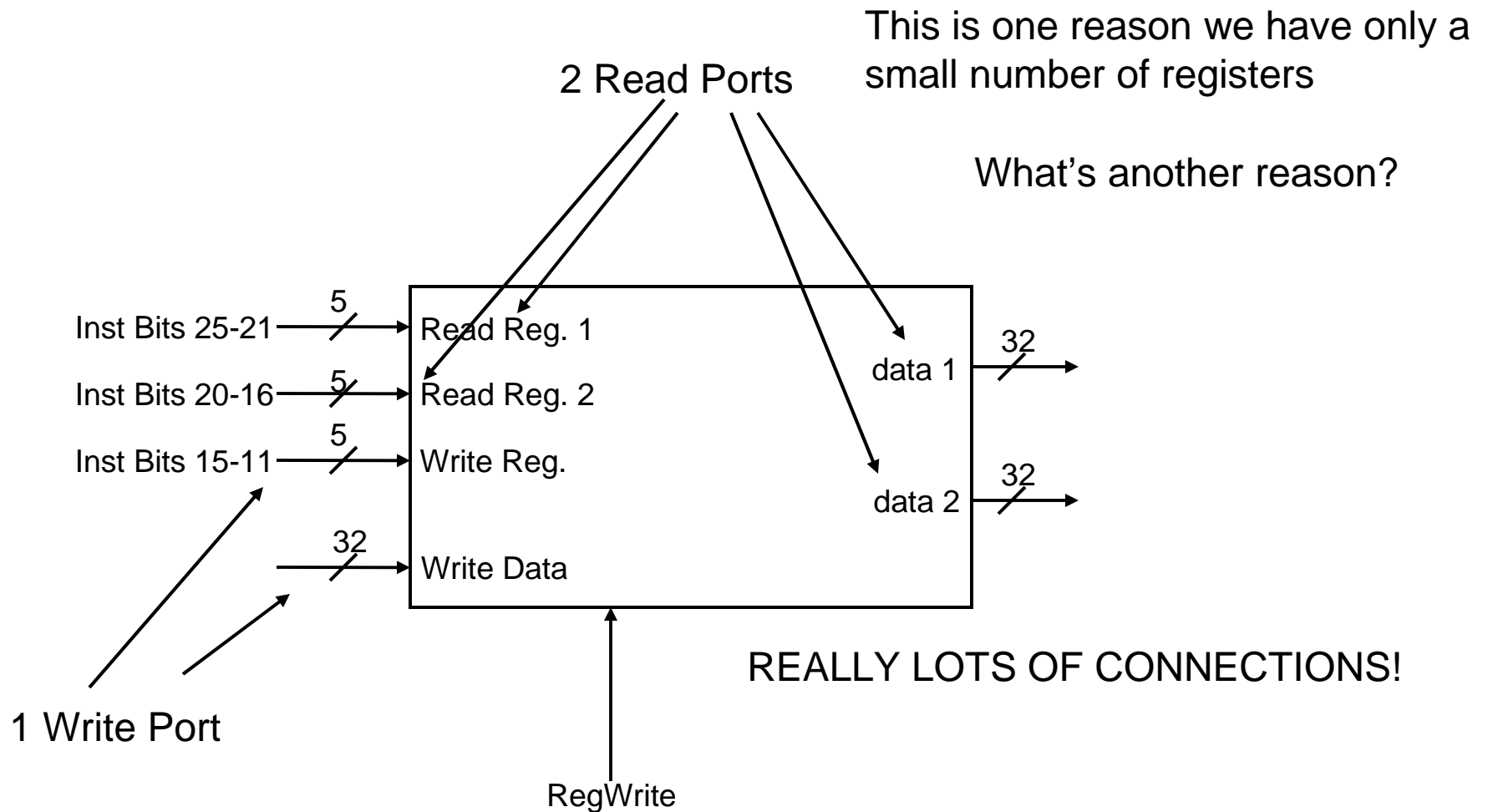


Implementing Logical Functions

Suppose we want to map M input bits to N output bits

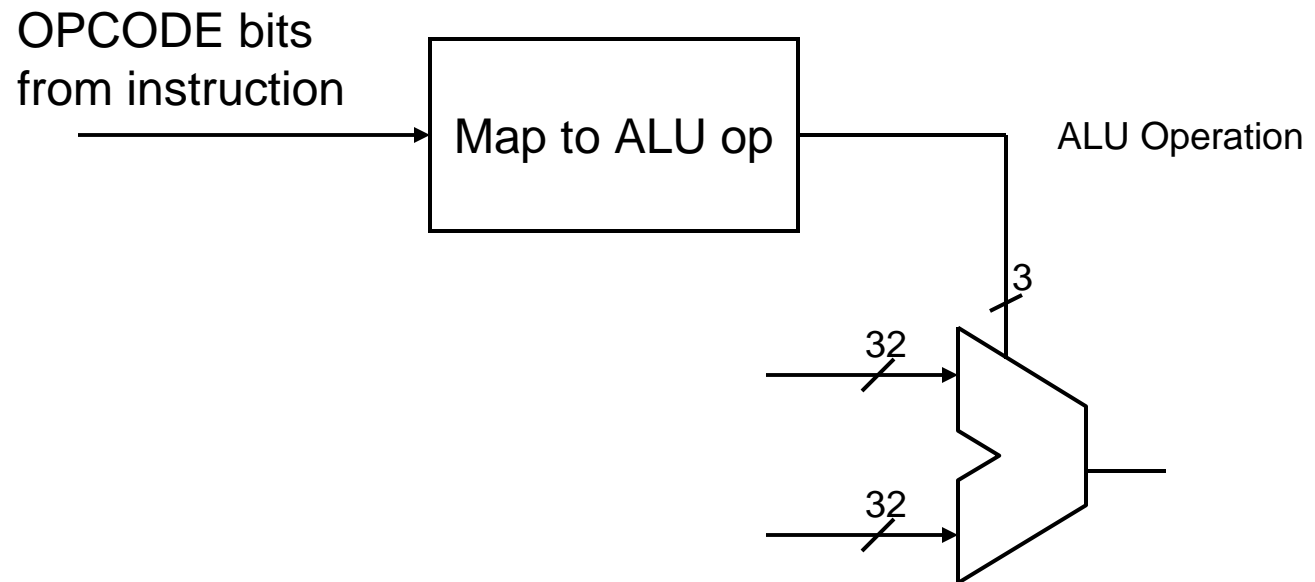For example, we need to take the OPCODE field from the instruction and determine what OPERATION to send to the ALU.




We can get 1 bit out with a MUX

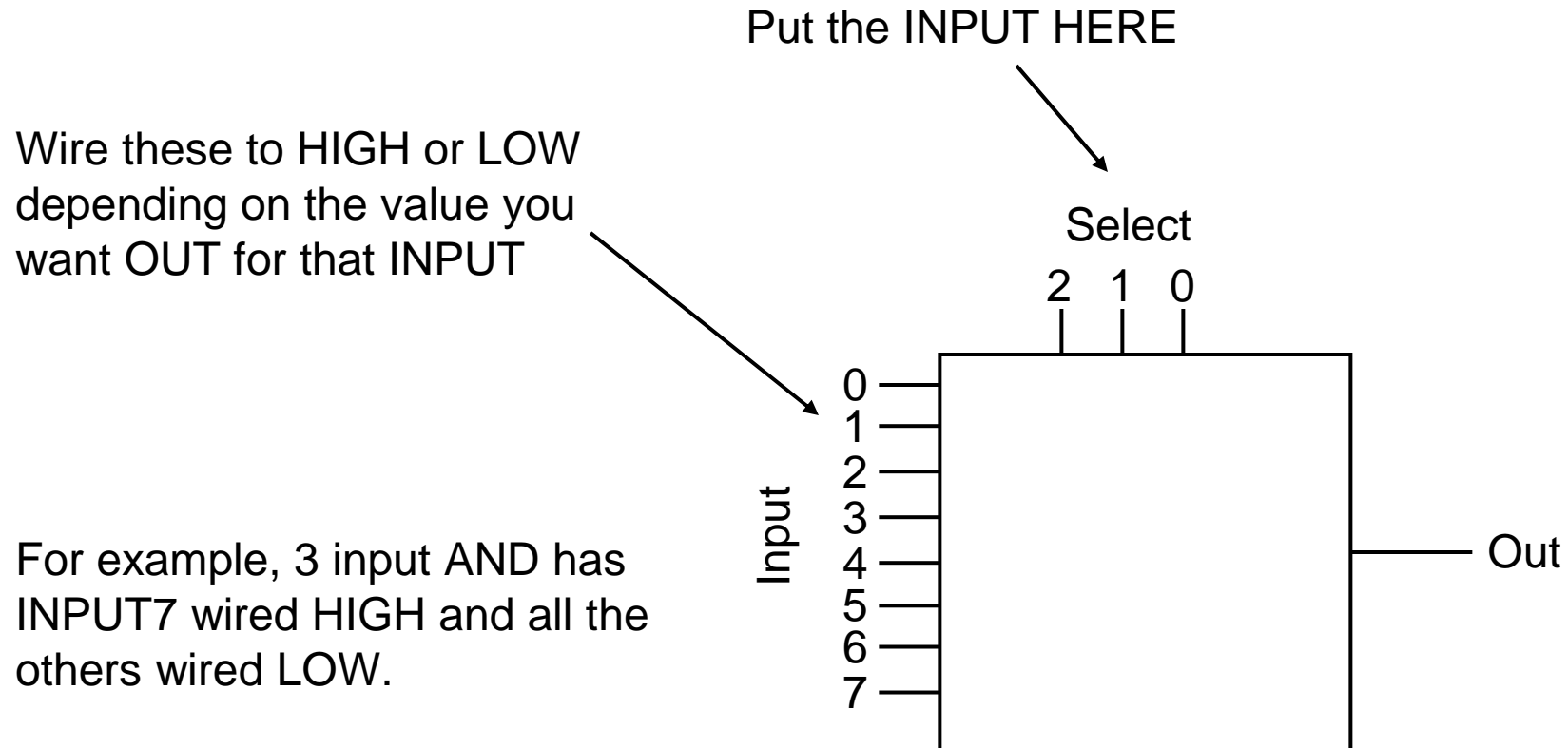


For example, 3 input AND has INPUT7 wired HIGH and all the others wired LOW.

Or use a ROM

 

Or use a PLA

Programmable Logic Array

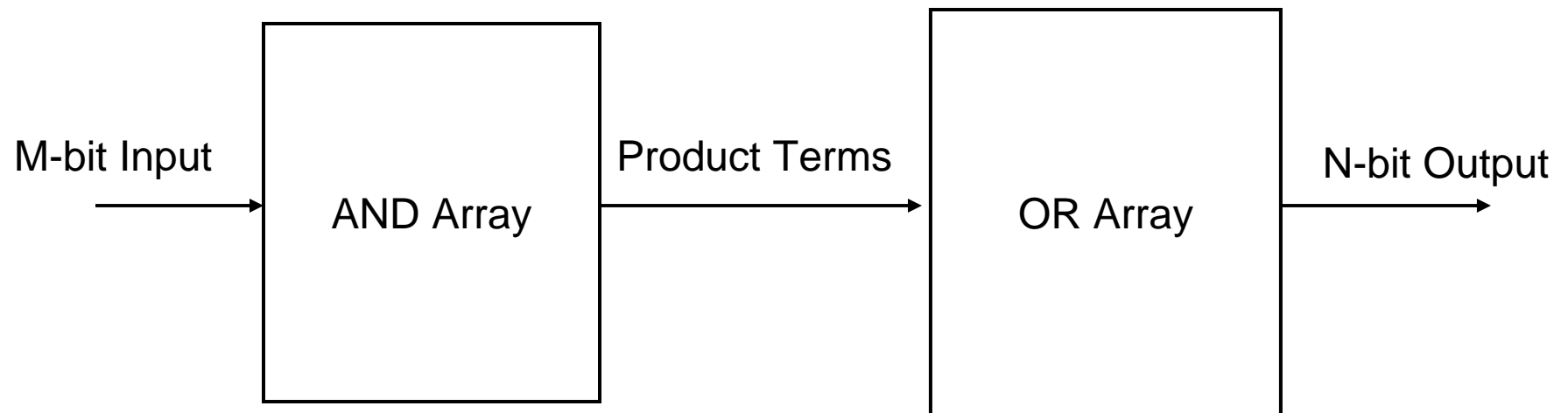

Think of the SUM of PRODUCTS form.

The AND Array generates the products of various input bits


The OR Array combines the products into various outputs

Finite State Machines


- A set of STATES
- A set of INPUTS
- A set of OUTPUTS
- A function to map the STATE and the INPUT into the next STATE and an OUTPUT

Remember “Shoots and Ladders”?

Traffic Light Controller

 

Implementing a FSM

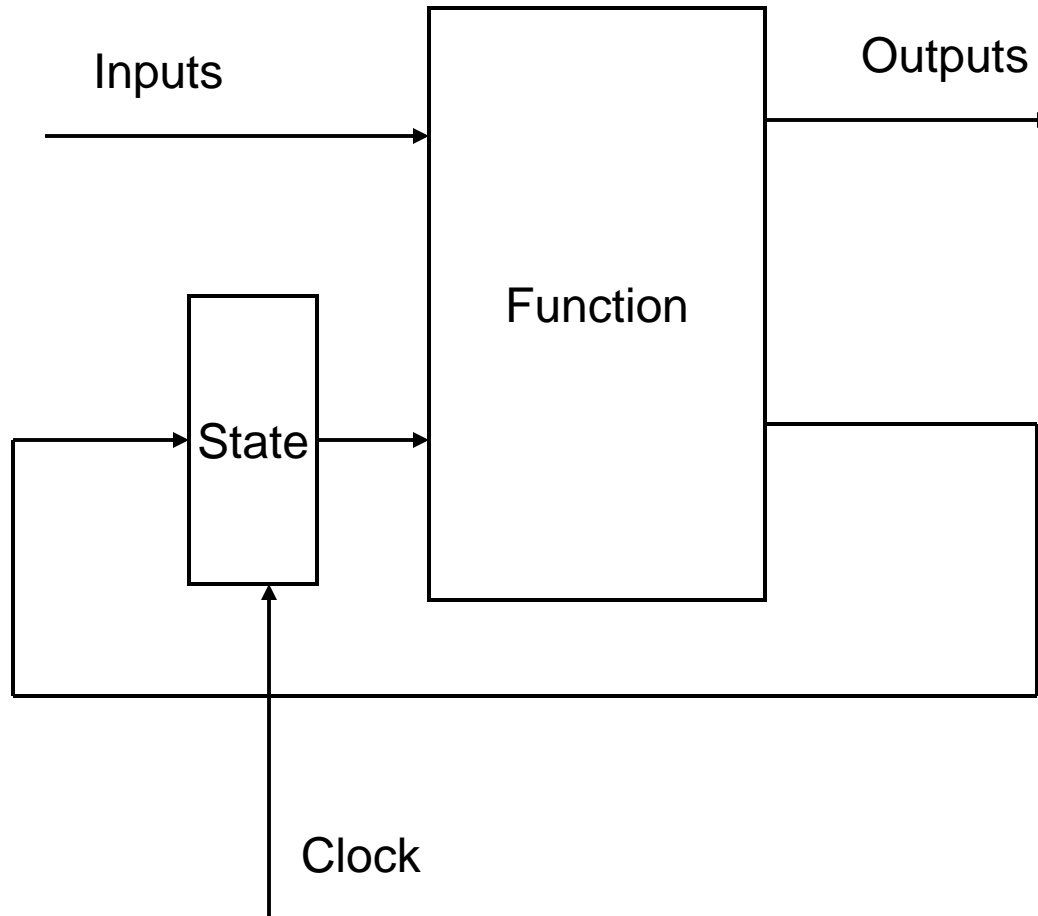

Recognizing Numbers

Recognize the regular expression for floating point numbers

$[\backslash t]^* [-+]? [0-9]^* (. [0-9]^*)? (e[-+]? [0-9]^+)?$

Examples:

+123.456e23

.456

1.5e-10

-123

“a” matches itself


“[abc]” matches one of a, b, or c

“[a-z]” matches one of a, b, c, d, ..., x, y, or z

“0*” matches zero or more 0’s (“”, “0”, “00”, “0000”)

“Z?” matches zero or 1 Z’s

FSM Diagram

 

FSM Table

IN : STATE à NEW STATE

' ' : start à start

'0' | '1' | ... | '9' : start à whole

'+' | '-' : start à sign

'.' : start à frac

'0' | '1' | ... | '9' : sign à whole

'.' : sign à frac

'0' | '1' | ... | '9' : whole à whole

'.' : whole à frac

' ' : whole à done

'e' : whole à exp

'e' : frac à exp

'0' | '1' | ... | '9' : frac à frac

' ' : frac à done

'0' | '1' | ... | '9' : exp à exp

' ' : exp à done

STATE ASSIGNMENTS

start = 0 = 000

sign = 1 = 001

whole = 2 = 010


frac = 3 = 011

exp = 4 = 100

done = 5 = 101

error = 6 = 110

FSM Implementation

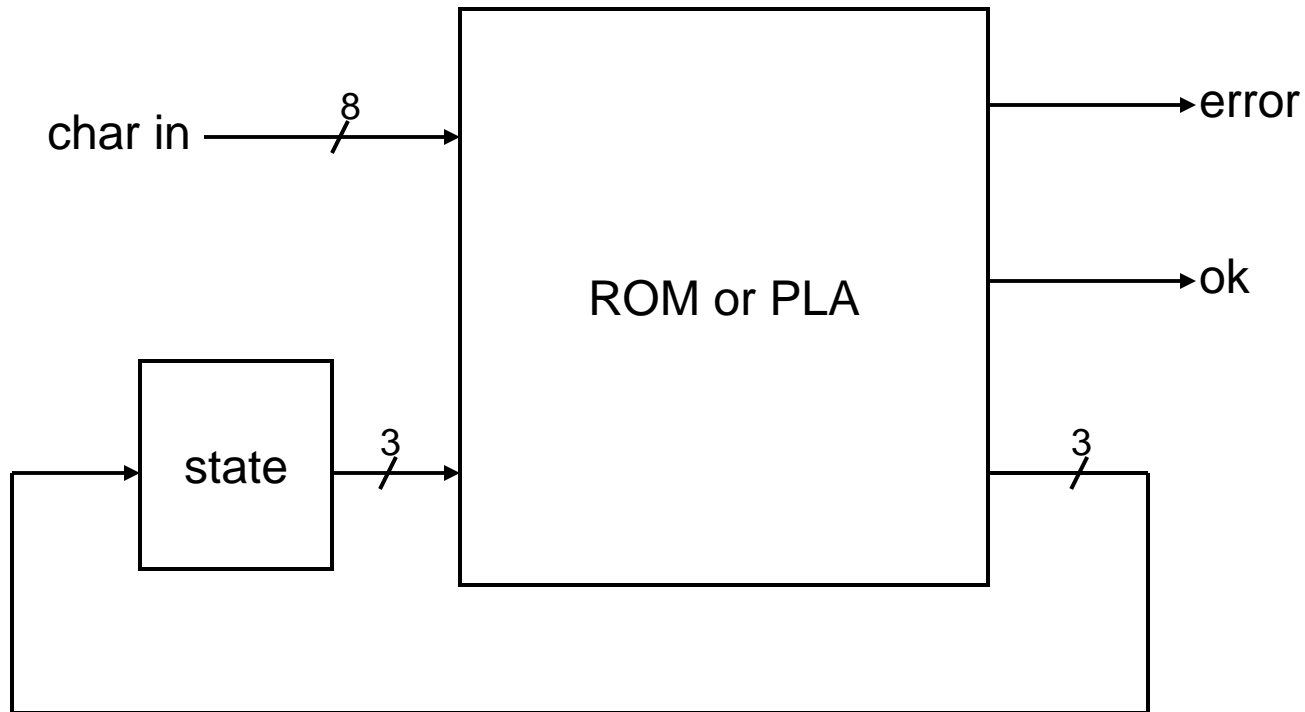

Our PLA has:

- 11 inputs
- 5 outputs

FSM Take Home

With *JUST* a register and some logic, we can implement complicated sequential functions like recognizing a FP number.

This is useful in its own right for compilers, input routines, etc.

The reason we're looking at it here is to see how designers implement the complicated sequences of events required to implement instructions

Think of the OP-CODE as playing the role of the input character in the recognizer. The character AND the state determine the next state (and action).