

State Machines

The first problem set is now online!
(Due on Jan. 31st, 2011)




Review

Much of what we call "computation" involves looking answers up in a table

- Reminiscent of those Flash Cards from grade school
- KEY IDEA: Discretize the space of allowable inputs and outputs
- DIGITAL: The ultimate discretization-- binary, only two choices, 0 and 1
- Enumerate all possible input combinations, and "memo"ize the answers (outputs)
- Leads to COMPOSABLE system blocks (i.e. gates, adders, multipliers, etc.)




Inputs			Outputs	
A	B	C	S_2	S_1
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

Composition


The key to building large systems...

Boxes around boxes...

 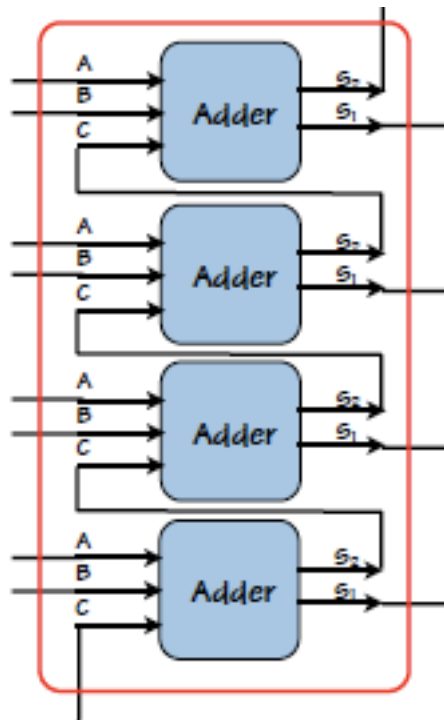 

One More Trick With Tables

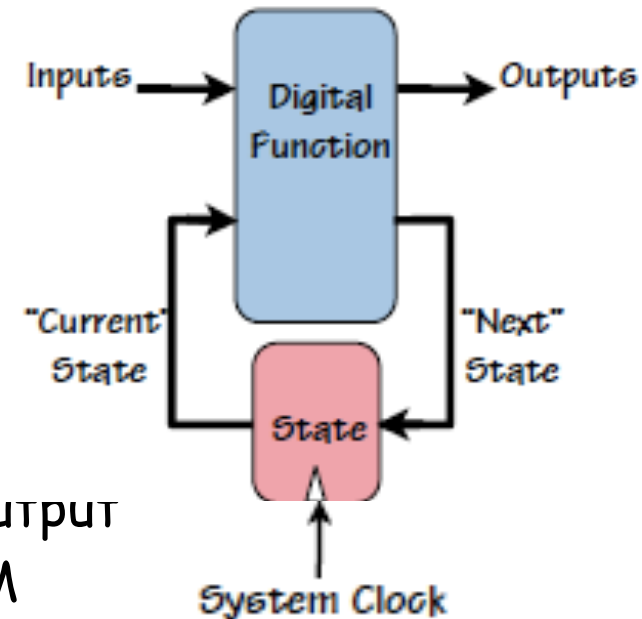
- Feedback - Feed some of our system's outputs back as inputs
- How do we make sure outputs are settled and ready to go?
- We *GATE* them with a special *STATE* block..
 - On the transition of a control signal, it simultaneously copies its inputs to its output
 - This control signal is called the *SYSTEM CLOCK*...
a.k.a. the "**Hertz*" specification you've heard about



State = Sequential Logic

This is one of the BIG ideas behind computers. State allows us to control sequences of events since the outputs aren't merely functions of the inputs, but also of the current state.

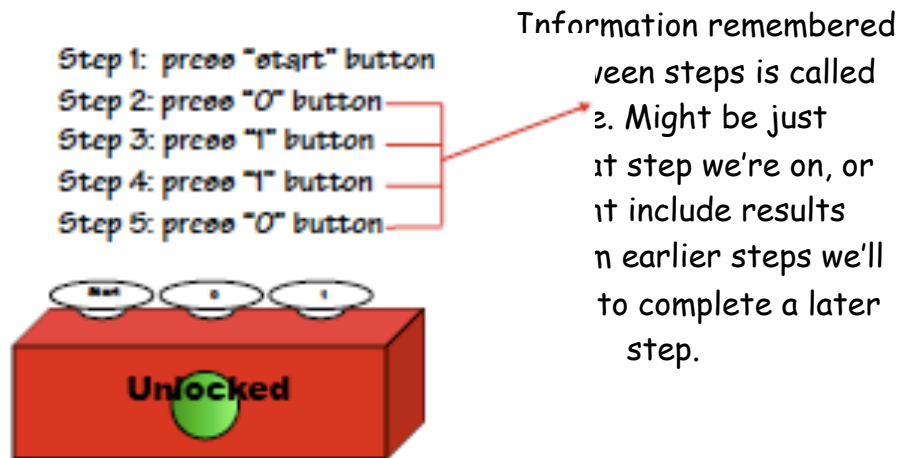Example: Digital combination lock w/ 3 buttons ("start", "0" and "1"):



Implementing a State Machine

We can easily extend our Lookup table approach to include state machines by

1) Adding a new input called the "CURRENT" State

2) Adding a new output called the "NEXT" state


Current state	"start"	"1"	"0"	Next state	unlock
---	1	---	---	start 000	0
start 000	0	0	1	digit1 001	0
start 000	0	1	0	error 101	0
start 000	0	0	0	start 000	0
digit1 001	0	1	0	digit2 010	0
digit1 001	0	0	1	error 101	0
digit1 001	0	0	0	digit1 001	0
digit2 010	0	1	0	digit3 011	0
---	0	0	1	unlock 100	0
---	0	1	0	error 101	1
unlock 100	0	0	1	error 101	1
unlock 100	0	0	0	unlock 100	1
error 101	0	---	---	error 101	0

This is
stopping the
loop for a
PROGRAM



6 different states → encode using 3 bits

Example State Machine: Roboant

 


SENSORS: antennae L and R, each 1 if in contact with something.
ACTUATORS: Forward Step F, ten-degree turns TL and TR (left, right)

GOAL: Make our ant smart enough to get out of a maze like:




STRATEGY: "Right antenna to the wall"

Lost in Space

 


Current	L	R	T L	T R	F	Next
LOST	0	0	0	0	1	LOST
LOST	-	1	0	0	1	???
LOST	1	-	0	0	1	???

 Action: Go forward until we hit something.




**"lost" is the
initial state**

Bonk!

 

Action: Turn left (CCW) until we don't touch anymore


Current	L	R	T L	T R	F	Next
LOST	0	0	0	0	1	LOST
LOST	1	-	0	0	1	RCCW
LOST	-	1	0	0	1	RCCW
RCCW	1	-	1	0	0	RCCW
RCCW	-	1	1	0	0	RCCW
RCCW	0	0	1	0	0	???

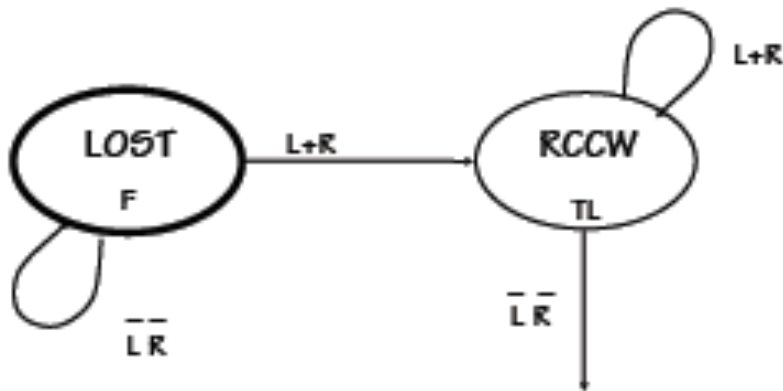

A Little to the Right...



 Action: Step and turn right a little, look for wall




Current	L	R	T L	T R	F	Next
LOST	0	0	0	0	1	LOST
LOST	1	-	0	0	1	RCCW
LOST	-	1	0	0	1	RCCW
RCCW	1	-	1	0	0	RCCW
RCCW	-	1	1	0	0	RCCW
RCCW	0	0	1	0	0	Wall
Wall	-	1	0	1	1	???
Wall	-	0	0	1	1	???

Then a Little to the Left




 Action: Step and turn left a little, till not touching (again)




Current	L	R	T L	T R	F	Next
LOST	0	0	0	0	1	LOST
LOST	1	-	0	0	1	RCCW
LOST	-	1	0	0	1	RCCW
RCCW	1	-	1	0	0	RCCW
RCCW	-	1	1	0	0	RCCW
RCCW	0	0	1	0	0	Wall1
Wall1	-	1	0	1	1	Wall2
Wall1	-	0	0	1	1	???
Wall2	0	0	1	0	1	Wall1
Wall2	0	1	1	0	1	Wall2
Wall2	1	-	1	0	1	RCCW

Dealing with Corners

 

 Action: Step and turn right until we hit perpendicular wall



Current	L	R	T L	T R	F	Next
LOST	0	0	0	0	1	LOST
LOST	1	-	0	0	1	RCCW
LOST	-	1	0	0	1	RCCW
RCCW	1	-	1	0	0	RCCW
RCCW	-	1	1	0	0	RCCW
RCCW	0	0	1	0	0	Wall1
Wall1	-	1	0	1	1	Wall2
Wall1	-	0	0	1	1	Corner
Wall2	0	0	1	0	1	Wall1
Wall2	0	1	1	0	1	Wall2
Wall2	1	-	1	0	1	RCCW
Corner	-	1	0	1	1	Wall2
Corner	-	0	0	1	1	Corner


Equivalent State Reduction

Observation: $S_i \equiv S_j$ if

 1. States have identical outputs; AND
2. Every input \rightarrow equivalent states.

Reduction Strategy:


Find pairs of equivalent states, MERGE them.



Current	L	R	T L	T R	F	Next
LOST	0	0	0	0	1	LOST
LOST	1	-	0	0	1	RCCW
LOST	-	1	0	0	1	RCCW
RCCW	1	-	1	0	0	RCCW
RCCW	-	1	1	0	0	RCCW
RCCW	0	0	1	0	0	Wall1
Wall1	-	1	0	1	1	Wall2
Wall1	-	0	0	1	1	Corner
Wall2	0	0	1	0	1	Wall1
Wall2	0	1	1	0	1	Wall2
Wall2	1	-	1	0	1	RCCW
Corner	-	1	0	1	1	Wall2
Corner	-	0	0	1	1	Corner

An Evolutionary Step

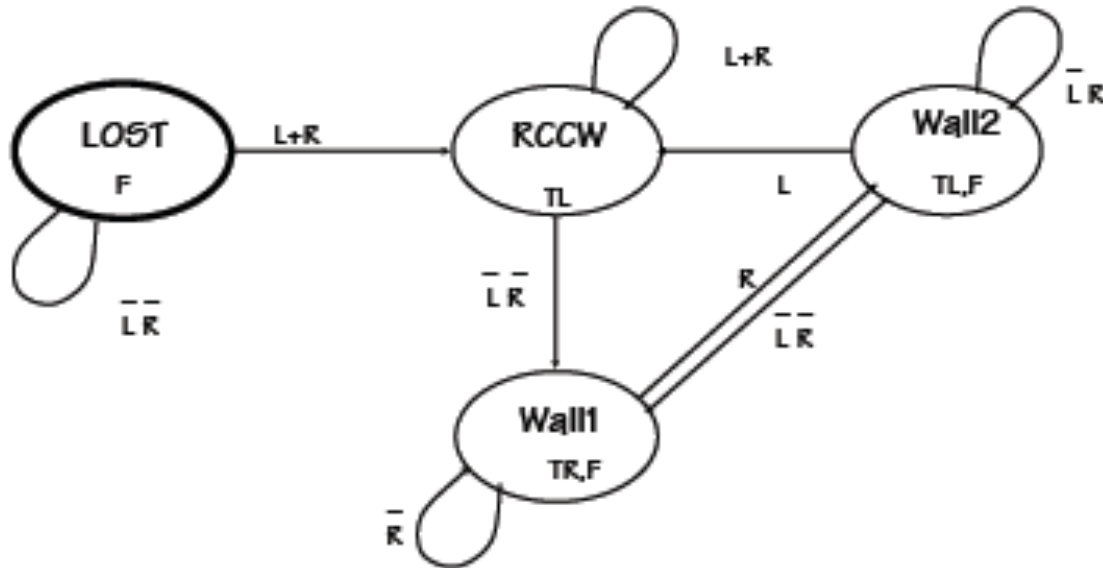Merge equivalent states Wall1 and Corner into a single new, combined state.




Current	L	R	T L	T R	F	Next
LOST	0	0	0	0	1	LOST
LOST	1	-	0	0	1	RCCW
LOST	0	1	0	0	1	RCCW
RCCW	1	-	1	0	0	RCCW
RCCW	0	1	1	0	0	RCCW
RCCW	0	0	1	0	0	Wall1
Wall1	-	1	0	1	1	Wall2
Wall1	-	0	0	1	1	Wall1
Wall2	0	0	1	0	1	Wall1
Wall2	0	1	1	0	1	Wall2
Wall2	1	-	1	0	1	RCCW

Behaves exactly as previous (5-state) state machine!

An Ant Schematic

 Are you telling me that my essence amounts to no more than 15 gates!



Super Roboant

F5M state table

```
; fsm from lecture
;
;now  L R S | next  L M F M E
;-----
lost  0 0 - | lost  0 0 1 0 0
lost  1 - - | rotatew 0 0 1 0 0
lost  0 1 - | rotatew 0 0 1 0 0
rotatew 0 0 - | wall1 1 0 0 0 0
rotatew 1 - - | rotatew 1 0 0 0 0
rotatew 0 1 - | rotatew 1 0 0 0 0
wall1 - 0 - | wall1 0 1 1 0 0
wall1 - 1 - | wall2 0 1 1 0 0
wall2 1 - - | rotatew 1 0 1 0 0
wall2 0 1 - | wall2 1 0 1 0 0
wall2 0 0 - | wall1 1 0 1 0 0
```

Maze selection

Plan view of maze

Simulation controls

Status display

state: "lost", inputs: L=0 R=0 S=0; step 0

Featuring an improved Roboant that can add crumbs (M), erase crumbs (E), and sense (S) crumbs along its path.