

The UNIVERSITY of NORTH CAROLINA at CHAPEL HILL

Comp 541 Digital Logic and Computer Design  
Fall 2014

Homework #1: Combinational Logic

Issued Fri 9/19/14; Due Mon 9/29/14 (hardcopy due in class)

Self-Study Questions (do not submit): Textbook exercises 1.9, 1.11, 1.21, 1.47, 1.87, 2.1, 2.3, 2.13, 2.15, 2.17, 2.27, 2.33, 2.35, 2.37, 2.43. Solutions: <http://booksite.elsevier.com/9780123944245>

Exercises to be submitted:

- Chapter 1 Exercises: 1.22, 1.46, 1.60[(c)-(d) only], 1.74, 1.88
- Redo Example 1.23 (page 34): Redo this example, but with the following numbers: 8 watt-hour battery, 500 MHz operation, 4 W of antenna broadcast power. All other numbers remain the same.
- Chapter 2 Exercises: 2.2[(c)-(d) only], 2.4[(c)-(d) only], 2.14, 2.24, 2.26, 2.40, 2.44, and Interview Question 2.2.
- Prove the Boolean Identity #15 on Slide #10 of Lecture 3 using any of the other identities on that slide:  $(X + Y)(X + Z) = X + YZ$ . Note: Show step-by-step Boolean simplification.
- For the Karnaugh Map shown below, draw the “ovals” on top of it showing the optimal implementation of the output  $Y$ . Write the resulting Boolean expression.

Y CD \ AB	AB			
	00	01	11	10
00	1	1	1	1
01	0	1	1	0
11	0	X	1	X
10	1	0	0	X