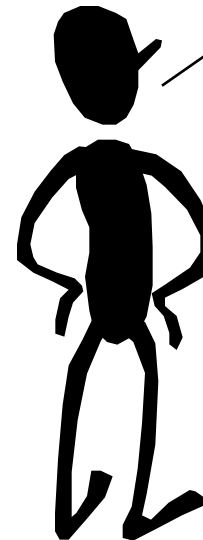


Binary Multipliers

The key trick of multiplication is memorizing a digit-to-digit table...
Everything else was just adding

×	0	1	2	3	4	5	6	7	8	9
0	0	0	0	0	0	0	0	0	0	0
1	0	1	2	3	4	5	6	7	8	9
2	0	2	4	6	8	10	12	14	16	18
3	0	3	6	9	12	15	18	21	24	27
4	0	4	8	12	16	20	24	28	32	36
5	0	5	10	15	20	25	30	35	40	45
6	0	6	12	18	24	30	36	42	48	54
7	0	7	14	21	28	35	42	49	56	63
8	0	8	16	24	32	40	48	56	64	72
9	0	9	18	27	36	45	54	63	72	81

×	0	1
0	0	0
1	0	1



You've got to be kidding... It can't be that easy

Binary Multiplication

The "Binary" Multiplication Table

X	0	1
0	0	0
1	0	1

Hey, that looks like an AND gate



Binary multiplication is implemented using the same basic longhand algorithm that you learned in grade school.

$$\begin{array}{r} A_3 \quad A_2 \quad A_1 \quad A_0 \\ \times B_3 \quad B_2 \quad B_1 \quad B_0 \\ \hline \end{array}$$



$A_j B_i$ is a "partial product" \longrightarrow

$$\begin{array}{r} A_3 B_0 \quad A_2 B_0 \quad A_1 B_0 \quad A_0 B_0 \\ A_3 B_1 \quad A_2 B_1 \quad A_1 B_1 \quad A_0 B_1 \\ A_3 B_2 \quad A_2 B_2 \quad A_1 B_2 \quad A_0 B_2 \\ + A_3 B_3 \quad A_2 B_3 \quad A_1 B_3 \quad A_0 B_3 \\ \hline \end{array}$$



Multiplying N-digit number by M-digit number gives (N+M)-digit result

Easy part: forming partial products (just an AND gate since B_i is either 0 or 1)
 Hard part: adding M, N-bit partial products

Multiplication: Implementation

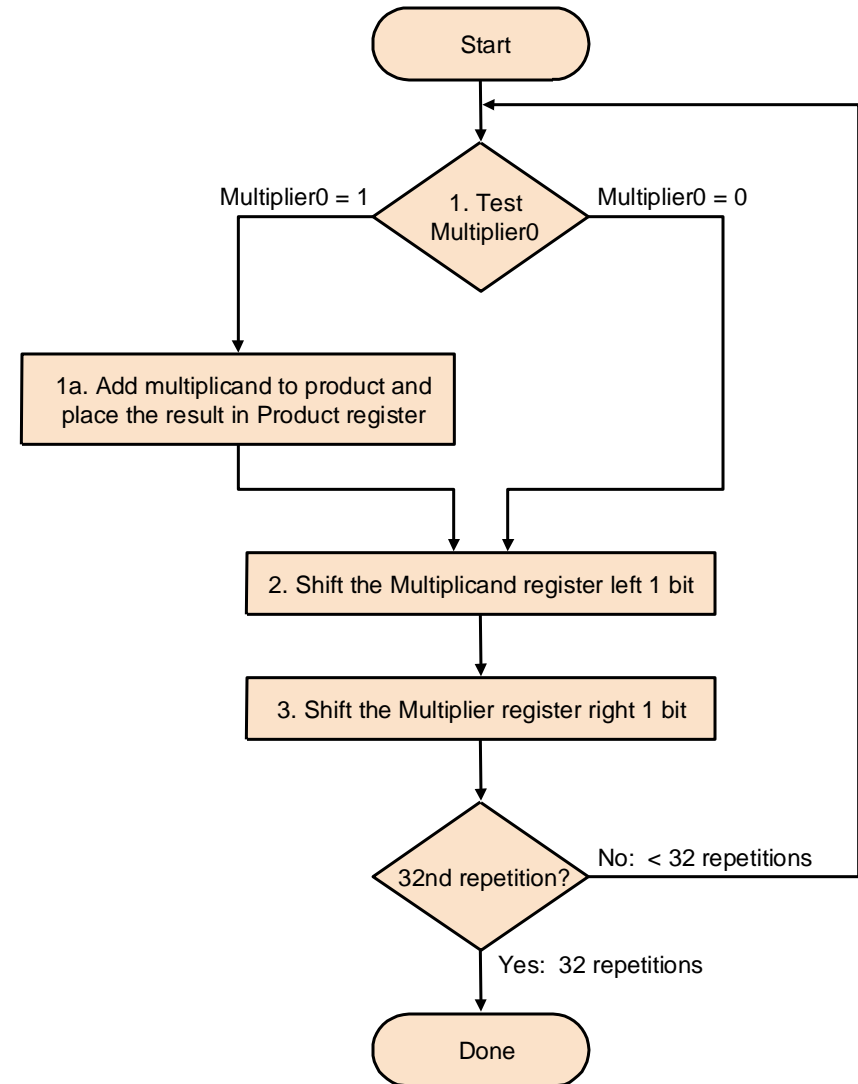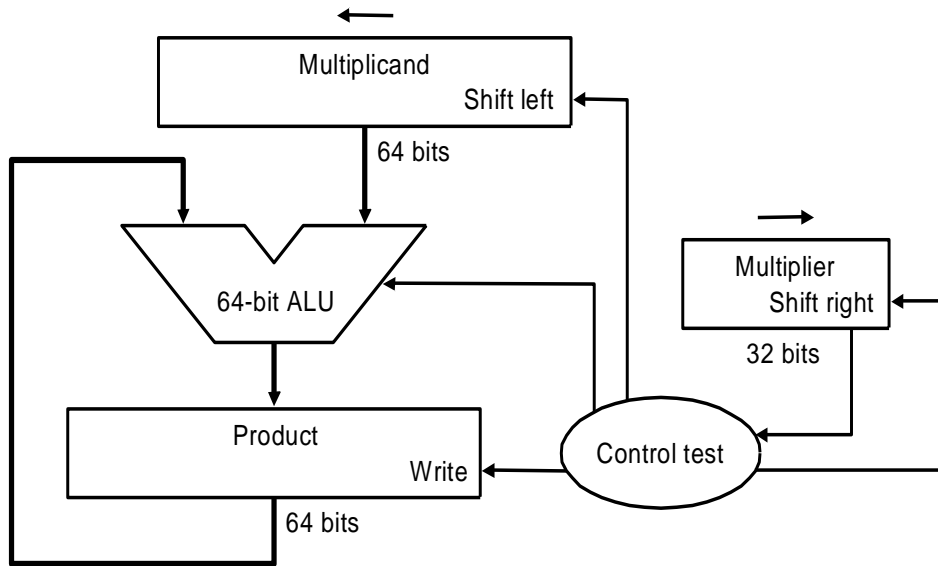


Second Version

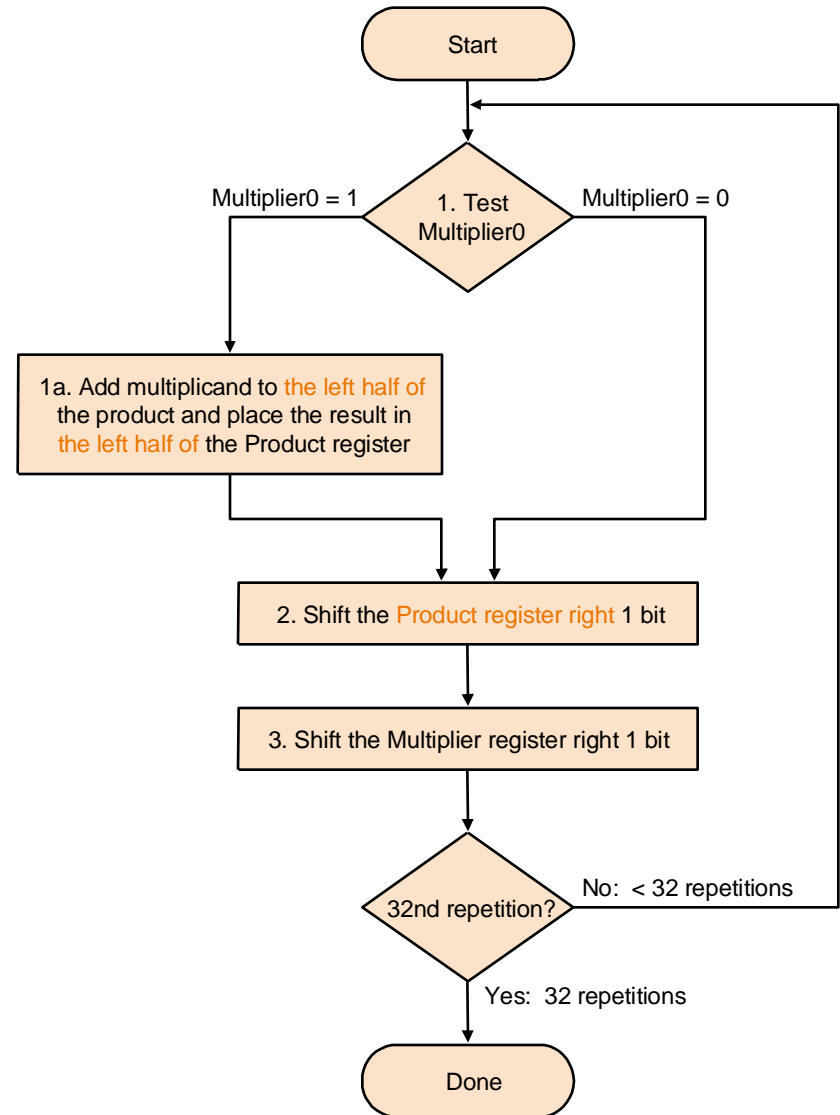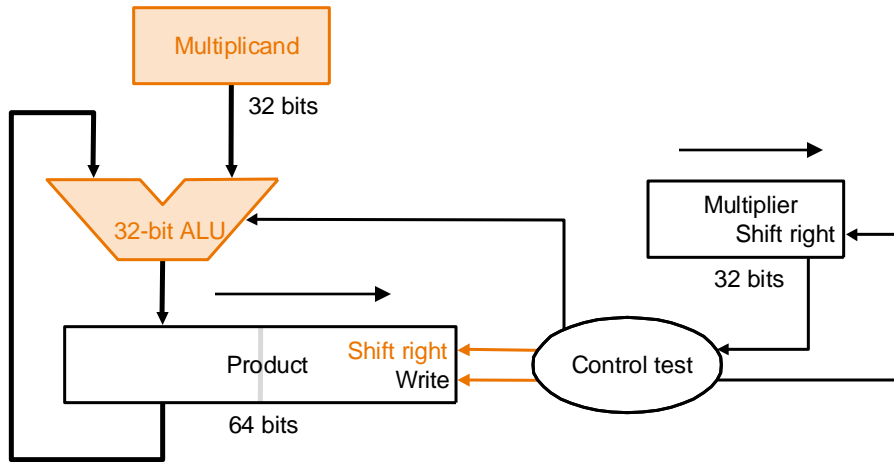


Example for second version

Iteration	Step	Multiplier	Multiplicand	Product
0	Initial	1011	0010	0000 0000
1	Test true shift right	1011 0101	0010	0010 0000 0001 0000
2	Test true shift right	0101 0010	0010	0011 0000 0001 1000
3	Test false shift right	0010 0001	0010	0001 1000 0000 1100
4	Test true shift right	0001 0000	0010	0010 1100 0001 0110

Final Version

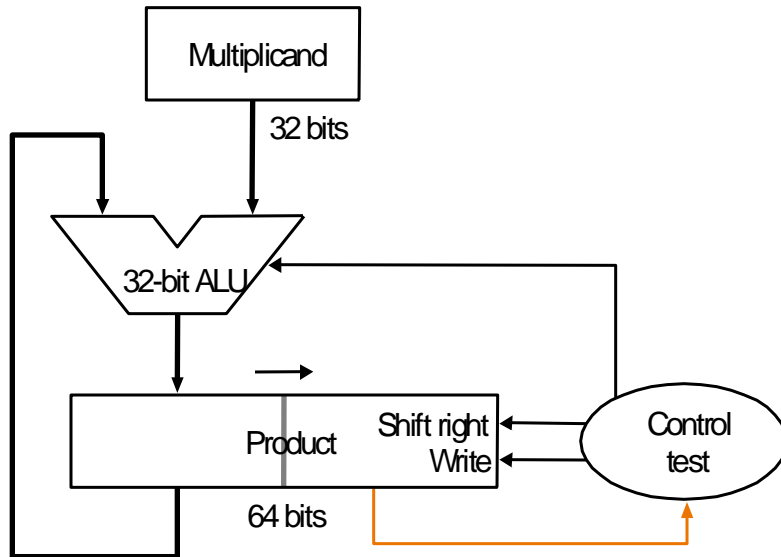

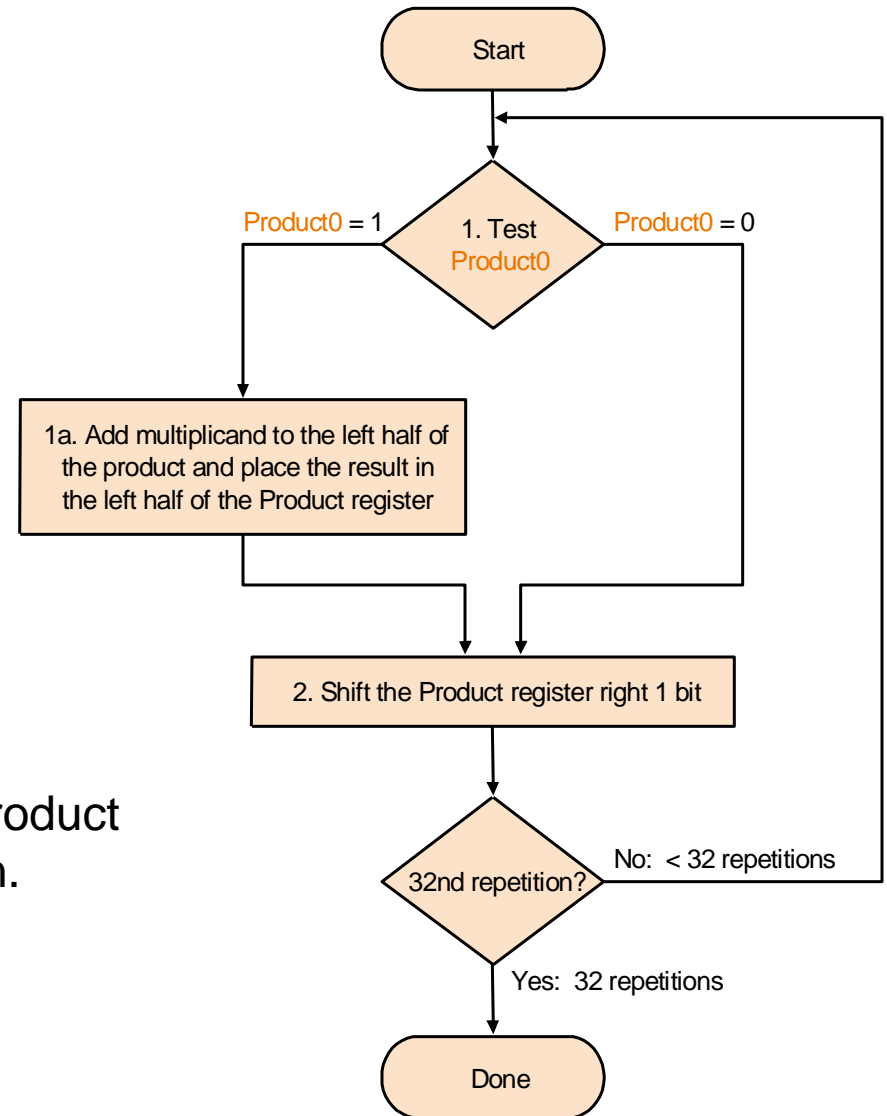The trick is to use the lower half of the product to hold the multiplier during the operation.




What about the sign?

Positive numbers are easy.

How about negative numbers?

Faster Multiply

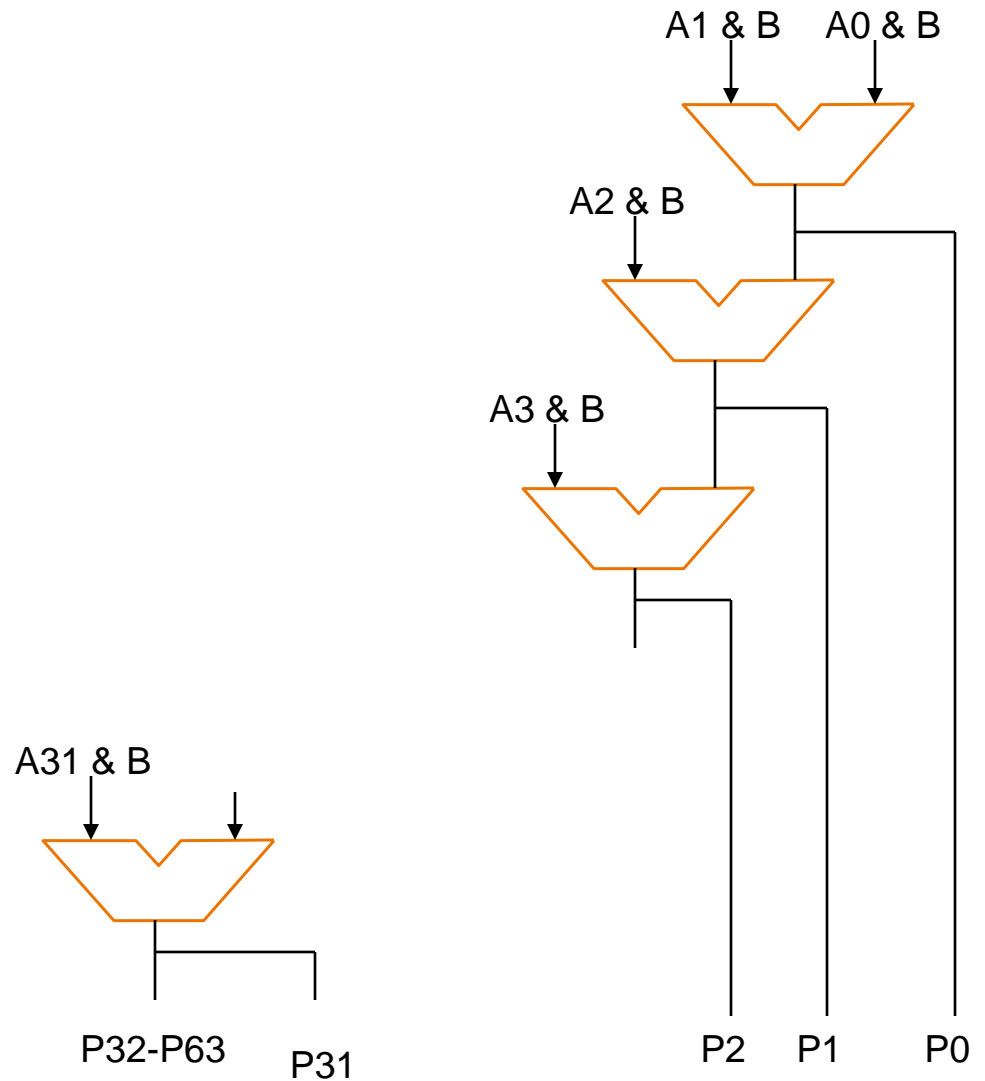

Division

