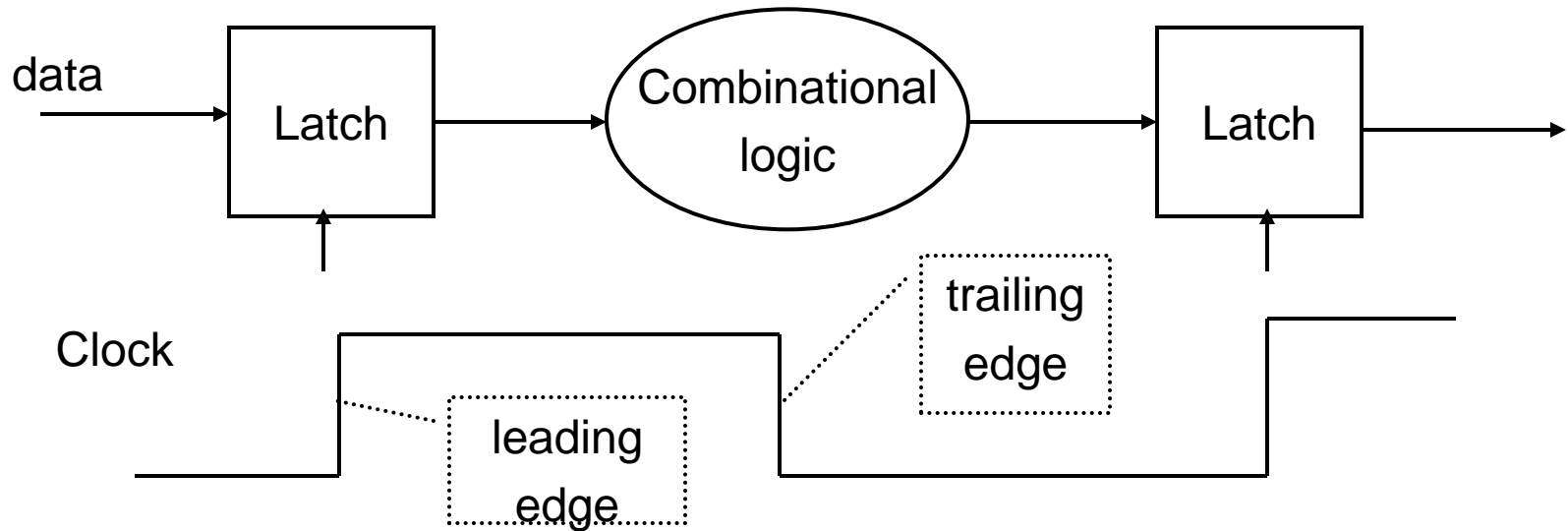


Control & Execution

Finite State Machines for Control

MIPS Execution


Synchronous Systems



On the leading edge of the clock, the input of a latch is transferred to the output and held.

We must be sure the output of the combinational logic has *settled* before the next leading clock edge.

Asynchronous Systems

 

No clock!


The data carries a “valid” signal along with it

System goes at greatest possible speed.

Only “computes” when necessary.


Everything we look at in this class will be synchronous

Fetching Sequential Instructions

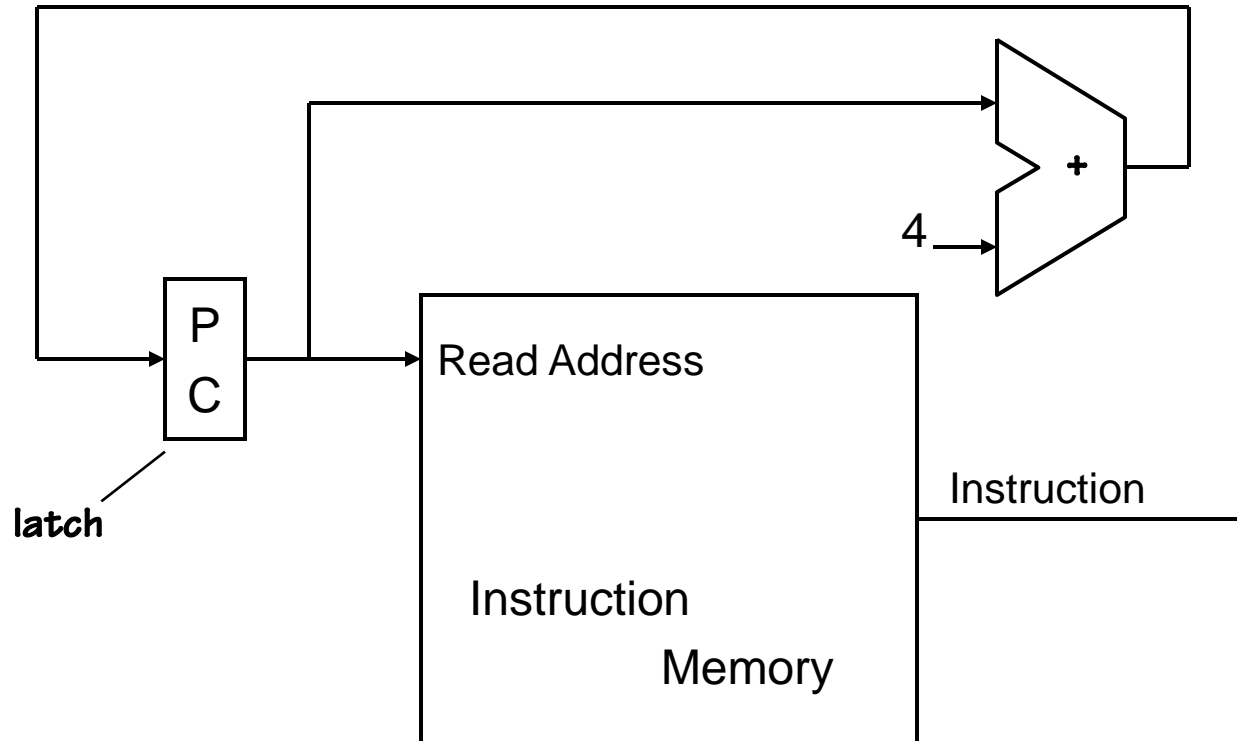


How about branch?

Datapath for R-type Instructions

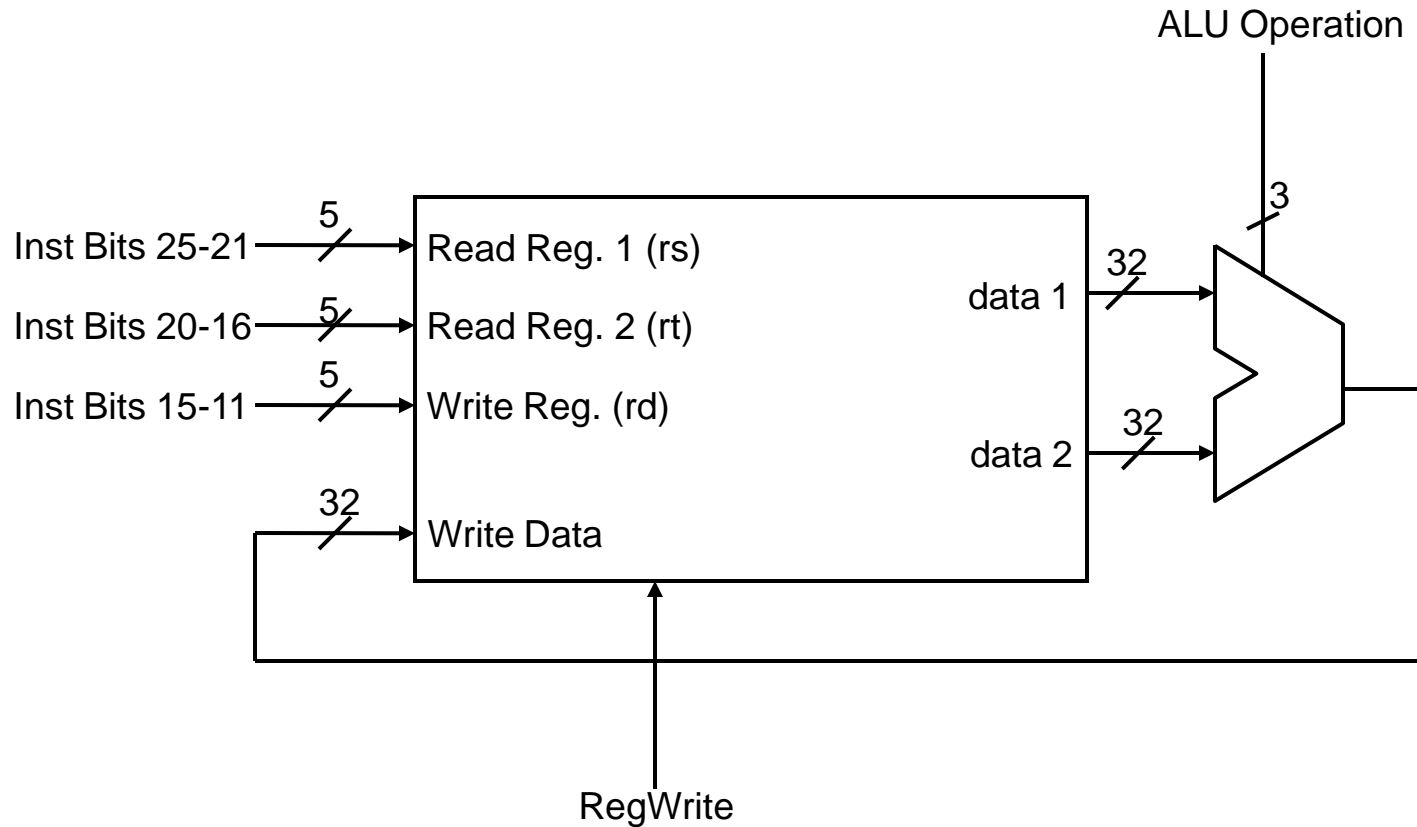


MUX Blocks

 

The select signal determines which of the inputs is connected to the output

Inside there is a 32 way MUX per bit

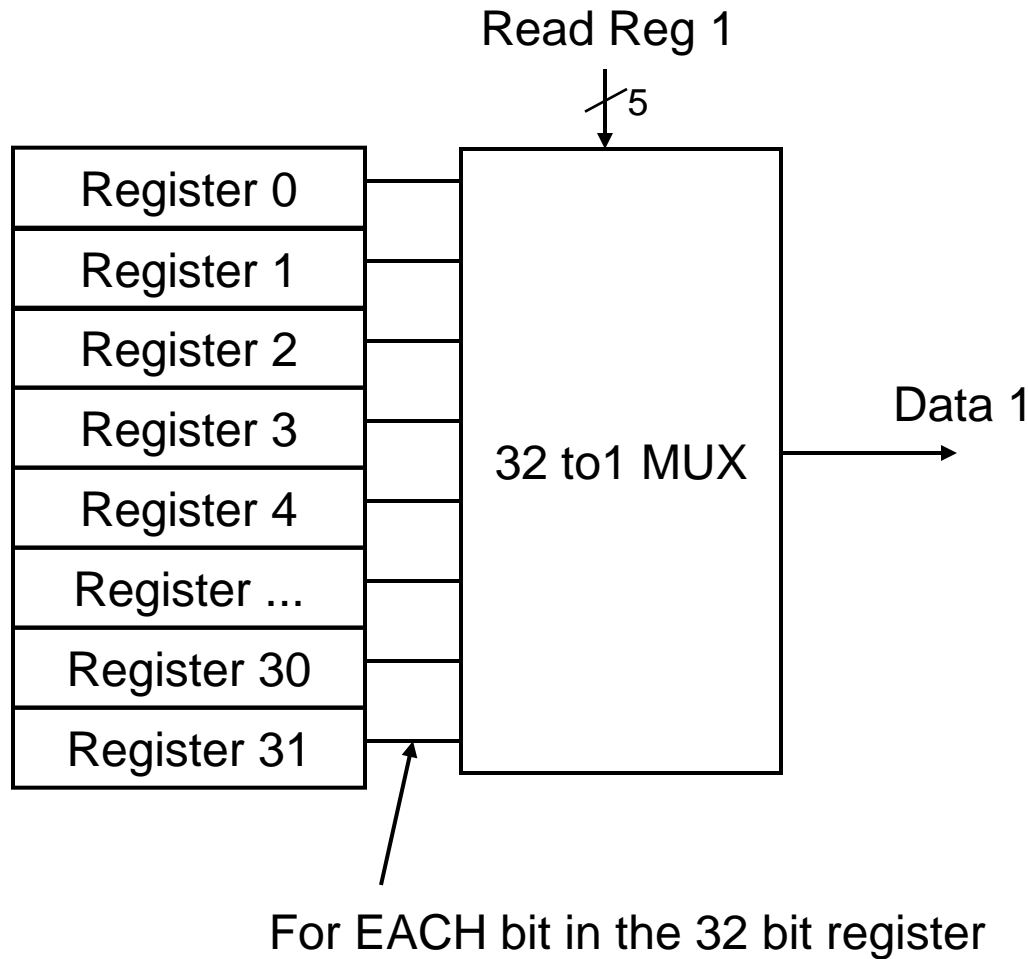


LOT'S OF
CONNECTIONS!

And this is just one port!
Remember, we have
data1 and data2 coming
out of the register file!

Our Register File has 3 ports

This is one reason we have only a small number of registers

What's another reason?

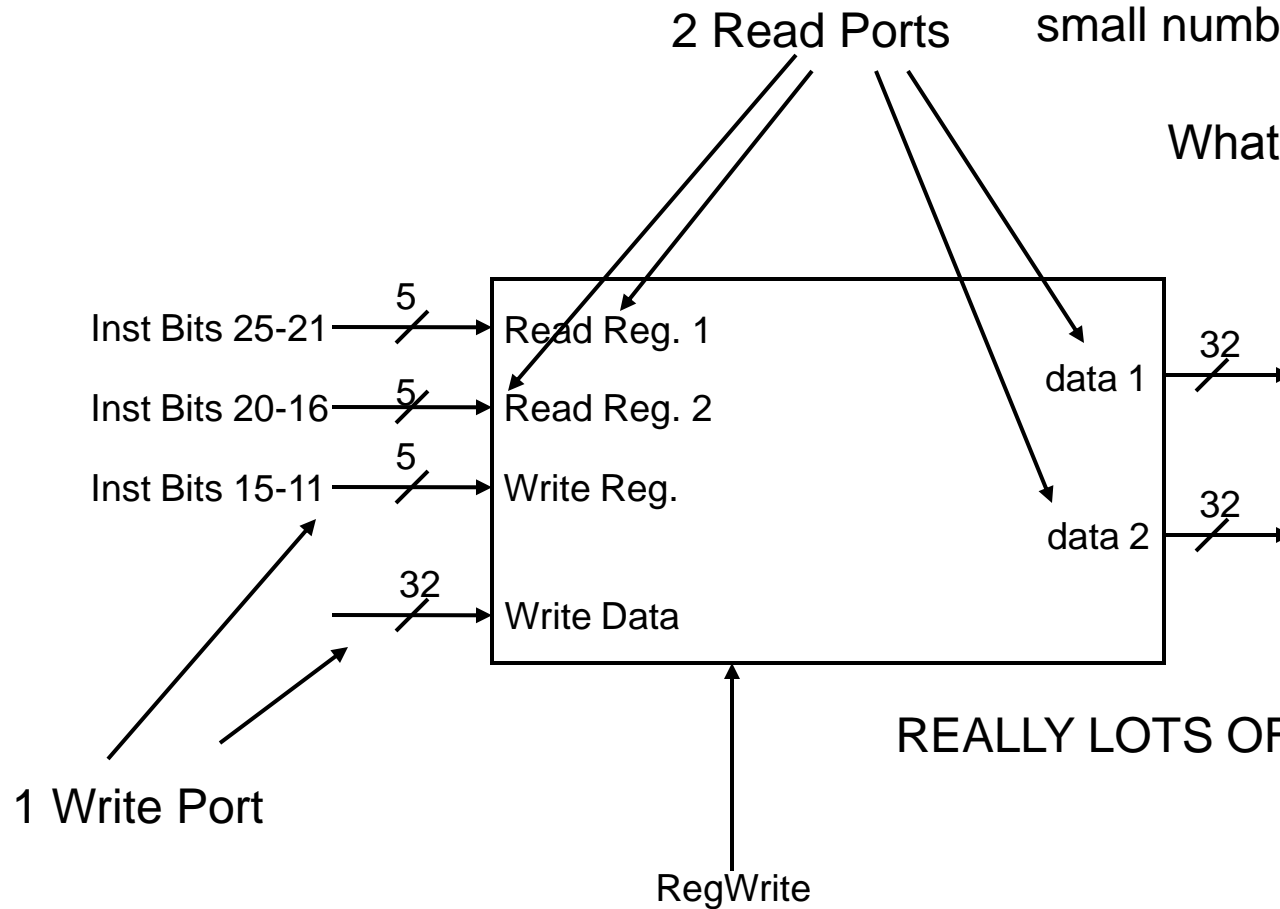


REALLY LOTS OF CONNECTIONS!


Implementing Logical Functions

Suppose we want to map M input bits to N output bits

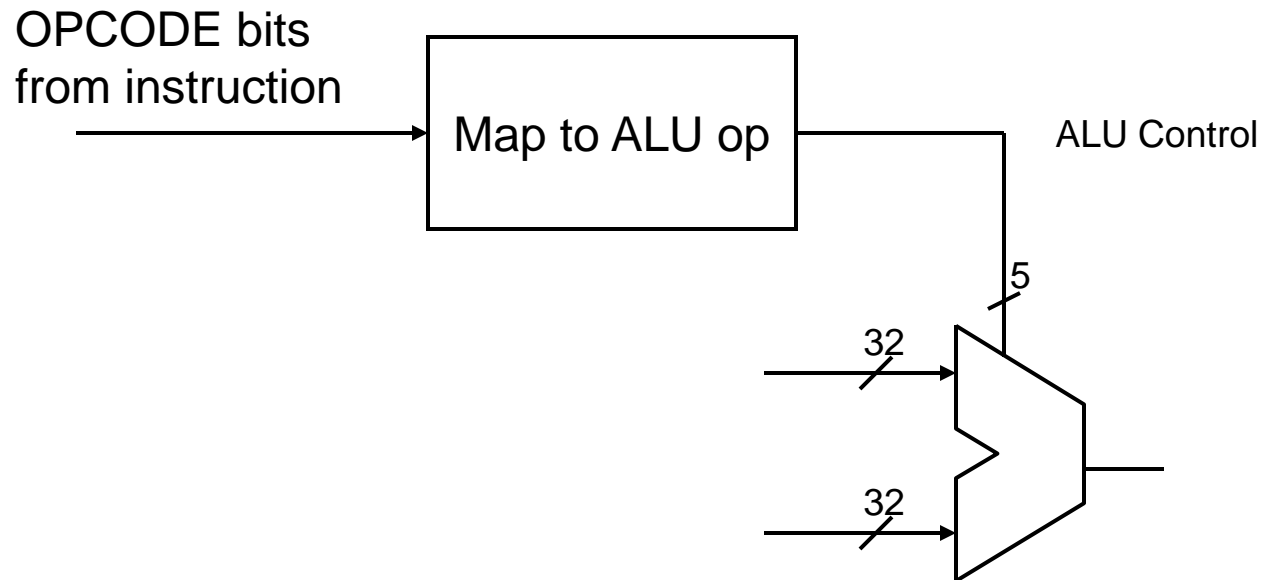For example, we need to take the OPCODE field from the instruction and determine what OPERATION to send to the ALU.




Remember our ALU?

 


Implementing Logical Functions

Suppose we want to map M input bits to N output bits

 
For example, we need to take the OPCODE field from the instruction and determine what OPERATION to send to the ALU.




We can get 1 bit out with a MUX

 

Or use a ROM

 

Or use sum-of-products

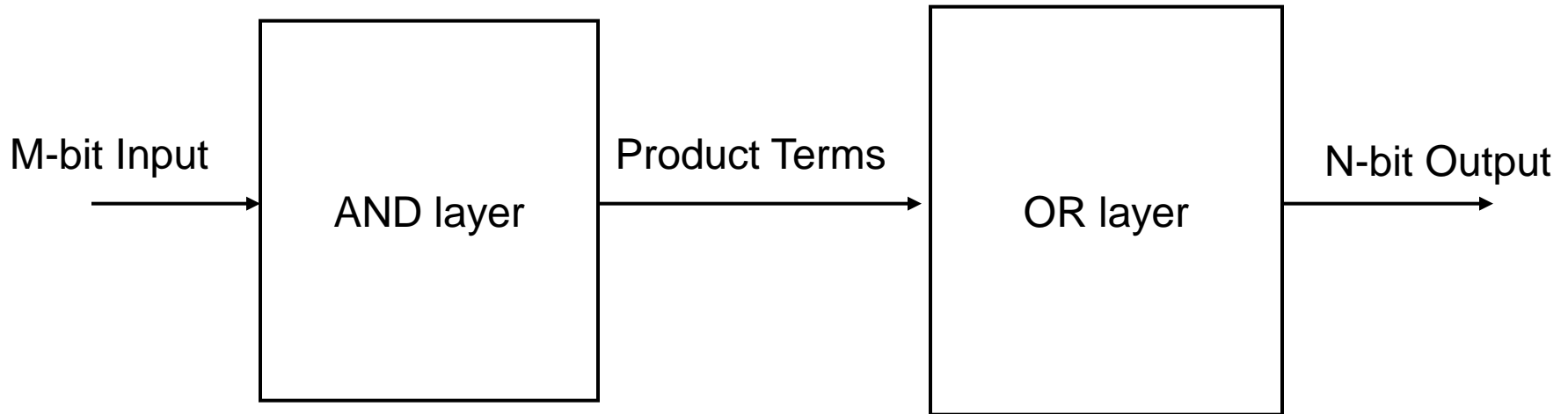

Think of the SUM of PRODUCTS form.

The AND layer generates the products of various input bits

The OR layer combines the products into various outputs

You could also use two NAND layers instead


Could be implemented using Boolean gates, or also using a “programmable logic array” (PLA) [similar to a PROM, but both the AND and the OR parts are programmable].

Finite State Machines

- A set of STATES
- A set of INPUTS
- A set of OUTPUTS
- A function to map the STATE and the INPUT into the next STATE and an OUTPUT

Remember automata?


Traffic Light Controller

 

Controller State Table

Inputs			Outputs		
State	NScar	EWcar	Next	NSlight	EWlight
NSgreen	0	0	NSgreen	1	0
NSgreen	0	1	EWgreen	0	1
NSgreen	1	0	NSgreen	1	0
NSgreen	1	1	EWgreen	0	1
EWgreen	0	0	EWgreen	0	1
EWgreen	0	1	EWgreen	0	1
EWgreen	1	0	NSgreen	1	0
EWgreen	1	1	NSgreen	1	0

Implementing an FSM

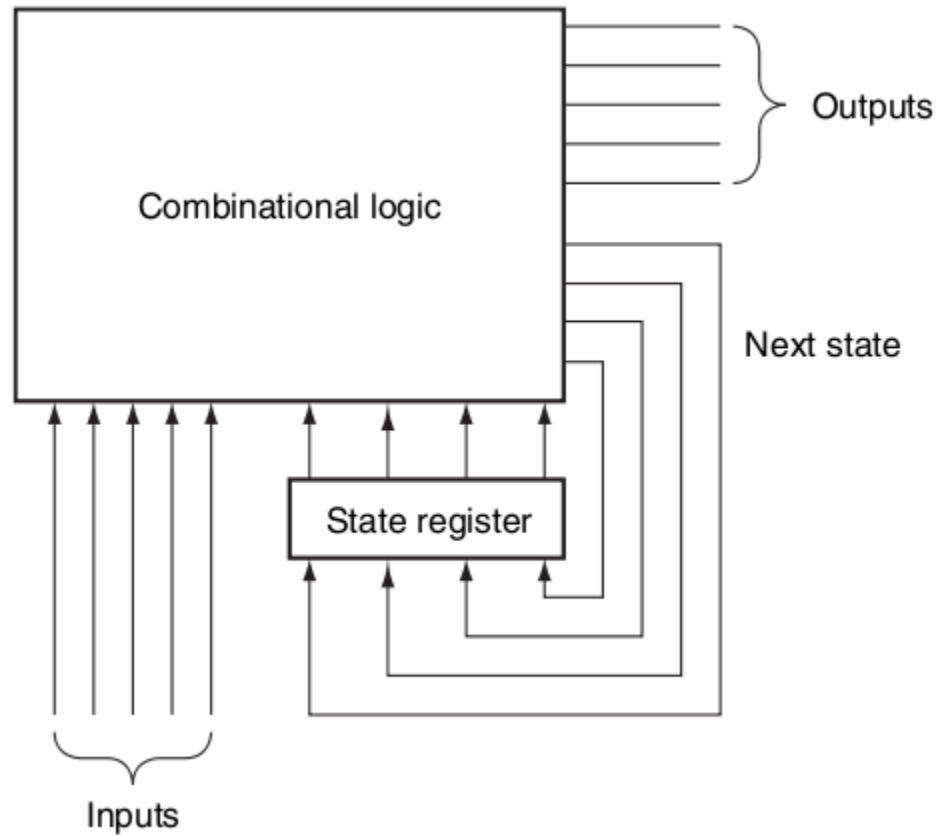

FSM Example: Recognizing Numbers

Recognize the regular expression for floating point numbers

$$[\backslash t]^* [-+]? [0-9]^* (. [0-9]^*)? (e[-+]? [0-9]^+)?$$

Examples:

+123.456e23

.456

1.5e-10

-123

“a” matches itself


“[abc]” matches one of a, b, or c

“[a-z]” matches one of a, b, c, d, ..., x, y, or z

“0*” matches zero or more 0’s (“”, “0”, “00”, “0000”)

“Z?” matches zero or 1 Z’s

FSM Diagram

 

FSM Table

IN : STATE → NEW STATE

' ' : start → start

'0' | '1' | ... | '9' : start → whole

'+' | '-' : start → sign

'.' : start → frac

'0' | '1' | ... | '9' : sign → whole

'.' : sign → frac

'0' | '1' | ... | '9' : whole → whole

'.' : whole → frac

' ' : whole → done

'e' : whole → exp

'e' : frac → exp

'0' | '1' | ... | '9' : frac → frac

' ' : frac → done

'0' | '1' | ... | '9' : exp → exp

' ' : exp → done

STATE ASSIGNMENTS

start = 0 = 000

sign = 1 = 001

whole = 2 = 010


frac = 3 = 011

exp = 4 = 100

done = 5 = 101

error = 6 = 110

FSM Implementation

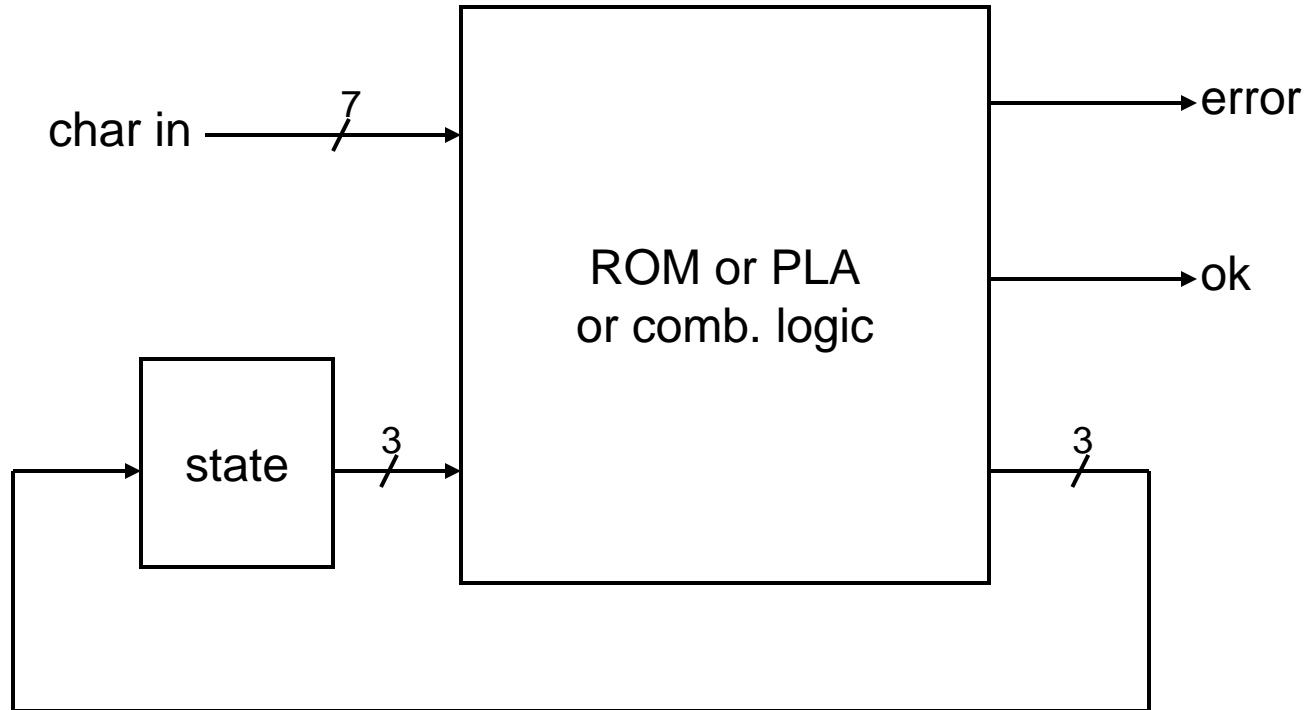

Our ROM has:

- 10 inputs
- 5 outputs

FSM Summary

With *JUST* a register and some logic, we can implement complicated sequential functions like recognizing a FP number.

This is useful in its own right for compilers, input routines, etc.

The reason we're looking at it here is to see how designers implement the complicated sequences of events required to implement instructions

Think of the OP-CODE as playing the role of the input character in the recognizer. The character AND the state determine the next state (and action).

Five Execution Steps

1. Instruction Fetch
2. Instruction Decode and Register Fetch
3. Execution, Memory Address Computation, or Branch Completion
4. Memory Access or R-type instruction completion
5. Memory Read Completion

INSTRUCTIONS TAKE FROM 3 - 5 CYCLES!

An FSM looks at the *op-code* to determine how many...

Step 1: Instruction Fetch

Use PC to get instruction and put it in the Instruction Register.

Increment the PC by 4 and put the result back in the PC.

Can be described succinctly using RTL "Register-Transfer Language"

$IR = \text{Memory}[PC] ;$ *IR is "Instruction Register"*

$PC = PC + 4 ;$

Step 2: Instruction Decode and Register Fetch

Read registers rs and rt in case we need them

Compute the branch address in case the instruction is a branch

RTL:

```
A = Reg[IR[25-21]] ;
```

```
B = Reg[IR[20-16]] ;
```

```
ALUOut = PC + (sign-extend(IR[15-0]) << 2) ;
```

We aren't setting any control lines based on the instruction type (we are busy "decoding" it in our control logic)

Step 3 (instruction dependent)

ALU is performing one of three functions, based on instruction type

Memory Reference:

`ALUOut = A + sign-extend(IR[15-0]) ;`

R-type:

`ALUOut = A op B ;`

Branch:

`if (A==B) PC = ALUOut ;`

Step 4 (R-type or memory-access)

Loads and stores access memory

$\text{MDR} = \text{Memory}[\text{ALUOut}] ;$ *MDR is Memory Data Register*
or
 $\text{Memory}[\text{ALUOut}] = \text{B} ;$

R-type instructions finish

$\text{Reg}[\text{IR}[15-11]] = \text{ALUOut} ;$

Step 5 Memory Read Completion

`Reg[IR[20-16]] = MDR;`

Summary:

Step name	Action for R-type instructions	Action for memory-reference instructions	Action for branches	Action for jumps
Instruction fetch	IR = Memory[PC] PC = PC + 4			
Instruction decode/register fetch	A = Reg [IR[25-21]] B = Reg [IR[20-16]] ALUOut = PC + (sign-extend (IR[15-0]) << 2)			
Execution, address computation, branch/ jump completion	ALUOut = A op B	ALUOut = A + sign-extend (IR[15-0])	if (A ==B) then PC = ALUOut	PC = PC [31-28] (IR[25-0]<<2)
Memory access or R-type completion	Reg [IR[15-11]] = ALUOut	Load: MDR = Memory[ALUOut] or Store: Memory [ALUOut] = B		
Memory read completion		Load: Reg[IR[20-16]] = MDR		