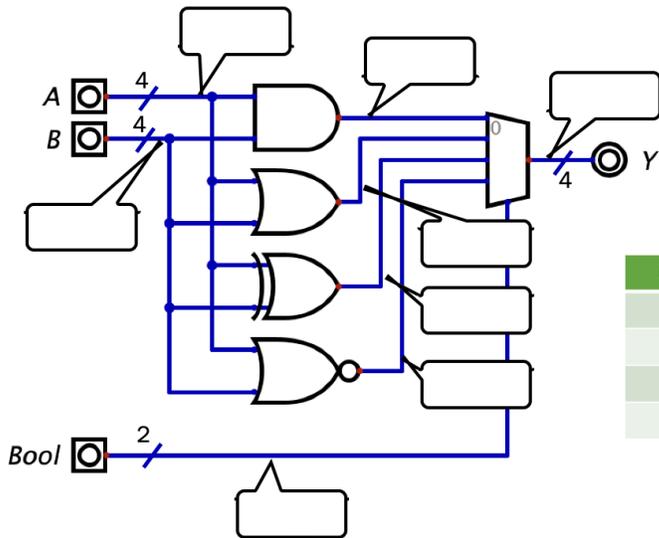


Question 1: Boolean Unit What are the values on each signal when we want to perform $Y = A \oplus B$, where A is 0b1010 and B is 0b0001?



Operation	Expression	Bool
AND	$A \times B$	0b00
OR	$A + B$	0b01
XOR	$A \oplus B$	0b10
NOR	$\overline{A + B}$	0b11

Question 2: ALU Control Table Fill in the table!

Operation	Sub	Bool	Shift	Math
A + B				
A - B				
B << A				
B >> A				
B >>> A				
A AND B				
A OR B				
A XOR B				
A NOR B				

Question 3: ALU Shift For the given operation $1 \ll 2$, trace the data path through the ALU and show:

1. Which functional unit is activated (Add/Sub, Bidirectional Shifter, Boolean Unit).
2. What the control signal setting must be (Math, Shift, Bool, or Sub).
3. The intermediate input/output values at each stage.
4. The final 4-bit Result produced.

