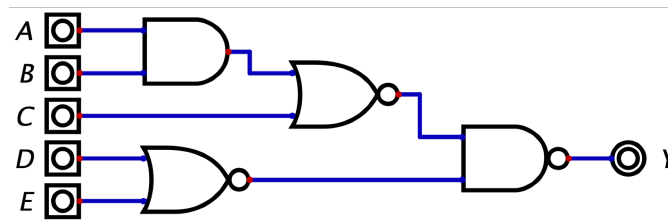


Question 1: CMOS Practice What function does this gate compute?



Question 2: Forming Equations from Logic Diagrams What equation does this circuit diagram represent?