

COMP311: *COMPUTER ORGANIZATION!*


Lecture 5: Logic Gates

tinyurl.com/comp311-fa25

Logistics Update

- First Written Assignment due Thursday 11:59pm
 - *Come to office hours!*
 - *If you turn it in by Wednesday at 5pm, we can get you graded feedback before the quiz.*
- First Quiz on Thursday. Topics will include:
 - *211 review*
 - Going between decimal, binary, hex
 - Two's complement,
 - Overflow
 - *Transistors*
 - *Boolean Algebra Equations + Logic Diagrams (TODAY!)*
- Review session tomorrow at 7:30pm (location TBD)

Refresher: Transistor Tracing

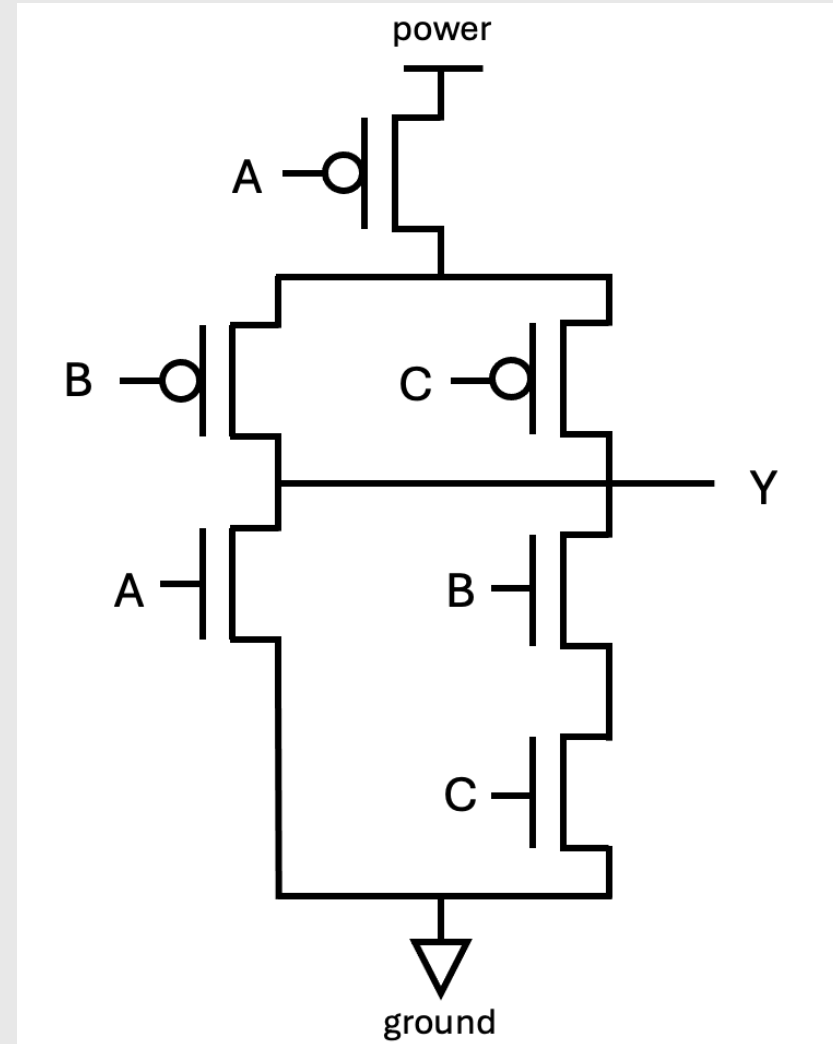





LOGIC GATES



Now can we design larger systems!

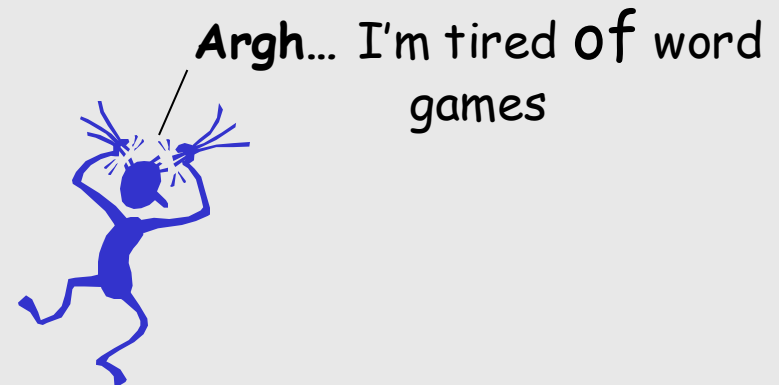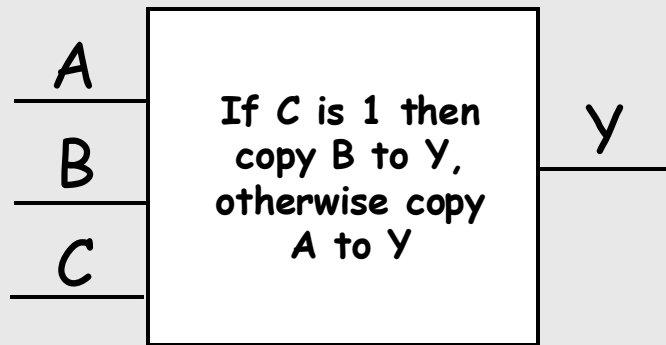We need to start somewhere – usually with a functional specification




****Every combinational function can be expressed as a table!****

“**Truth tables**” are a concise description of the combinational system’s function, where an output is specified for **every** input combination.

Inverter/Not Gate

n inputs
 \Rightarrow rows 2^n

Symbol

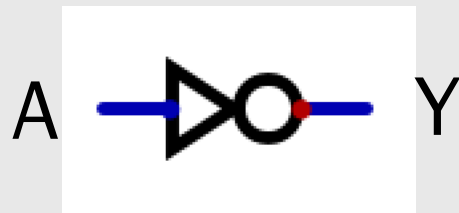

Truth Table

A	Y
0	1
1	0

Equation 2^n

$$Y = \bar{A}$$

$2^1 \Rightarrow 2$ rows ✓

What Gates can we build?

Recall, we need to design our gates using a pull-up network of pMOS transistors and a pull-down network of nMOS transistors

What gates can we
- build?
- define?

Let's start by
considering only
2-input gates.

AND		OR		NAND		NOR	
AB	Y	AB	Y	AB	Y	AB	Y
00	0	00	0	00	1	00	1
01	0	01	1	01	1	01	0
10	0	10	1	10	1	10	0
11	1	11	1	11	0	11	0

How many possible 2-input gates are there?

KEY IDEA: As many as there are 2-input truth tables.

All the gates!

There are only 16 possible 2-input gates... Let's examine all of them. Some we already know, others are just silly.

I N P U T A B	Z	A	A		B		X									
	E	N	>		>		O	O								
	O	D	B	A	A	B	R	R								
	00	00	00	00	00	00	00	00	1	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	0	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

How many of these gates can be implemented using a single CMOS gate?





Do we really need all of these gates?

Nope! Once we realize that we can describe all of them using just AND, OR, and NOT

Composing gates: AND and OR

Each can be constructed using a pair of CMOS gates

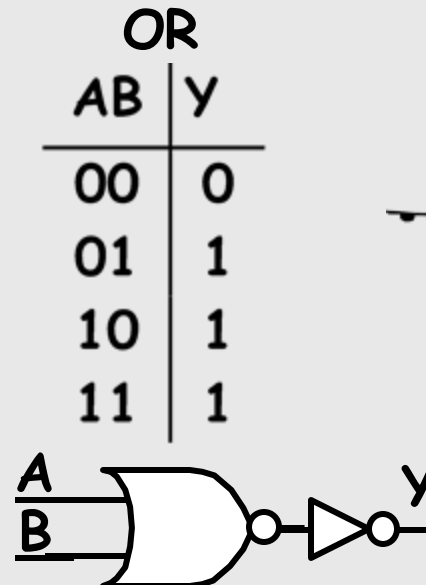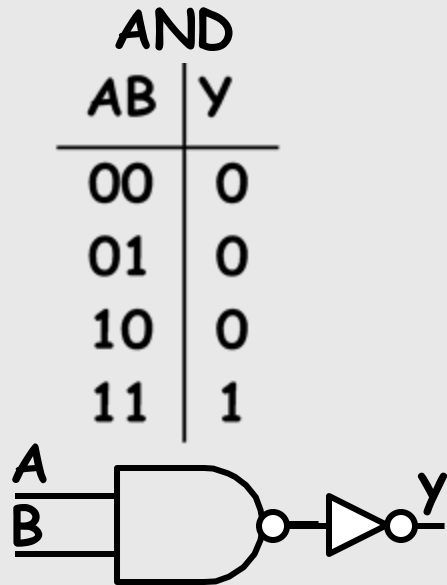AND is just NAND with an inverter, and OR is just NOR with an inverted output.




These two gates are particularly important. Using them will allow us to develop a systematic approach for constructing any combinational function.

One will do!


A UNIVERSAL gate is one that can be used to implement
ANY COMBINATIONAL FUNCTION. There are many
UNIVERSAL gates, but not all gates are UNIVERSAL.

NANDs and NORs are UNIVERSAL!

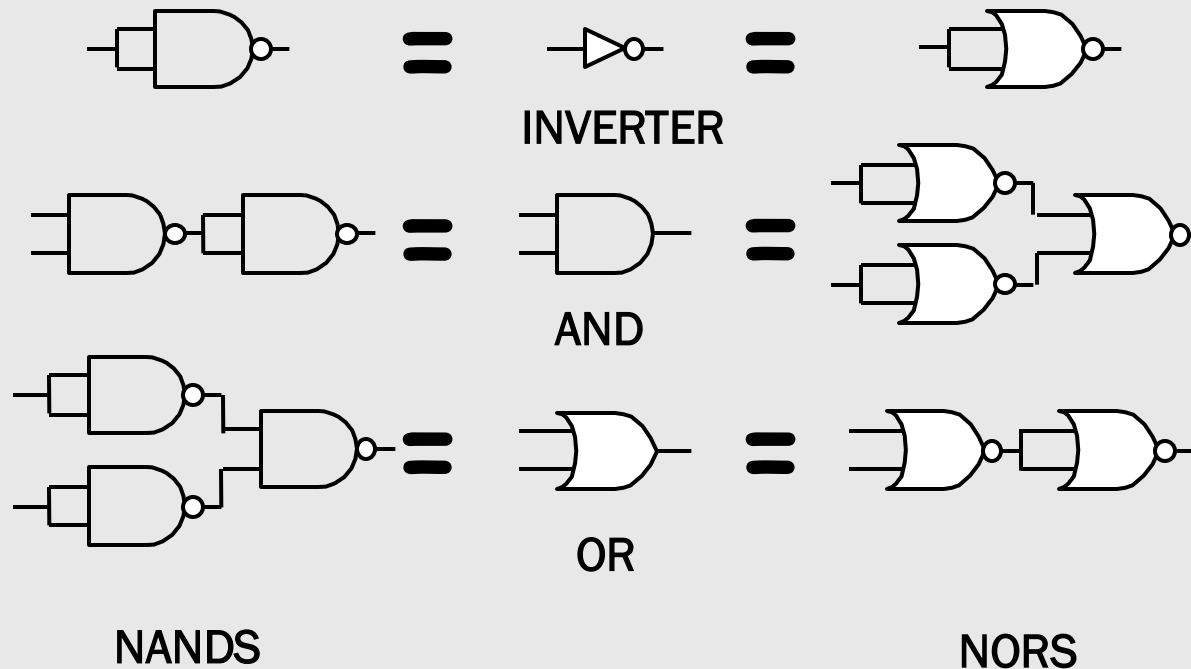

AND Gate

Symbol

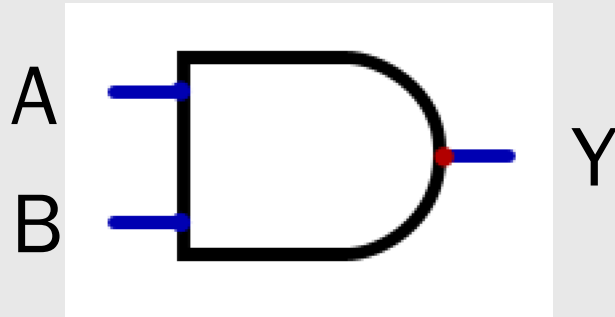

Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Equation

$$Y = \overline{A \times B}$$


$$Y = AB$$

$$Y = A \neq B$$

$$Y = A \cdot B$$

OR Gate

Symbol

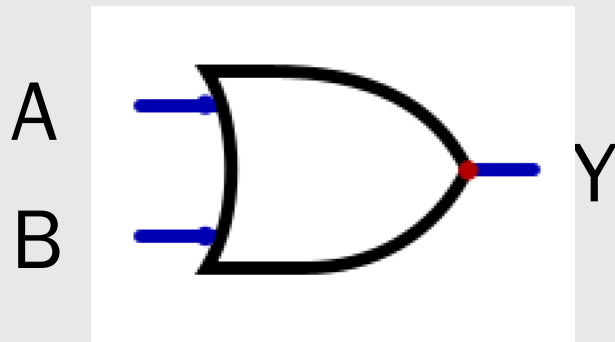

Truth Table


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Equation

$$Y = A + B$$

XOR Gate

Symbol

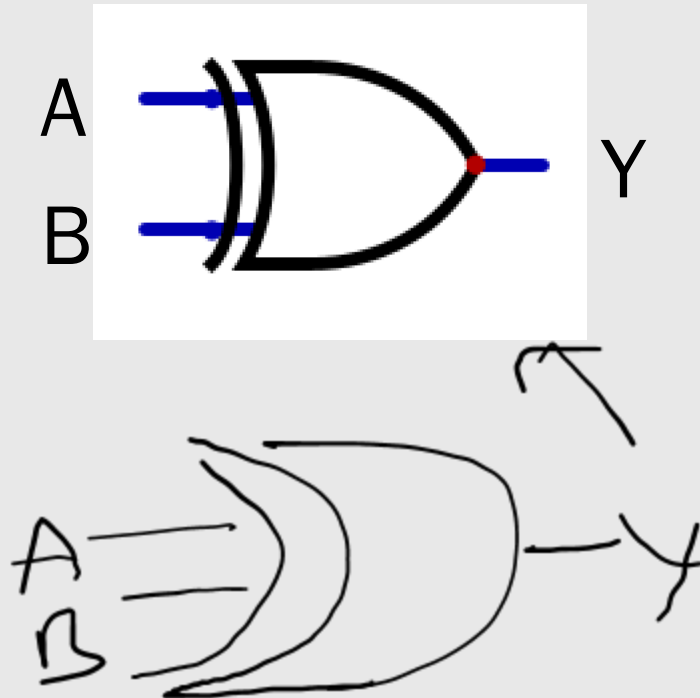

Truth Table

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


Equation

$$Y = A \oplus B$$



NAND

Symbol

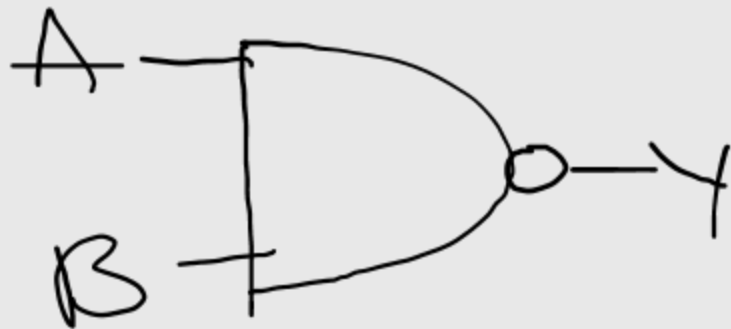

Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


Y¹
0
0
0
1

Equation

$$Y = \overline{A \times B}$$



or

$$Y = \overline{AB}$$

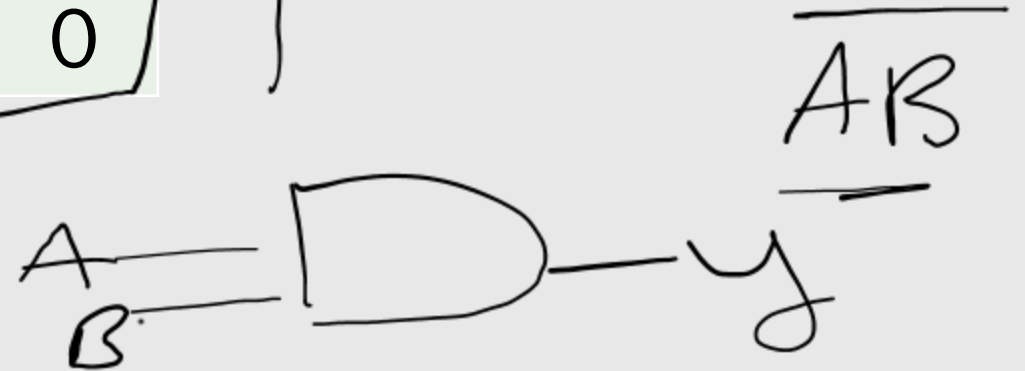

NOR

Symbol

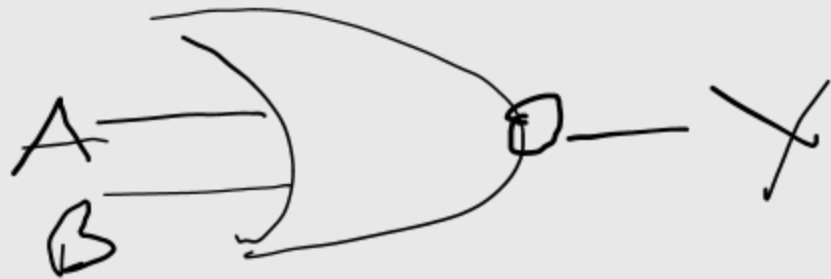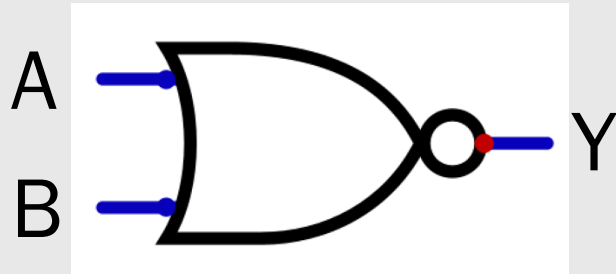

Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


0 1 1 1

Equation

$$Y = \overline{A + B}$$

XNOR Gate

Symbol

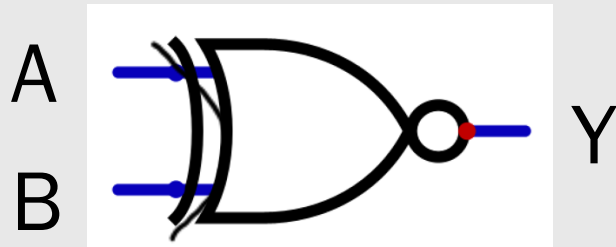


Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Equation

$$Y = \overline{A \oplus B}$$

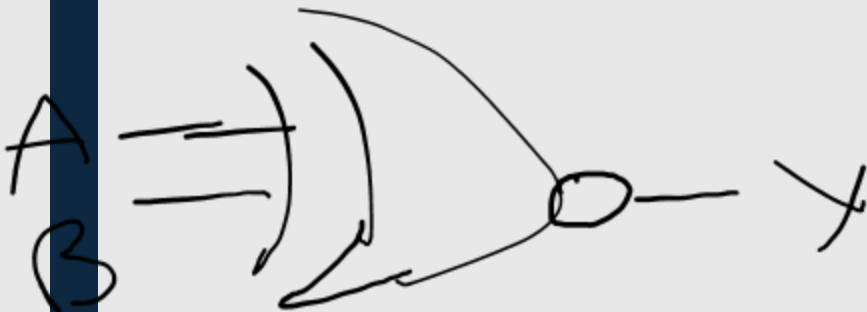




FORMING EQUATIONS FROM LOGIC DIAGRAMS




Ex1: Forming Equations from Logic Diagrams

$$Y = AB + CD$$

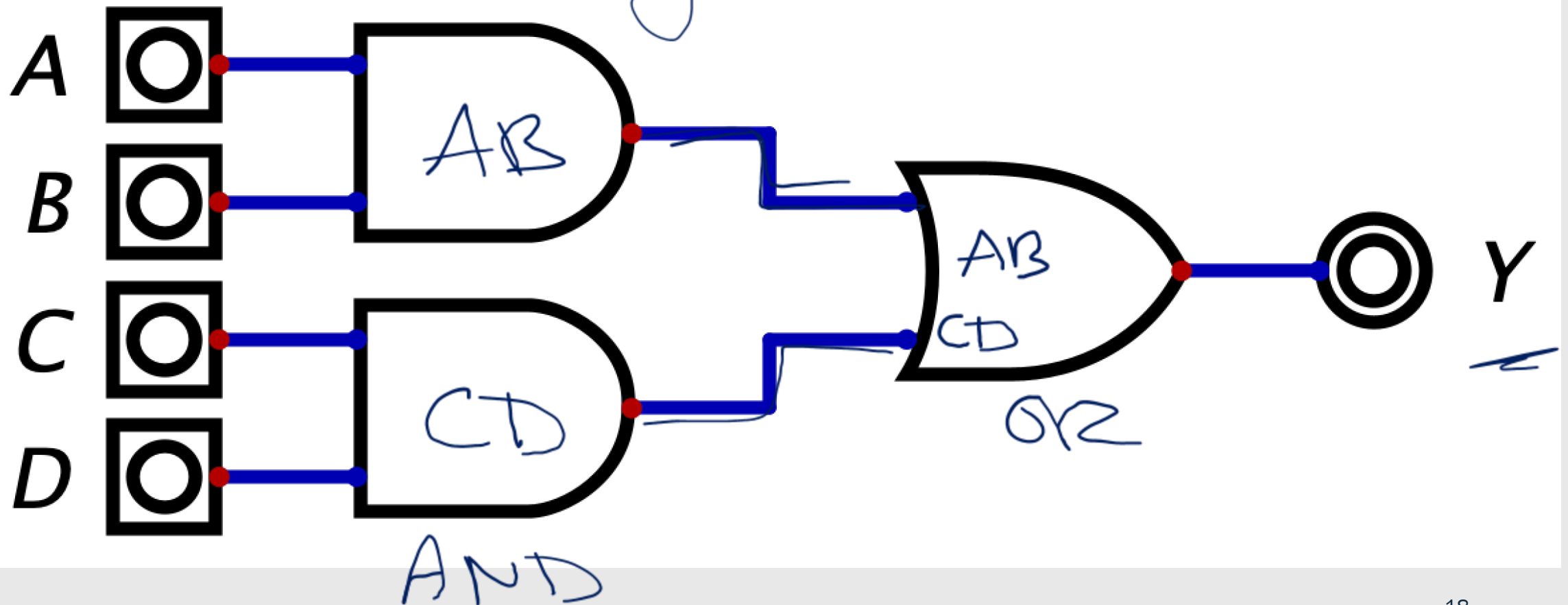


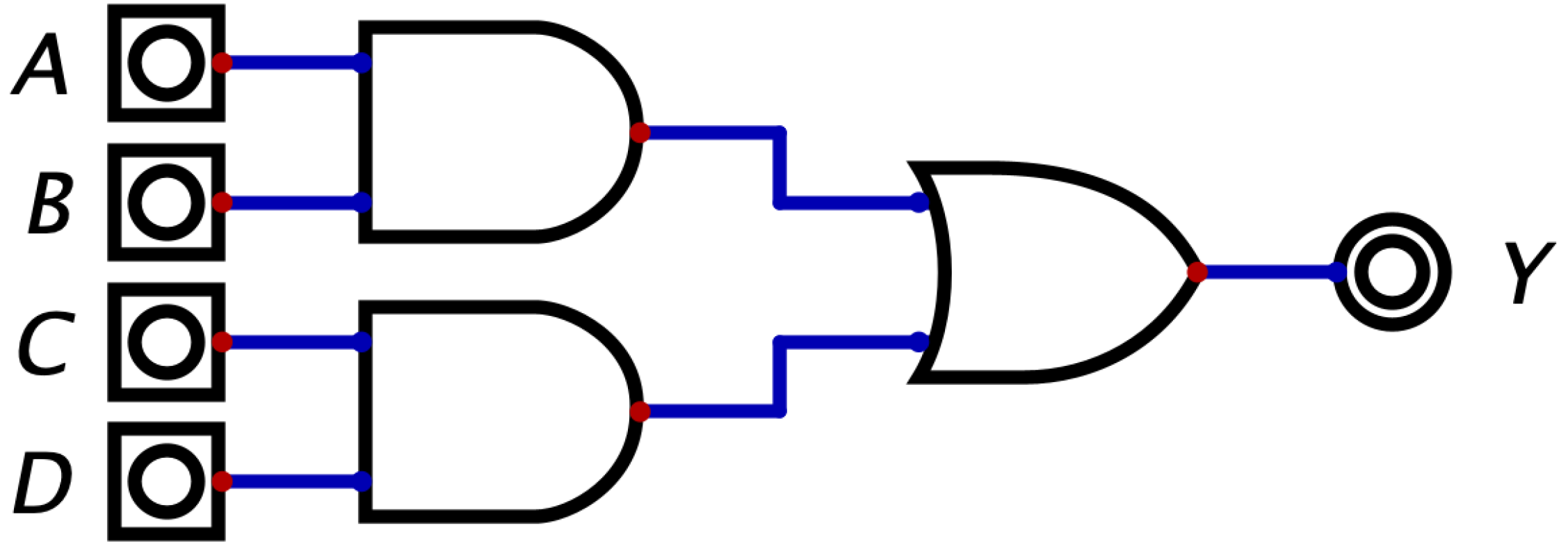Ex1: Forming Equations from Logic Diagrams




$$Y = AB + CD$$

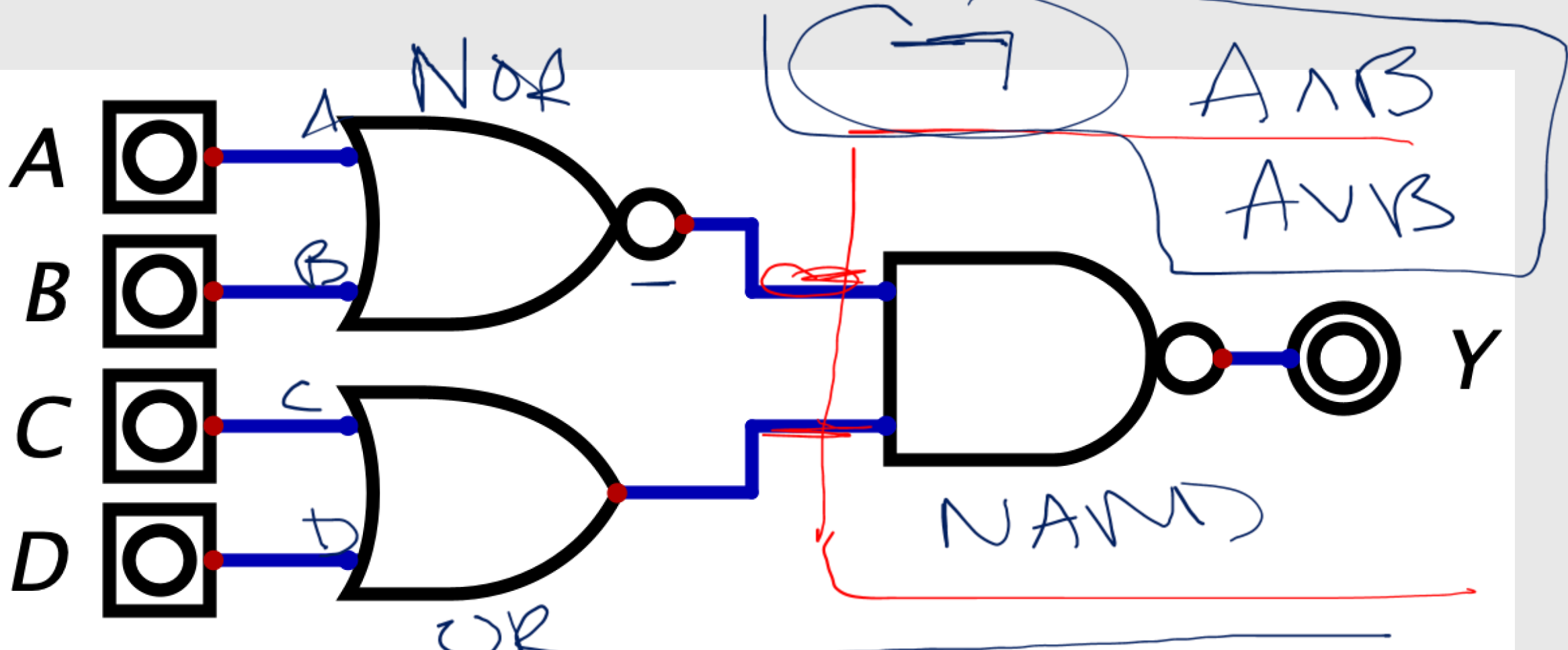Ex2: Forming Equations from Logic Diagrams




$$\rightarrow y = (A + B)(C + D)$$

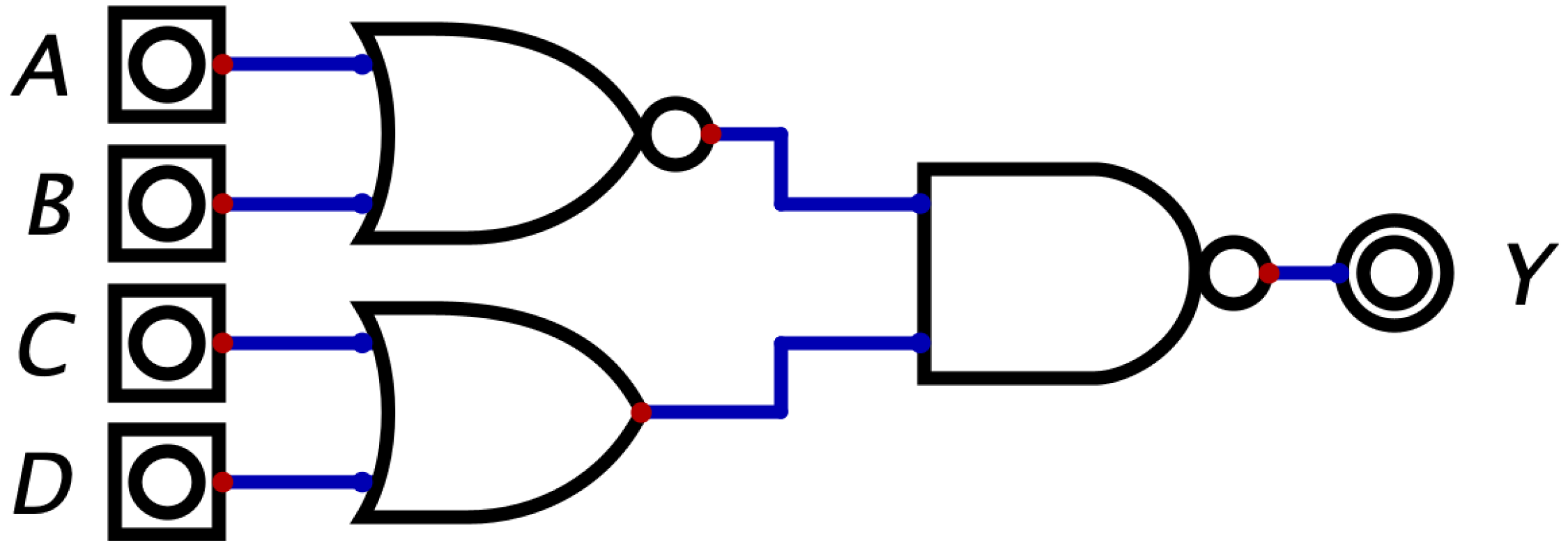Ex2: Forming Equations from Logic Diagrams




$$Y = \overline{(\overline{A + B})(C + D)}$$

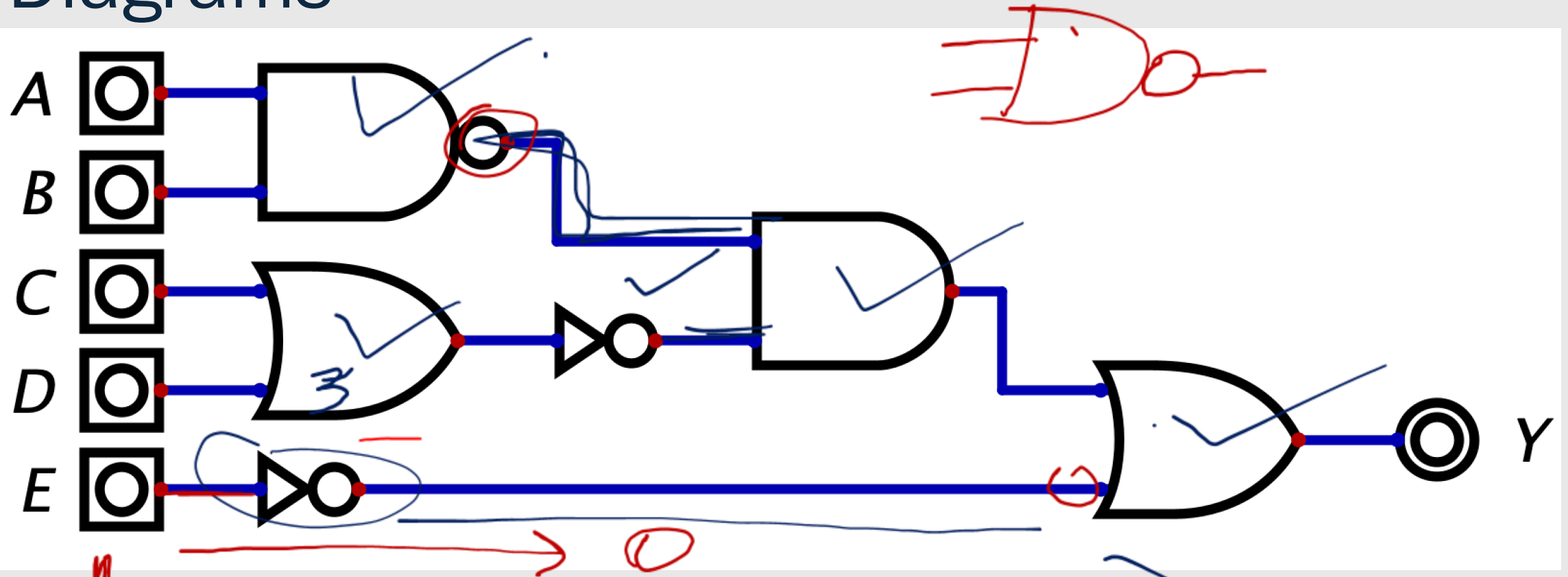Ex3: Forming Equations from Logic Diagrams




$$Y = \overline{(AB)} \cdot \overline{(C + D)} + \overline{E}$$

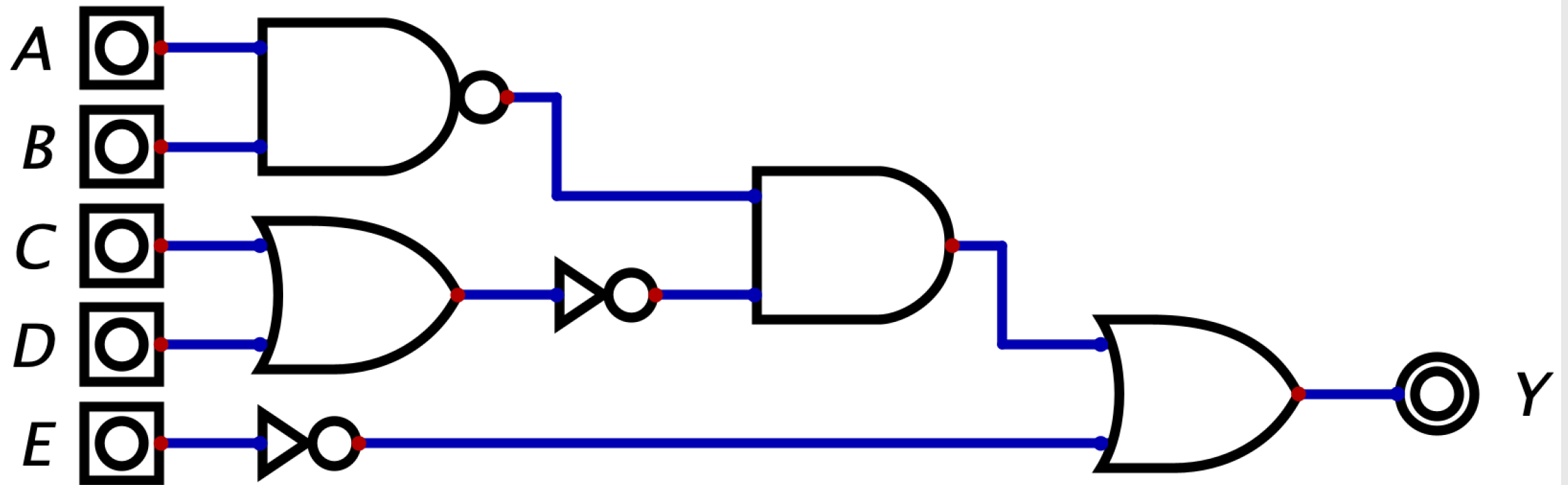Ex3: Forming Equations from Logic Diagrams



$$Y = (\overline{AB})(\overline{C + D}) + \overline{E}$$

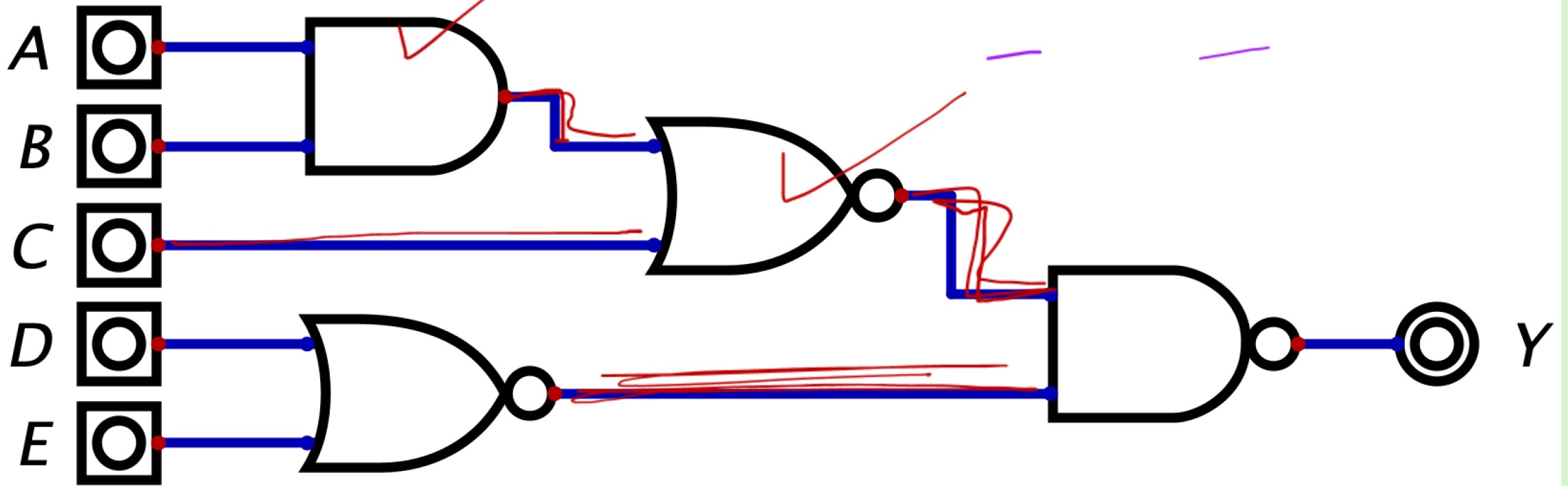
EX4: Forming Equations from Logic Diagrams




$$Y = (\overline{AB} + C)(D + E)$$




Forming Equations from Logic Diagrams

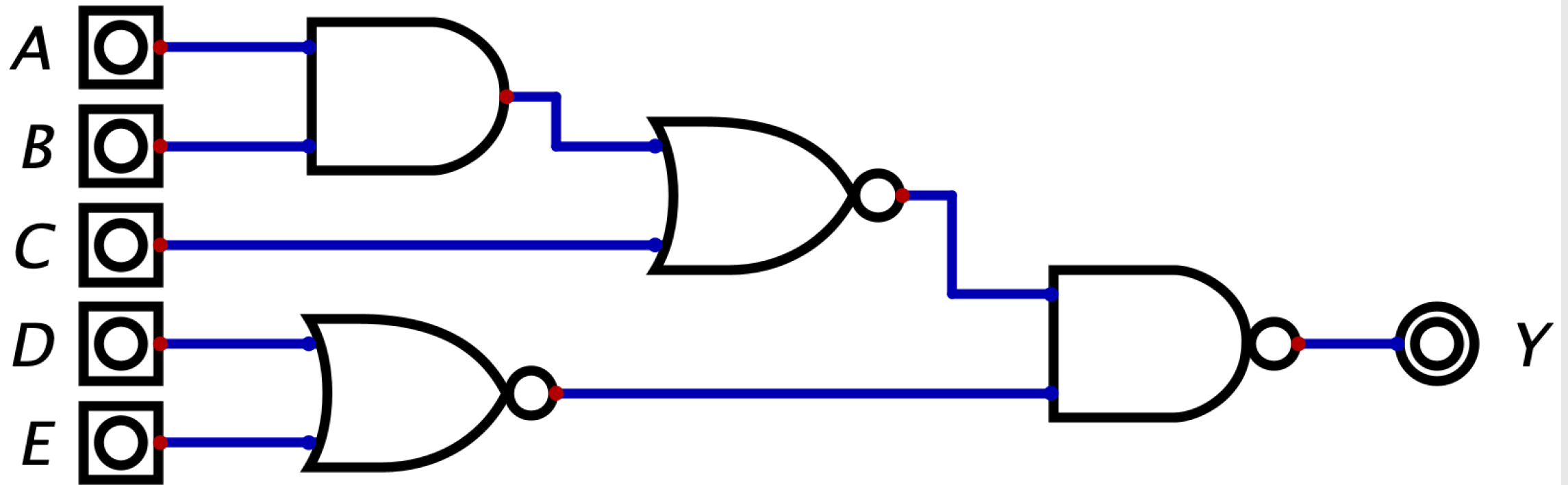

$$Y = \overline{(\overline{AB + C})(\overline{D + E})}$$




FORMING LOGIC DIAGRAMS FROM EQUATIONS

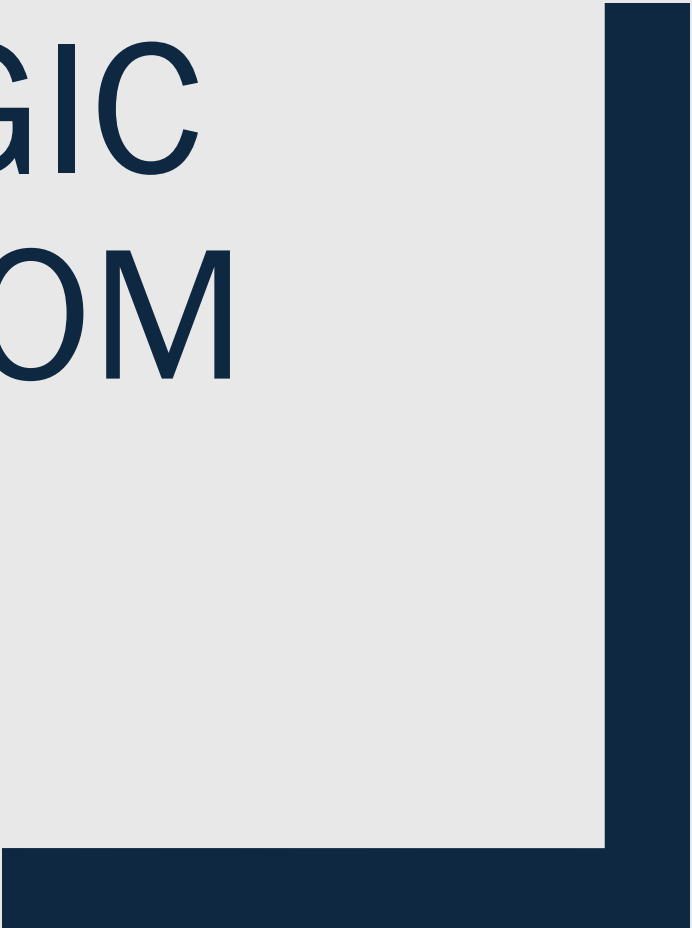


Ex1: Forming Logic Diagrams from Equations

$$Y = \overline{(A + B)}C$$

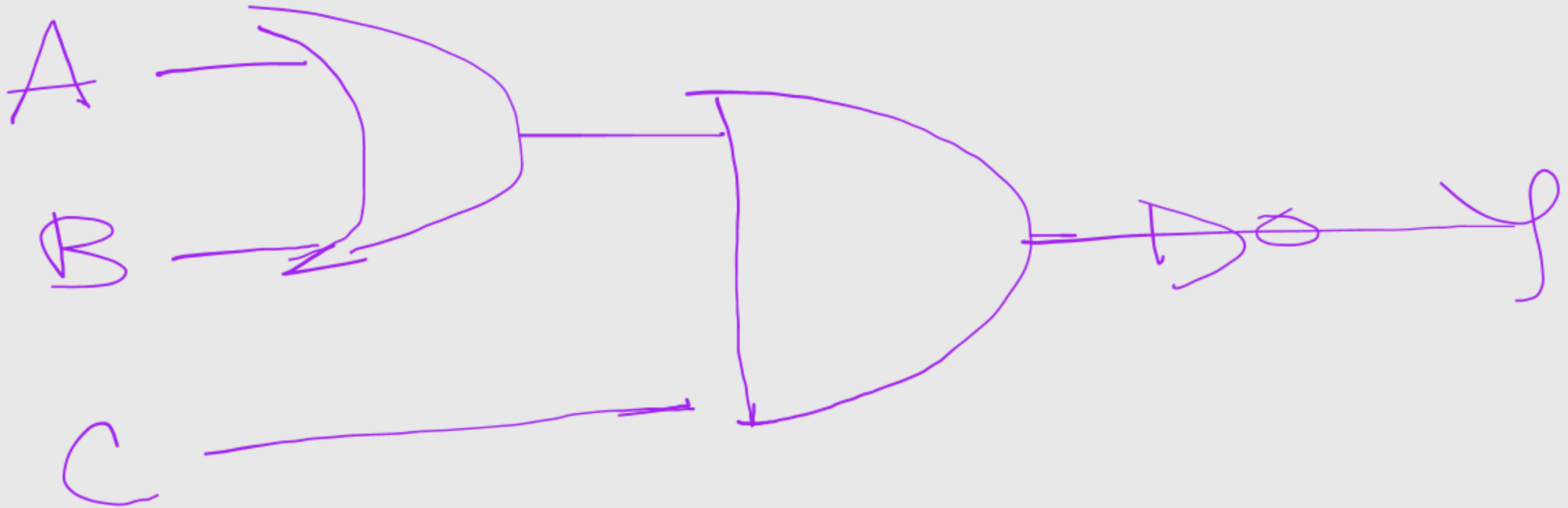


Ex1: Forming Logic Diagrams from Equations

$$Y = \overline{(A + B)C}$$

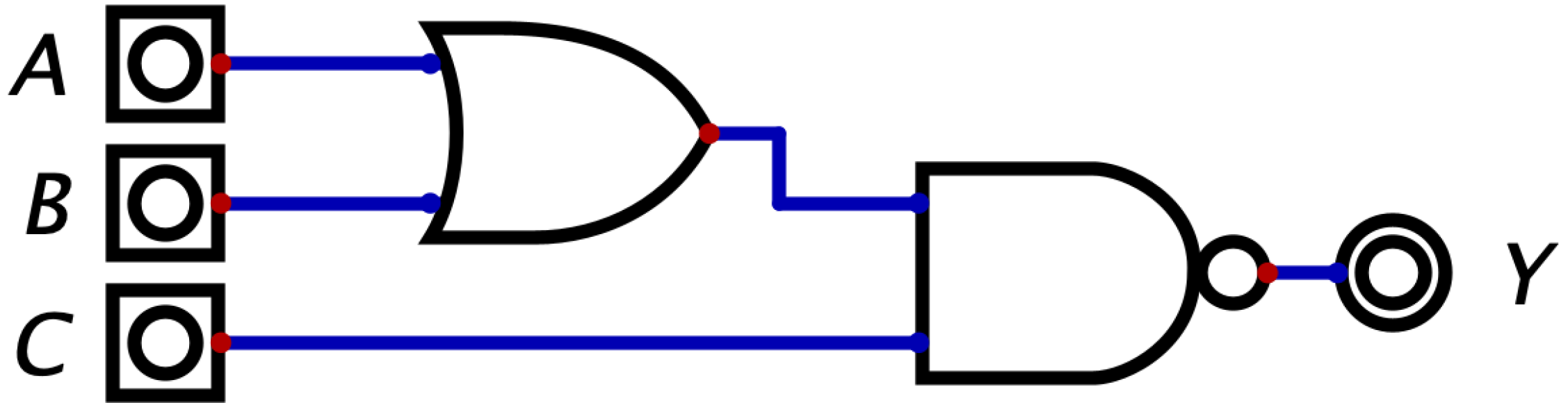


Ex2: Forming Logic Diagrams from Equations

$$Y = \overline{(A + B)}CD$$

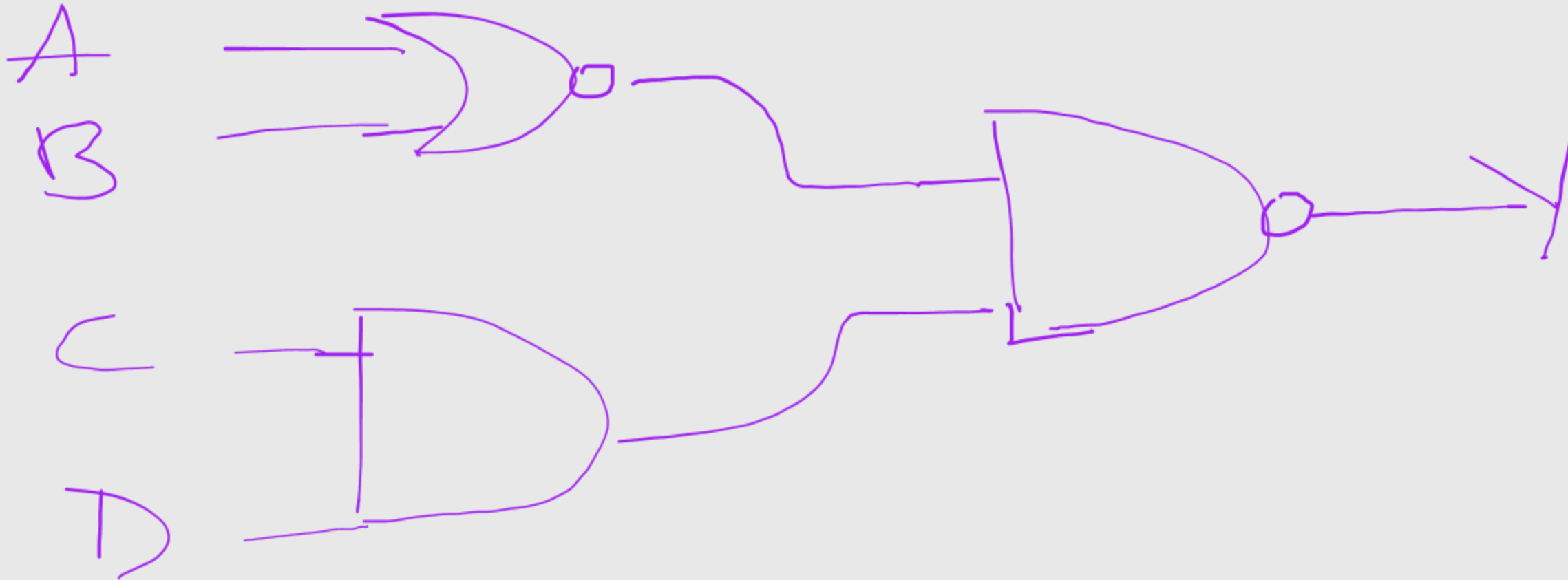

Ex2: Forming Logic Diagrams from Equations

$$Y = \overline{(A + B)}CD$$

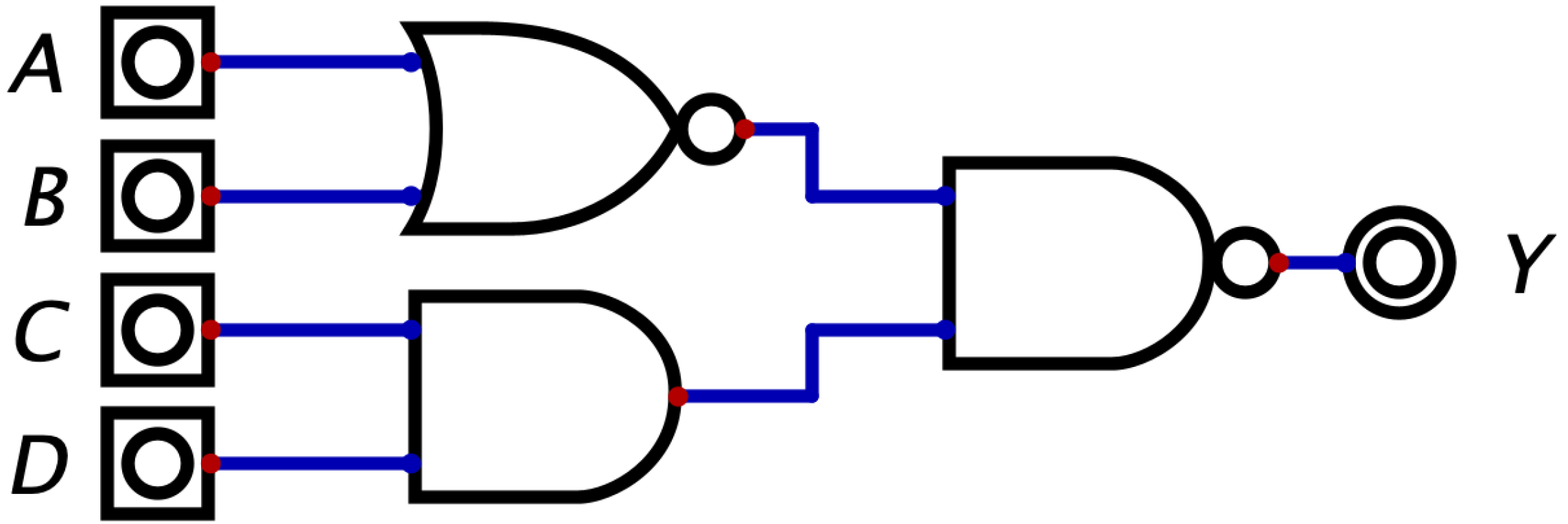


Ex3: Forming Logic Diagrams from Equations

$$Y = (\overline{A + B})(\overline{CD}) + E$$


Ex3: Forming Logic Diagrams from Equations

$$Y = \overline{(A + B)(\overline{CD})} + E$$

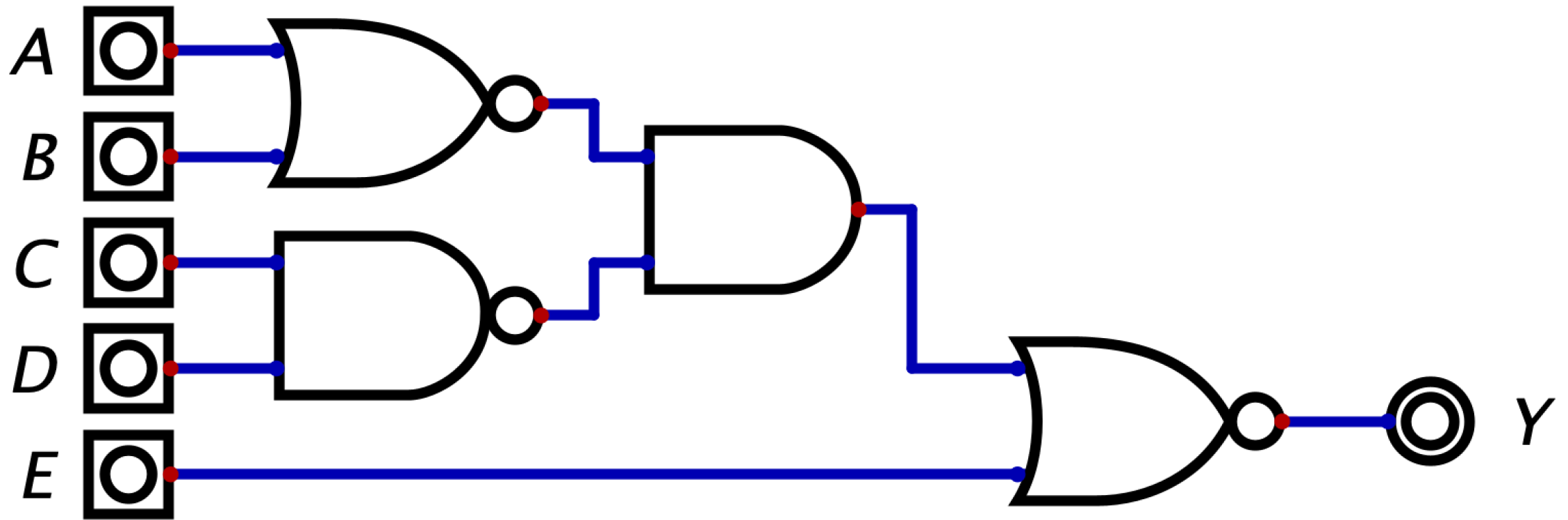


EX4: Forming Logic Diagrams from Equations
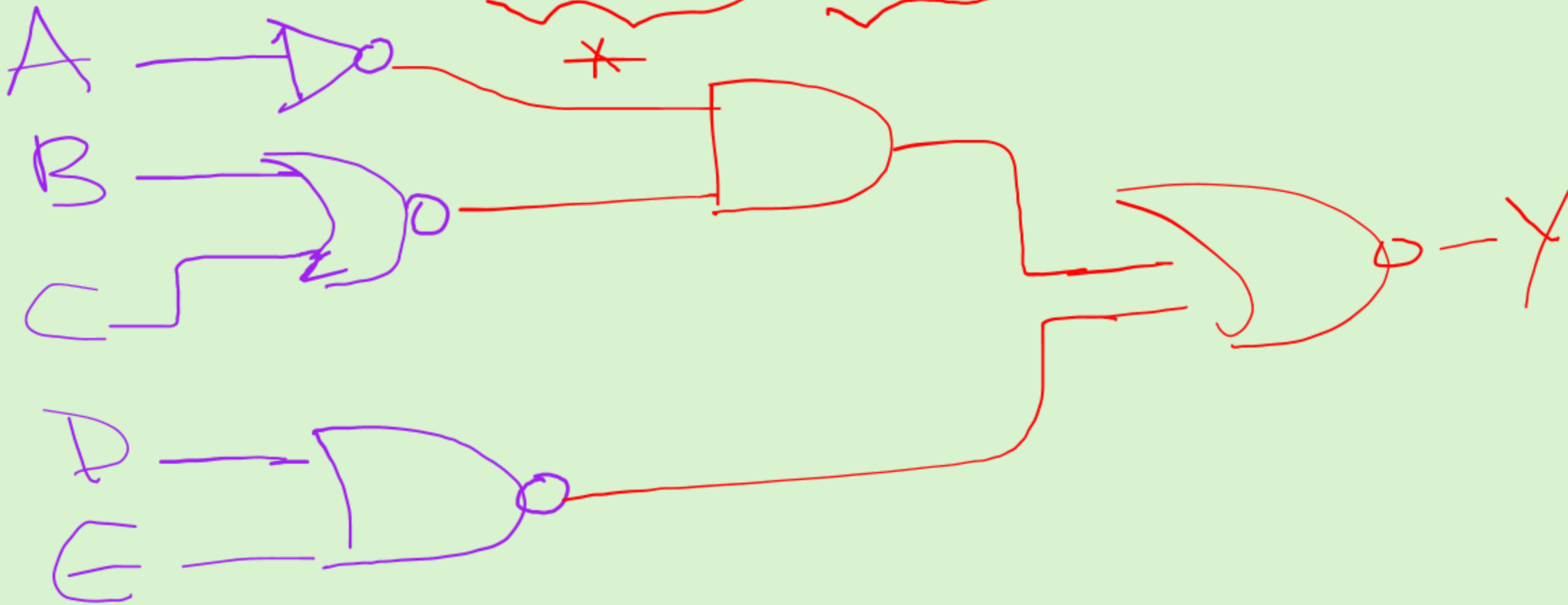
$$Y = (\bar{A})(\overline{B + C}) + \overline{DE}$$



Forming Logic Diagrams from Equations
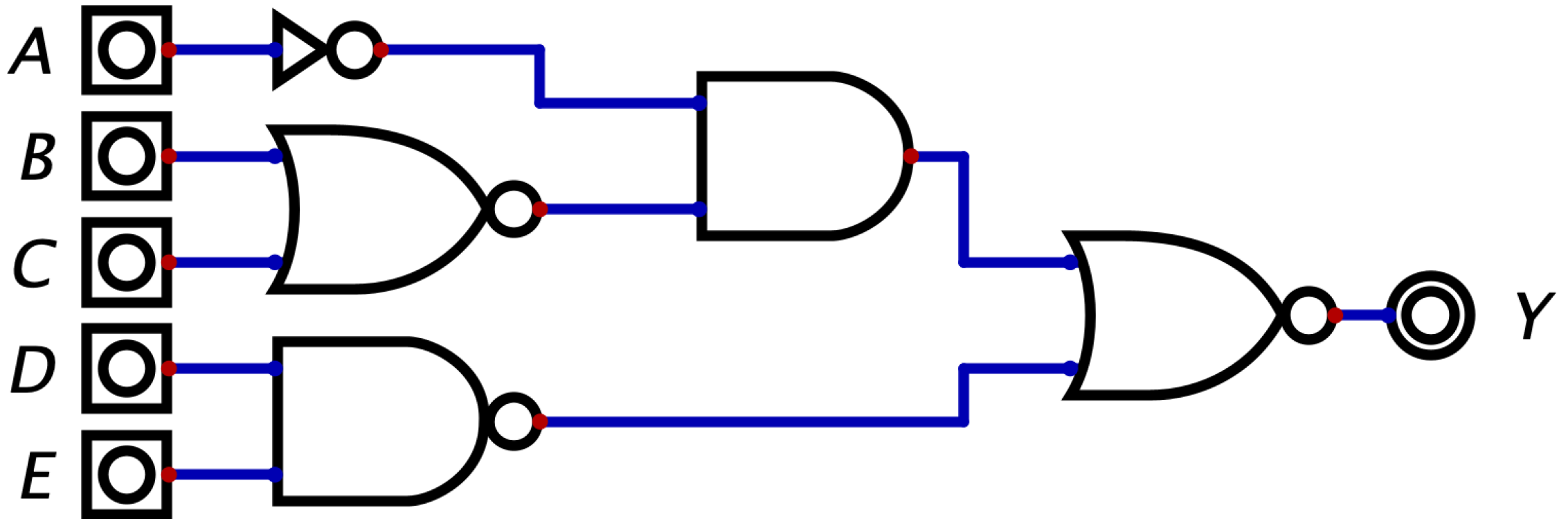
$$Y = \overline{(\bar{A})(\overline{B + C}) + \overline{DE}}$$





FORMING TRUTH TABLES FROM EQUATIONS

Ex1: Forming Truth Tables from Equations

$$Y = A + \bar{B}$$

$\rightarrow 1 + 0 \Rightarrow$

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	1

2 inputs \Rightarrow 4 rows

Ex1: Forming Truth Tables from Equations

$$Y = A + \bar{B}$$

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	1

3 inputs \implies 8 rows

Ex2: Forming Truth Tables from Equations

$$Y = \overline{AB} + \bar{C}$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Ex2: Forming Truth Tables from Equations

$$Y = AB + \bar{C}$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Ex3: Forming Truth Tables from Equations

$$Y = A + \bar{A}B\bar{C}$$

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Ex3:Forming Truth Tables from Equations

$$Y = A + \bar{A}B\bar{C}$$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Ex4: Forming Truth Tables from Equations

$$Y = \bar{A}\bar{B} + \overline{AB}$$

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Ex4: Forming Truth Tables from Equations

$$Y = \bar{A}\bar{B} + \overline{AB}$$

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0