

COMP311: *COMPUTER ORGANIZATION!*

Lecture 10: Adder Circuits (& More!)

tinyurl.com/comp311-fa25

Logistics!

- Written Assignment due next week!
- Lab 2 will be released today
- Quiz on Tuesday! Review session at 5pm on Monday (Location TBD)
- Quiz Topics
 - *Boolean Algebra + Simplification; SOP form*
 - *K-Maps*
 - *”Don’t Cares” (in relation to K-Maps, Truth Table Minimization)*
 - *Transistor Minimization (the lecture where we converted things into NAND/NOR gates)*
 - *Multiplexors*

Name	OR Form	AND Form
Identity	$A + 0 = A$	$A \cdot 1 = A$
Null	$A + 1 = 1$	$A \cdot 0 = 0$
Idempotent	$A + A = A$	$A \cdot A = A$
Complement	$\bar{A} + A = 1$	$A \cdot \bar{A} = 0$
Commutative	$A + B = B + A$	$A \cdot B = B \cdot A$
Associative	$(A + B) + C = A + (B + C)$	$(A \cdot B) \cdot C = A \cdot (B \cdot C)$
Distributive	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$	$A + (B \cdot C) = (A + B) \cdot (A + C)$
Absorption 1	$A + AB = A$	$A(A + B) = A$
Absorption 2	$A + \bar{A}B = A + B$	$\bar{A}(A + B) = \bar{A}B$
De Morgan's	$\overline{A \cdot B} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A} \cdot \bar{B}$

Table 1: Boolean Laws

Gate	Number of Transistors
Inverter	2
n-input NAND	2n
n-input NOR	2n
n-input AND	2n + 2
n-input OR	2n + 2

Table 2: Transistor Count

Reminder of where we are going!

A Circuit for If-Statements

if ($S == 0$)

$Y = A$

elseif ($S == 1$)

$Y = B$

Implementing an if-statement

Truth Table


S	A	B	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

S	A	B	Y
0	0	X	0
0	1	X	1
1	X	0	0
1	X	1	1

Equation


$$Y = \underline{A}\bar{S} + \underline{B}S$$

Diagram

 


 2:1 Multiplexer (2:1 mux)

- A circuit that chooses an output from among two inputs based on the value of a select signal




2:1 Multiplexer Schematic
(Gate Diagram)

 

2:1 Multiplexer Symbol

 4:1 Multiplexer (4:1 mux)

- A circuit that chooses an output from among four inputs based on the value of a select signal



When $S = 0b00$, $Y = A$


When $S = 0b01$, $Y = B$

When $S = 0b10$, $Y = C$

When $S = 0b11$, $Y = D$

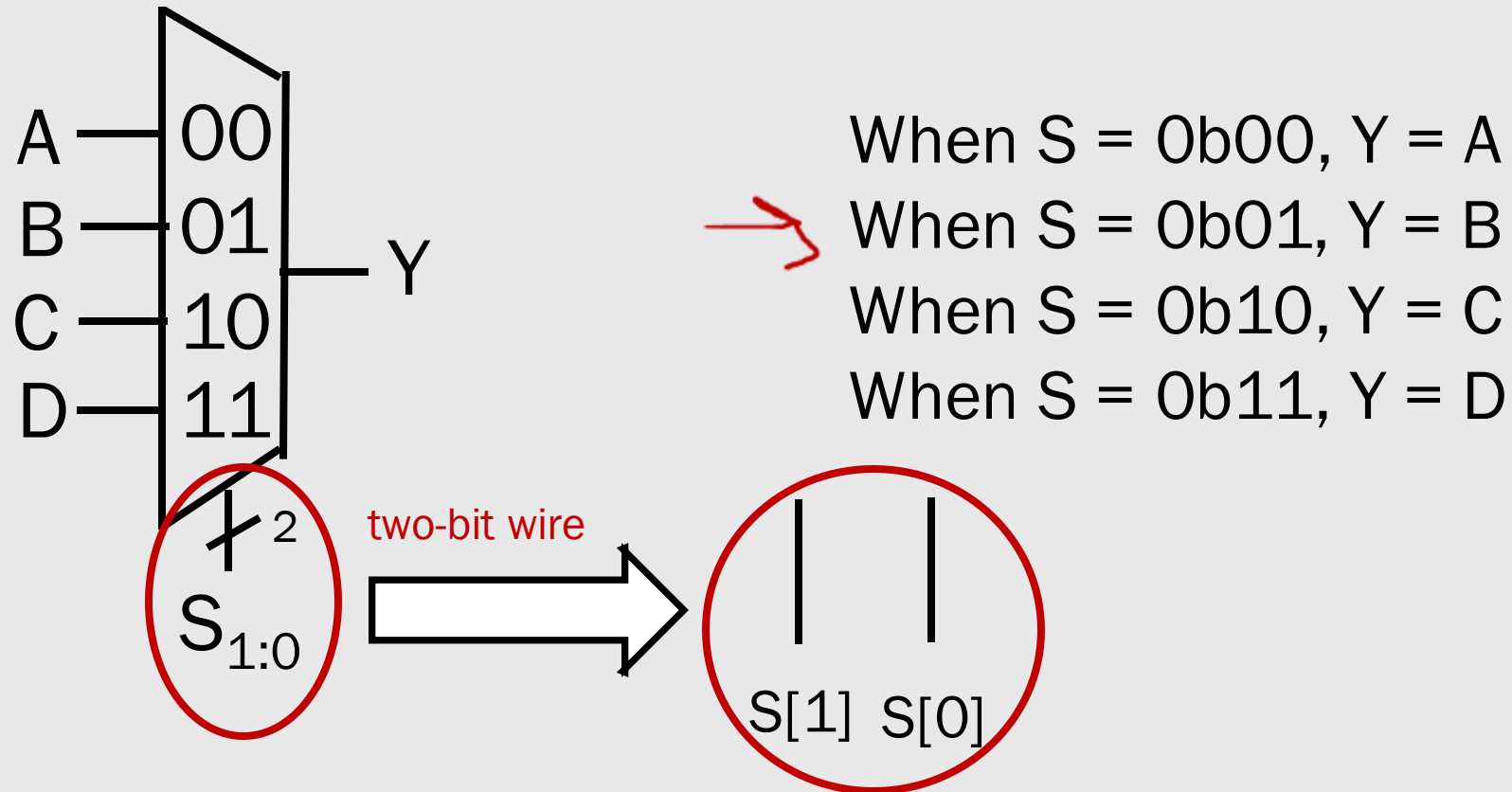4:1 Multiplexer (4:1 mux)

- A circuit that chooses an output from among four inputs based on the value of a select signal



Create the gate-level implementation of a 4:1 Multiplexer (4:1 mux)

1. Draw the truth table
2. Find the equation
3. Draw the schematic

Create the gate-level implementation of a 4:1 Multiplexer (4:1 mux)

S1	S0	A	B	C	D	Y
0	0	0	X	X	X	0
0	0	1	X	X	X	1
0	1	X	0	X	X	0
0	1	X	1	X	X	1
1	0	X	X	0	X	0
1	0	X	X	1	X	1
1	1	X	X	X	0	0
1	1	X	X	X	1	1

$$Y = A\bar{S}_1\bar{S}_0 + B\bar{S}_1S_0 + CS_1\bar{S}_0 + D S_1S_0$$

4:1 Multiplexer (4:1 mux)

Equation

$$Y = A\bar{S}_1\bar{S}_0 + B\bar{S}_1S_0 + CS_1\bar{S}_0 + D S_1S_0$$


Diagram

4:1 Multiplexer (4:1 mux)

Equation

$$Y = A\bar{S}_1\bar{S}_0 + B\bar{S}_1S_0 + CS_1\bar{S}_0 + D S_1S_0$$

Diagram

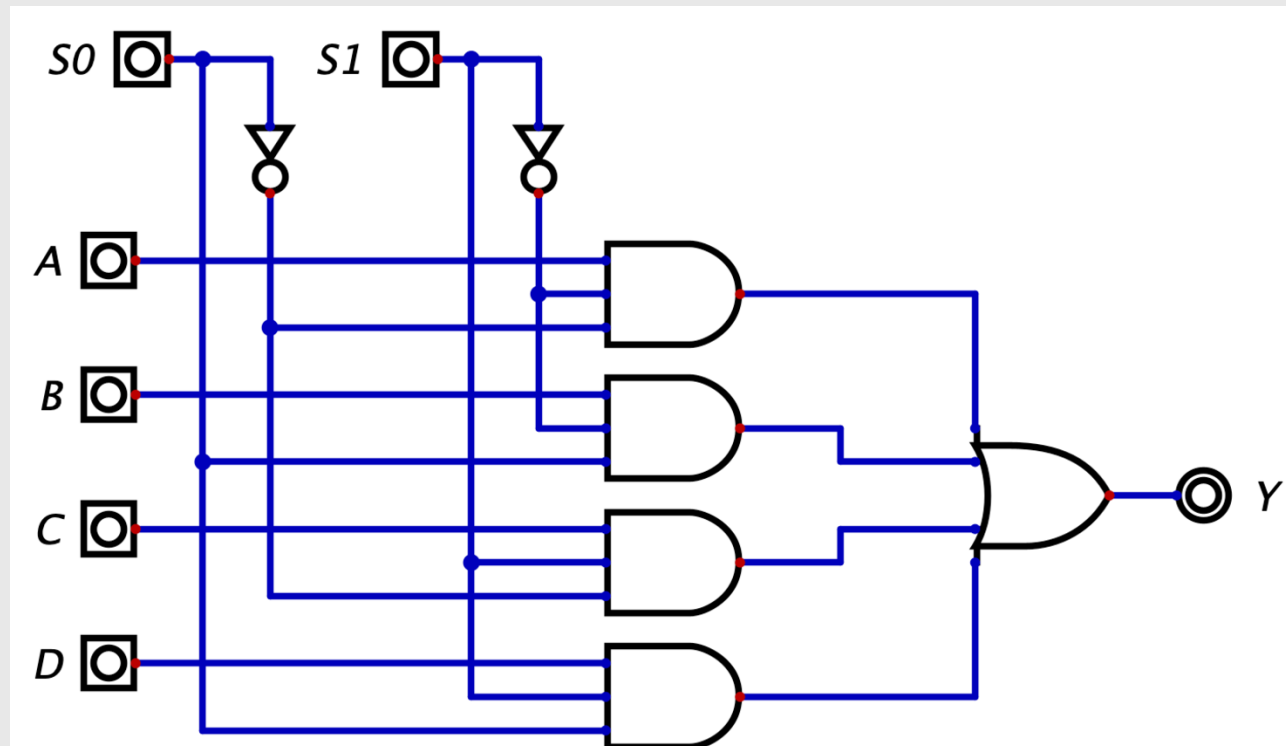

Multiplexers

- Create a 4:1 multiplexer out of 2:1 multiplexers.

A

B

C

D

S_1

S_0


S_1	S_0	Y
0	0	A
0	1	B
1	0	C
1	1	D

Y

Multiplexers

- Create a 4:1 multiplexer out of 2:1 multiplexers.

S1	S0	Y
0	0	A
0	1	B
1	0	C
1	1	D

 




ADDER CIRCUIT!



Recall: Binary Addition

$$\begin{array}{r} + 101 \\ 111 \\ \hline \end{array}$$

Recall: Binary Addition

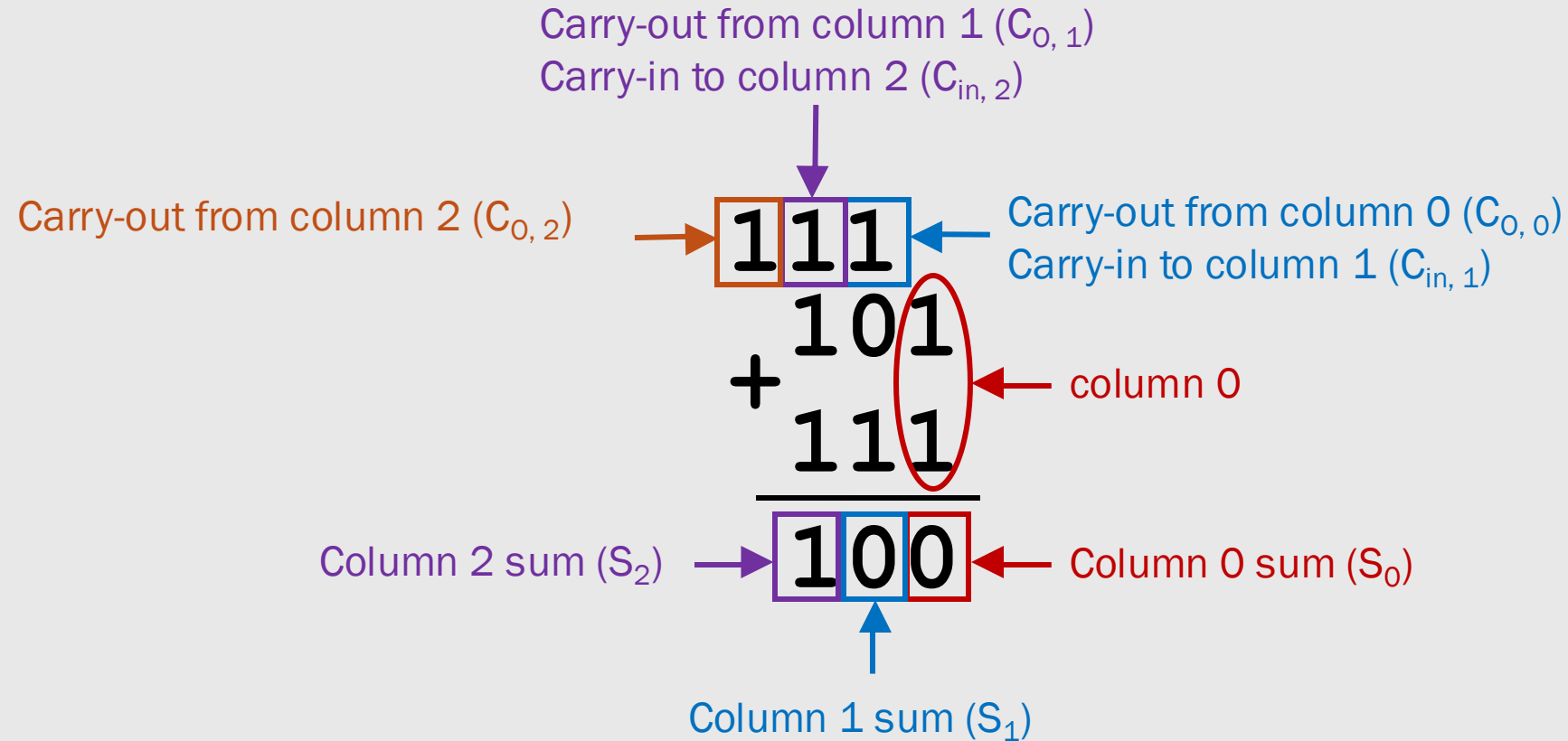

Half Adder


- We'll start off by building a circuit that can add together two one-bit values
- This circuit will be able to add together the two bits in column 0

$$\begin{array}{r} 111 \\ + 101 \\ \hline 111 \\ \hline 100 \end{array}$$

Half Adder

- We'll start off by building a circuit that can add together two one-bit values
- This circuit will be able to add together the two bits in column 0
 
$$\begin{array}{r} 111 \leftarrow \text{Output: } C_0 \\ + 101 \leftarrow \text{Input: } A \\ + 111 \leftarrow \text{Input: } B \\ \hline 100 \leftarrow \text{Output: } S \end{array}$$



Half Adder

A	B	C ₀	S
0	0		
0	1		
1	0		
1	1		

$$\begin{array}{r} + 0 \\ 0 \\ \hline \end{array}$$


$$\begin{array}{r} + 0 \\ 1 \\ \hline \end{array}$$

$$\begin{array}{r} + 1 \\ 0 \\ \hline \end{array}$$

$$\begin{array}{r} + 1 \\ 1 \\ \hline \end{array}$$

Half Adder

A	B	C ₀	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

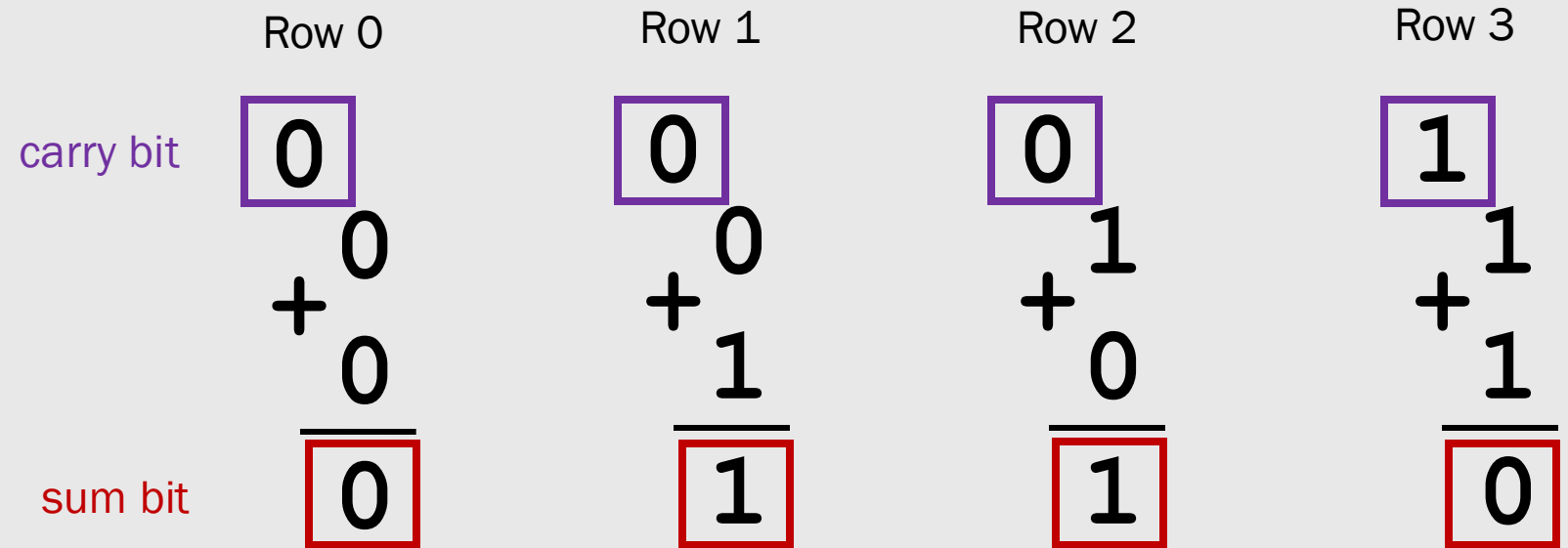


Half Adder

A	B	C_0	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_0 = AB$$

 

Full Adder

- We need to build a circuit that can add together three one-bit values


$$\begin{array}{r} 111 \\ + 101 \\ + 111 \\ \hline 100 \end{array}$$

Full Adder


- This circuit will be able to add together the three bits in column 1

Output: C_o

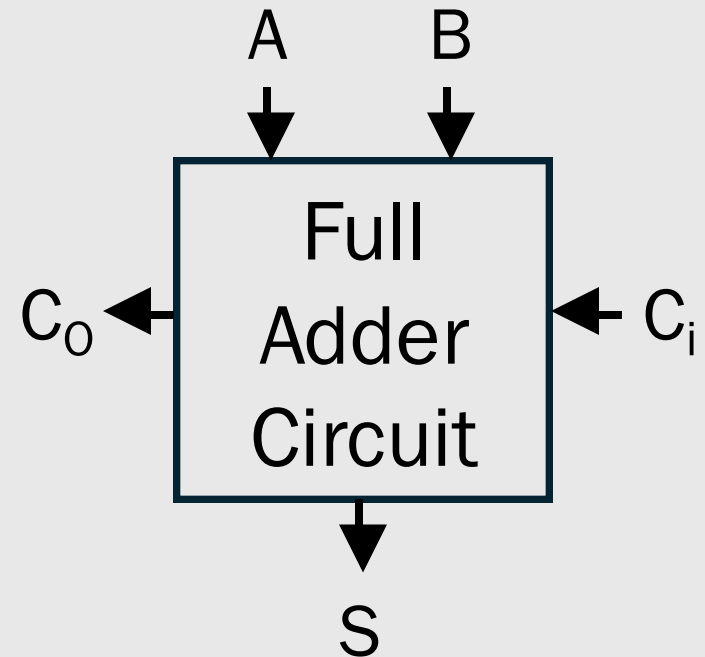
$$\begin{array}{r} \text{Input: } C_i \\ 111 \\ + \text{Input: } A \\ 101 \\ + \text{Input: } B \\ 111 \\ \hline \text{Output: } S \\ 100 \end{array}$$



Recall: 3-input XOR

 

logically
equivalent
circuits

 

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

For any number of inputs, the output is 1 when an odd number of inputs is 1

Transistor Count

Gate	# of Transistors
NOT	2
n-input AND	$2n + 2$
n-input OR	$2n + 2$
n-input NAND	$2n$
n-input NOR	$2n$
2-input XOR	12
3-input XOR	28
2-input XNOR	12
3-input XNOR	28

Create the gate-level implementation of a full adder

1. Draw the truth table
2. Find the equation
3. Draw the schematic. Try to minimize the circuit.
4. How many transistors does your solution use?

Full Adder

A	B	C_i	C_o	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Equations

Full Adder

Diagram

How many transistors are in this design?

Full Adder

A	B	C _i	C _o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_i$$


A \ BC _i	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$C_o = AC_i + AB + BC_i$$

Full Adder

$$S = A \oplus B \oplus C_i$$


$$C_o = AC_i + AB + BC_i$$

 

Full Adder: transistor minimization

$$S = A \oplus B \oplus C_i$$

$$C_o = AC_i + AB + BC_i$$

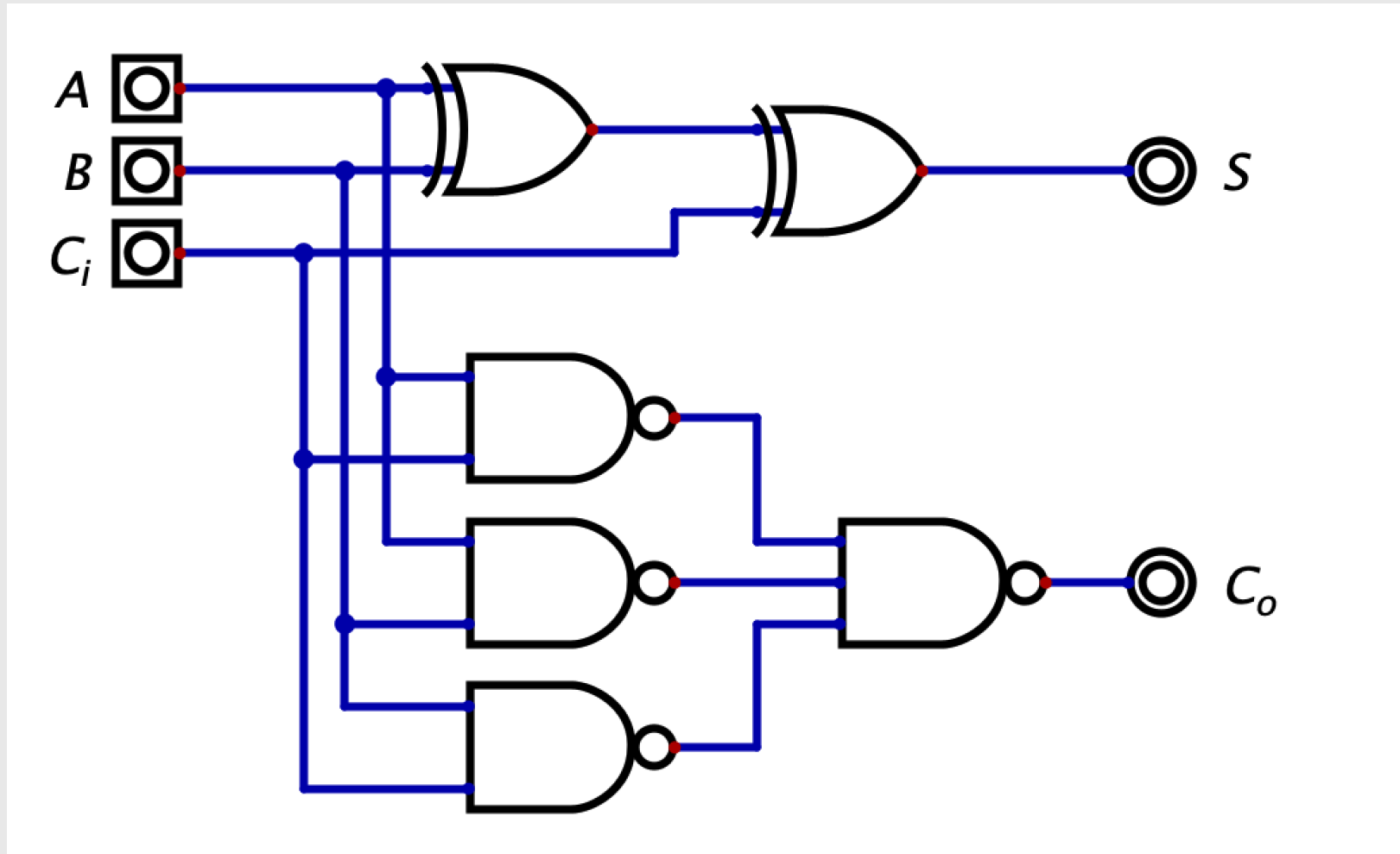




Full Adder: transistor minimization

$$S = A \oplus B \oplus C_i$$

$$C_o = AC_i + AB + BC_i$$

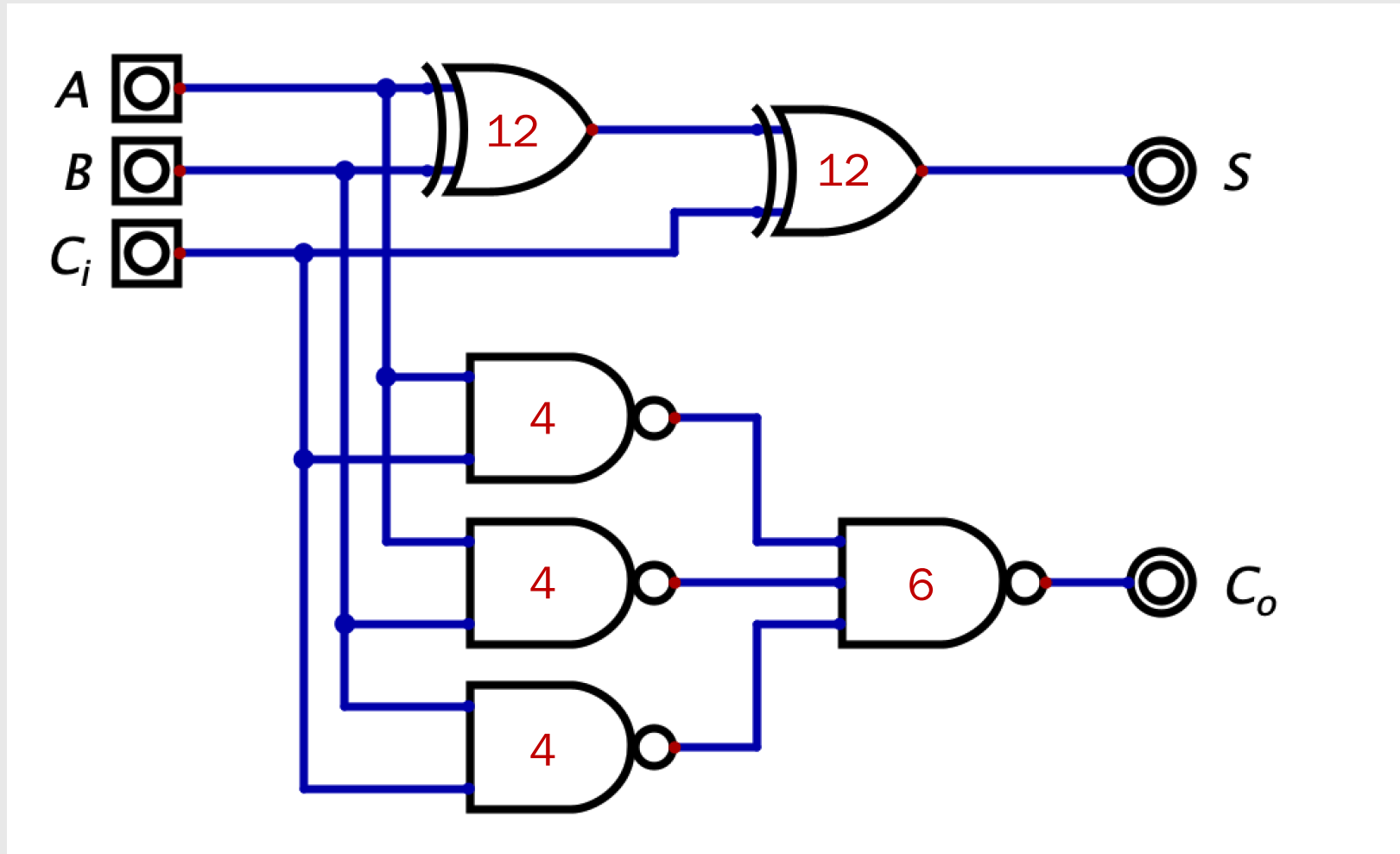

Transistor count = 42

Full Adder: Alternate implementation

A	B	C _i	C _o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C$$

$$C_o =$$

Full Adder: Alternate Implementation

A	B	C_i	C_o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C$$

$$C_o = \bar{A}BC_i + A\bar{B}C_i + AB\bar{C}_i + ABC_i$$

$$C_o = \bar{A}BC_i + A\bar{B}C_i + AB(\bar{C}_i + C_i)$$

$$C_o = \bar{A}BC_i + A\bar{B}C_i + AB$$


$$C_o = C_i(\bar{A}B + A\bar{B}) + AB$$

$$C_o = C_i(A \oplus B) + AB$$

Full Adder: Alternate Implementation

$$S = A \oplus B \oplus C_i$$


$$C_o = C_i(A \oplus B) + AB$$

 

Full Adder: Alternate Implementation

$$S = A \oplus B \oplus C_i$$


$$C_o = C_i(A \oplus B) + AB$$

 

Full Adder: Reducing Transistor Count


$$S = A \oplus B \oplus C_i$$

$$C_o = C_i(A \oplus B) + AB$$

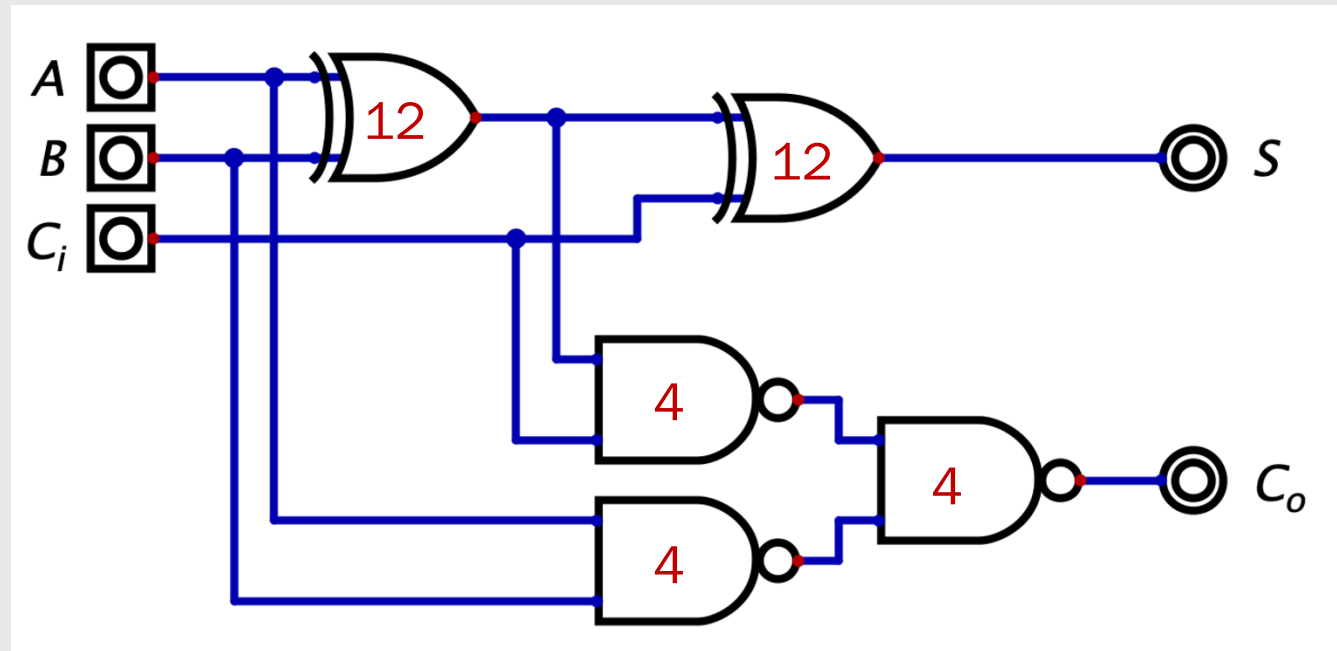

Transistor Count: 36

Full Adder Abstraction

 


4-bit Adder

$$\begin{array}{cccc} C_{0,3} & C_{0,2} & C_{0,1} & C_{0,0} \\ + & A_3 & A_2 & A_1 & A_0 \\ & B_3 & B_2 & B_1 & B_0 \\ \hline S_3 & S_2 & S_1 & S_0 \end{array}$$

4-bit Adder


- How would you use 4 full-adders to add together A and B?

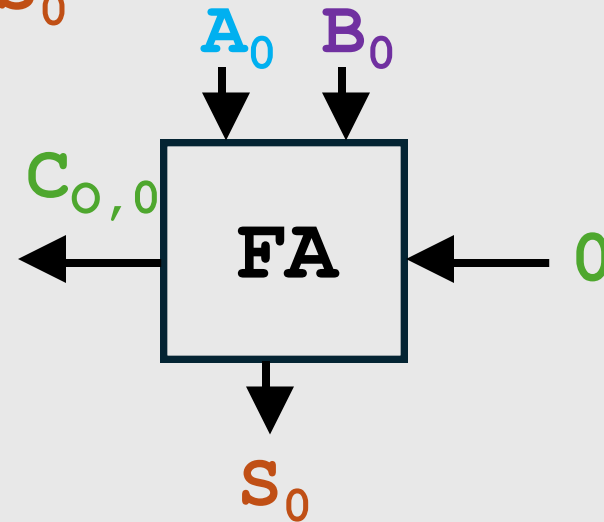
$$\begin{array}{cccc} C_{0,3} & C_{0,2} & C_{0,1} & C_{0,0} \\ + & A_3 & A_2 & A_1 & A_0 \\ & B_3 & B_2 & B_1 & B_0 \\ \hline S_3 & S_2 & S_1 & S_0 \end{array}$$




4-bit Adder
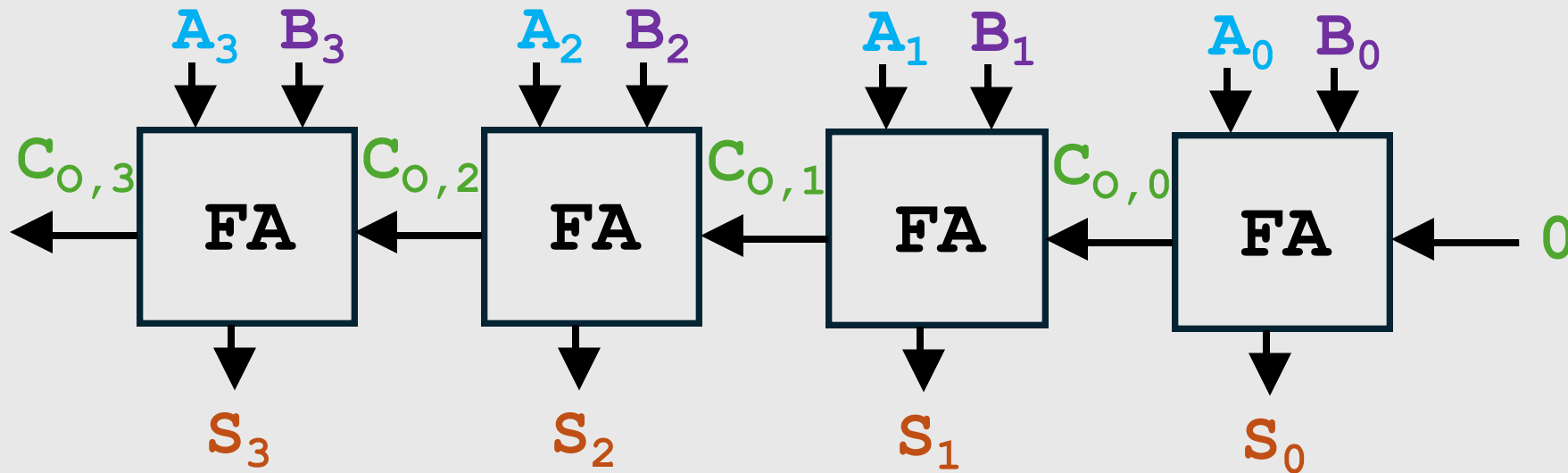
$$\begin{array}{r} C_{0,3} \ C_{0,2} \ C_{0,1} \ C_{0,0} \\ + \ A_3 \ A_2 \ A_1 \ A_0 \\ \quad B_3 \ B_2 \ B_1 \ B_0 \\ \hline S_3 \ S_2 \ S_1 \ S_0 \end{array}$$





ADDER-SUBTRACTOR CIRCUIT



Recall: Two's Complement

Ex: Represent -15 in two's complement with 7 bits

- To represent a negative number, take the positive representation of the number, flip the bits, and add 1

Unsigned: 0b 000 1111

Flip bits: 0b 111 0000

Add one: 0b 111 0001

Recall Two's Complement Subtraction

$$\begin{array}{r} -10 \\ - 4 \\ \hline -14 \end{array}$$

$$\begin{array}{r} 10110_2 \\ - 00100_2 \\ \hline \end{array}$$

$$A - B == A + (-B)$$



Equivalent
Operations

$$\begin{array}{r} -10 \\ + -4 \\ \hline -14 \end{array}$$

$$\begin{array}{r} 10110_2 \\ + 11100_2 \\ \hline 10010_2 \end{array}$$

Subtraction

- Instead of building a separate circuit for subtraction, we will modify the ripple carry adder such that it can perform addition and subtraction
- When we want to perform $A - B$
 - *We will actually perform $A + (-B)$*
 - *We need to modify our circuit such that it can negate B*

Subtraction

- Let's say that we want to perform the operation $A - B$ where $A = 5$ and $B = 1$.
- We will modify the circuit such that it can flip each bit of B and add 1.

$$\begin{array}{r} 0101_2 \\ - 0001_2 \\ \hline \end{array}$$

$$\begin{array}{r} 0101_2 \\ + 1110_2 \\ + 1_2 \\ \hline 0100_2 \end{array}$$

Keep A the same

Flip the bits of B

Add 1

Subtractor


A_3 B_3

A_2 B_2

A_1 B_1


A_0 B_0

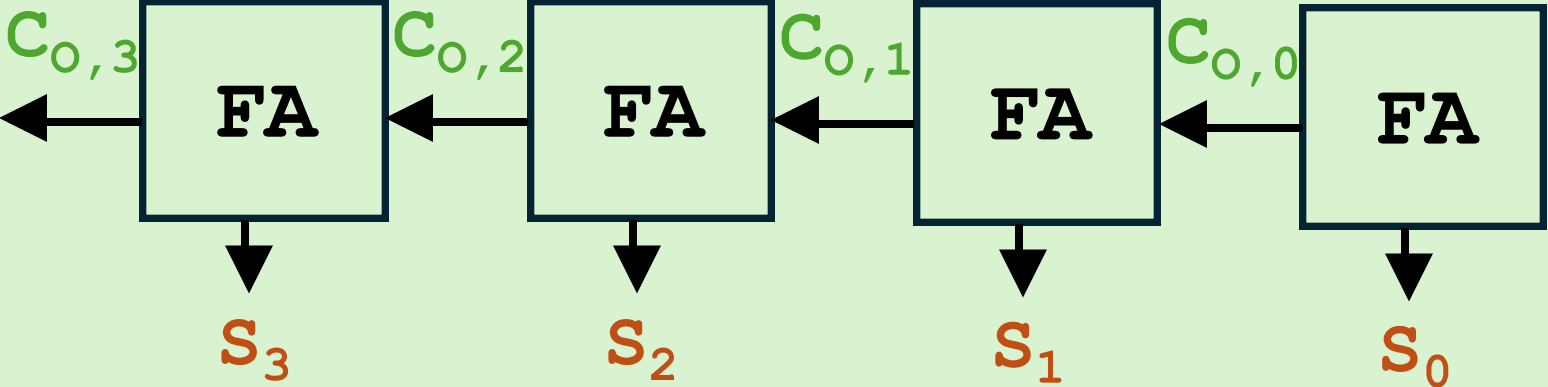How would you wire up this circuit to have it correctly perform subtraction?





Subtractor

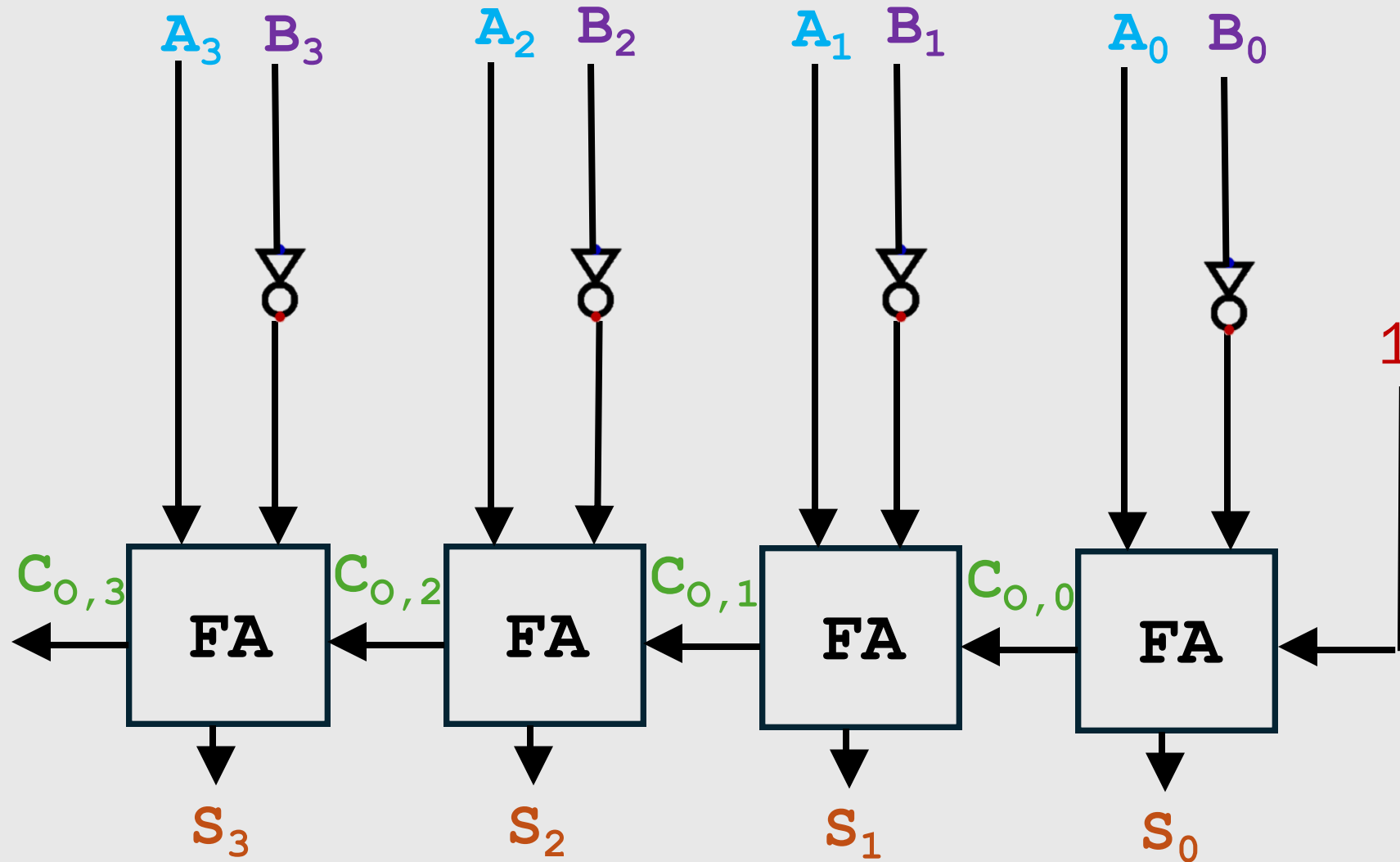


Adder/subtractor

A_3 B_3

A_2 B_2

A_1 B_1

A_0 B_0

 


K If $K == 0$, $A + B$
If $K == 1$, $A - B$

Hints

- To perform subtraction, we must take the 2's complement of B. To take 2's complement, we must flip the bits and add one.
 - *What component can we use to flip bits?*
 - *Where in the circuit can we add 1?*

Adder/Subtractor Implementation 1

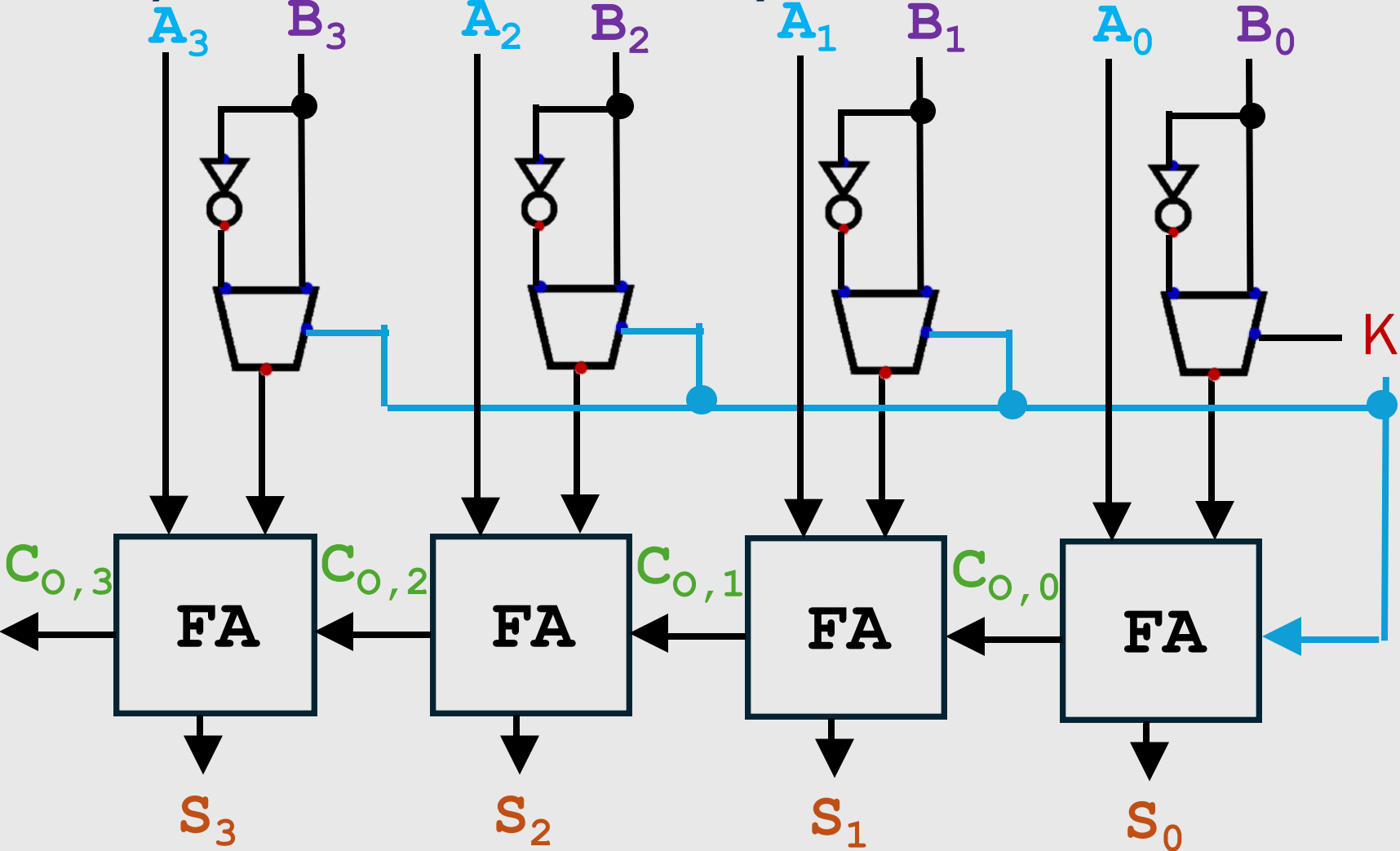

XOR

$$N \oplus 1 = \bar{N}$$


$$N \oplus 0 = N$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

If we XOR B_i with K

- When $K = 0$, $B_i \oplus K = B_i$
- When $K = 1$, $B_i \oplus K = \bar{B}_i$

Adder/Subtractor Implementation 2

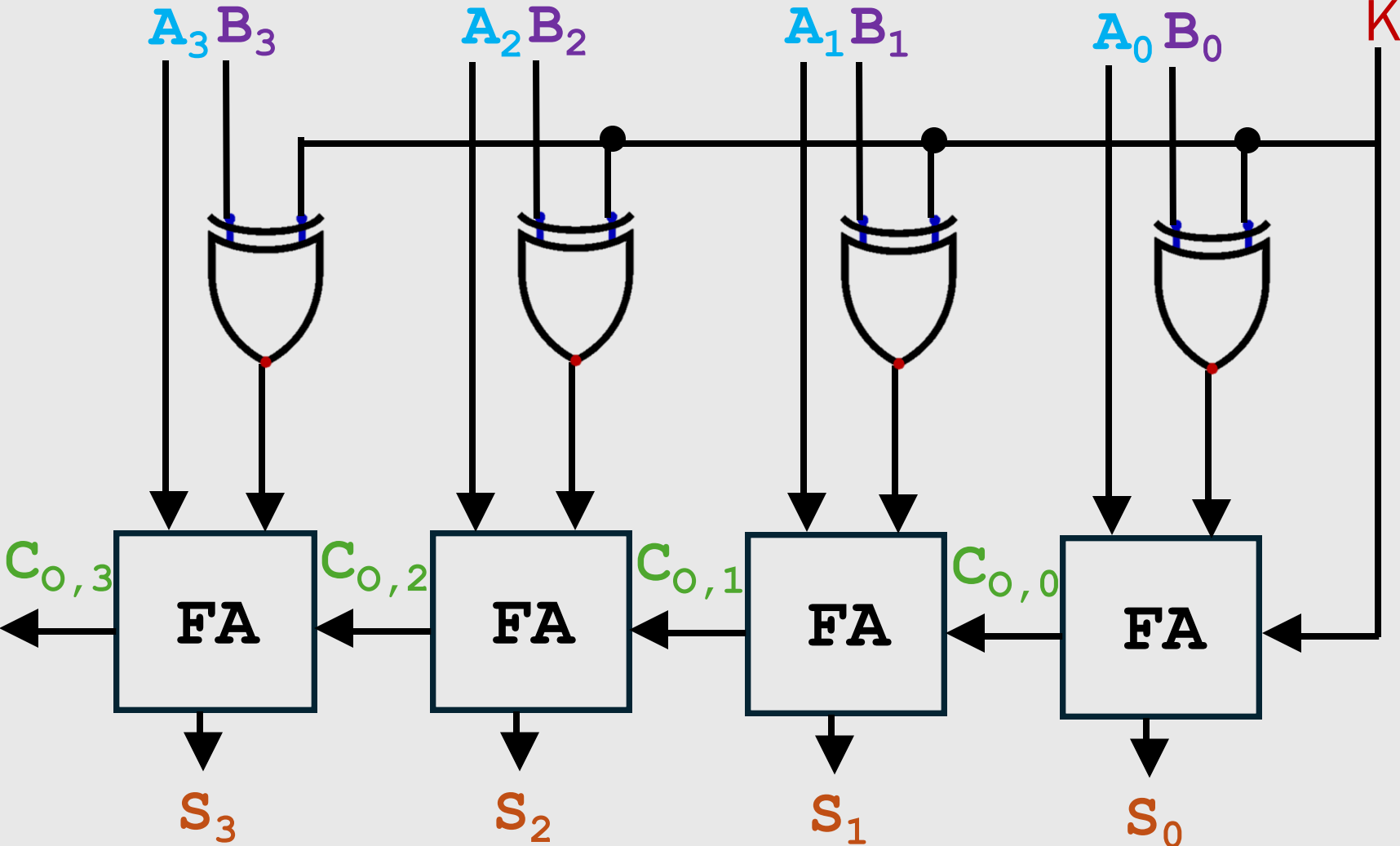



COMPARATOR CIRCUITS




Example Program

```
if (A == B) {  
    C = D * 4;  
} else {  
    C = D - (E + F);  
}
```


Equality Comparator

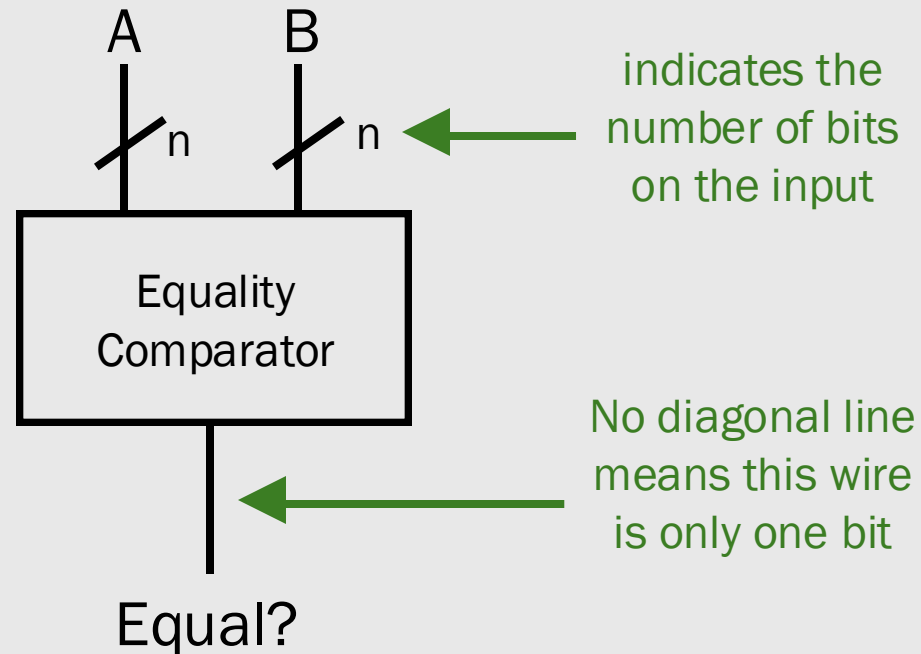Determines whether the two inputs are equal




Equality Comparator

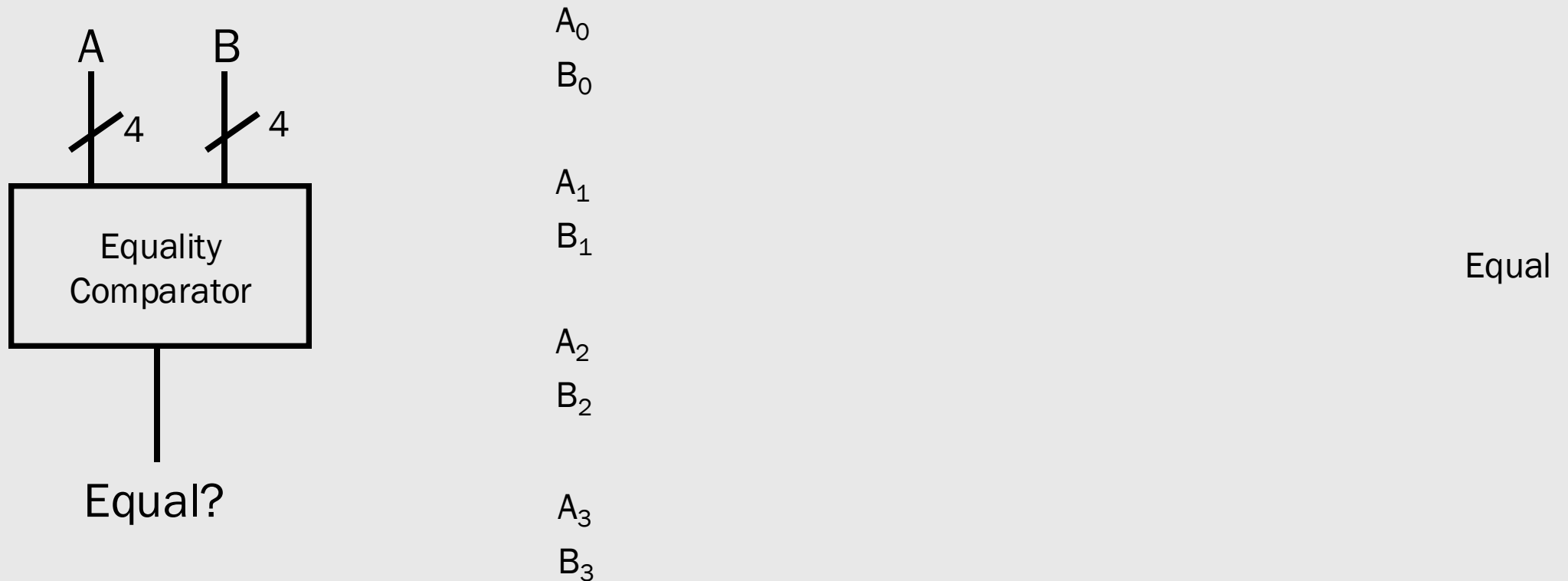
Design a 4-bit equality comparator that will output 1 if the inputs are equal and 0 if the inputs are not equal



Equality Comparator Solution 1

 

Equality Comparator Solution 2

 



LEFT SHIFT

Left Shifting

- Let's say my input, A, is a 4-bit number: 0b1101

Shift Amount	Result
0	
1	
2	
3	
4	
5	
6	
7	
8	

Left Shifting

- Let's say my input, A, is a 4-bit number: 0b1101

Shift Amount	Result
0	0b1101
1	0b1010
2	0b0100
3	0b1000
4	0b0000
5	0b0000
6	0b0000
7	0b0000
8	0b0000

Shift Amount

- Let's say my input, A, is a 4-bit number: 0b1101

Shift Amount	Result
0	0b1101
1	0b1010
2	0b0100
3	0b1000
4	0b0000
5	0b0000
6	0b0000
7	0b0000
8	0b0000

If we shift A by more than 3 bits, the result will always be 0. We want to make our shifter circuit as simple as possible, so we will only support a shift amount range of 0-3.

Shift Amount

Shift Amount	Result
0	0b1101
1	0b1010
2	0b0100
3	0b1000
4	0b0000
5	0b0000
6	0b0000
7	0b0000
8	0b0000

We need to be able to shift by up to 3 bits.

To represent the numbers 0-3, we need 2 bits.

Shift Amount

Shift Amount	Result
0	0b10101
1	0b01010
2	0b10100
3	0b01000
4	0b10000
5	0b00000
6	0b00000
7	0b00000
8	0b00000

We need to be able to shift by up to 4 bits.

To represent the numbers 0-4, we need 3 bits.

Shift Amount

- If I have an n -bit number, how many bits are needed for the shift amount?




Shift Amount

- If I have an n -bit number, how many bits are needed for the shift amount?
 - $\text{ceil}(\log_2 n)$

Left Shift

 - Design a circuit that can perform a left shift operation on a 4-bit number.



Left Shift

Output Value

	Y_3	Y_2	Y_1	Y_0
0				
1				
2				
3				

Shift
Amount

Input: $A_3A_2A_1A_0$

Left Shift


Output Value

Shift
Amount

	Y_3	Y_2	Y_1	Y_0
0	A_3	A_2	A_1	A_0
1	A_2	A_1	A_0	0
2	A_1	A_0	0	0
3	A_0	0	0	0

Left Shift

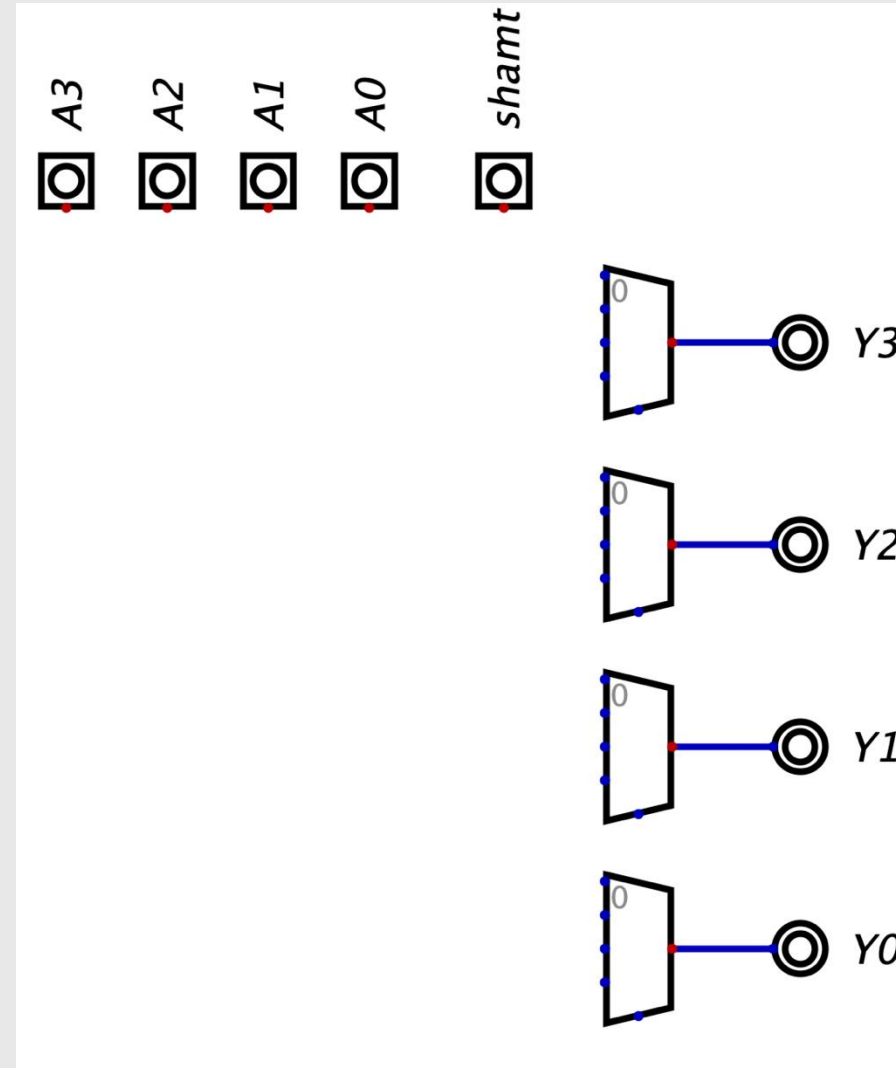- Design a circuit that can perform a variable left shift on a 4-bit number.
 - *shamt* is a 2-bit input
 - you may use ground for 0





Left Shift

- Design a circuit that can perform a variable left shift on a 4-bit number.

