

COMP311: *COMPUTER ORGANIZATION!*

Lecture 12: ALU!!

tinyurl.com/comp311-fa25



LEFT SHIFT

Left Shifting

- Let's say my input, A, is a 4-bit number: 0b1101

Shift Amount	Result
0	
1	
2	
3	
4	
5	
6	
7	
8	

Left Shifting

- Let's say my input, A, is a 4-bit number: 0b1101

Shift Amount	Result
0	0b1101
1	0b1010
2	0b0100
3	0b1000
4	0b0000
5	0b0000
6	0b0000
7	0b0000
8	0b0000

Shift Amount

- Let's say my input, A, is a 4-bit number: 0b1101

Shift Amount	Result
0	0b1101
1	0b1010
2	0b0100
3	0b1000
4	0b0000
5	0b0000
6	0b0000
7	0b0000
8	0b0000

If we shift A by more than 3 bits, the result will always be 0. We want to make our shifter circuit as simple as possible, so we will only support a shift amount range of 0-3.

Shift Amount

Shift Amount	Result
0	0b1101
1	0b1010
2	0b0100
3	0b1000
4	0b0000
5	0b0000
6	0b0000
7	0b0000
8	0b0000

We need to be able to shift by up to 3 bits.

To represent the numbers 0-3, we need 2 bits.

Shift Amount

Shift Amount	Result
0	0b10101
1	0b01010
2	0b10100
3	0b01000
4	0b10000
5	0b00000
6	0b00000
7	0b00000
8	0b00000

We need to be able to shift by up to 4 bits.

To represent the numbers 0-4, we need 3 bits.

Shift Amount


- If I have an n -bit number, how many bits are needed for the shift amount?

Shift Amount

- If I have an n -bit number, how many bits are needed for the shift amount?
 - $\text{ceil}(\log_2 n)$

Left Shift

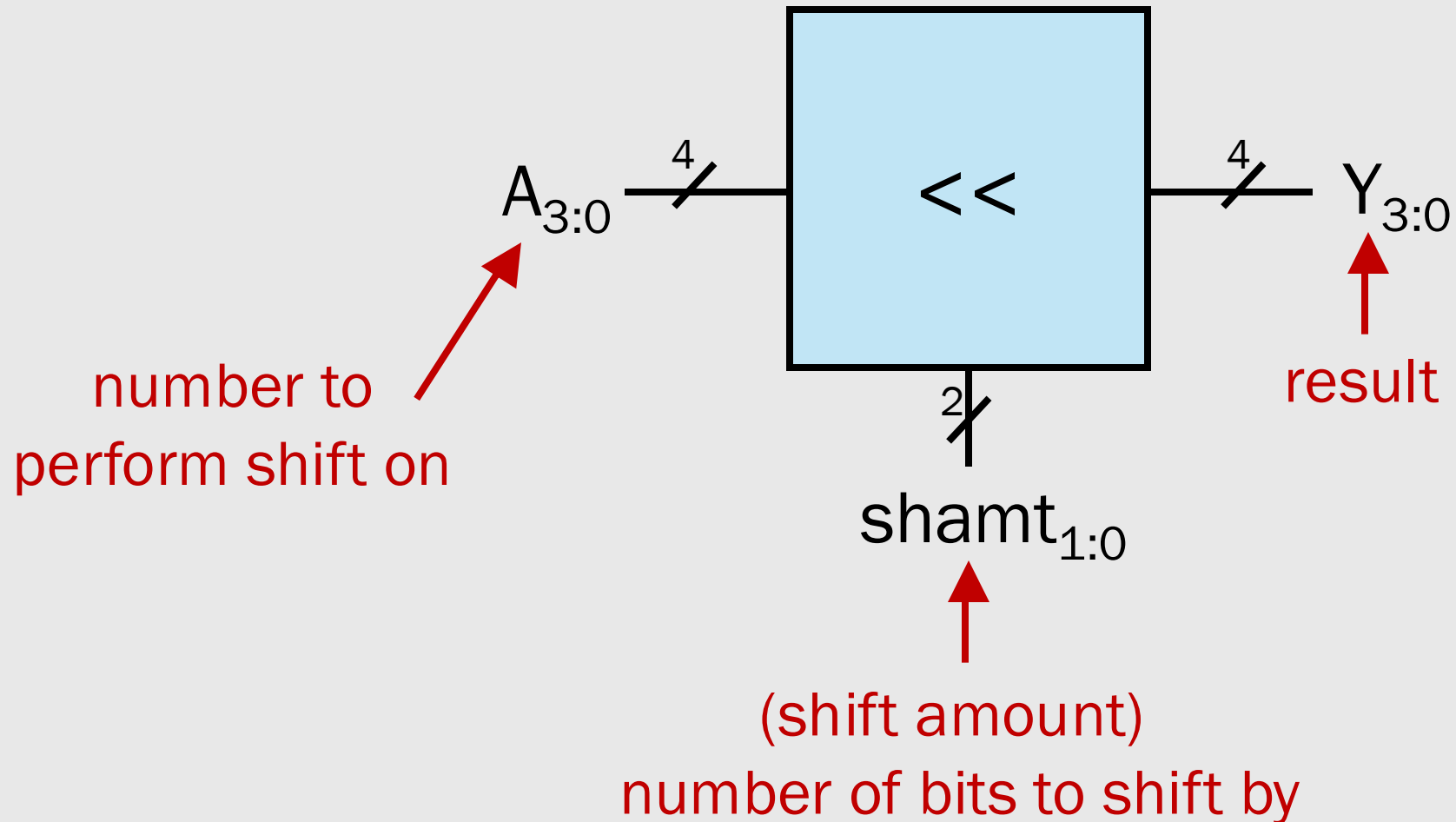- Design a circuit that can perform a left shift operation on a 4-bit number.



Left Shift

Output Value

	Y_3	Y_2	Y_1	Y_0
0				
1				
2				
3				

Shift
Amount

Input: $A_3A_2A_1A_0$

Left Shift


Output Value

Shift
Amount

	Y_3	Y_2	Y_1	Y_0
0	A_3	A_2	A_1	A_0
1	A_2	A_1	A_0	0
2	A_1	A_0	0	0
3	A_0	0	0	0

Left Shift

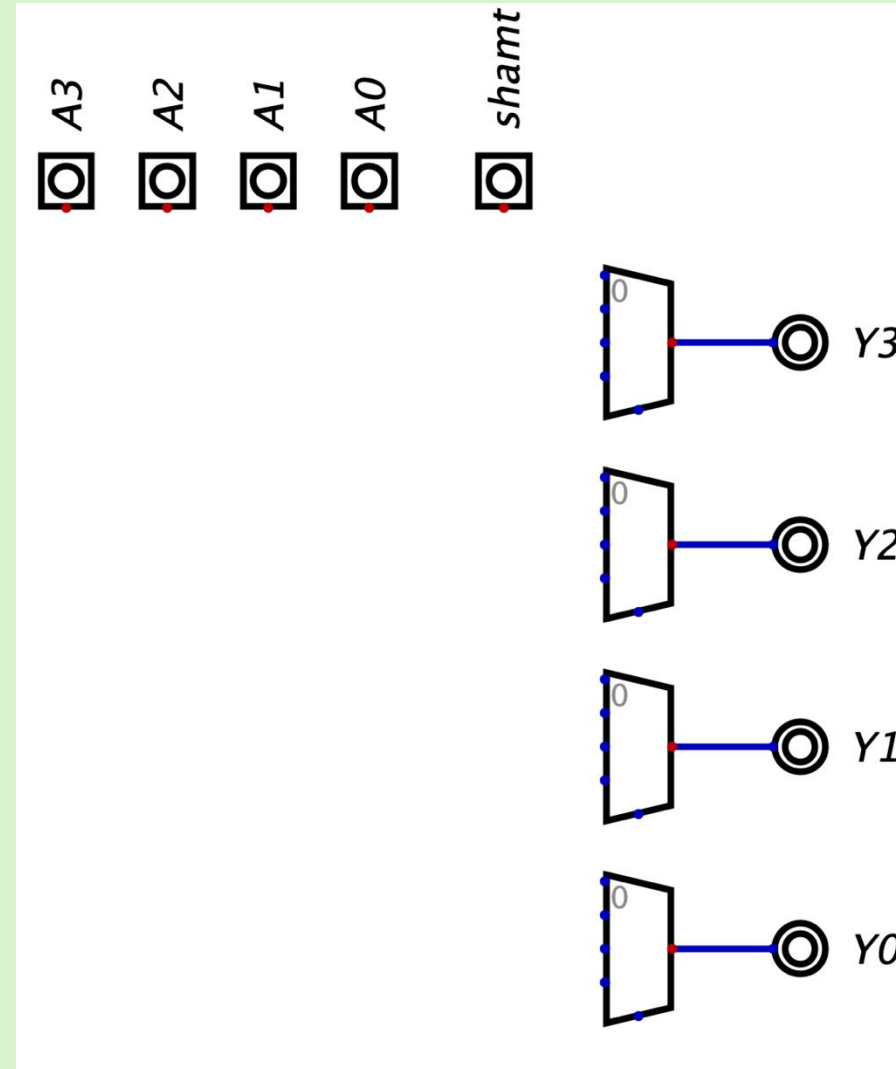
- Design a circuit that can perform a variable left shift on a 4-bit number.
 - *shamt* is a 2-bit input
 - *you may use ground for 0*






Left Shift

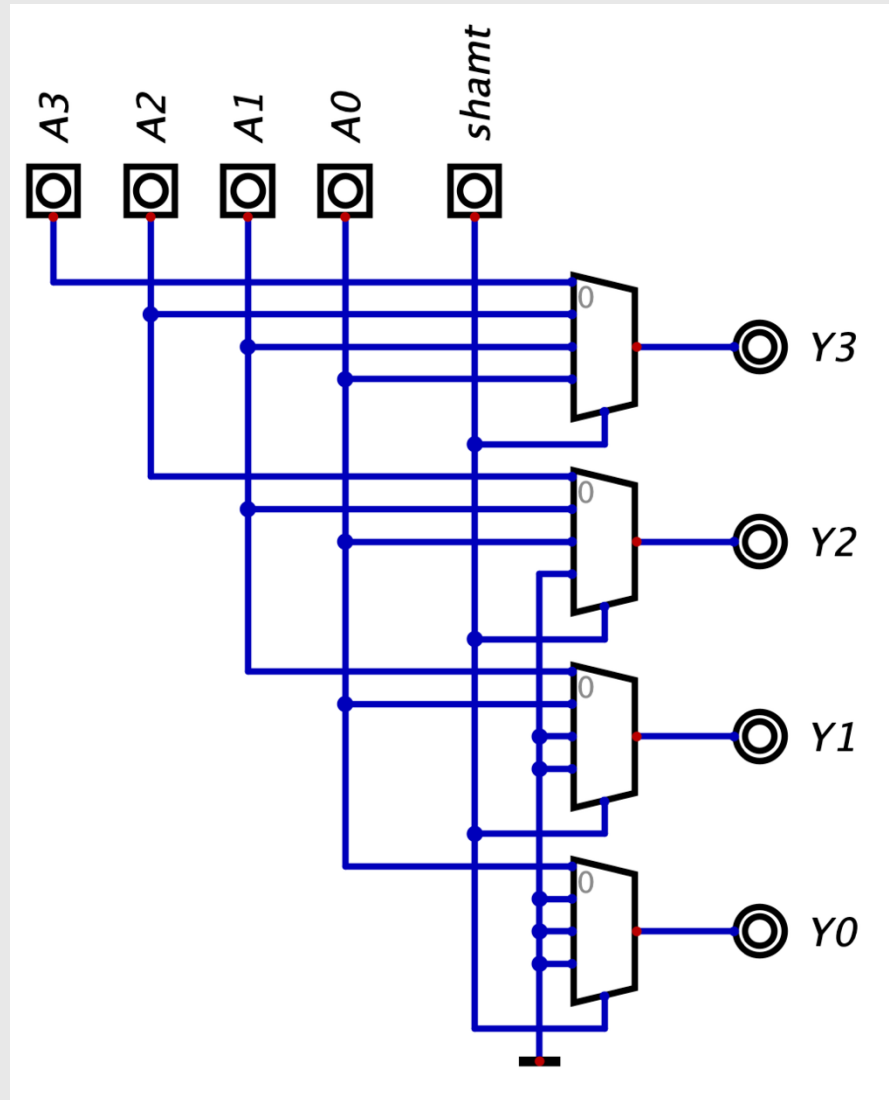- Design a circuit that can perform a variable left shift on a 4-bit number.




ARITHMETIC LOGIC UNIT (ALU) 😊

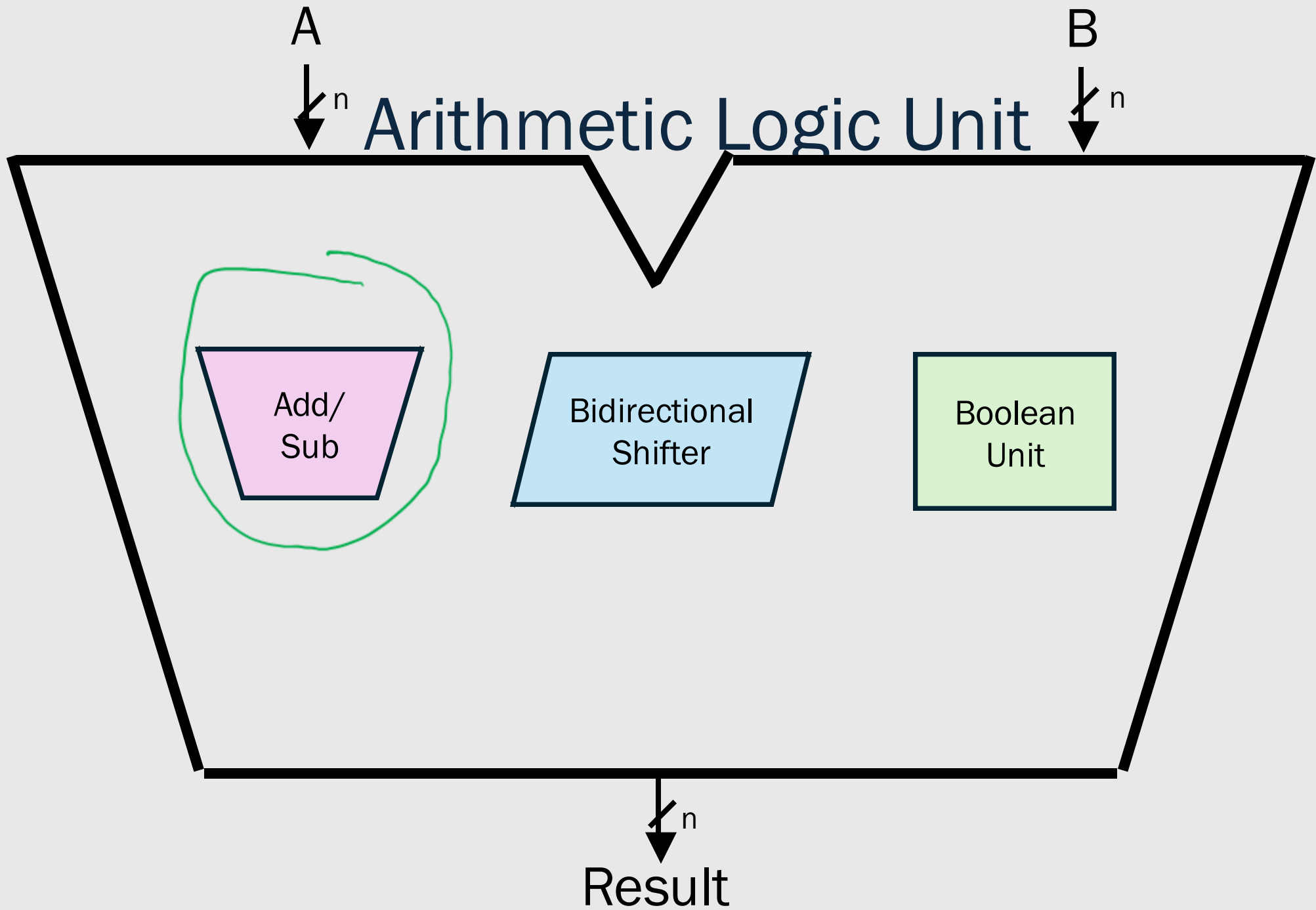


4-bit AND

Symbol


 


Implementation

 


Ex: 0b1111 AND 0b1010 Implementation

Symbol

  


Ex: 0b1111 AND 0b1010

Symbol

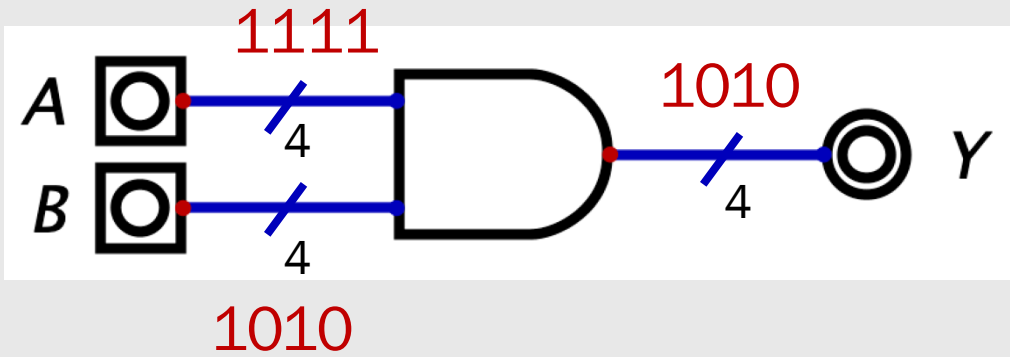


Implementation

 


4-bit OR


Symbol

 

Implementation

 


Boolean Unit

 


Operation	Expression	Bool
AND	$A \times B$	0b00
OR	$A + B$	0b01
XOR	$A \oplus B$	0b10
NOR	$\overline{A + B}$	0b11

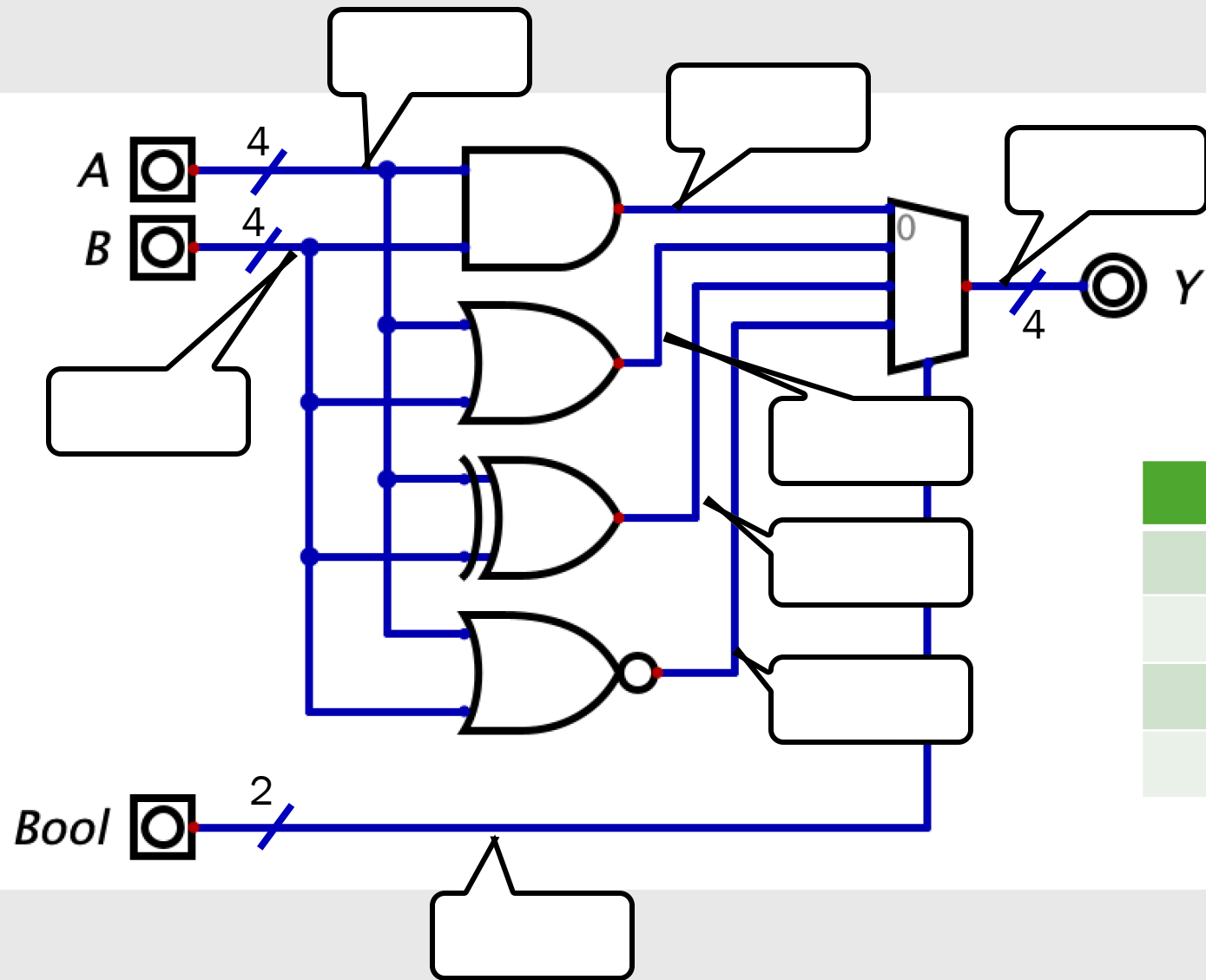Let's say $n = 4$. I want to perform $Y = A \text{ AND } B$ where A is 5 and B is 4.




Operation	Expression	Bool
AND	$A \times B$	0b00
OR	$A + B$	0b01
XOR	$A \oplus B$	0b10
NOR	$\overline{A + B}$	0b11

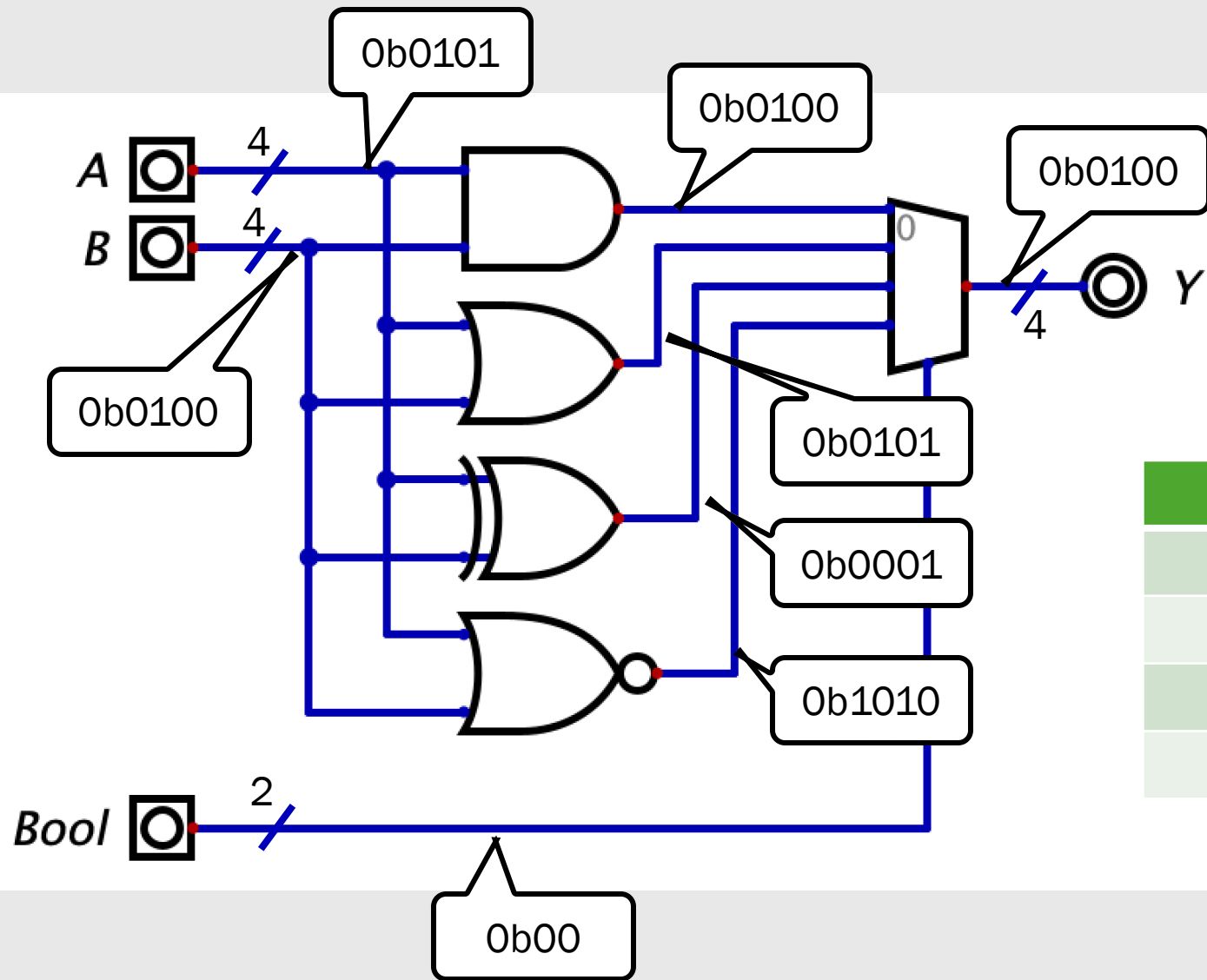Let's say $n = 4$. I want to perform $Y = A \text{ AND } B$ where A is 5 and B is 4.




Operation	Expression	Bool
AND	$A \times B$	0b00
OR	$A + B$	0b01
XOR	$A \oplus B$	0b10
NOR	$\overline{A + B}$	0b11

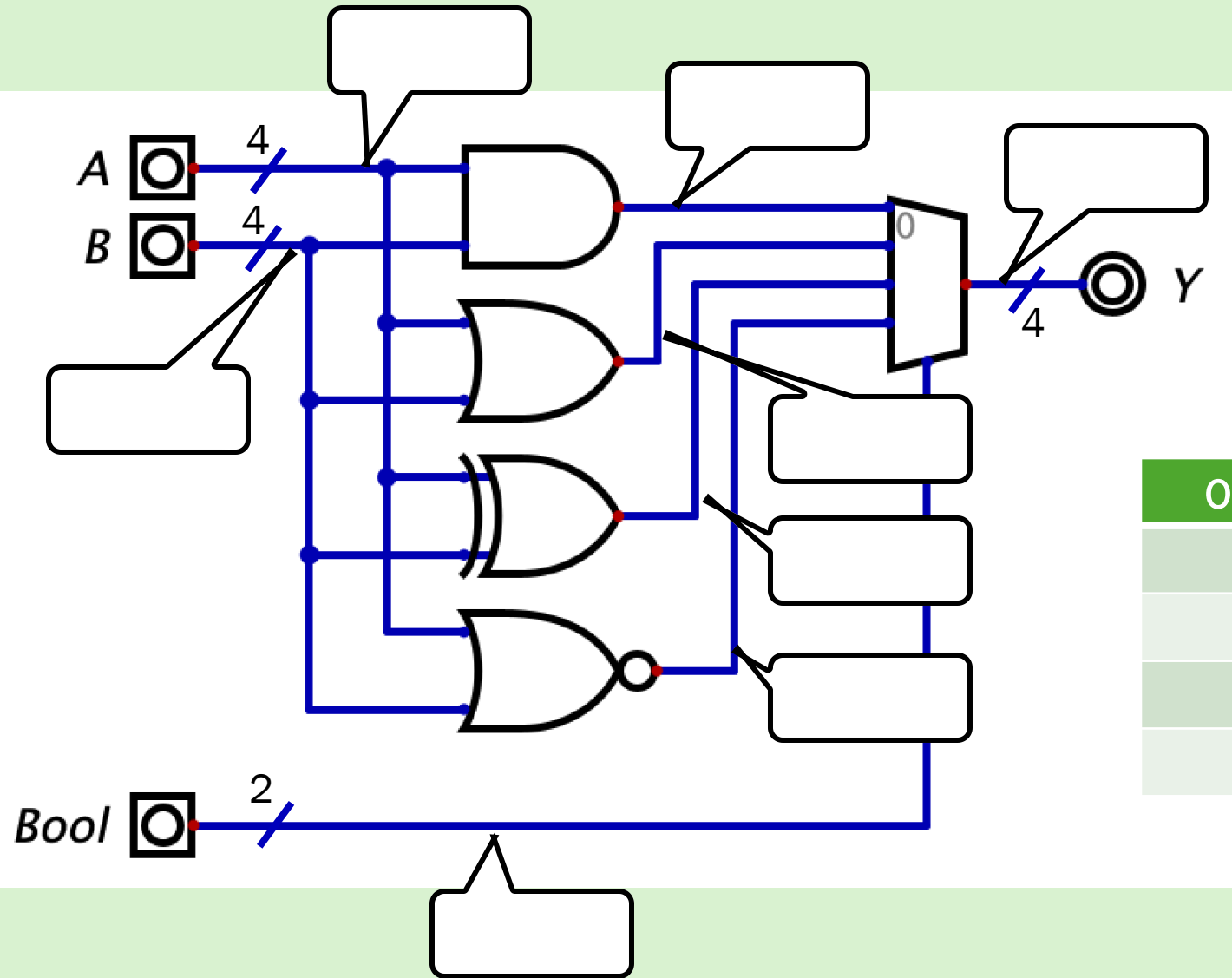What are the values on each signal when we want to perform $Y = A \text{ XOR } B$ where A is $0b1010$ and B is $0b0001$?



Operation	Expression	Bool
AND	$A \times B$	0b00
OR	$A + B$	0b01
XOR	$A \oplus B$	0b10
NOR	$\overline{A + B}$	0b11

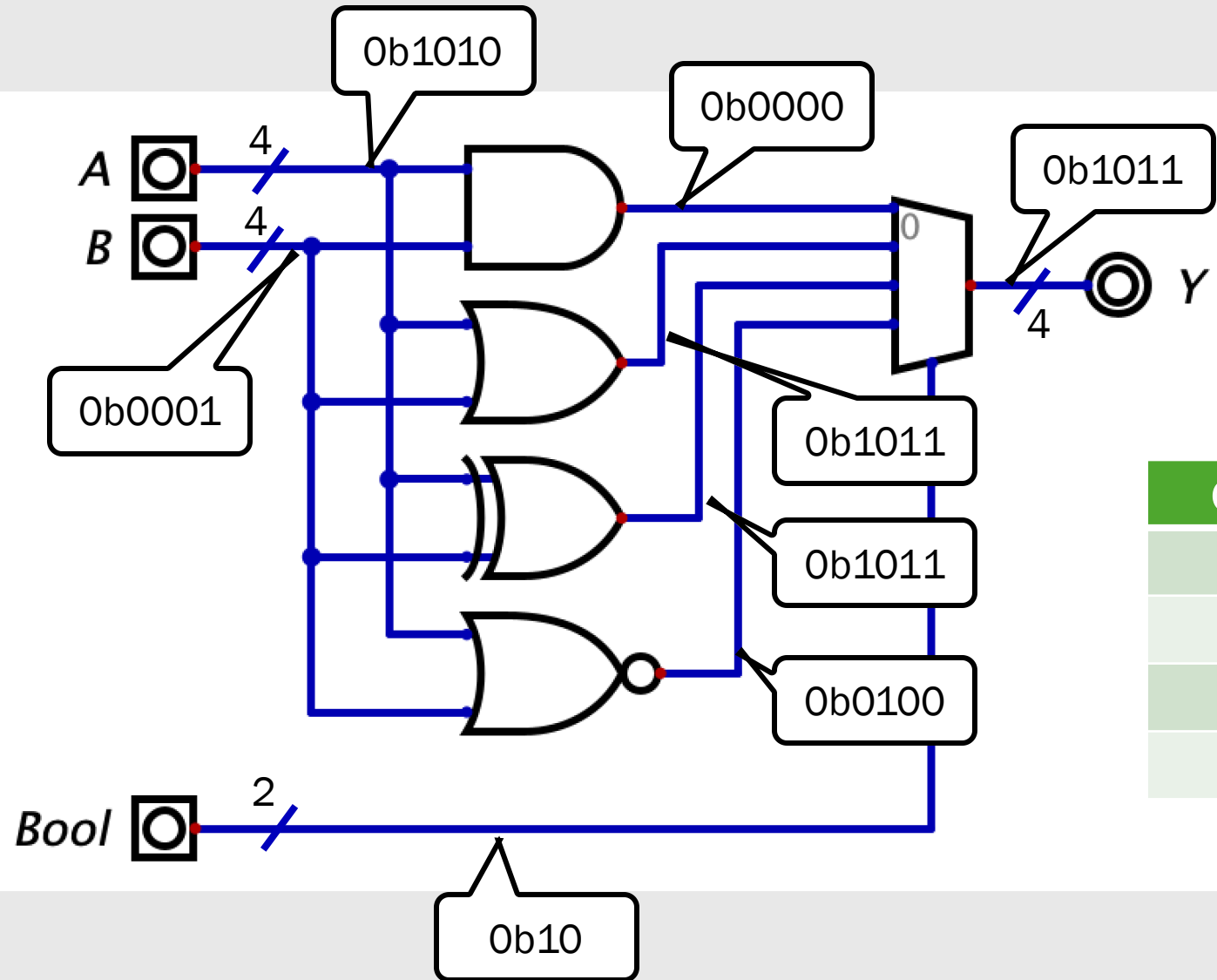What are the values on each signal when we want to perform $Y = A \text{ XOR } B$ where A is $0b1010$ and B is $0b0001$?




Operation	Expression	Bool
AND	$A \times B$	$0b00$
OR	$A + B$	$0b01$
XOR	$A \oplus B$	$0b10$
NOR	$\overline{A + B}$	$0b11$

Bidirectional Shifter

- The left bit tells you the direction of the shift (left or right)
- The right bit tells you the type of shift (arithmetic or logical)
- Logical and arithmetic **left shift** are the same


Operation	Expression	Bool
Left Shift	$B \ll A$	0 0
None	N/A	0 1
Logical Right Shift	$B \gg A$	1 0
Arithmetic Right Shift	$B \ggg A$	1 1

Add/Sub

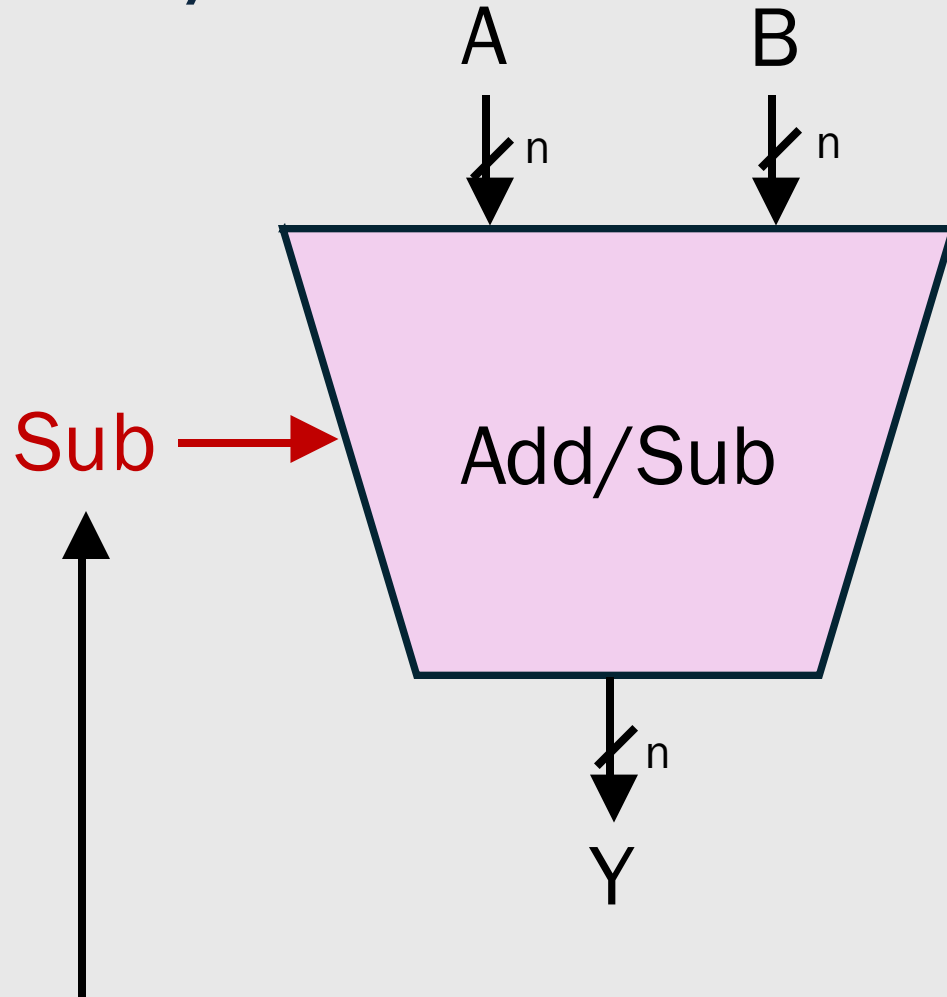


Control signal: Tells the circuit which operation to perform


Operation	Expression	Sub
Add	$A + B$	0
Sub	$A - B$	1

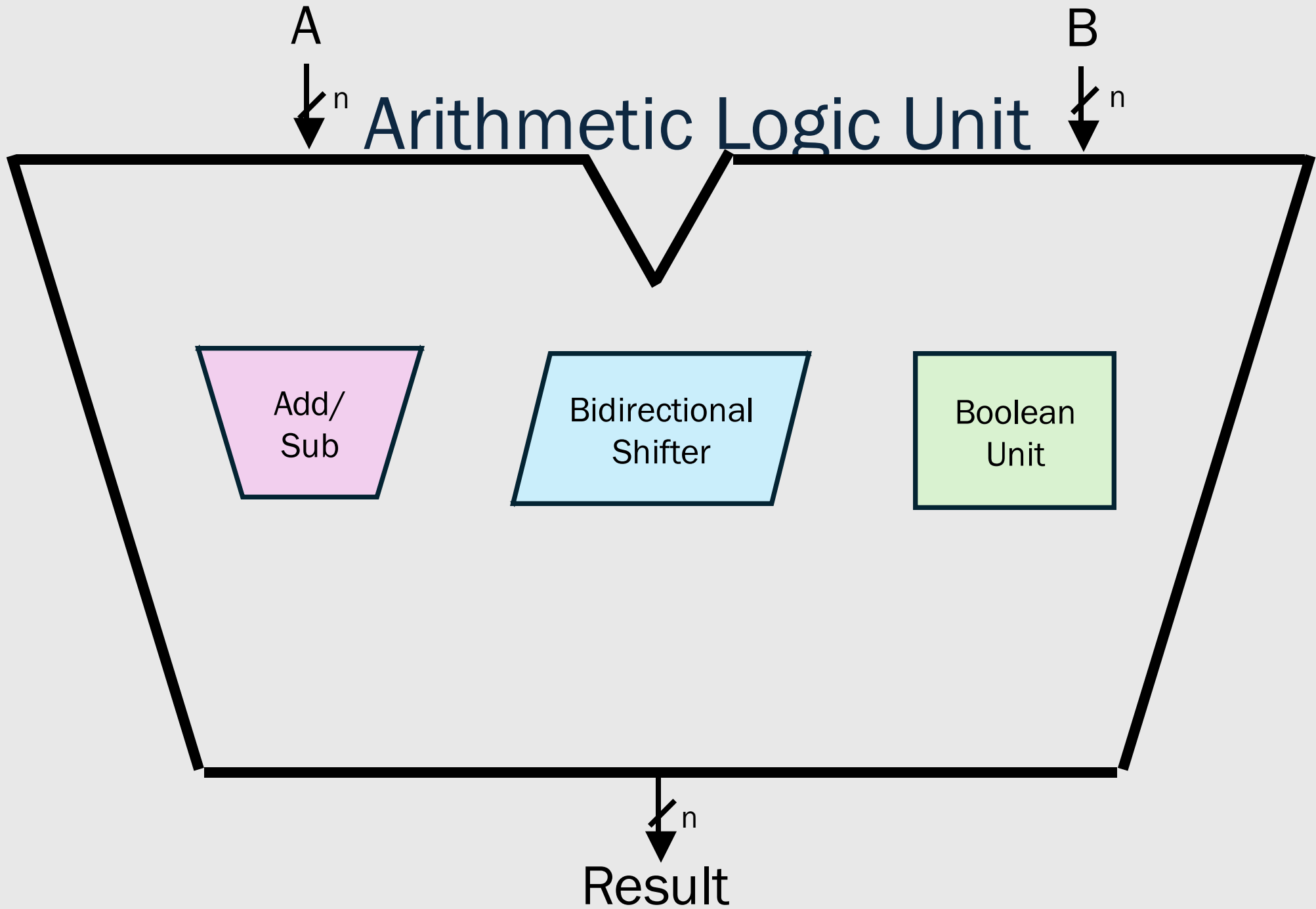


Wiring up Add/Sub

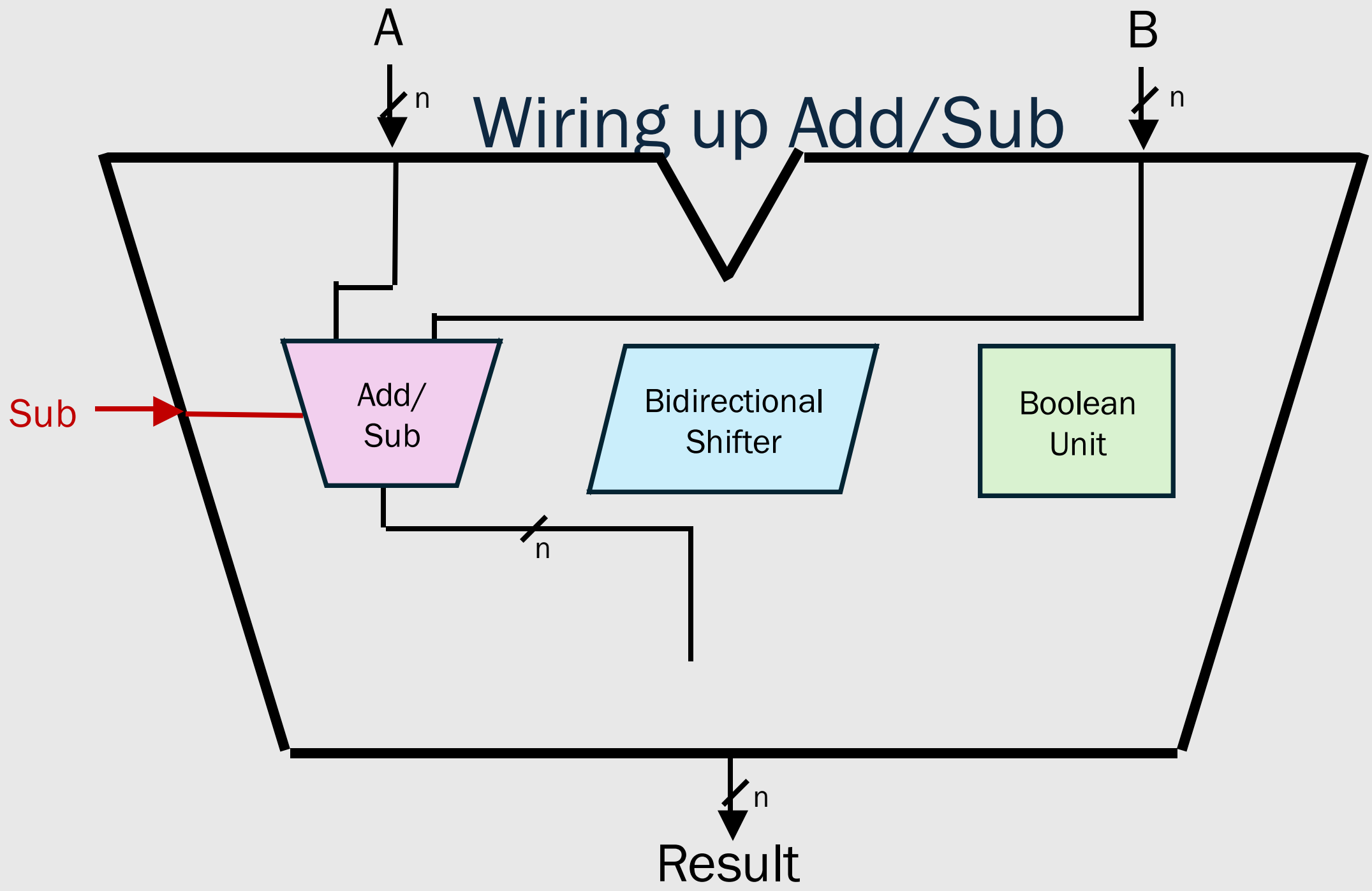


Wiring up Boolean Unit

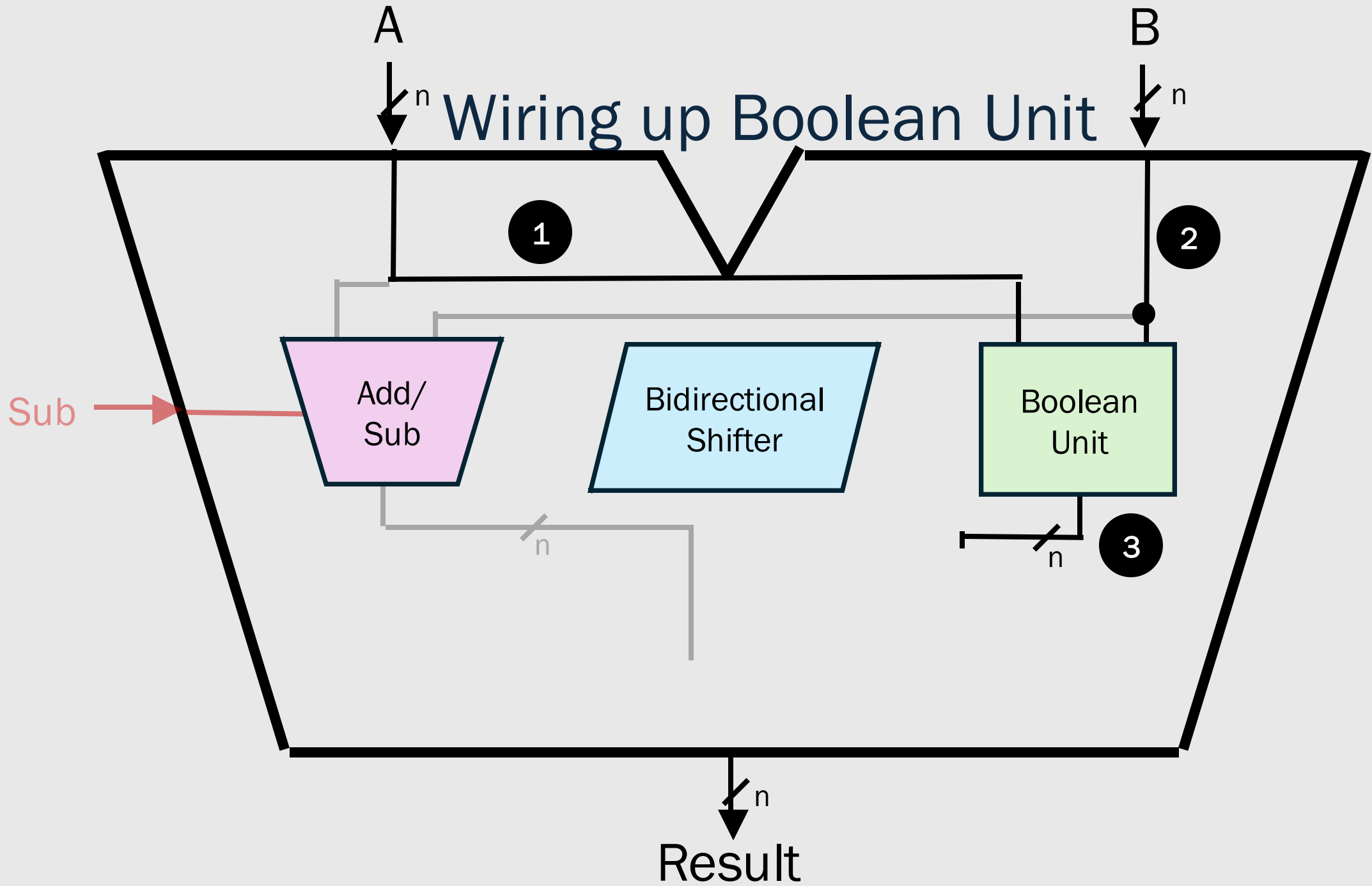


Wiring up Shifter

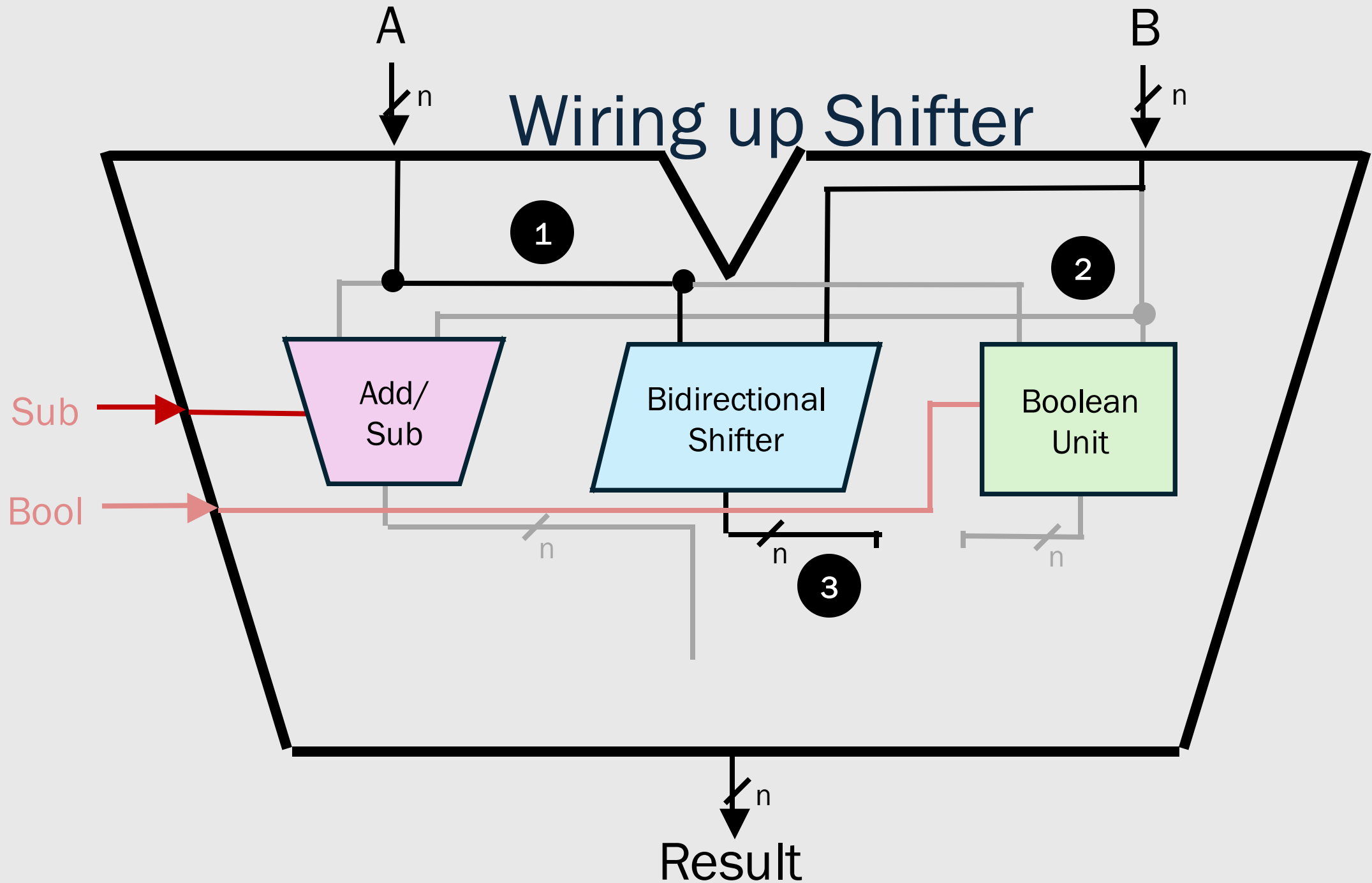


Wiring up Shifter

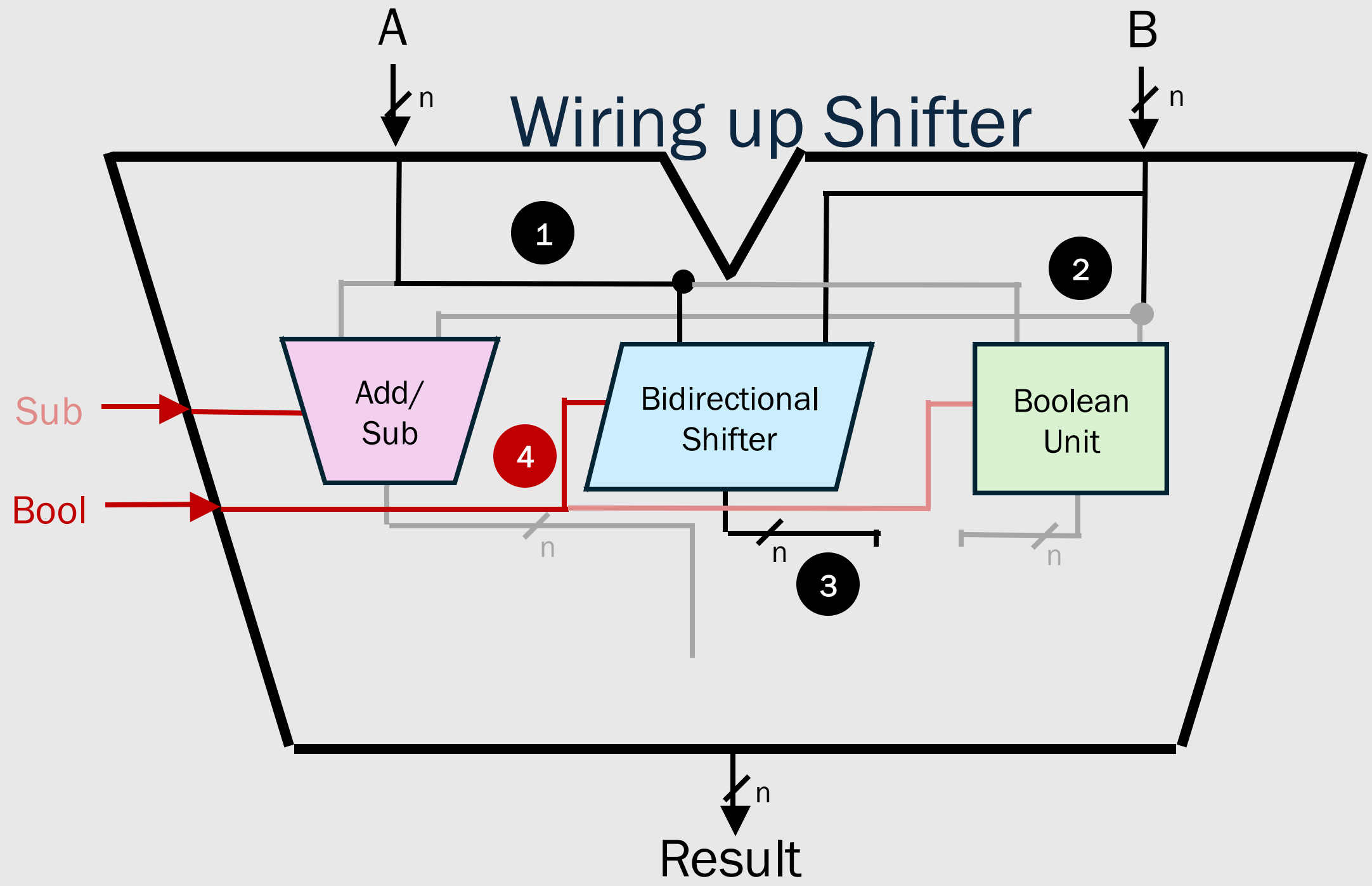


Selecting Outputs

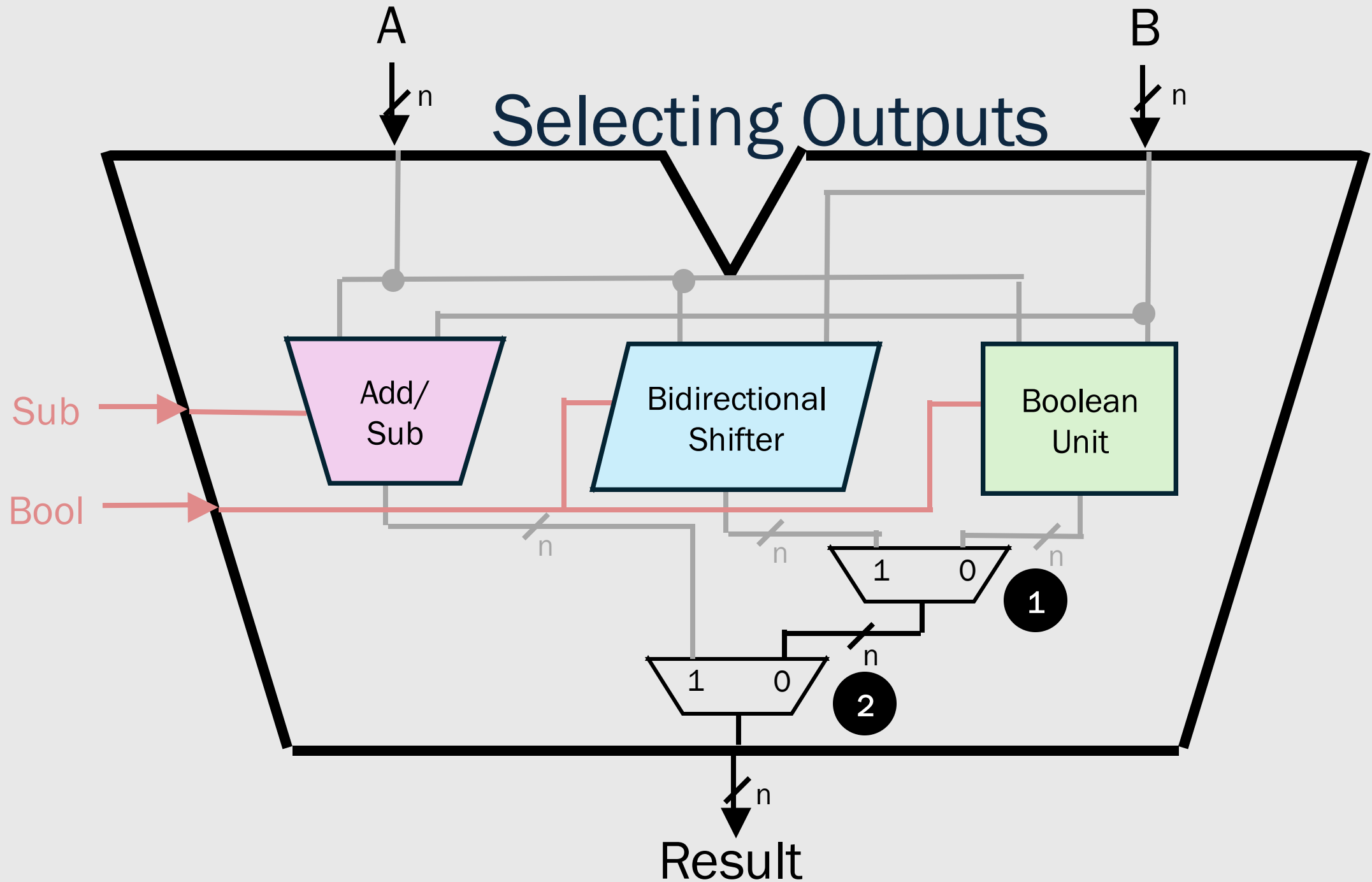

Selecting Outputs

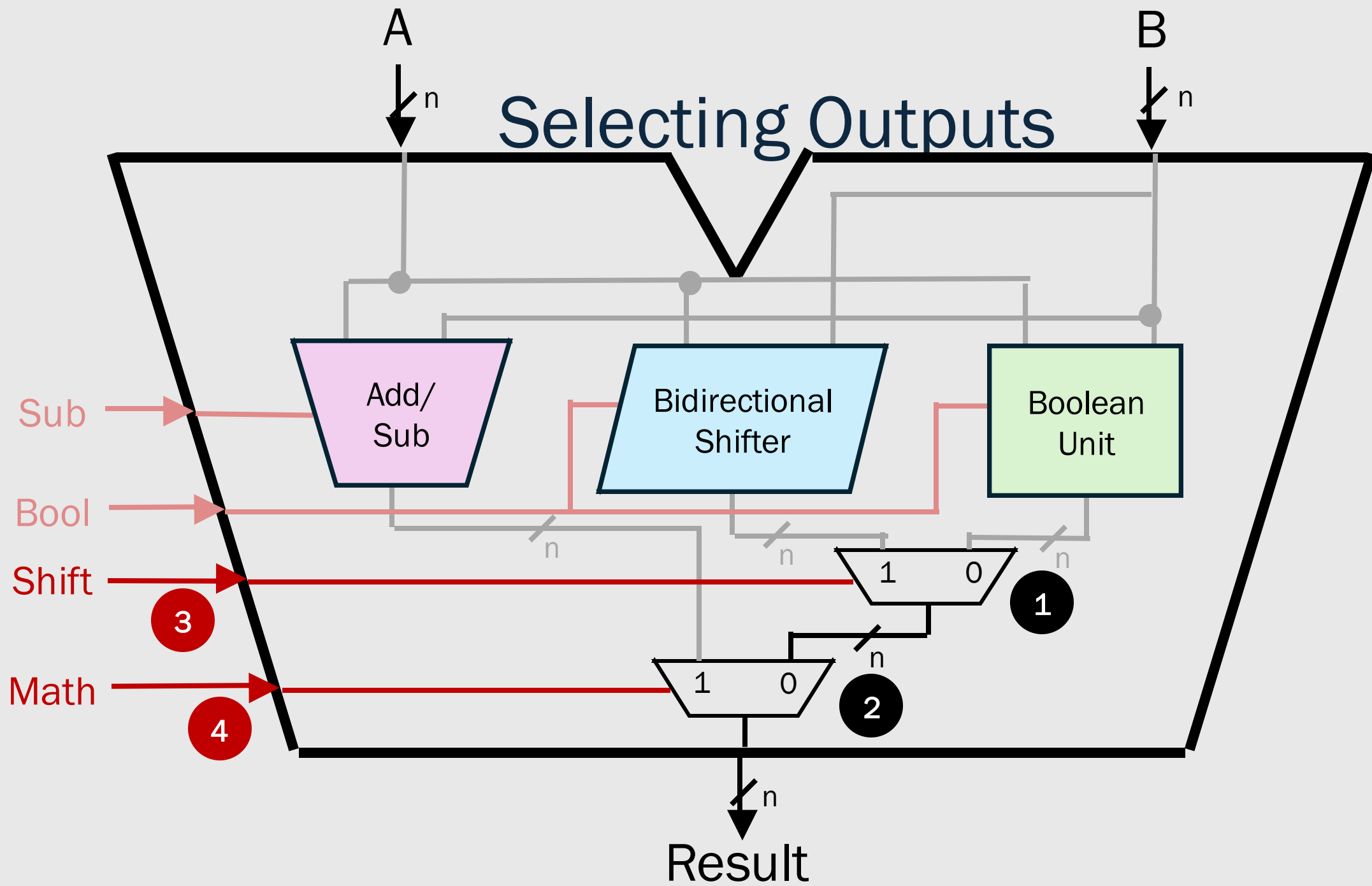

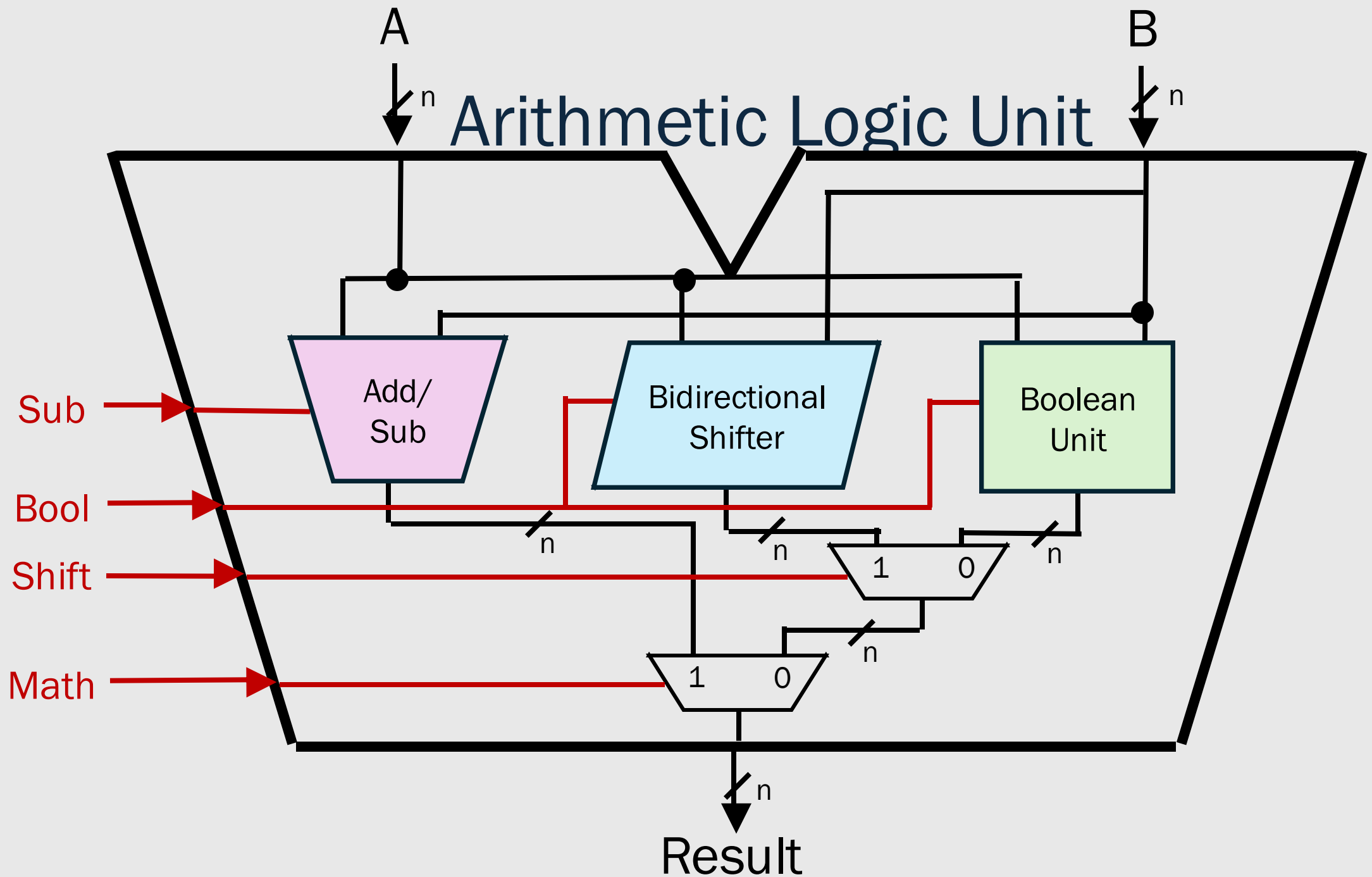

ALU Control Bits

Operation	Expression	Sub
Add	$A + B$	0
Sub	$A - B$	1

Operation	Expression	Bool
Left Shift	$B \ll A$	00
Logical Right Shift	$B \gg A$	10
Arithmetic Right Shift	$B \ggg A$	11

Operation	Expression	Bool
AND	$A \times B$	00
OR	$A + B$	01
XOR	$A \oplus B$	10
NOR	$\overline{A + B}$	11

Operation	Sub	Bool	Shift	Math
$A + B$				
$A - B$				
$B \ll A$				
$B \gg A$				
$B \ggg A$				
$A \text{ AND } B$				
$A \text{ OR } B$				
$A \text{ XOR } B$				
$A \text{ NOR } B$				


ALU Control Bits


Operation	Expression	Sub
Add	$A + B$	0
Sub	$A - B$	1

Operation	Expression	Bool
Left Shift	$B \ll A$	00
Logical Right Shift	$B \gg A$	10
Arithmetic Right Shift	$B \ggg A$	11

Operation	Expression	Bool
AND	$A \times B$	00
OR	$A + B$	01
XOR	$A \oplus B$	10
NOR	$\overline{A + B}$	11


Operation	Sub	Bool	Shift	Math
$A + B$	0b0	0bXX	0bX	0b1
$A - B$	0b1	0bXX	0bX	0b1
$B \ll A$	0bX	0b00	0b1	0b0
$B \gg A$	0bX	0b10	0b1	0b0
$B \ggg A$	0bX	0b11	0b1	0b0
$A \text{ AND } B$	0bX	0b00	0b0	0b0
$A \text{ OR } B$	0bX	0b01	0b0	0b0
$A \text{ XOR } B$	0bX	0b10	0b0	0b0
$A \text{ NOR } B$	0bX	0b11	0b0	0b0

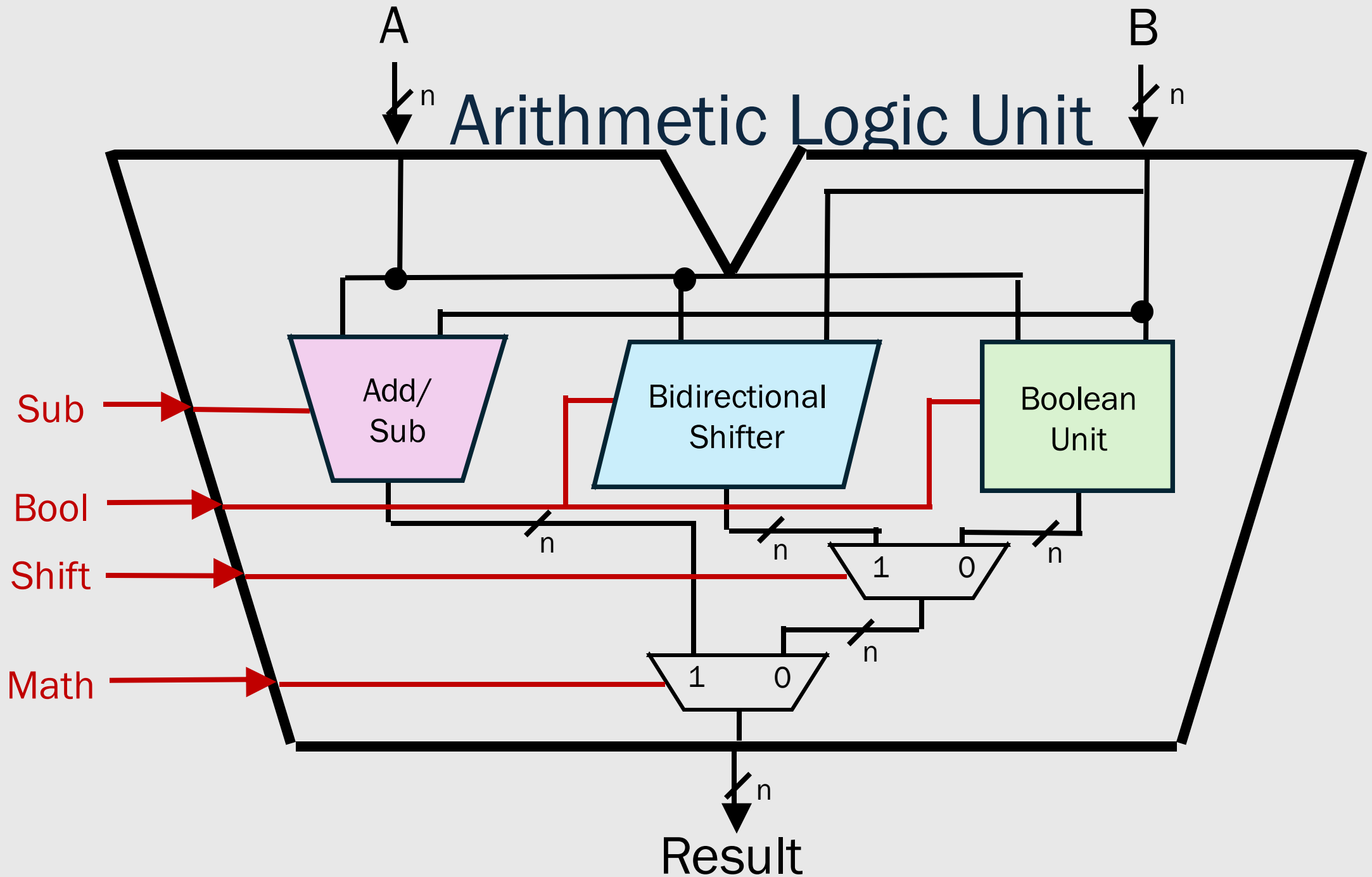

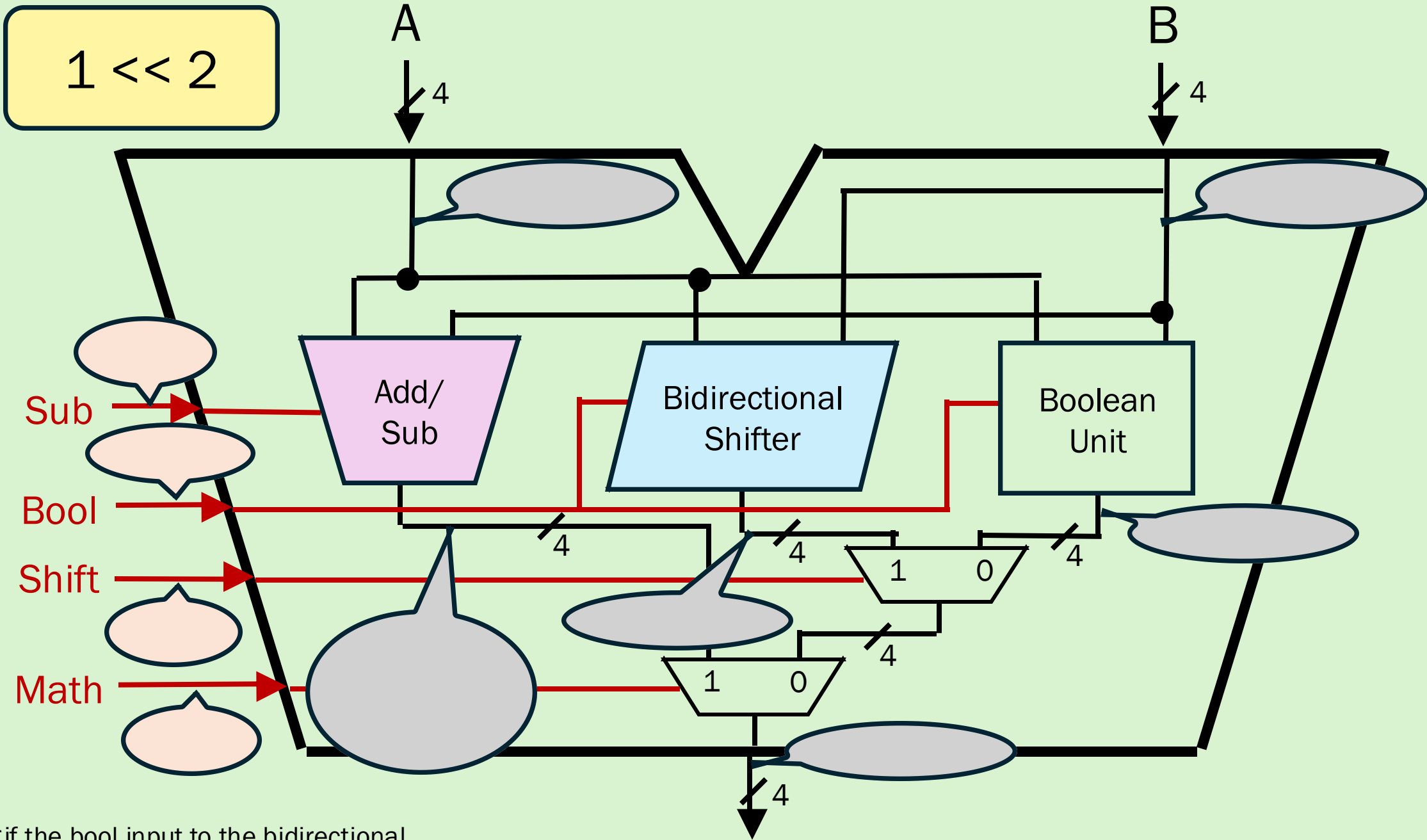

*if the bool input to the bidirectional shifter is 0b01, output 0

Result

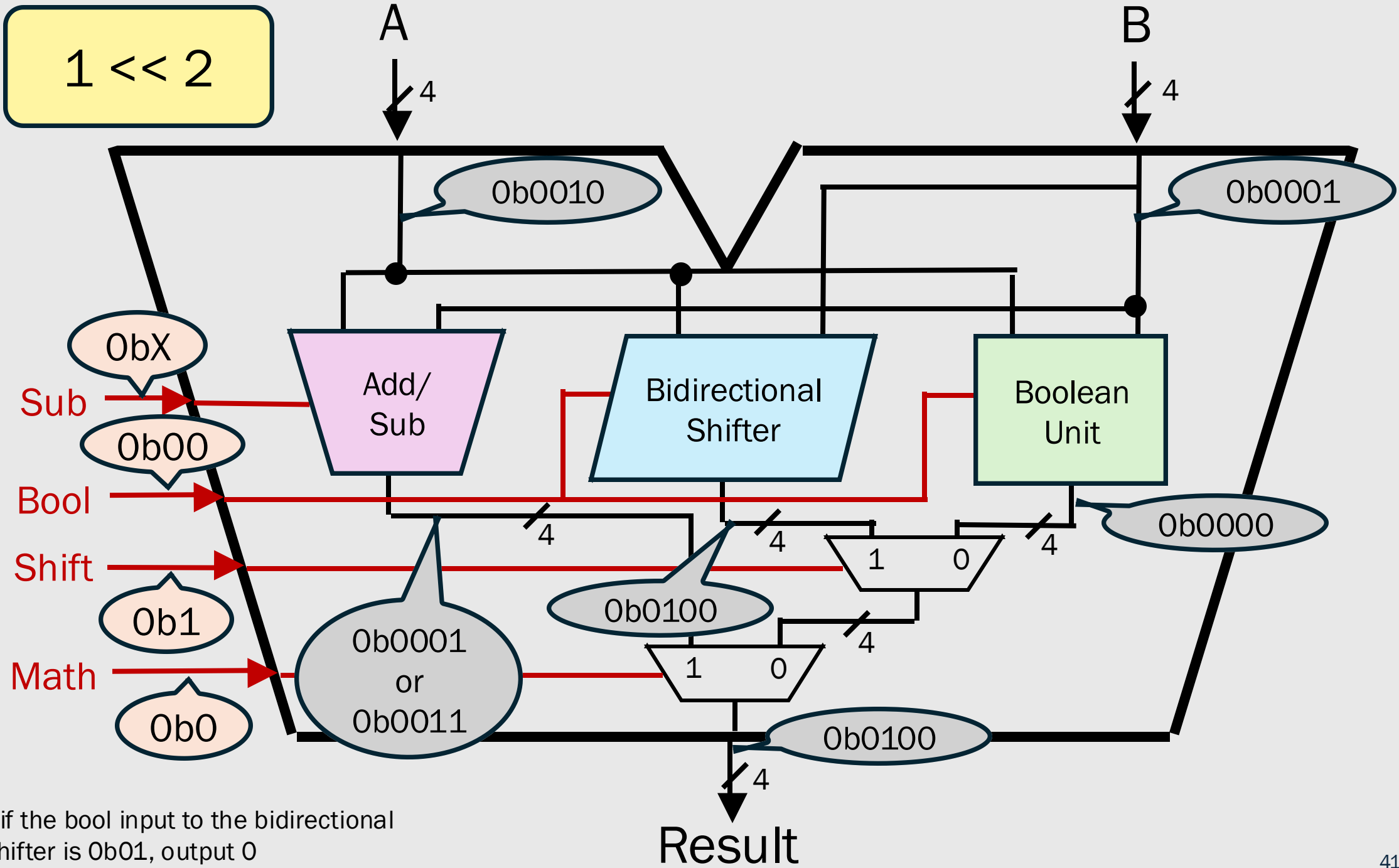

*if the bool input to the bidirectional shifter is 0b01, output 0

