

pollev.com/kakiryan

COMP311: *COMPUTER ORGANIZATION!*

Lecture 15: Registers, Timing Analysis cont.

tinyurl.com/comp311-fa25






FLIP FLOPS AND REGISTERS



D Flip-Flop

 


Clock

Rising Edge

Falling Edge

Period

 

Clock


- The clock is a one-bit signal that oscillates (or toggles) back and forth between 0 and 1
- The purpose of the clock is to ensure that our circuits stay in sync
- The period of the clock is the time between one rising edge to the next. The clock spends an equal time in low and high states.
 - *The period determines how fast our circuit runs*
 - *The shorter the period – or in other words the higher the frequency – the faster our circuit will run*

D Flip-Flop

- Positive-edge triggered
 - Stores D when the clock goes from 0 to 1
- Negative-edge triggered
 - Stores D when the clock goes from 1 to 0




 Positive Edge Triggered D Flip-Flop Waveform Diagram



assume Q starts at 0

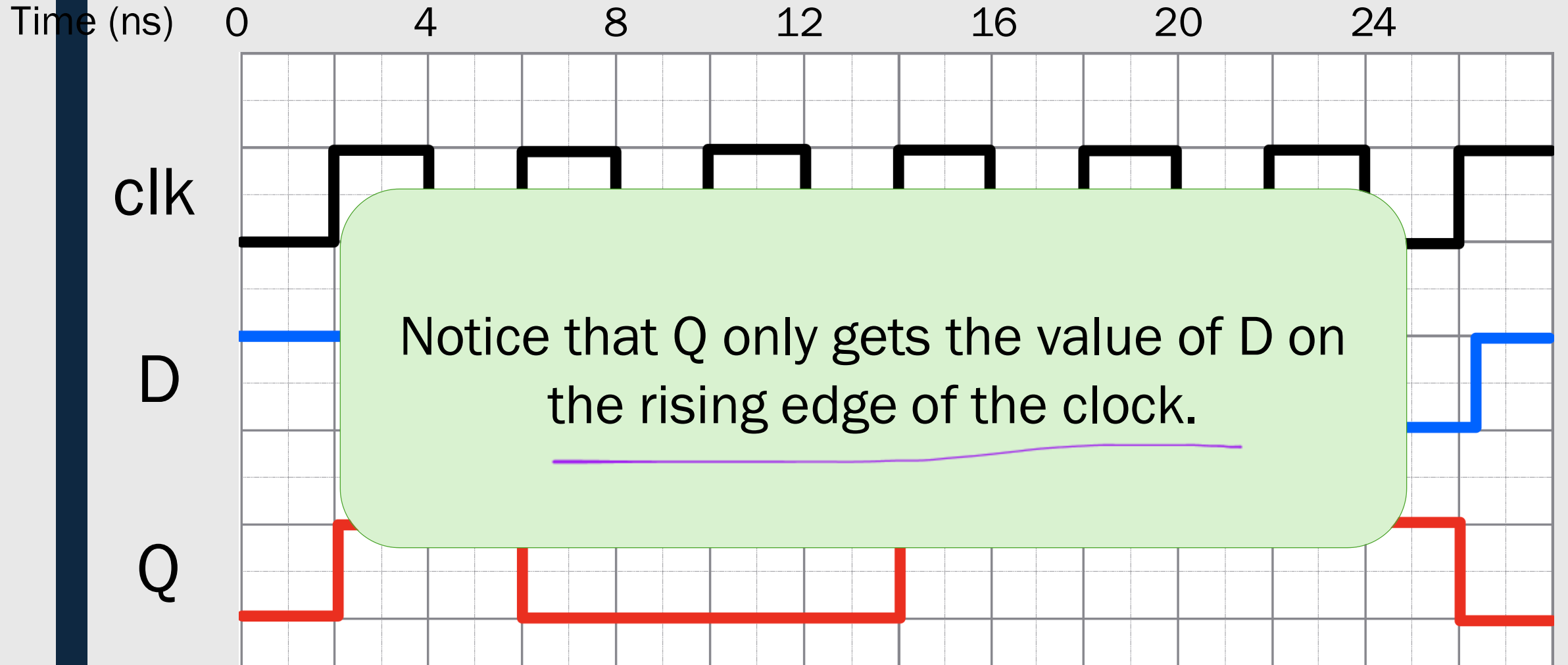
Positive Edge Triggered D Flip-Flop Waveform Diagram




assume Q starts at 0

Clock to Q Delay

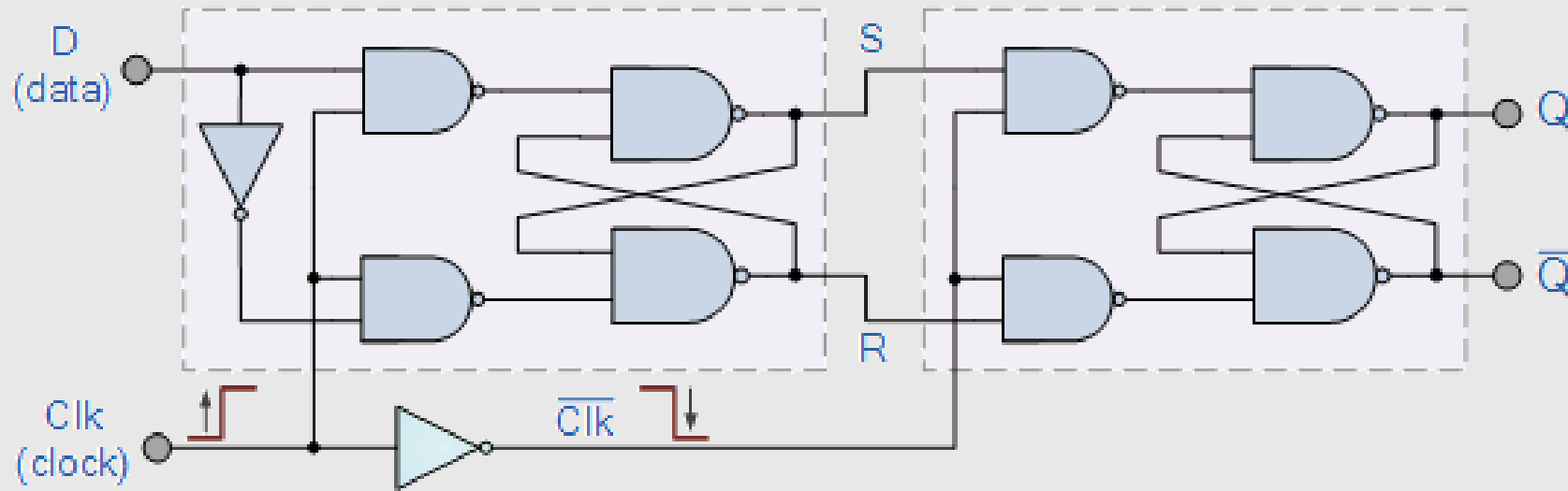- The amount of time it takes for D to appear on the output after the clock trigger



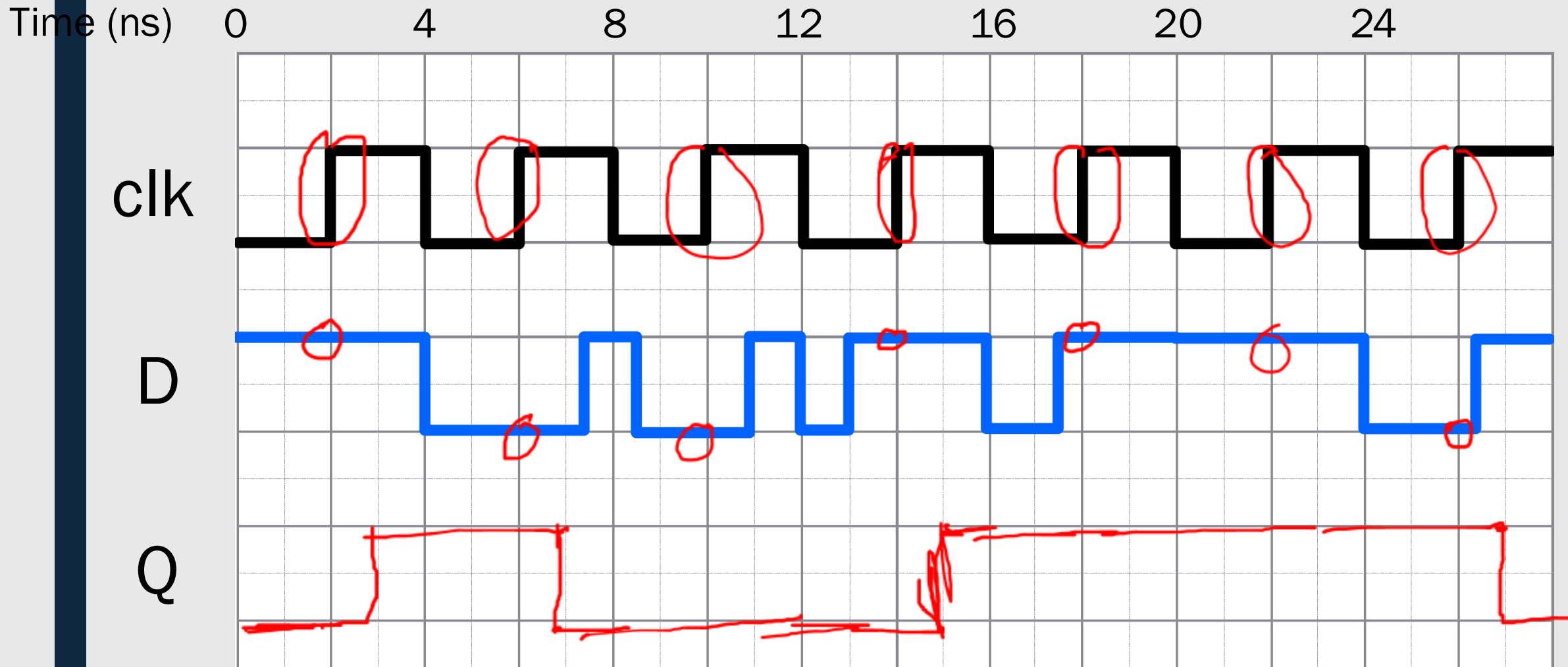
Positive Edge Triggered Flip-Flop Waveform Diagram with clk-to-q Delay




assume Q starts at 0

clk-to-q delay = 1 ns

 Positive Edge Triggered Flip-Flop Waveform Diagram with clk-to-q Delay



 
Positive Edge Triggered Flip-Flop Waveform Diagram with clk-to-q Delay



assume Q starts at 0

clk-to-q delay = 1 ns

 Positive Edge Triggered Flip-Flop Waveform Diagram with clk-to-q Delay




assume Q starts at 0


clk-to-q delay = 1 ns

Registers

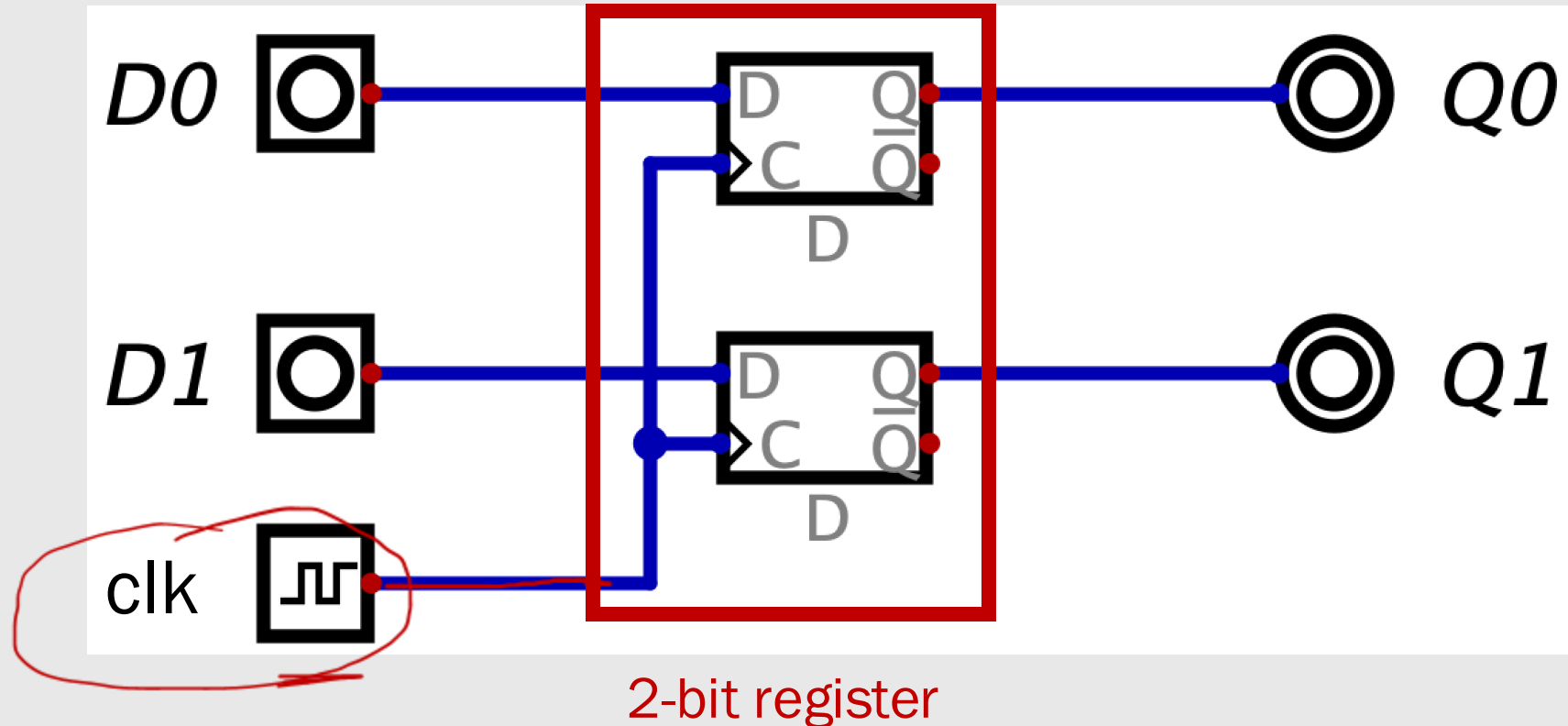
- To store multi-bit values, we can combine multiple FFs together into what is known as a register



N-bit Positive Edge Triggered Register

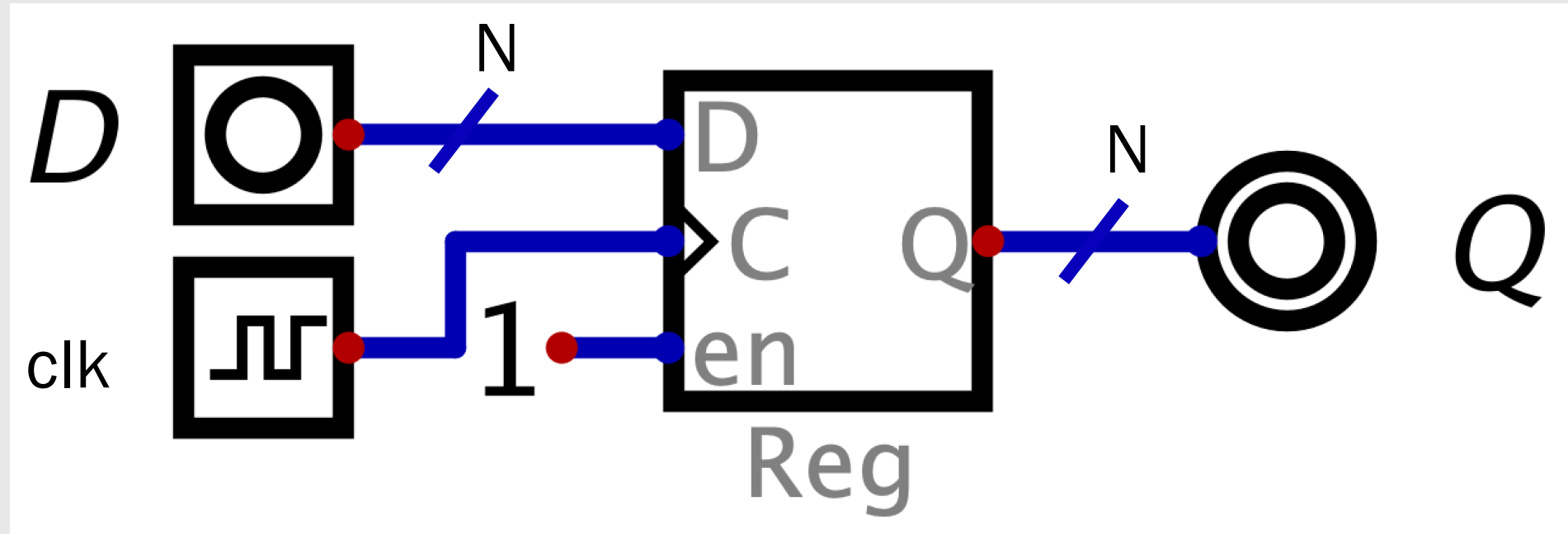

N-bit Positive Edge Triggered Register

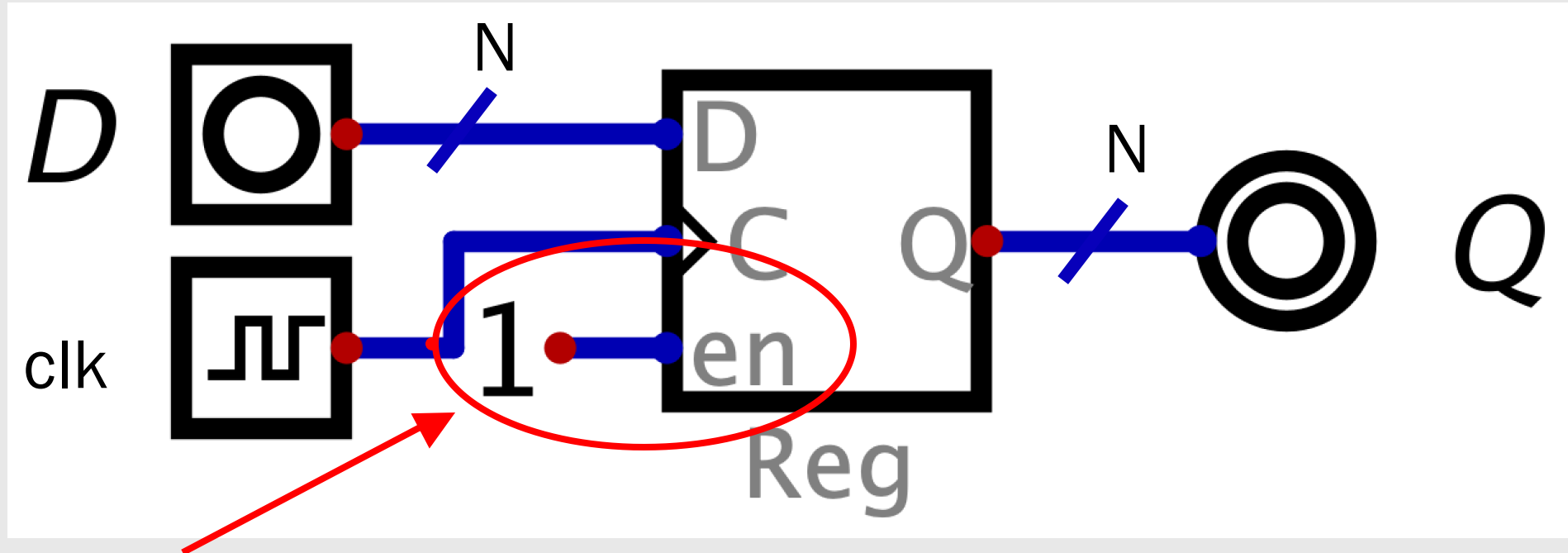

Enable

- If 1, the register will read D on the rising edge of the clock
- If 0, the register will not read D



TIMING ANALYSIS



Back-to-Back Additions


- We want to perform the following additions

1. - $7 + 7$ $A + B$
2. - $18 + 7$ $A + B$
3. - $30 + 8$ $A + B$


- This is a 10-bit adder, so none of these operations will overflow.

- C_o will be 0 for all of these operations

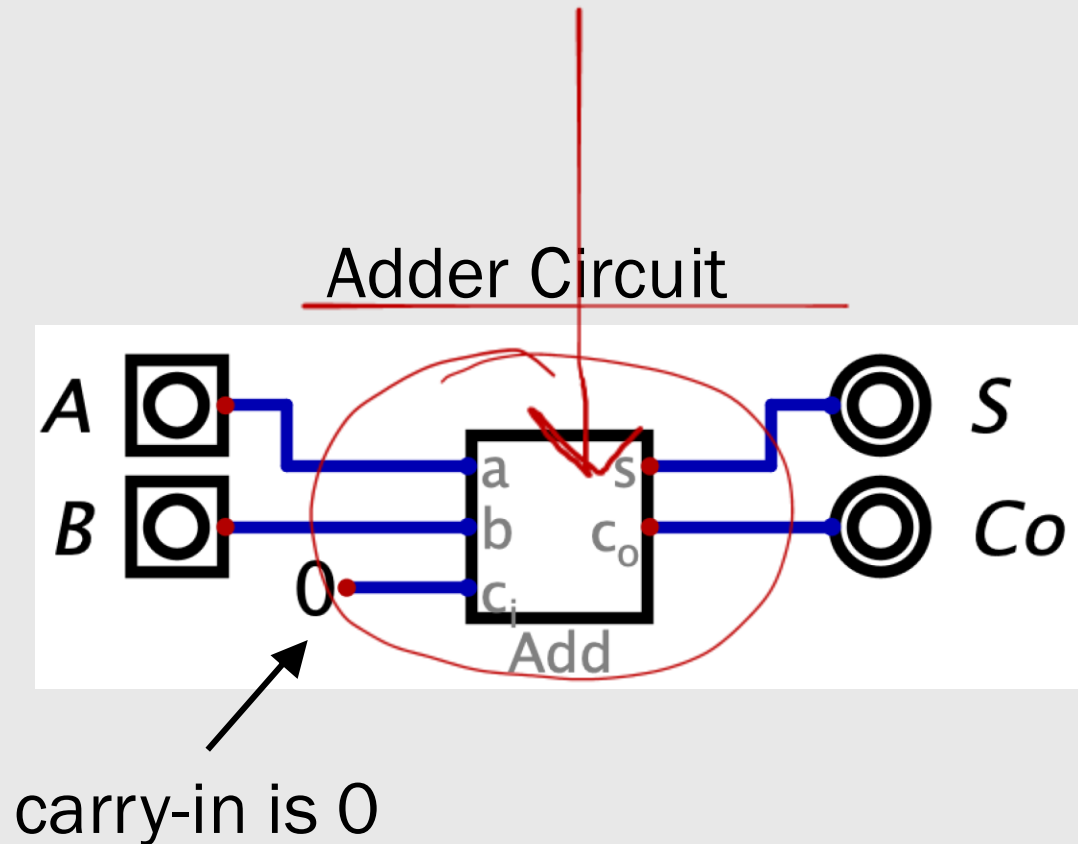- Let's say that the propagation delay of our adder circuit is 600ps



$t = 0\text{ps}$

 

At time $t = 0\text{ps}$, we will set the input A to 7 and the input B to 7. S and C_o will start at 0.

$t = 0\text{ps}$




A = 7

B = 7

S = 0

C_o = 0

$t = 0\text{ps}$

 

At time $t = 600\text{ps}$. The adder will finish its computation, so $S = 14$ and $Co = 0$.

We are now ready to perform the next addition. We will set $A = 18$ and $B = 7$.

$t = 0\text{ps}$

$t = 600\text{ps}$

$A = 7$

$B = 7$

$S = 0$

$Co = 0$


$A = 18$

$B = 7$

$\rightarrow S = 14$


$Co = 0$

$t = 0\text{ps}$

 


At time $t = 1200\text{ps}$. The adder will finish its computation, so $S = 25$ and $Co = 0$.

 We are now ready to perform the next addition. We will set $A = 30$ and $B = 8$.




t = 0ps

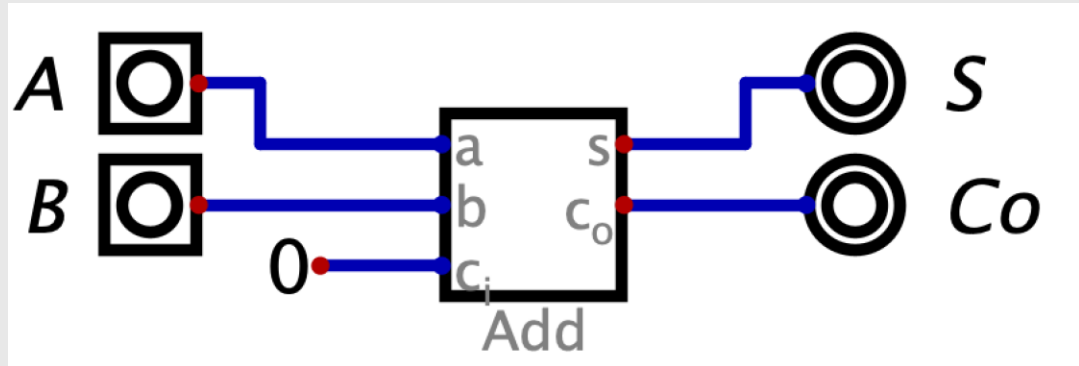


At time t = 1800ps. The adder will finish its computation, so S = 38 and Co = 0.

 
We don't have any more additions to perform, so we'll set A and B to 0.



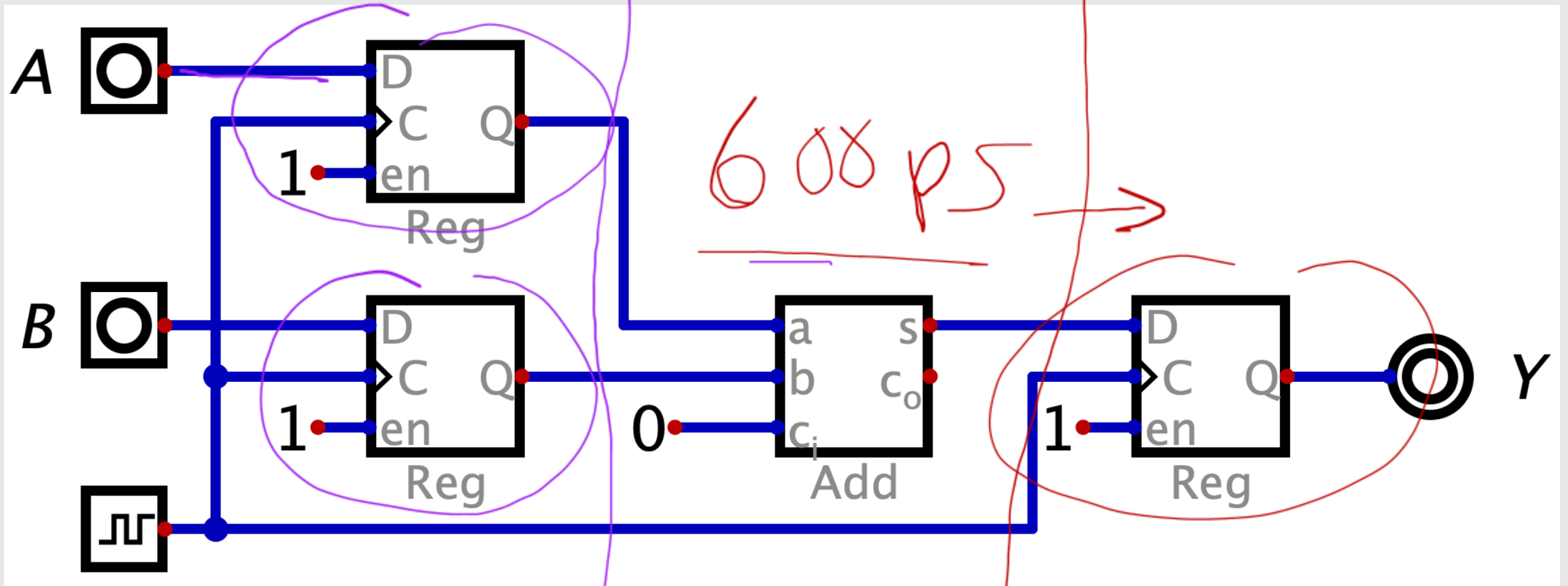
Using Registers to Set Inputs and Read Outputs at the Correct Times



Timing

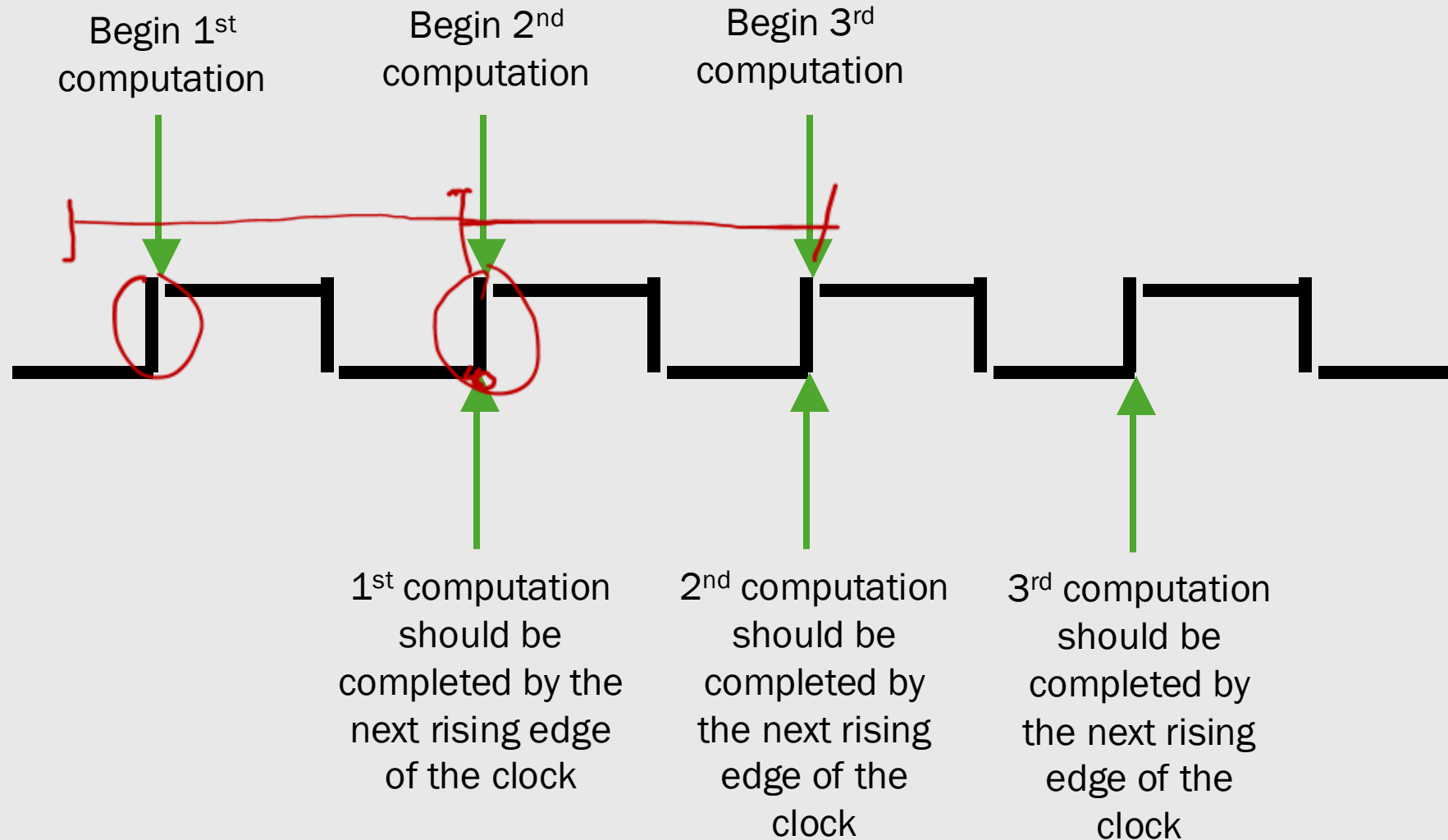

Timing

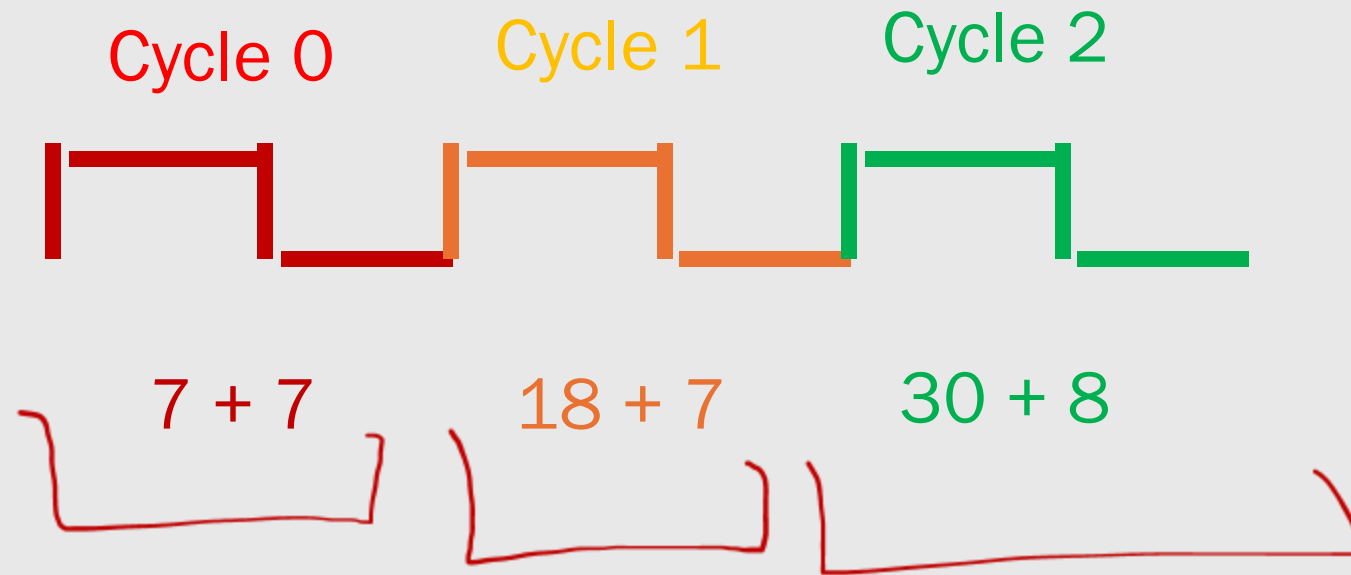


Starting State

0 + 0

0 + 0

0 + 0

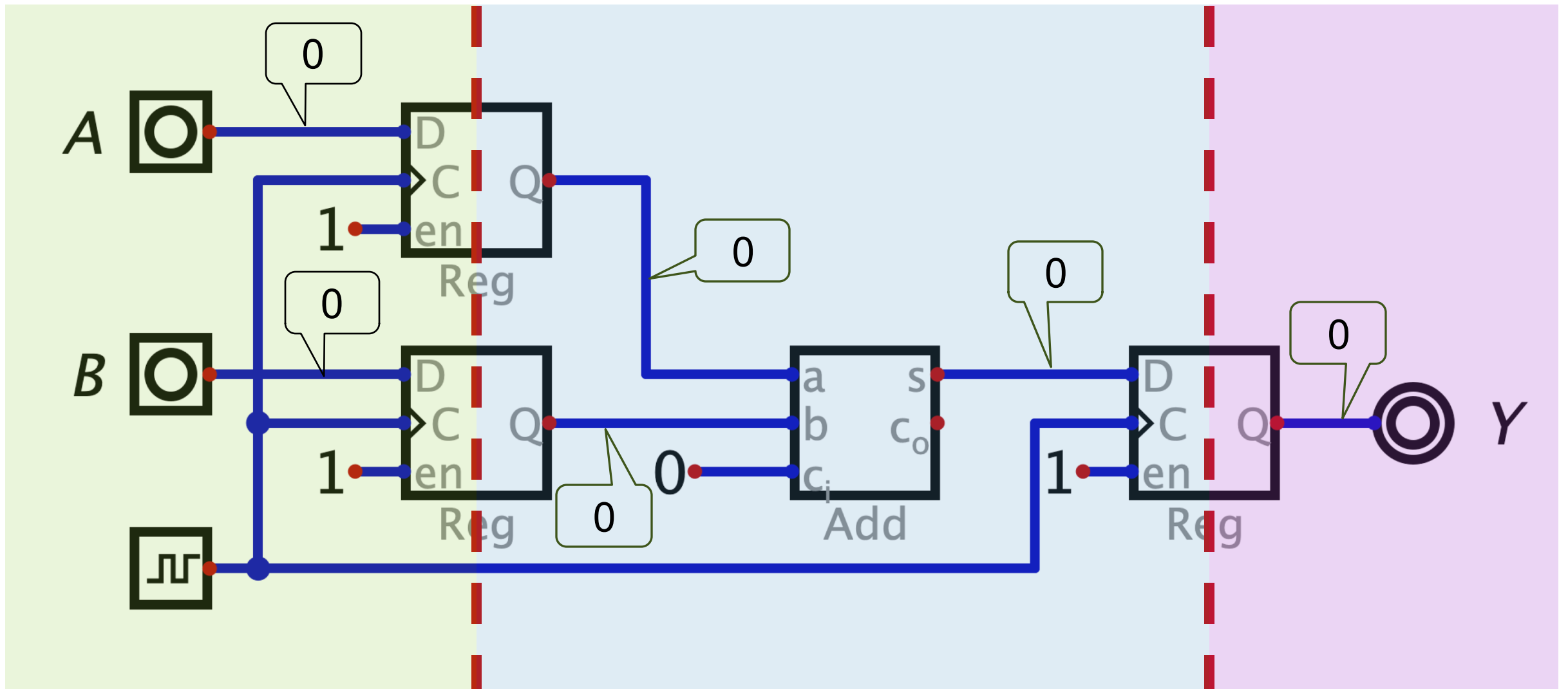


Cycle 0: On rising edge


7 + 7

0 + 0

0 + 0

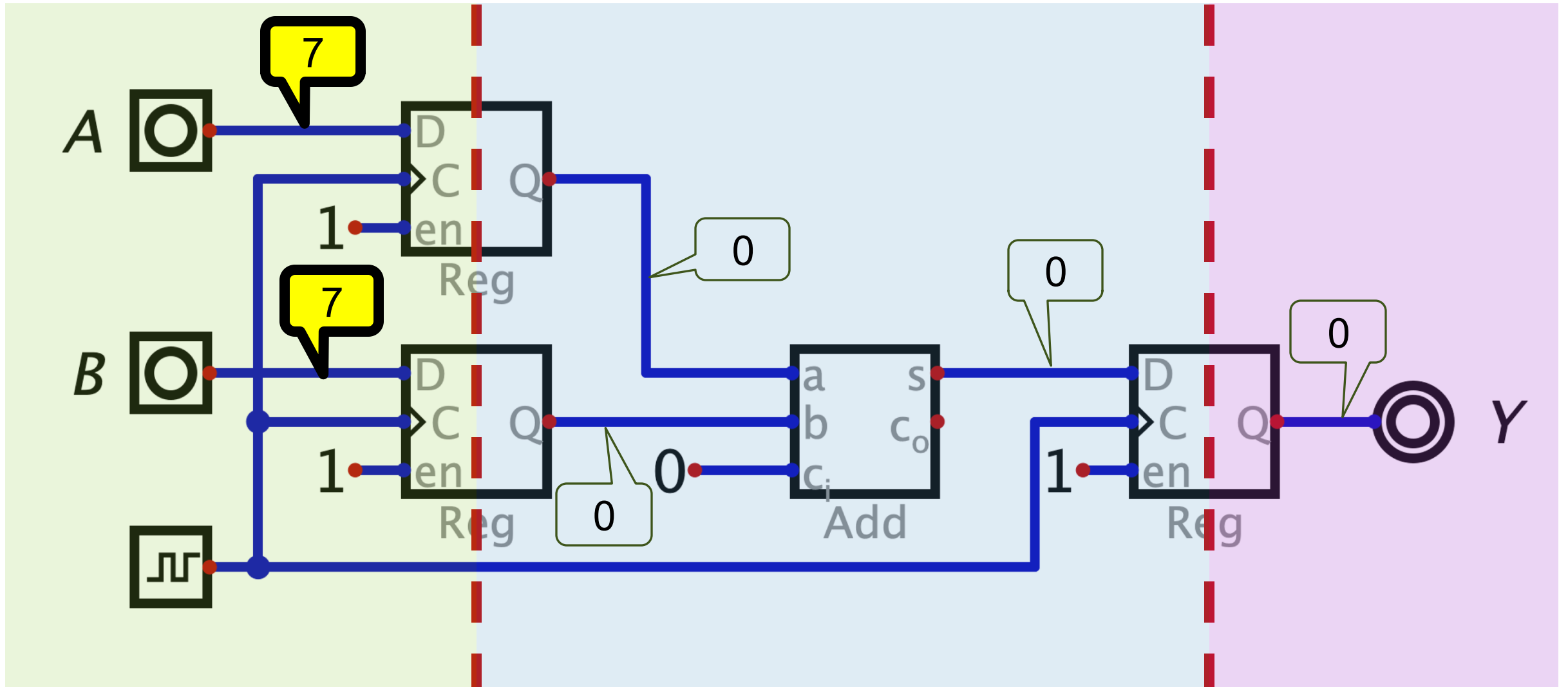


Cycle 0: After clk-to-q delay

 

7 + 7

7 + 7

0 + 0

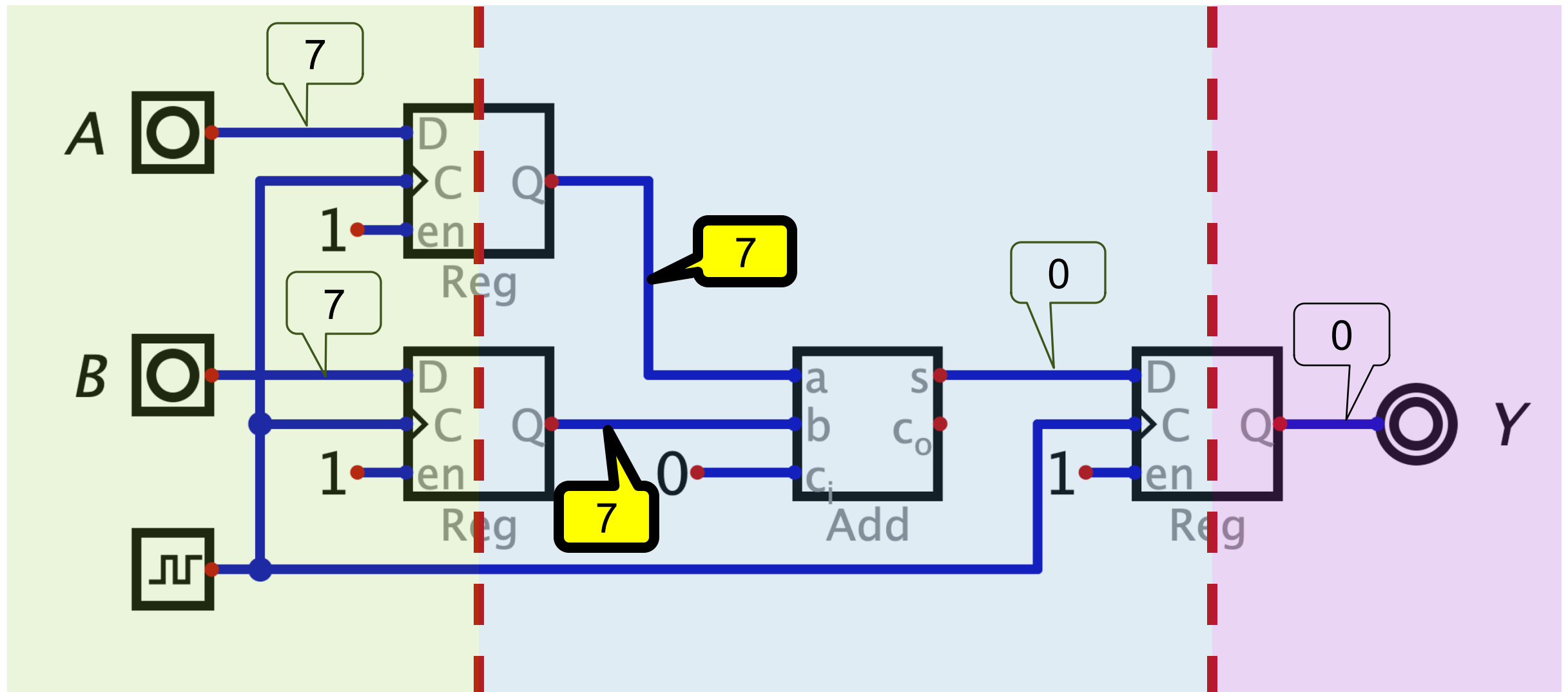


Cycle 0: After adder propagation delay



7 + 7

7 + 7

0 + 0

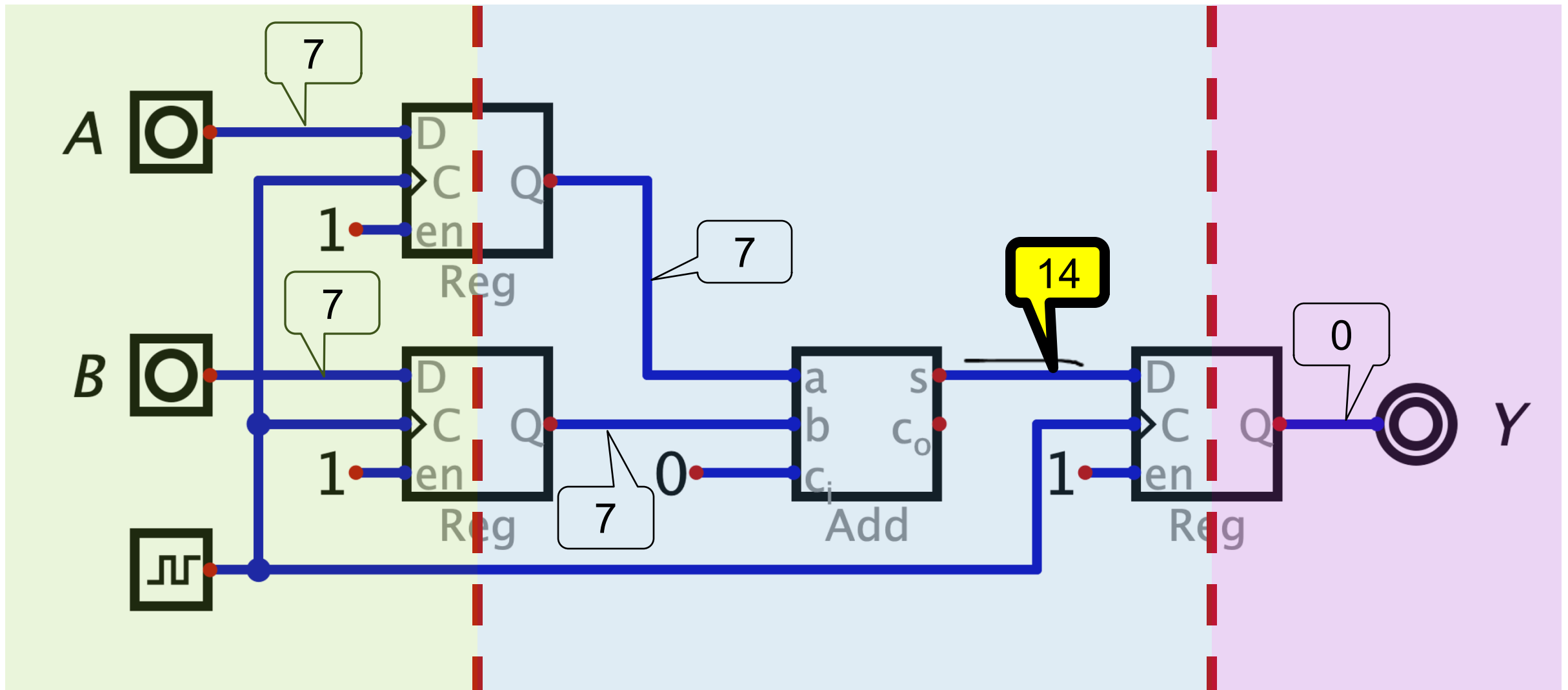


Cycle 1: On rising edge



$$18 + 7$$

$$7 + 7$$

$$0 + 0$$

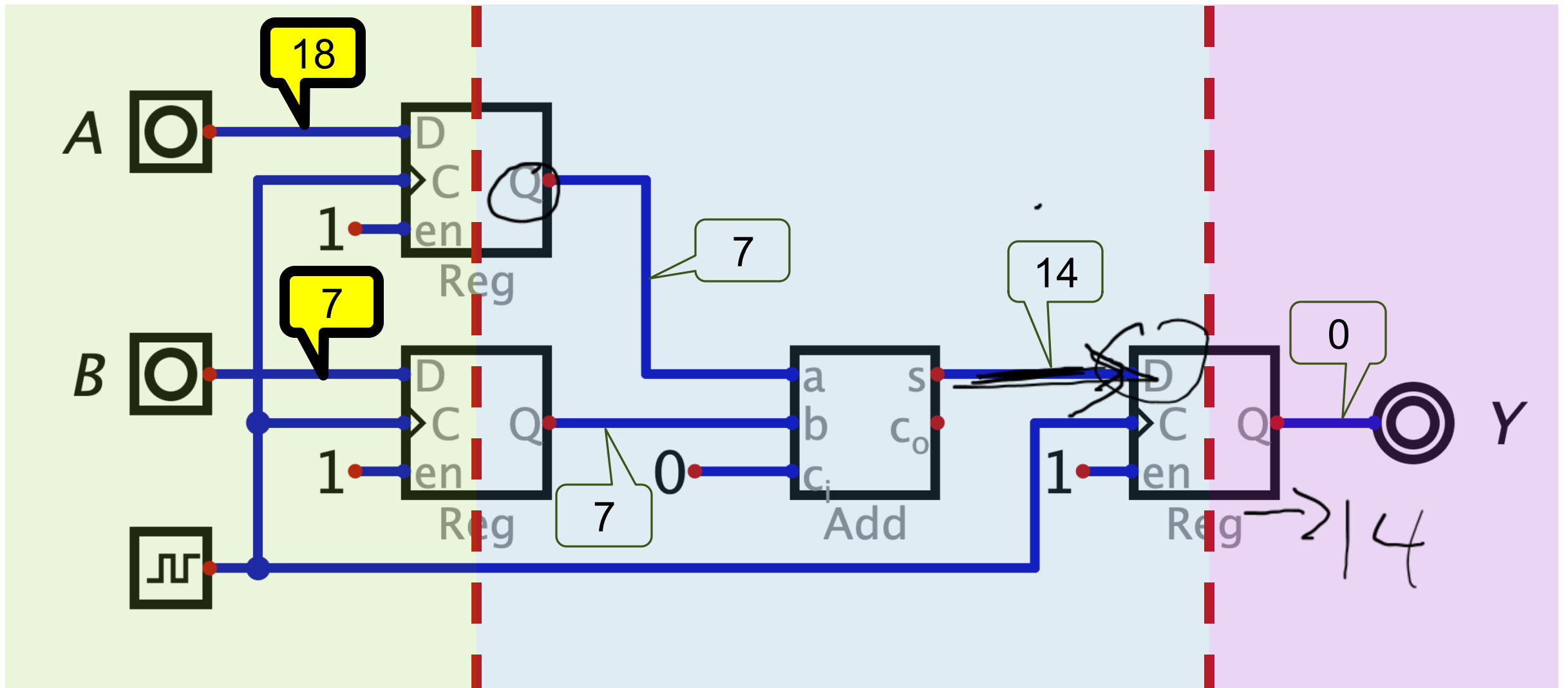


Cycle 1: After clk-to-q delay

18 + 7

18 + 7

7 + 7

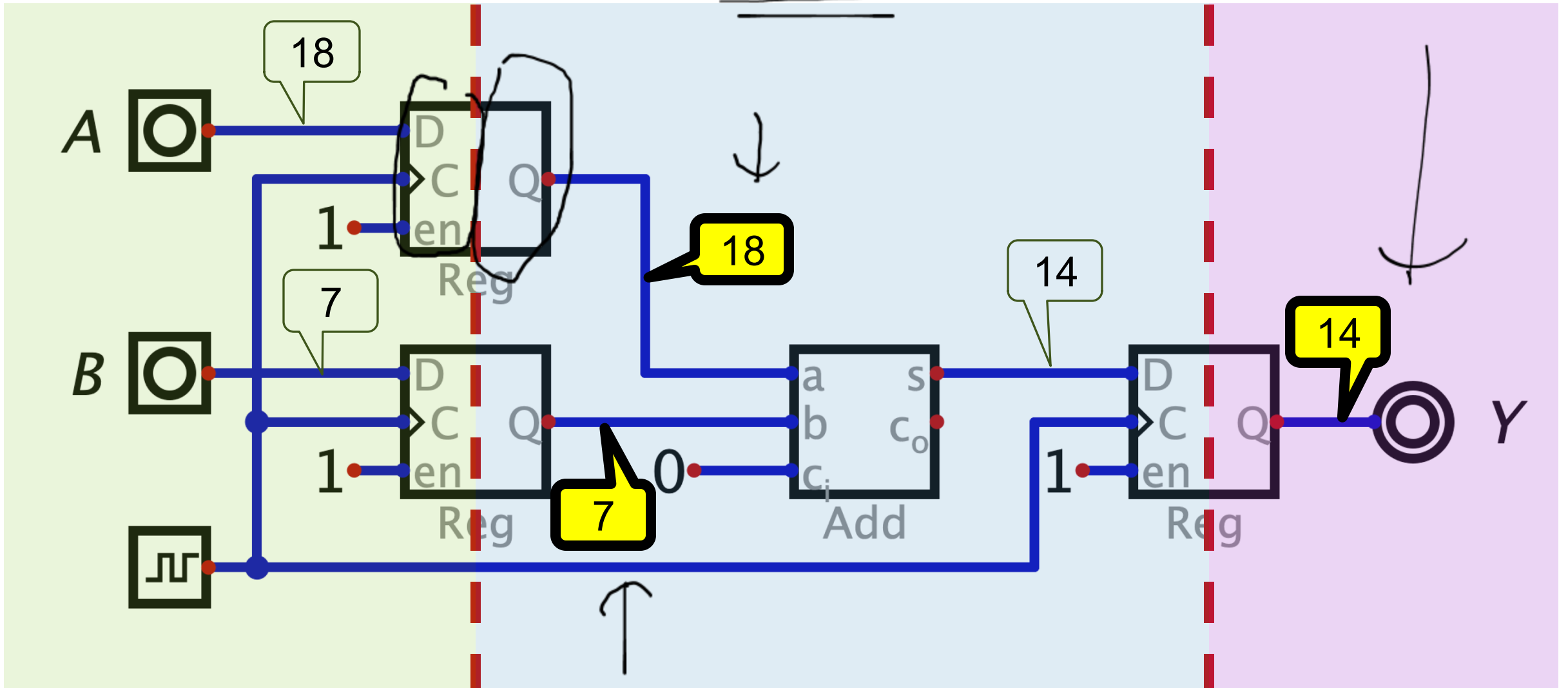


Cycle 1: After adder propagation delay

18 + 7

18 + 7

7 + 7

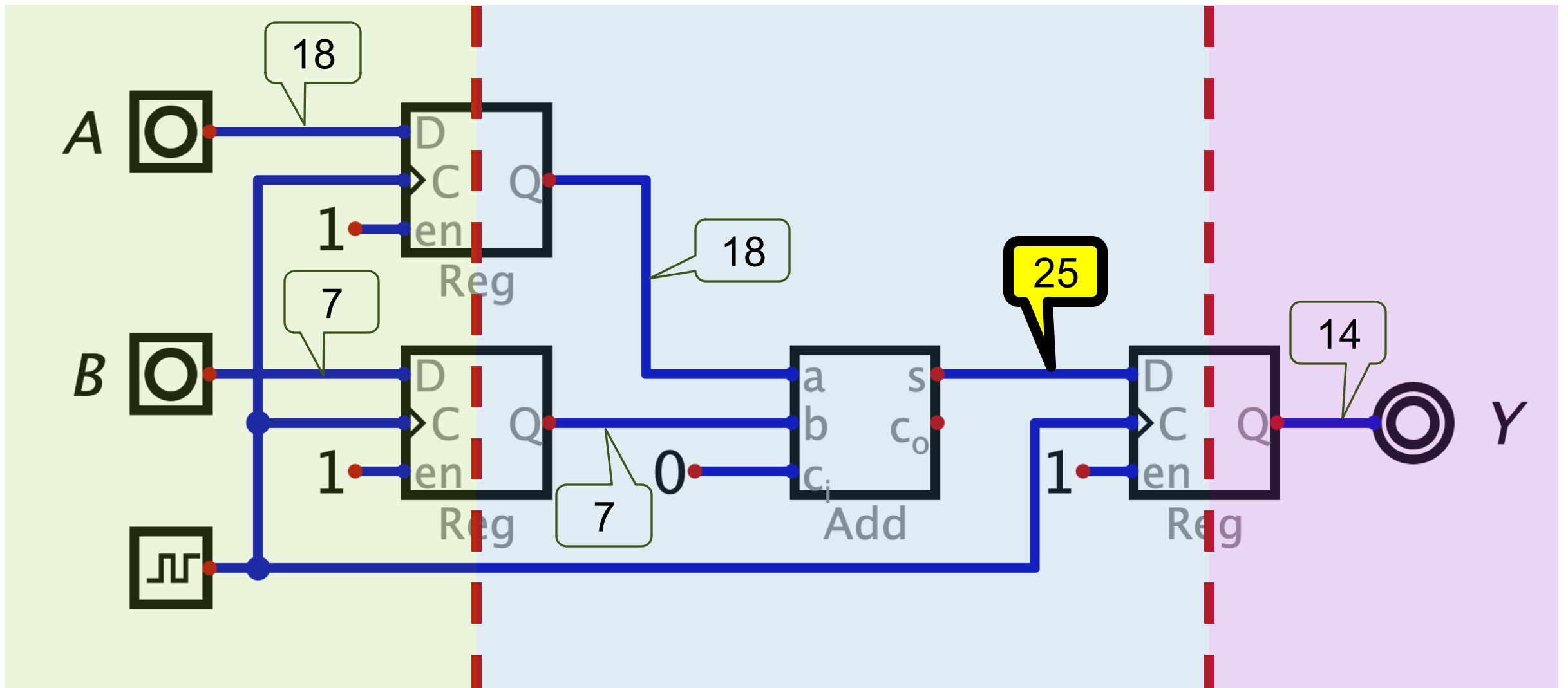


Cycle 2: On Rising Edge

$30 + 8$

$18 + 7$

$7 + 7$

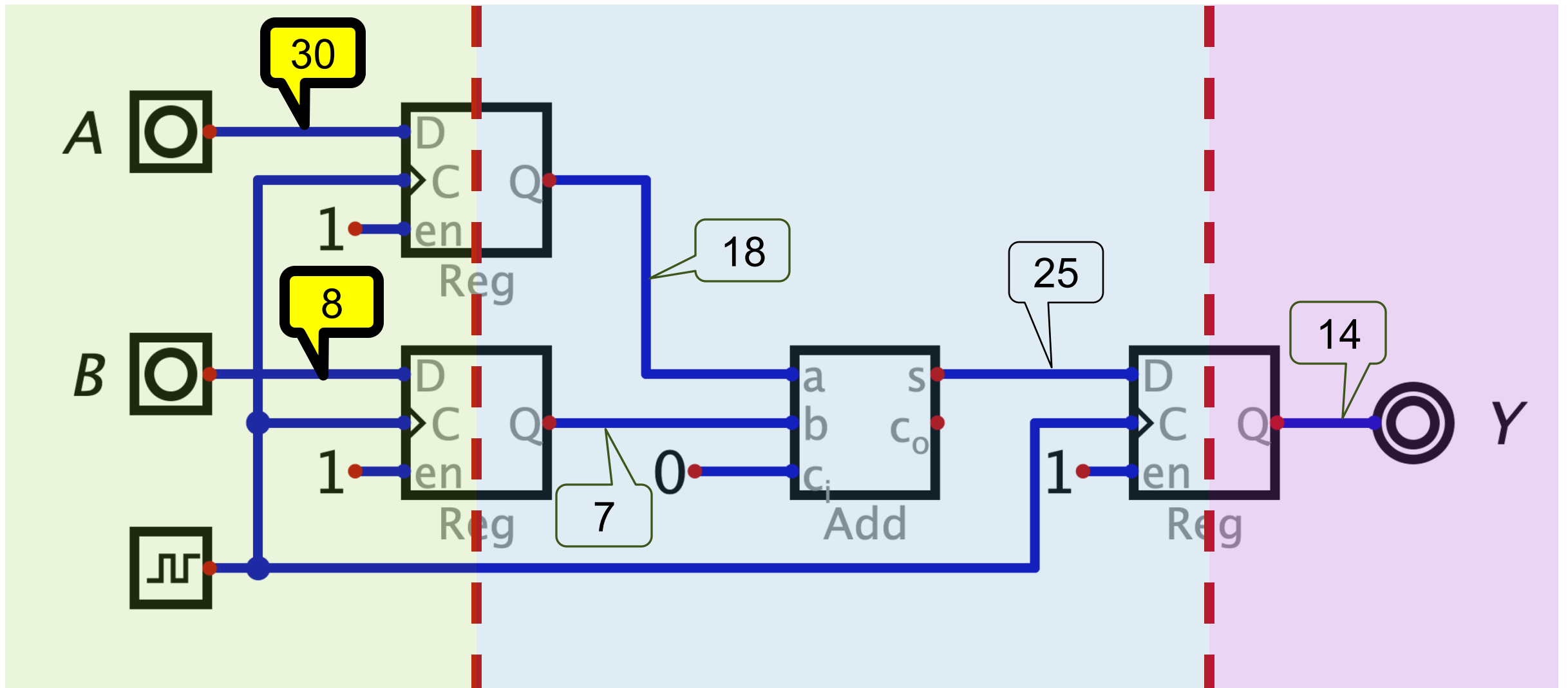


Cycle 2: After clk-to-q Delay

30 + 8

30 + 8

18 + 7

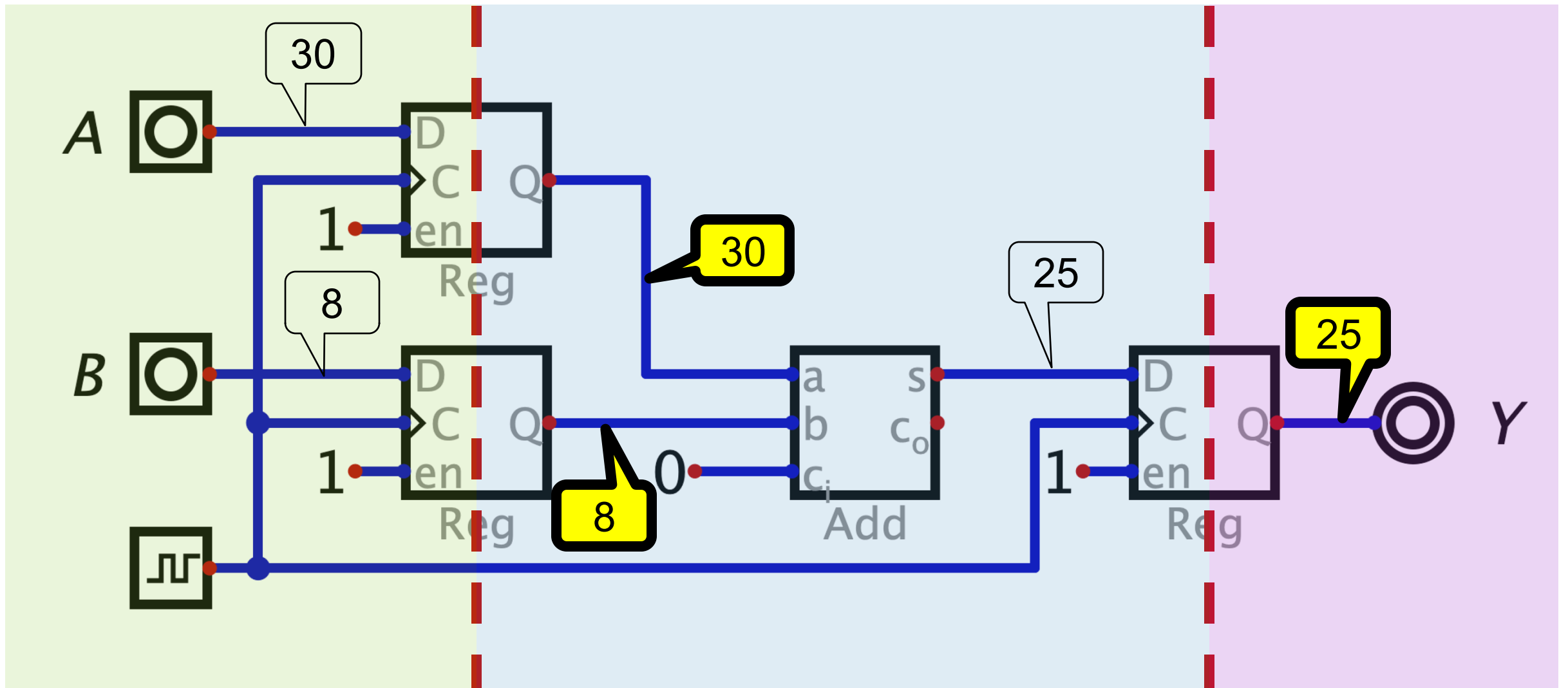


Cycle 2: After Adder Propagation Delay

30 + 8

30 + 8

18 + 7

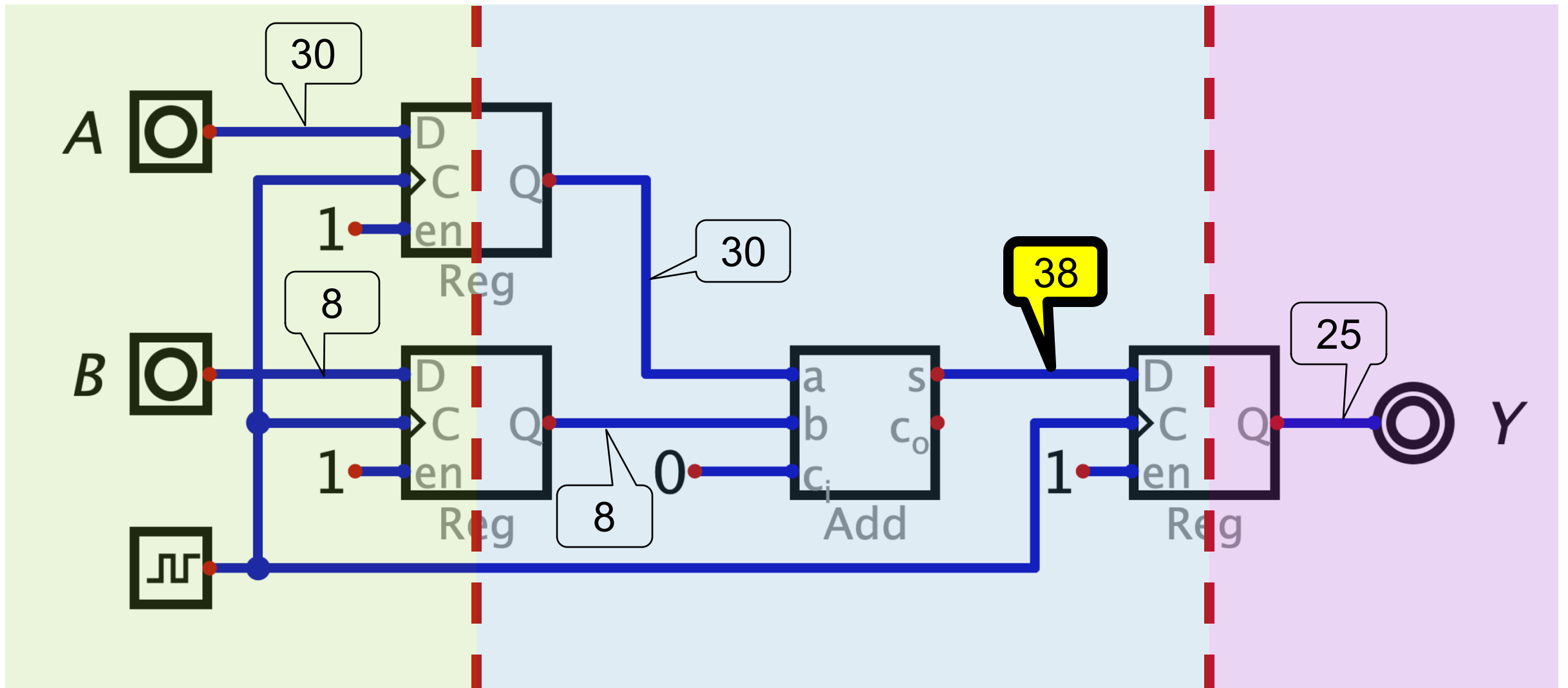


Cycle 3: On Rising Edge

$0 + 0$

$30 + 8$

$18 + 7$

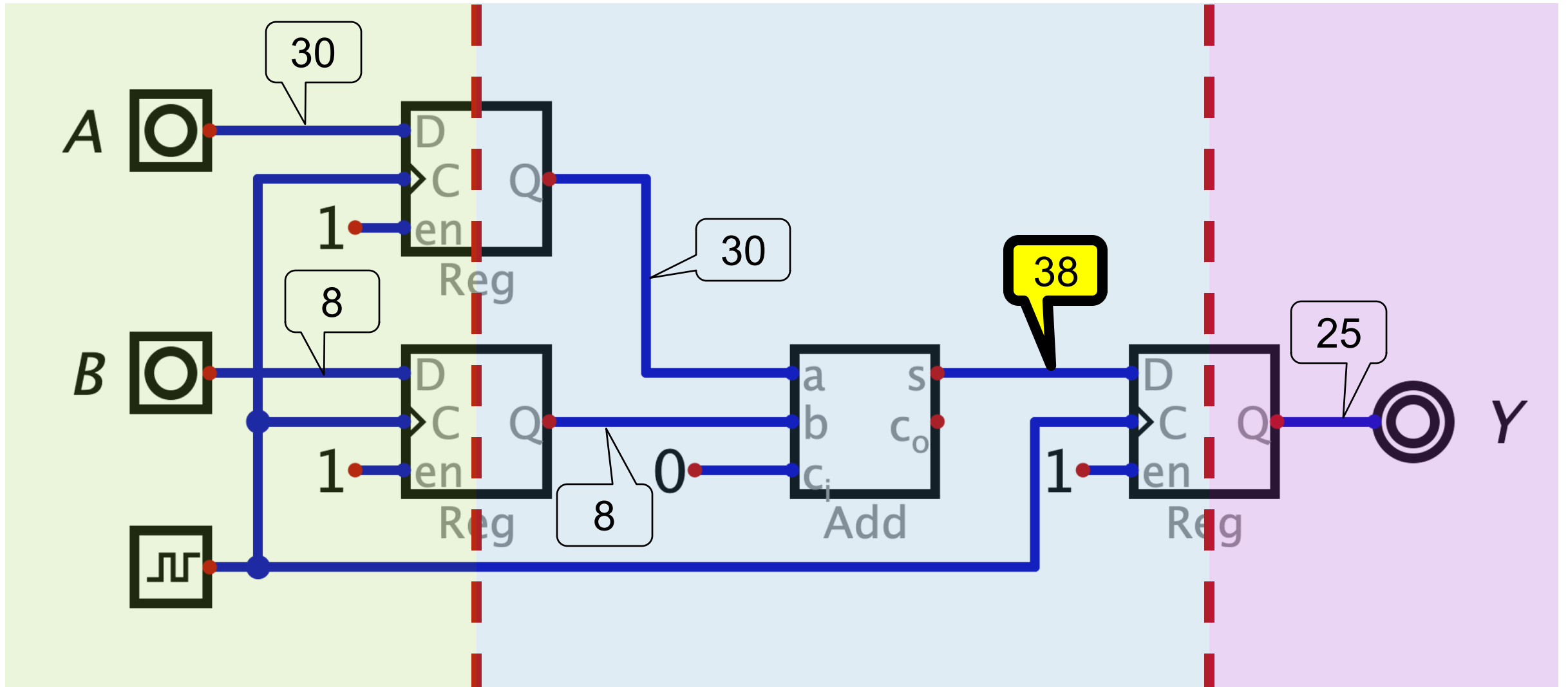


Cycle 3: After clk-to-q Delay

0 + 0

0 + 0

30 + 8

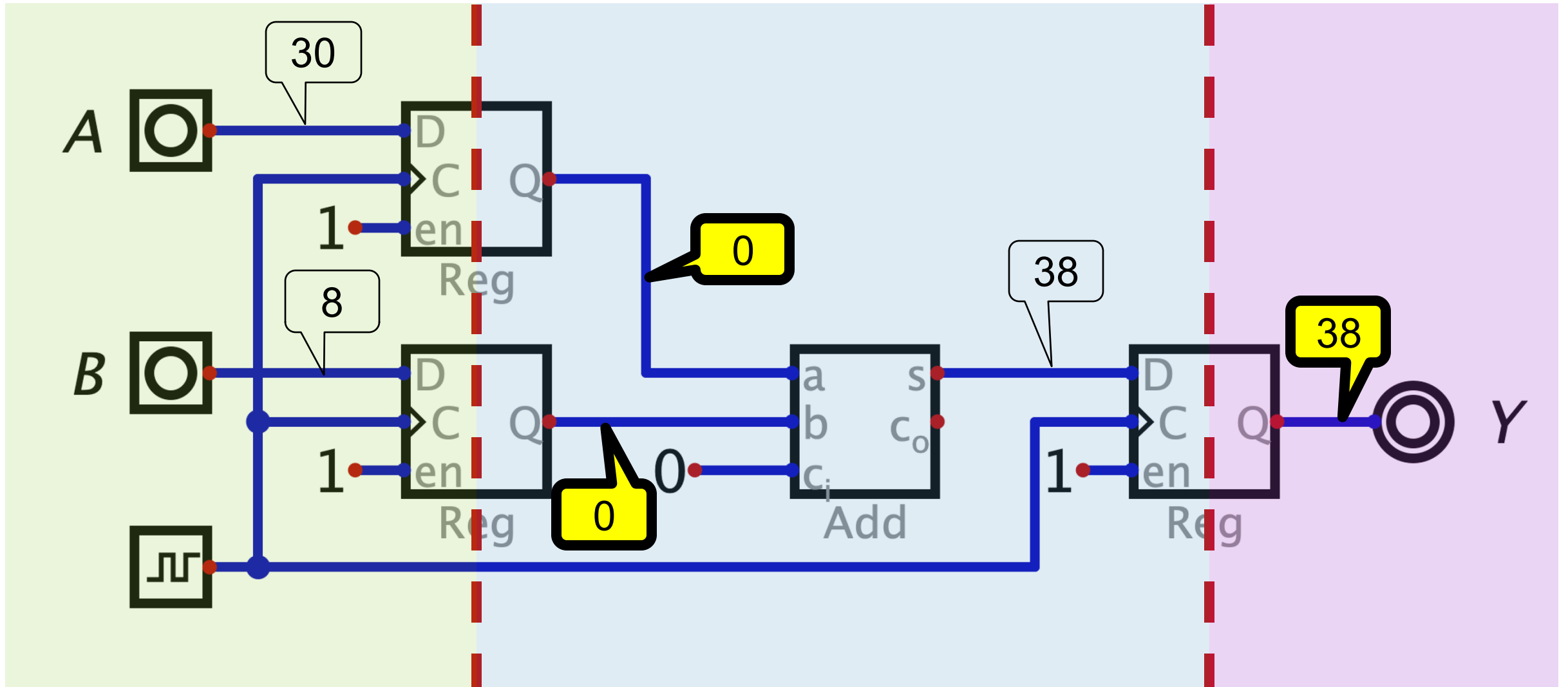


Delays

- Adder propagation delay = 600ps
- Register clk-to-q delay = 50ps
- These delays are innate properties of the components
- We can calculate these delays by finding the longest combinational delay
- We cannot change these values without changing the components


Clock Period

- We can adjust the clock period based on our needs
- There is a minimum clock period at which the circuit will work properly
- We can set our clock period to any value \geq min clock period


Ex1: Clock period = 700ps, clk-to-q delay = 50ps,
adder propagation delay = 600ps

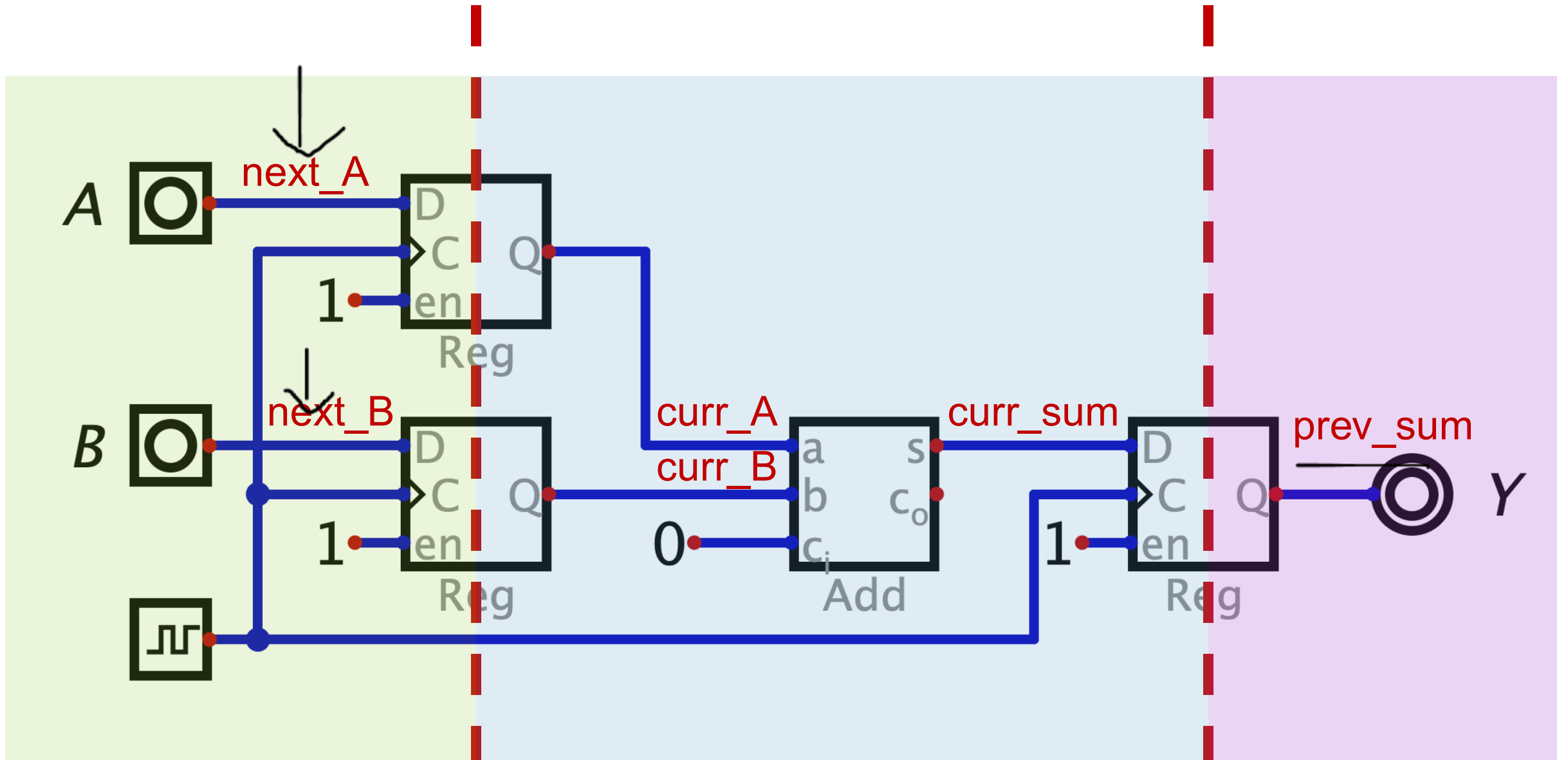

Cycle 0: 7 + 7

 


 adder propagation delay = 600 ps
 clk-to-q delay is 50ps
 clock period = 700ps




Signal	Starting State	t = 0 A = 7 B = 7	t = 50ps A = 7 B = 7	t = 650ps A = 7 B = 7	t = 700 ps A = 18 B = 7
next_A	0				
next_B	0				
curr_A	0				
curr_B	0				
curr_sum	0				
prev_sum	0				

Cycle 0: 7 + 7

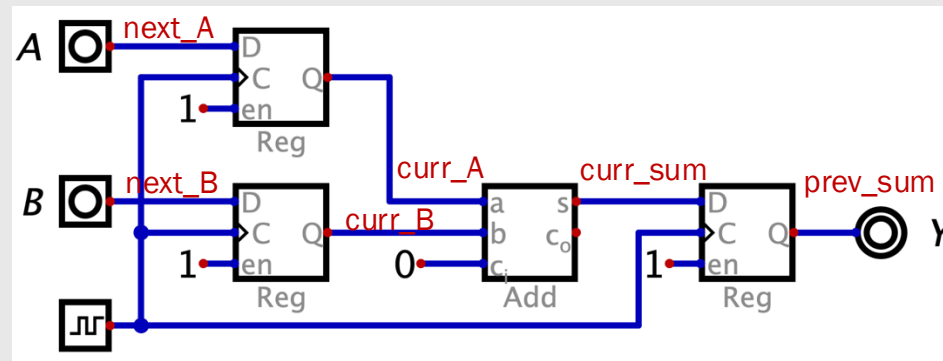


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 700ps




Signal	Starting State	t = 0 A = 7 B = 7	t = 50ps A = 7 B = 7	t = 650ps A = 7 B = 7	t = 700 ps A = 18 B = 7
next_A	0	7	7	7	18
next_B	0	7	7	7	7
curr_A	0	0	7	7	7
curr_B	0	0	7	7	7
curr_sum	0	0	0	14	14
prev_sum	0	0	0	0	0

Cycle 1: 18 + 7

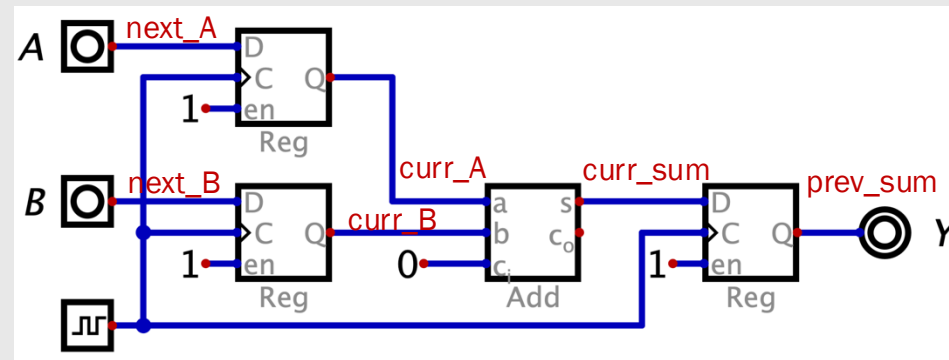


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 700ps




Signal	t = 700 ps A = 18 B = 7	t = 750 ps A = 18 B = 7	t = 1350 ps A = 18 B = 7	t = 1400 ps A = 30 B = 8
next_A	18			
next_B	7			
curr_A	7			
curr_B	7			
curr_sum	14			
prev_sum	0			

Cycle 1: 18 + 7

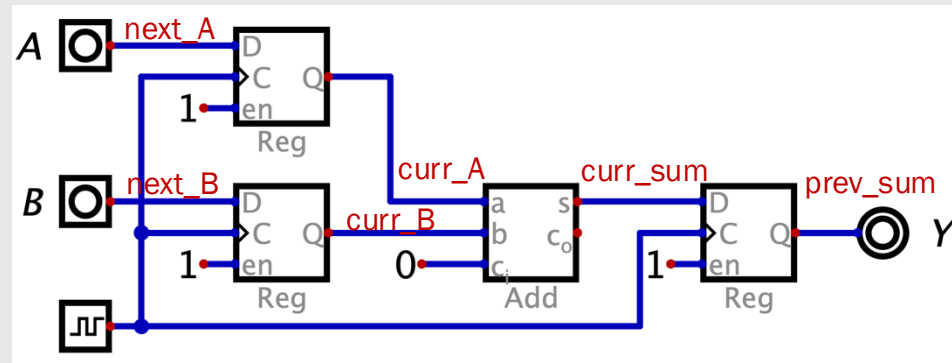


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 700ps




Signal	t = 700 ps A = 18 B = 7	t = 750 ps A = 18 B = 7	t = 1350 ps A = 18 B = 7	t = 1400 ps A = 30 B = 8
next_A	18	18	18	30
next_B	7	7	7	8
curr_A	7	18	18	18
curr_B	7	7	7	7
curr_sum	14	14	25	25
prev_sum	0	14	14	14

Cycle 2: 30 + 8

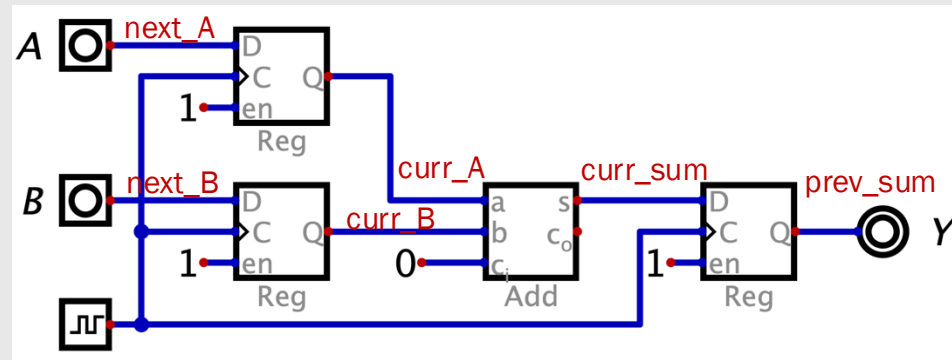


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 700ps




Signal	t = 1400 ps A = 30 B = 8	t = 1450 ps A = 30 B = 8	t = 2050 ps A = 30 B = 8	t = 2100 ps A = 15 B = 30
next_A	30			
next_B	8			
curr_A	18			
curr_B	7			
curr_sum	25			
prev_sum	14			

Cycle 2: 30 + 8

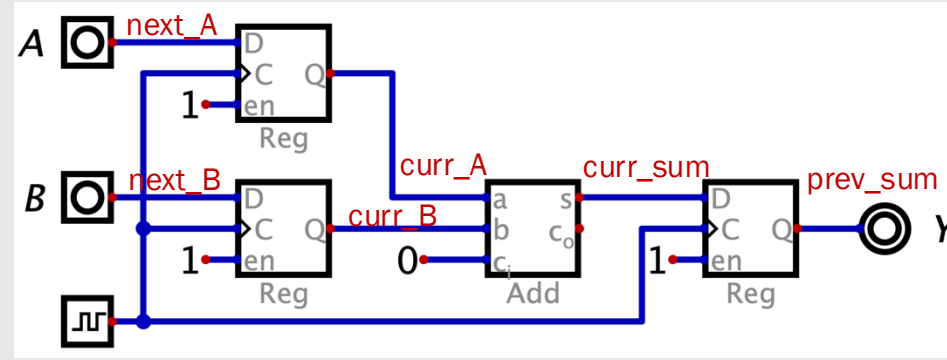


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 700ps




Signal	t = 1400 ps A = 30 B = 8	t = 1450 ps A = 30 B = 8	t = 2050 ps A = 30 B = 8	t = 2100 ps A = 15 B = 30
next_A	30	30	30	15
next_B	8	8	8	30
curr_A	18	30	30	30
curr_B	7	8	8	8
curr_sum	25	25	38	38
prev_sum	14	25	25	25


Ex1: Clock period = 700ps, clk-to-q delay = 50ps,
adder propagation delay = 600ps

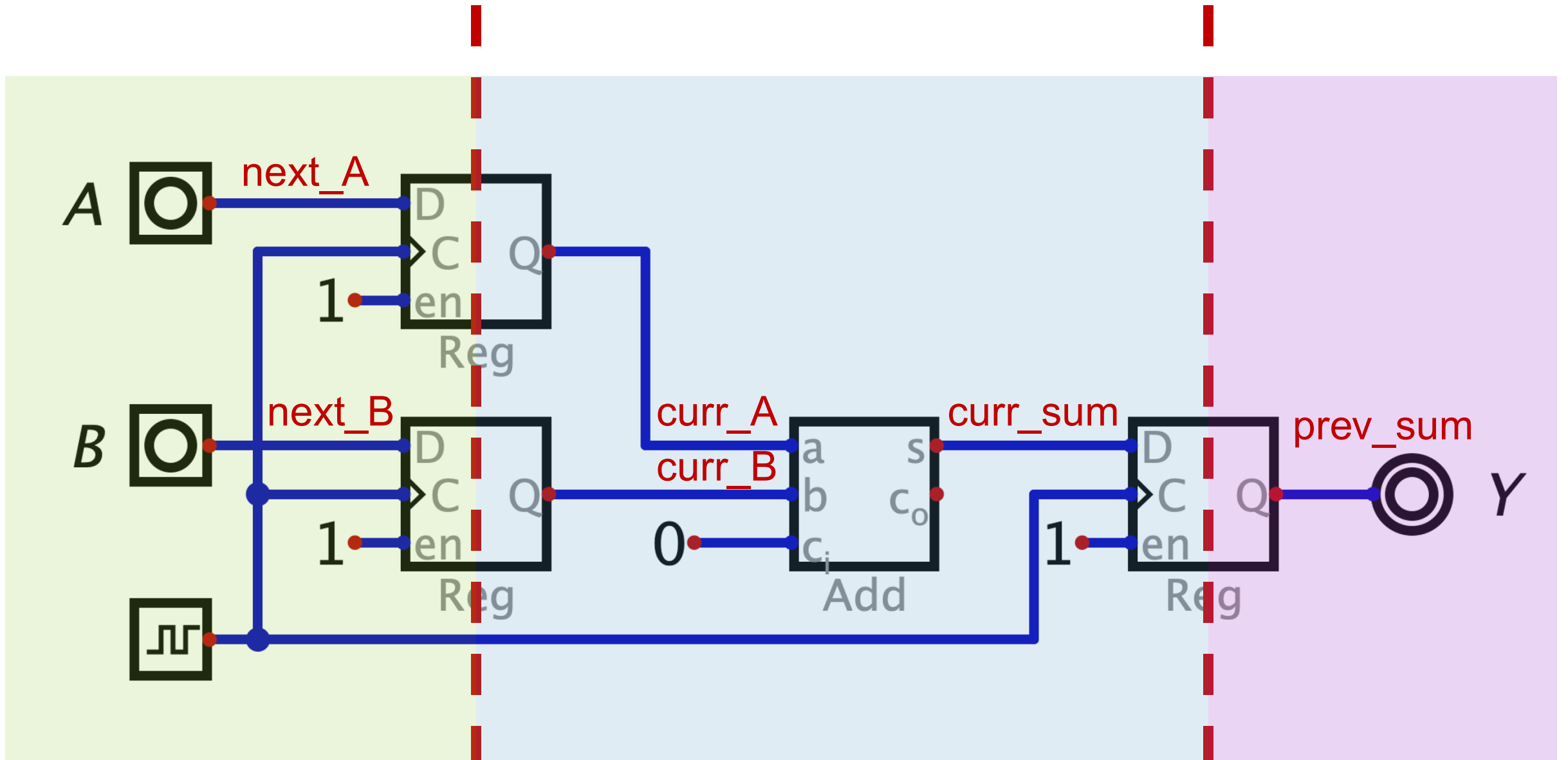

Cycle 3: 15 + 30

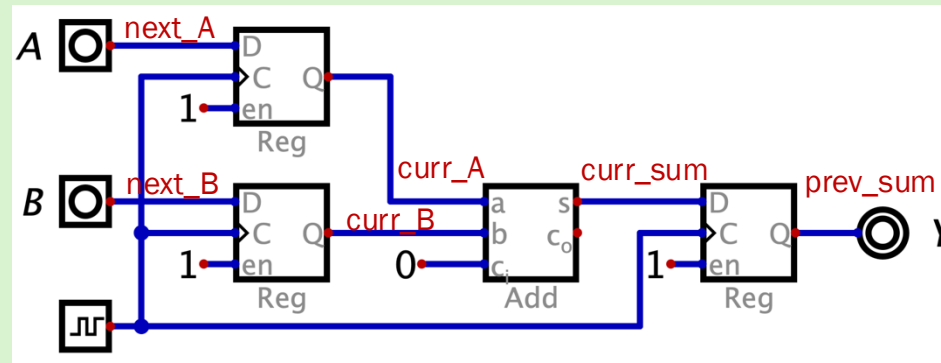

 
adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 700ps



Signal	<u>t = 2100 ps</u> A = 15 B = 30	<u>t = 2150 ps</u> A = 15 B = 30	<u>t = 2750 ps</u> A = 20 B = 30	<u>t = 2800 ps</u> A = 20 B = 30
next_A	15			
next_B	30			
curr_A	30			
curr_B	8			
curr_sum	38			
prev_sum	25			


Not a typo!
 What will happen in this case?

Cycle 3: 15 + 3

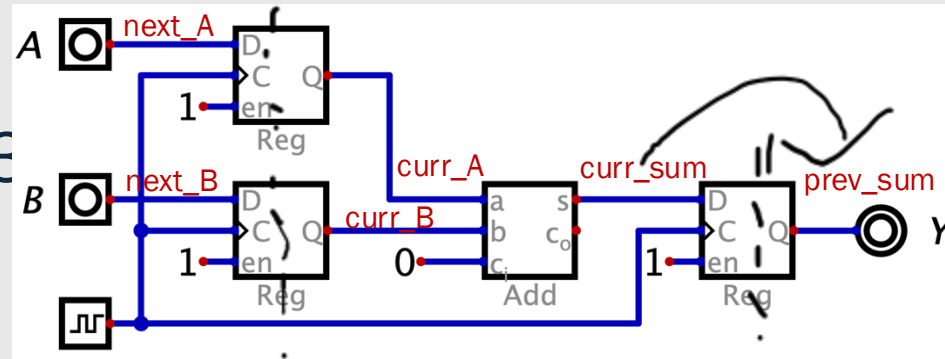

adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 700ps

[2100, 2800)

 


Signal	t = 2100 ps A = 15 B = 30	t = 2150 ps A = 15 B = 30	t = 2750 ps A = 20 B = 30	t = 2800 ps A = 20 B = 30
next_A	15	15	20	20
next_B	30	30	30	30
curr_A	30	15	15	15
curr_B	8	30	30	30
curr_sum	38	38	45	45
prev_sum	25	38	38	38

Not a typo!
 What will happen in this case?


Input A updating at $t = 2750\text{ps}$

- Our addition will work the same as before!
- The register prevents the value of A from moving forward until the rising edge of the clock
- We can update the inputs anytime from $t = 2150\text{ps}$ to $t = 2800\text{ps}$
 - *(aka until the next rising edge)*
- The value will simply just stay at the input of the register until the rising edge of the clock

Cycle 4: 20 + 30

 


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 700ps



Signal	t = 2800 ps A = 20 B = 30	t = 2850 ps A = 20 B = 30	t = 3450 ps A = 20 B = 30	t = 3500 ps A = 0 B = 0
next_A	20	20	20	0
next_B	30	30	30	0
curr_A	15	20	20	20
curr_B	30	30	30	30
curr_sum	45	45	50	50
prev_sum	38	45	45	45

Clock Period = 700ps

 

clk-to-q delay = 50ps

adder propagation delay = 600ps

idle time = 50ps