

pollev.com/kakiryan

COMP311: *COMPUTER ORGANIZATION!*

Lecture 16: Timing Analysis, Pipelining Intro

tinyurl.com/comp311-fa25



Quiz Topics & Logistics Updates

- Another ALU tracing problem
 - Multiplexers – Review Question 3 from WA3
 - Waveform Diagrams
 - Flip flops & Registers
 - Clk-to-Q Delay
 - Timing Analysis Tables – See WA4
-
- WA4 was released! Due in 1.5 wks

Undergrad Systems Reading Group!! 😊


- Mondays at 4pm!
- FB141
- Snacks provided!
- All are welcome!!
 - *No background in CS research necessary*
- If you are interested in being added to the mailing list, send me an email!




TIMING ANALYSIS




Timing

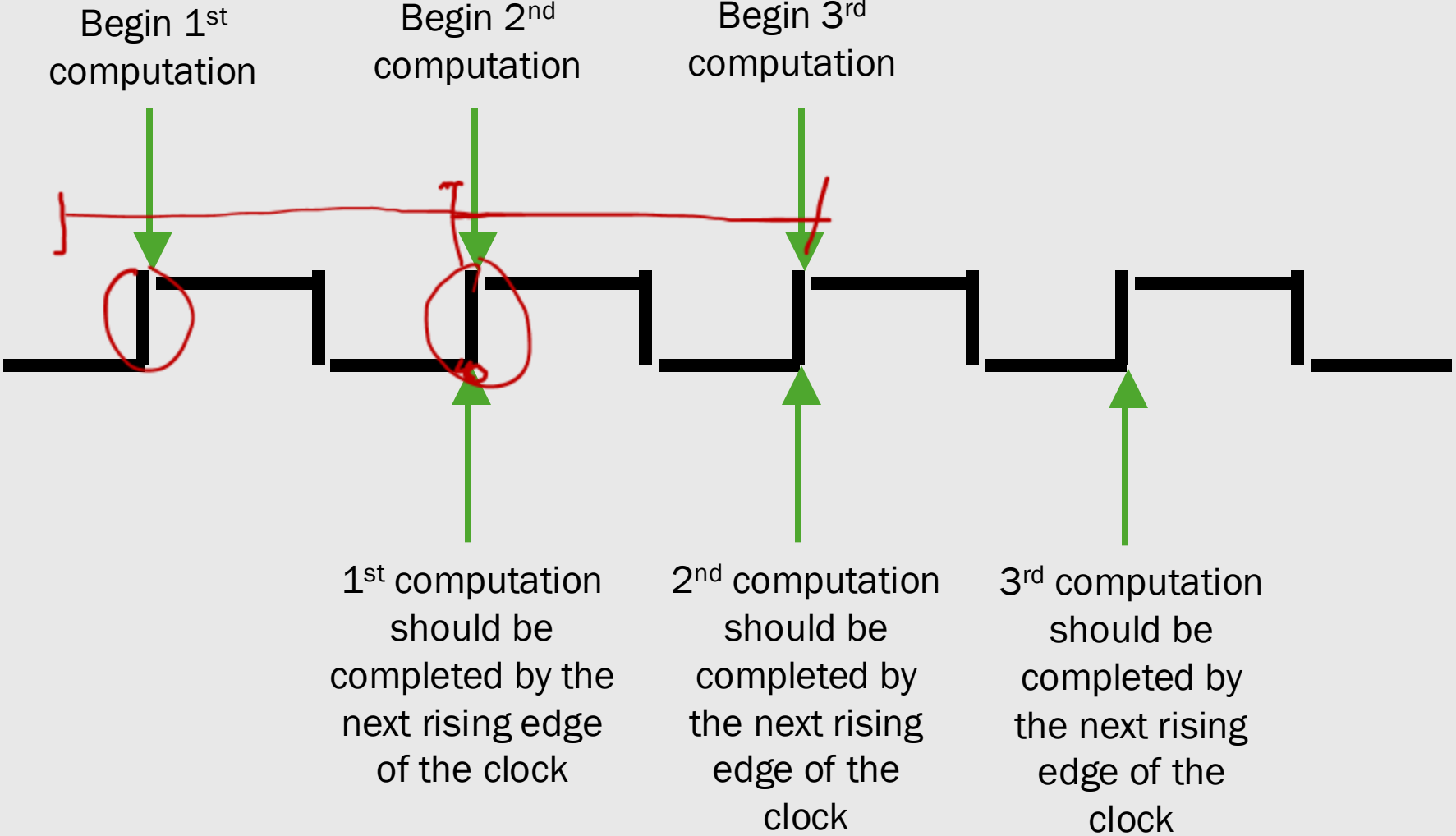


Timing

 


Ex1: Clock period = 700ps, clk-to-q delay = 50ps,
adder propagation delay = 600ps

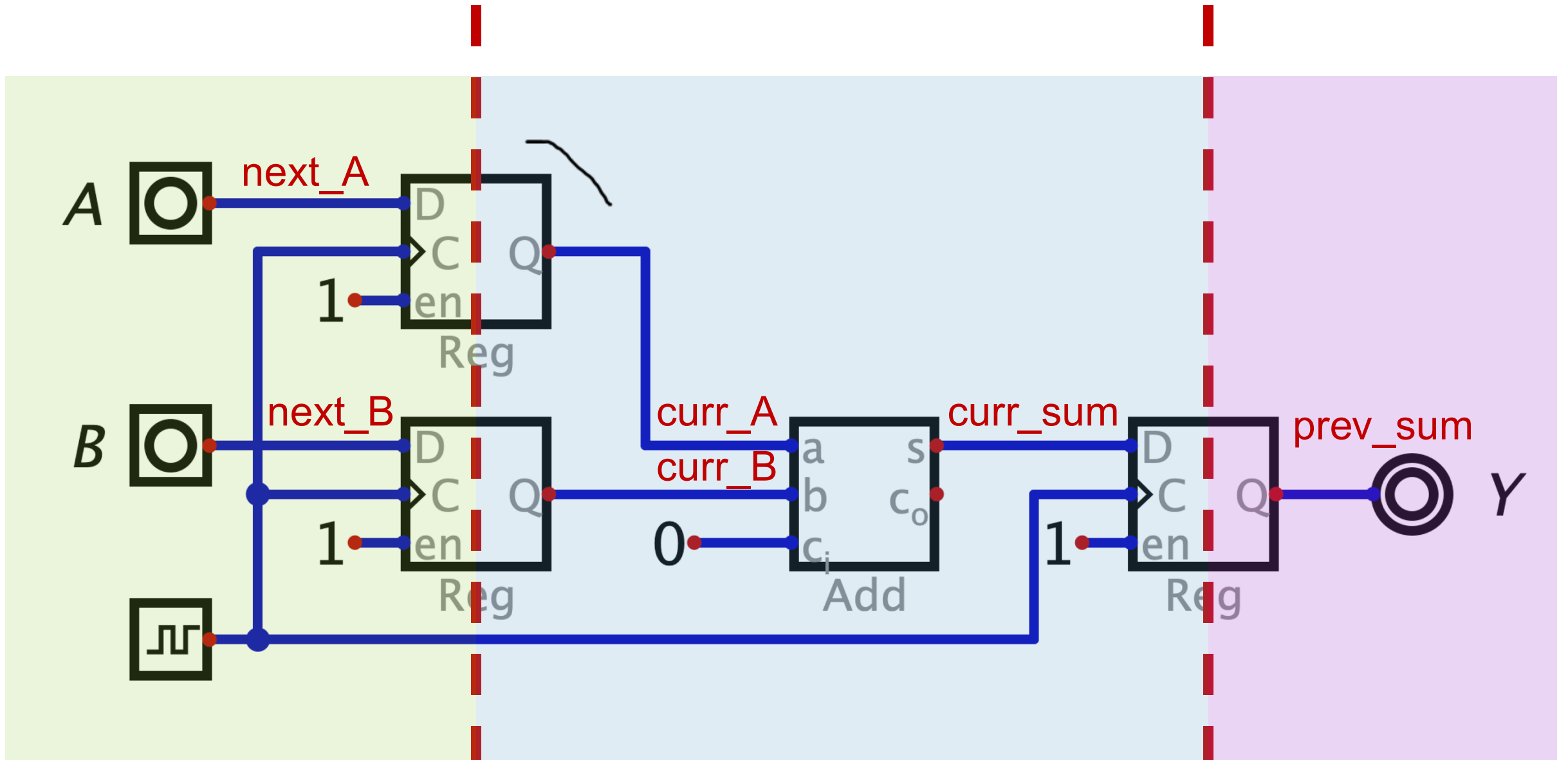

Cycle 3: 15 + 30

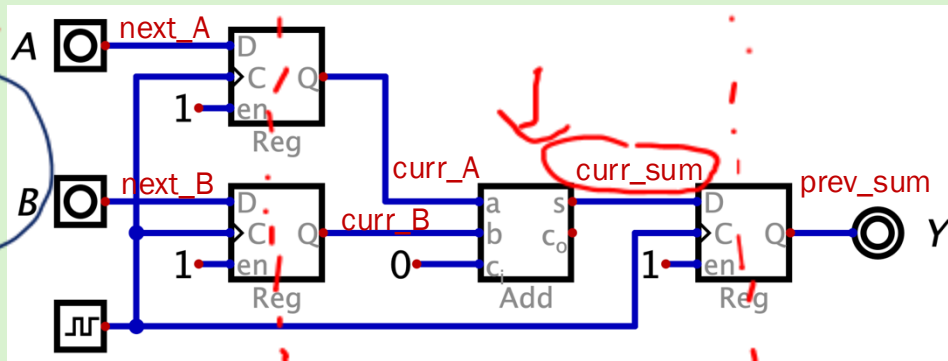

 
adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 700ps




Signal	t = 2100 ps	t = 2150 ps	t = 2750 ps	t = 2800 ps
next_A	15	15	20	20
next_B	30	30	30	30
curr_A	30	15	15	15
curr_B	8	30	30	30
curr_sum	38	38	45	45
prev_sum	25	38	38	38

Not a typo!
 What will happen in this case?

Cycle 3: 15 + 30

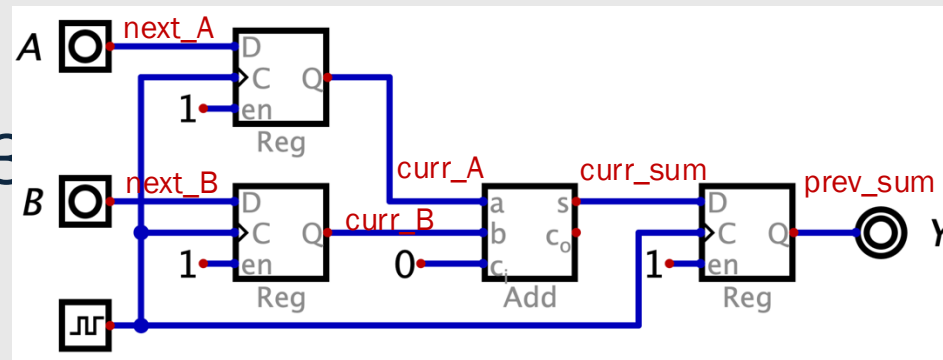

 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 700ps




Signal	t = 2100 ps A = 15 B = 30	t = 2150 ps A = 15 B = 30	t = 2750 ps A = 20 B = 30	t = 2800 ps A = 20 B = 30
next_A	15	15	20	20
next_B	30	30	30	30
curr_A	30	15	15	15
curr_B	8	30	30	30
curr_sum	38	38	45	45
prev_sum	25	38	38	38

Not a typo!
 What will happen in this case?


Input A updating at $t = 2750\text{ps}$

- Our addition will work the same as before!
- The register prevents the value of A from moving forward until the rising edge of the clock
- We can update the inputs anytime from $t = 2150\text{ps}$ to $t = 2800\text{ps}$
 - *(aka until the next rising edge)*
- The value will simply just stay at the input of the register until the rising edge of the clock

Cycle 4: 20 + 30

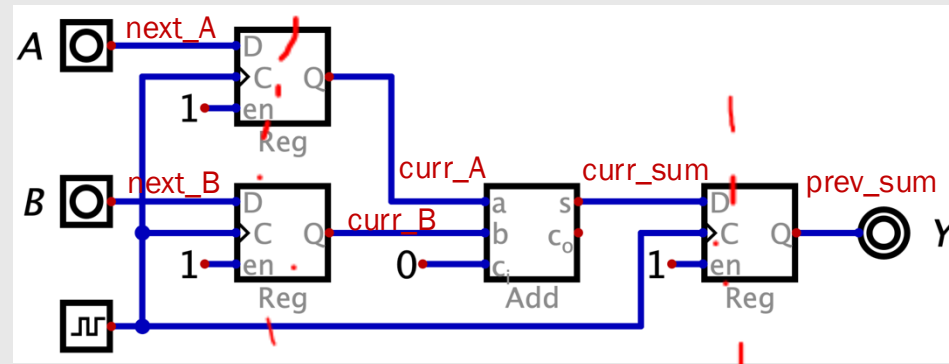


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 700ps




Signal	t = 2800 ps A = 20 B = 30	t = 2850 ps A = 20 B = 30	t = 3450 ps A = 20 B = 30	t = 3500 ps A = 0 B = 0
next_A	20	20	20	0
next_B	30	30	30	0
curr_A	15	20	20	20
curr_B	30	30	30	30
curr_sum	45	45	50	50
prev_sum	38	45	45	45

Cycle 4: 20 + 30

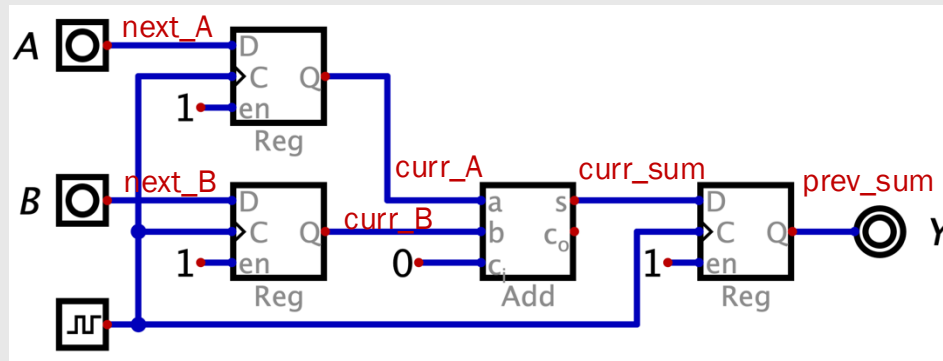


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 700ps



Signal	t = 2800 ps A = 20 B = 30	t = 2850 ps A = 20 B = 30	t = 3450 ps A = 20 B = 30	t = 3500 ps A = 0 B = 0
next_A	20	20	20	0
next_B	30	30	30	0
curr_A	15	20	20	20
curr_B	30	30	30	30
curr_sum	45	45	50	50
prev_sum	38	45	45	45

Clock Period = 700ps

 


→ clk-to-q delay = 50ps


→ adder propagation delay = 600ps

idle time = 50ps

Ex2: Clock period = 650ps, clk-to-q delay = 50ps,
adder propagation delay = 600ps

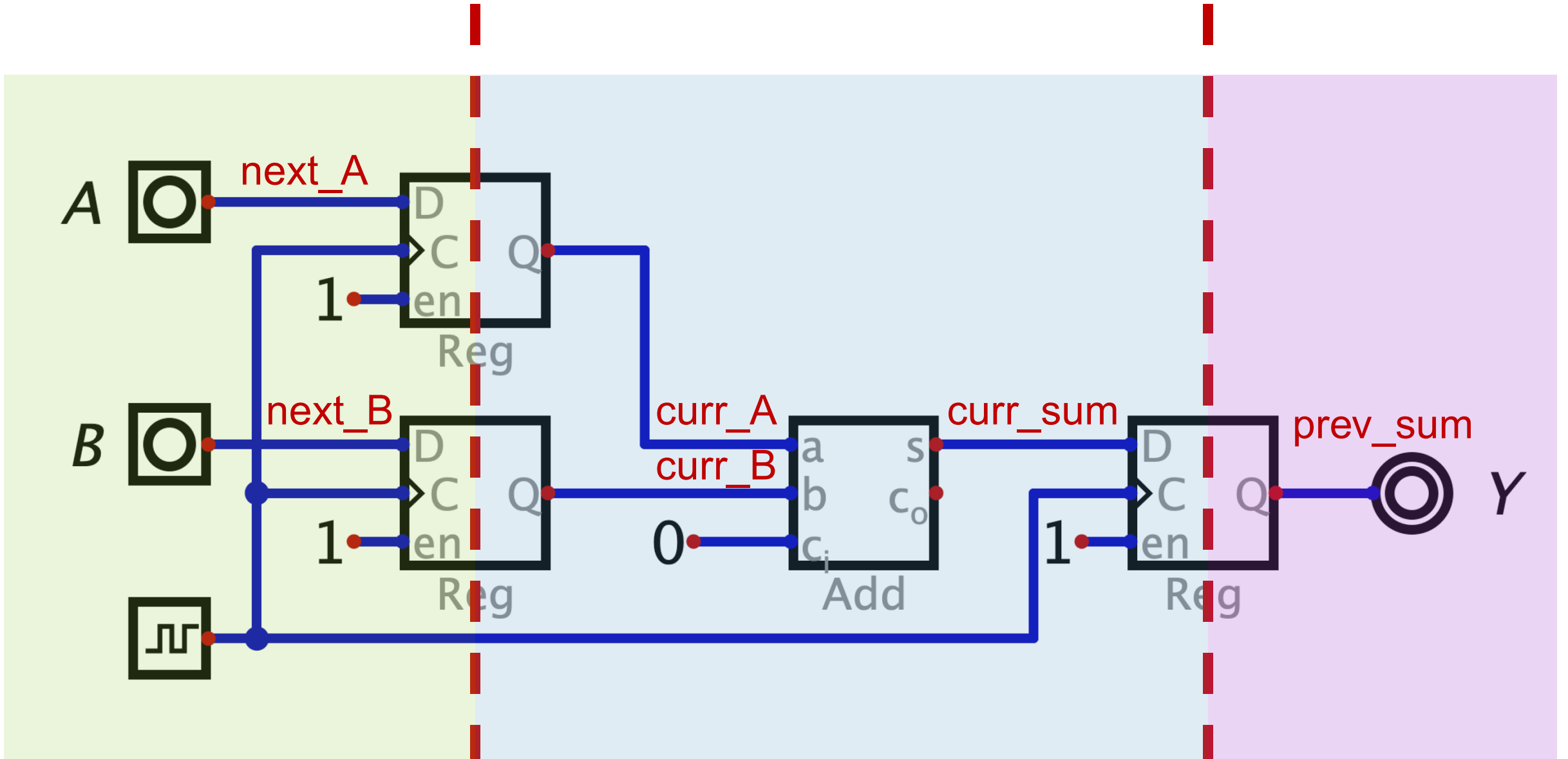

Cycle 0: 7 + 7

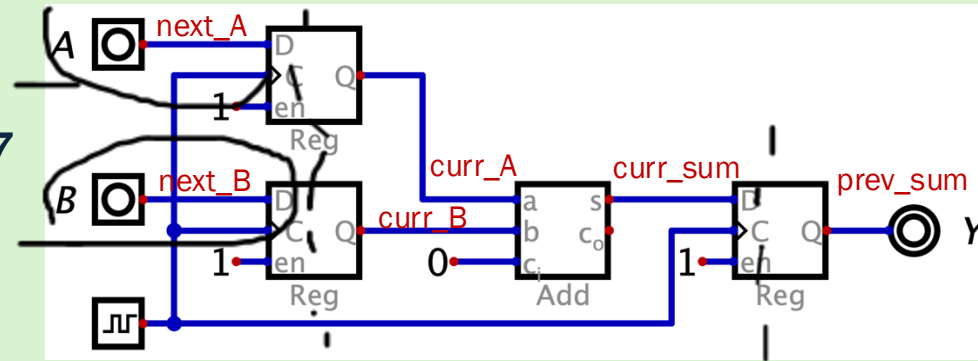

adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 650ps


0 ps

650 ps

1300 ps


1950 ps

2600 ps

 


Signal	Starting State	t = 0 A = 7 B = 7	t = 50ps A = 7 B = 7	t = 650 ps A = 18 B = 7
next_A	0	7	7	18
next_B	0	7	7	7
curr_A	0	0	7	7
curr_B	0	0	7	7
curr_sum	0	0	0	14
prev_sum	0	0	0	0

Cycle 1: 18 + 7

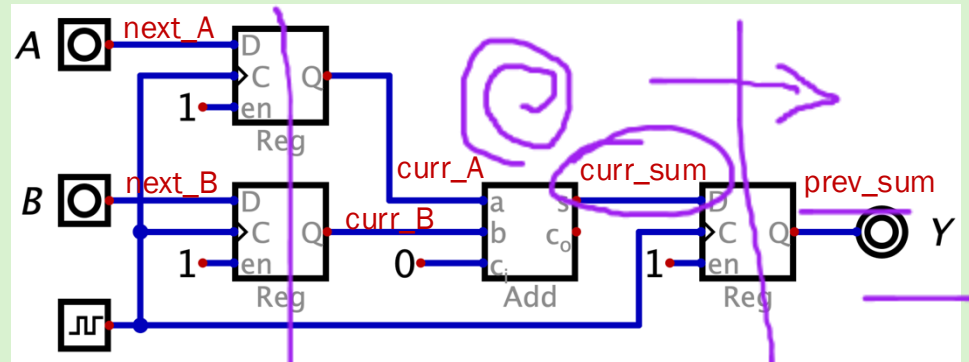


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 650ps




Signal	t = 650 ps A = 18 B = 7	t = 700 ps A = 18 B = 7	t = 1300 ps A = 30 B = 8
next_A	18		
next_B	7		
curr_A	7		
curr_B	7		
curr_sum	14		
prev_sum	0		

Cycle 2: 30 + 8

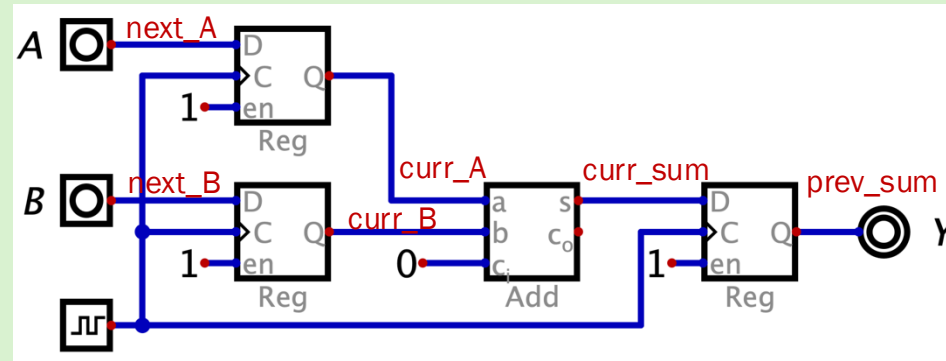


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 650ps




Signal	t = 1300 ps A = 30 B = 8	t = 1350 ps A = 30 B = 8	t = 1950 ps A = 15 B = 30
next_A	30		
next_B	8		
curr_A	18		
curr_B	7		
curr_sum	25		
prev_sum	14		

Cycle 3: 15 + 30

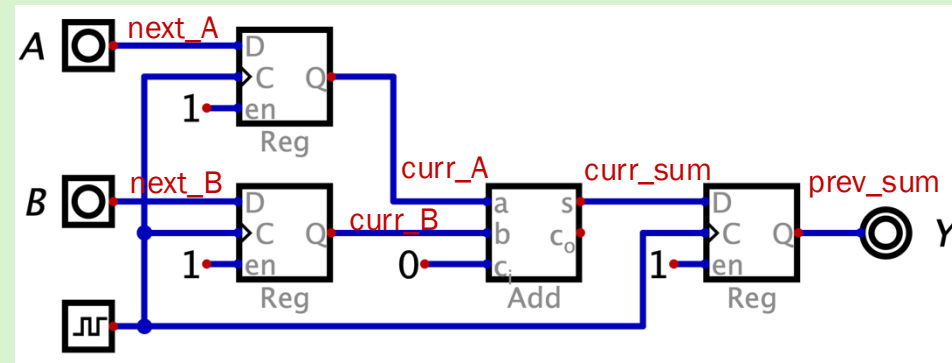


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 650ps




Signal	t = 1950 ps A = 15 B = 30	t = 2000 ps A = 15 B = 30	t = 2600 ps A = 20 B = 30
next_A	15		
next_B	30		
curr_A	30		
curr_B	8		
curr_sum	38		
prev_sum	25		

Cycle 4: 20 + 30

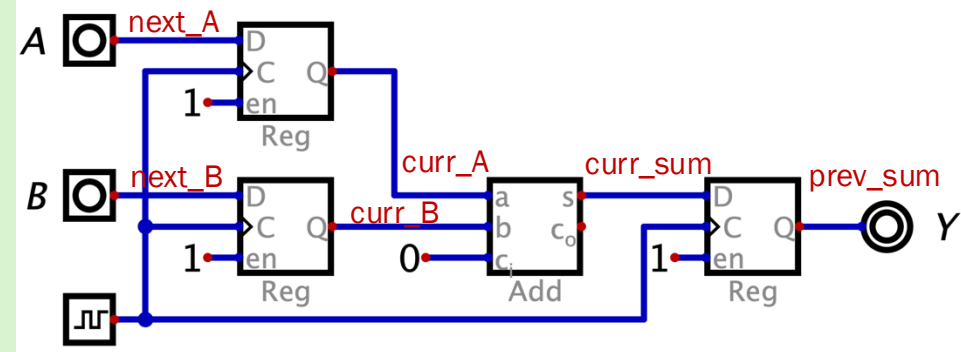


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 650ps




Signal	t = 2600 ps A = 20 B = 30	t = 2650 ps A = 20 B = 30	t = 3250 ps A = 0 B = 0	t = 3300 ps A = 0 B = 0
next_A	20			
next_B	30			
curr_A	15			
curr_B	30			
curr_sum	45			
prev_sum	38			

Cycle 4: 20 + 30

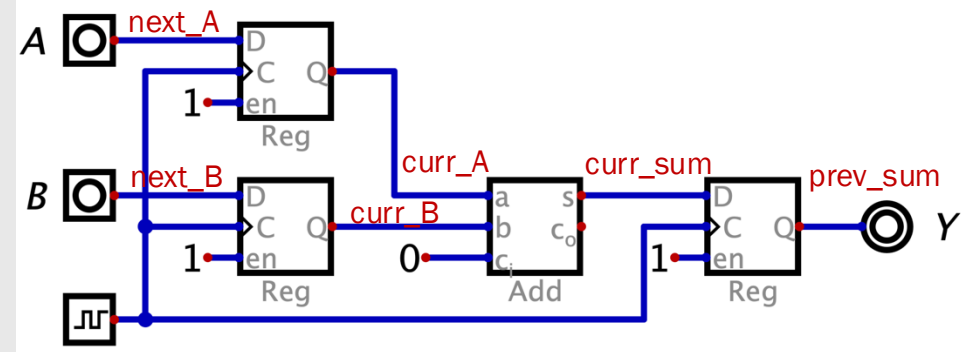


 adder propagation delay = 600 ps
 clk-to-q delay = 50ps
 clock period = 650ps



Signal	t = 2600 ps A = 20 B = 30	t = 2650 ps A = 20 B = 30	t = 3250 ps A = 0 B = 0	t = 3300 ps A = 0 B = 0
next_A	20	20	0	0
next_B	30	30	0	0
curr_A	15	20	20	0
curr_B	30	30	30	0
curr_sum	45	45	50	50
prev_sum	38	45	45	50

Clock Period = 650ps

 


clk-to-q delay = 50ps

adder propagation delay = 600ps


Comparing Clock Periods

- Our circuit functioned correctly at both of the clock periods we tried
 - *650ps and 700ps*
- Our five addition operations finished faster when we set our clock period to 650ps compared to 700ps

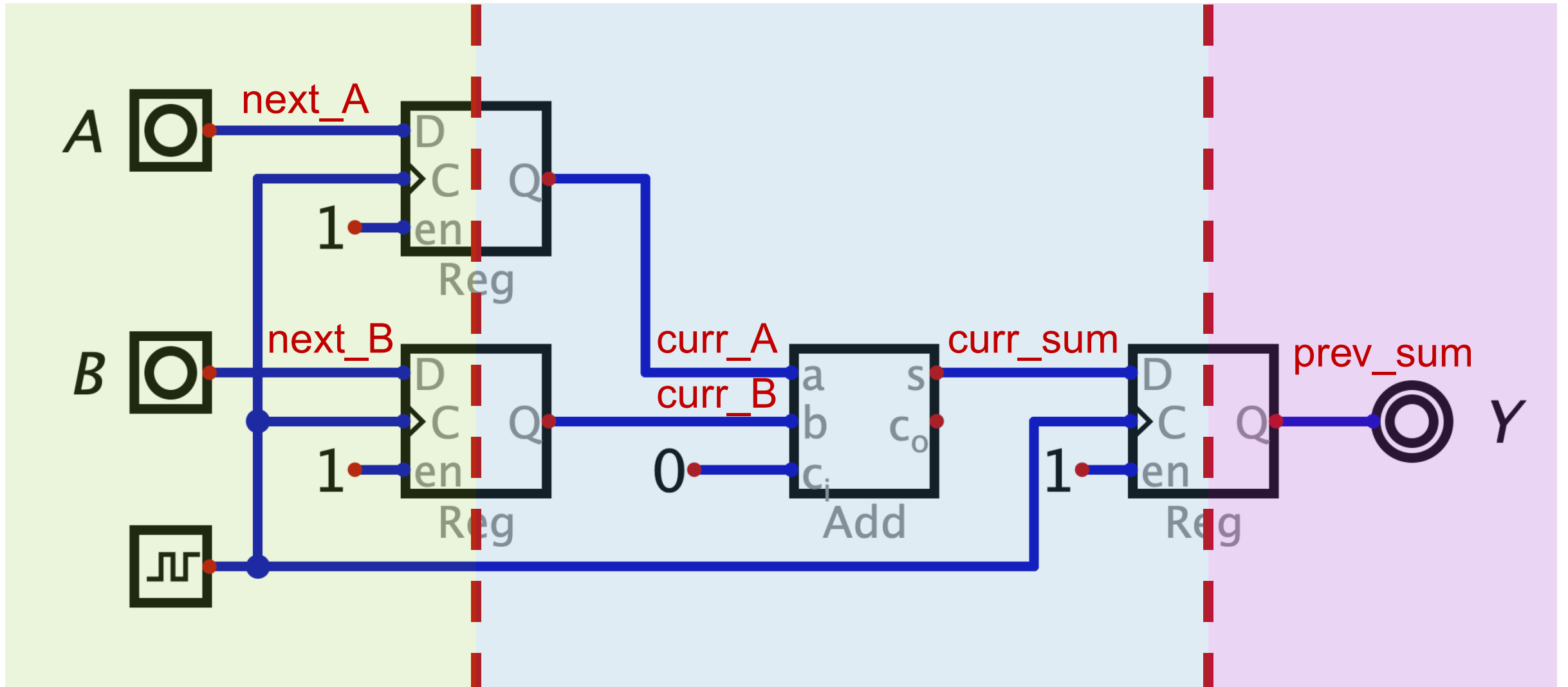
Ex3: Clock period = 500ps, clk-to-q delay = 50ps, adder propagation delay = 600ps



Cycle 0 & 1: 7 + 7

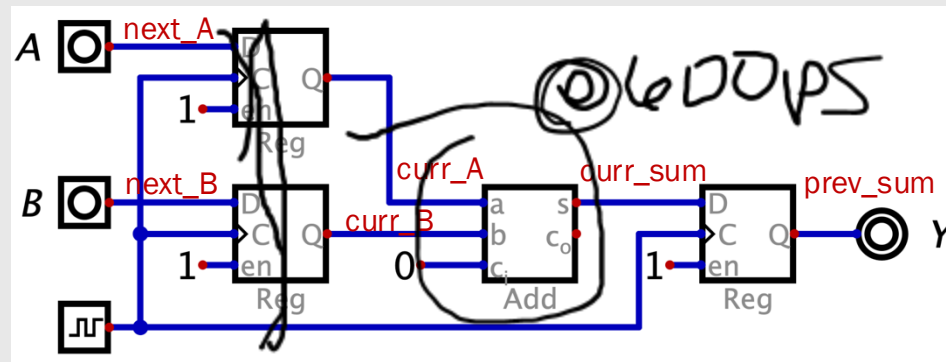


 adder propagation delay = 600 ps
 clk-to-q delay is 50ps
 clock period = 500ps




Signal	Starting State	t = 0 A = 7 B = 7	t = 50ps A = 7 B = 7	t = 500ps A = 18 B = 7	t = 550ps A = 18 B = 7
next_A	0	7	7	18	18
next_B	0	7	7	7	7
curr_A	0	0	7	7	18
curr_B	0	0	7	7	7
curr_sum	0	0	0	7 7	7 7
prev_sum	0	0	0	0	7 7

Cycle 0 & 1: 7 + 7

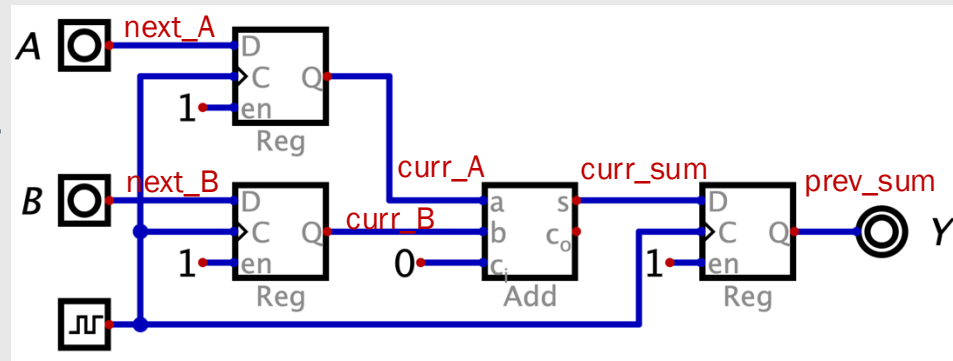


 adder propagation delay = 600 ps
 clk-to-q delay is 50ps
 clock period = 500ps



Signal	Starting State	t = 0 A = 7 B = 7	t = 50ps A = 7 B = 7	t = 500ps A = 18 B = 7	t = 550ps A = 18 B = 7
next_A	0	7	7	18	18
next_B	0	7	7	7	7
curr_A	0	0	7	7	18
curr_B	0	0	7	7	7
curr_sum	0	0	0	??	??
prev_sum	0	0	0	0	??

Clock Period = 500ps

 


clk-to-q delay = 50ps

adder propagation delay = 600ps


Clock Period = 500ps

- Our circuit does not operate correctly with a period of 500ps
- Why?
 - *The adder cannot finish its operation before the next rising edge of the clock*
 - *The output register ends up reading garbage*

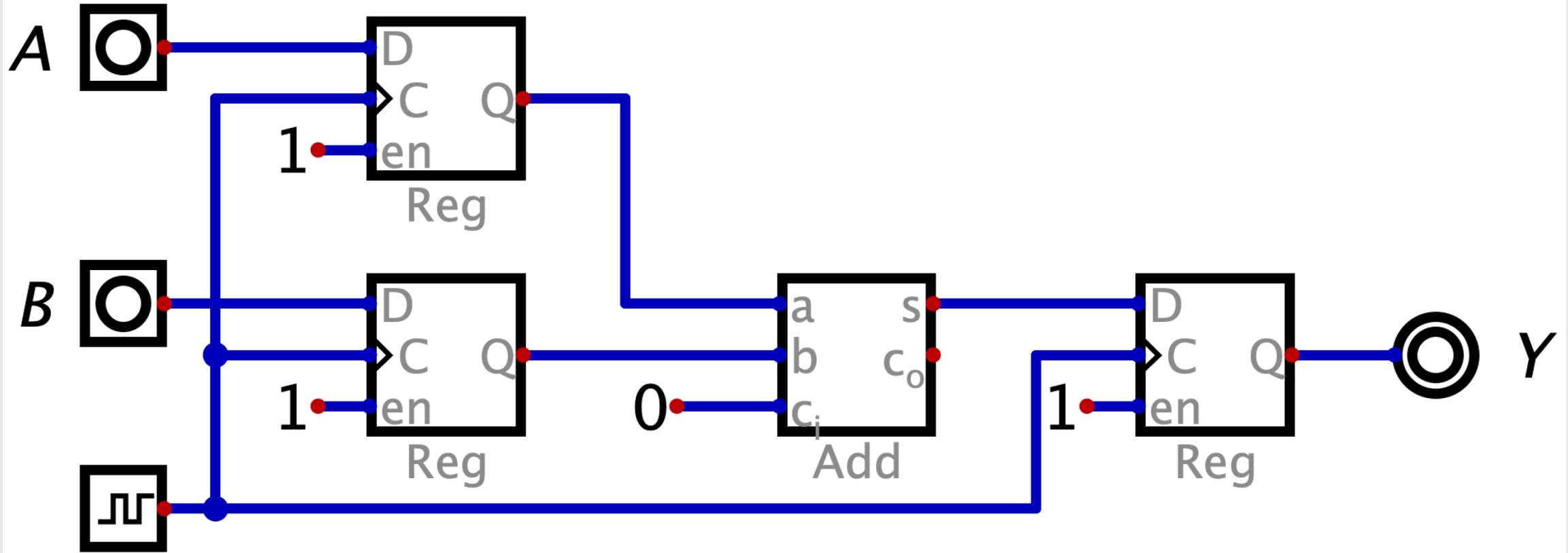Take Away: How to determine the minimum clock period?



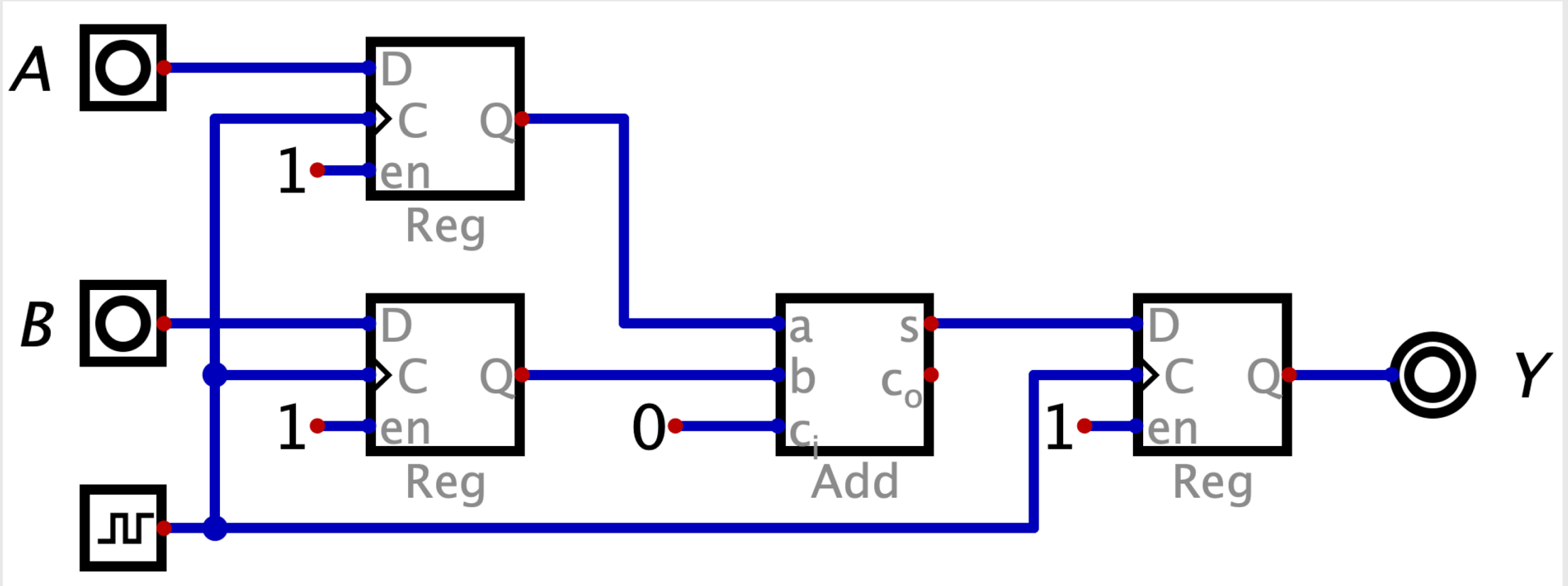
Take Away: How to determine the minimum clock period?



min clock period = clk-to-q delay of the input registers + adder propagation delay


Min Clock Period

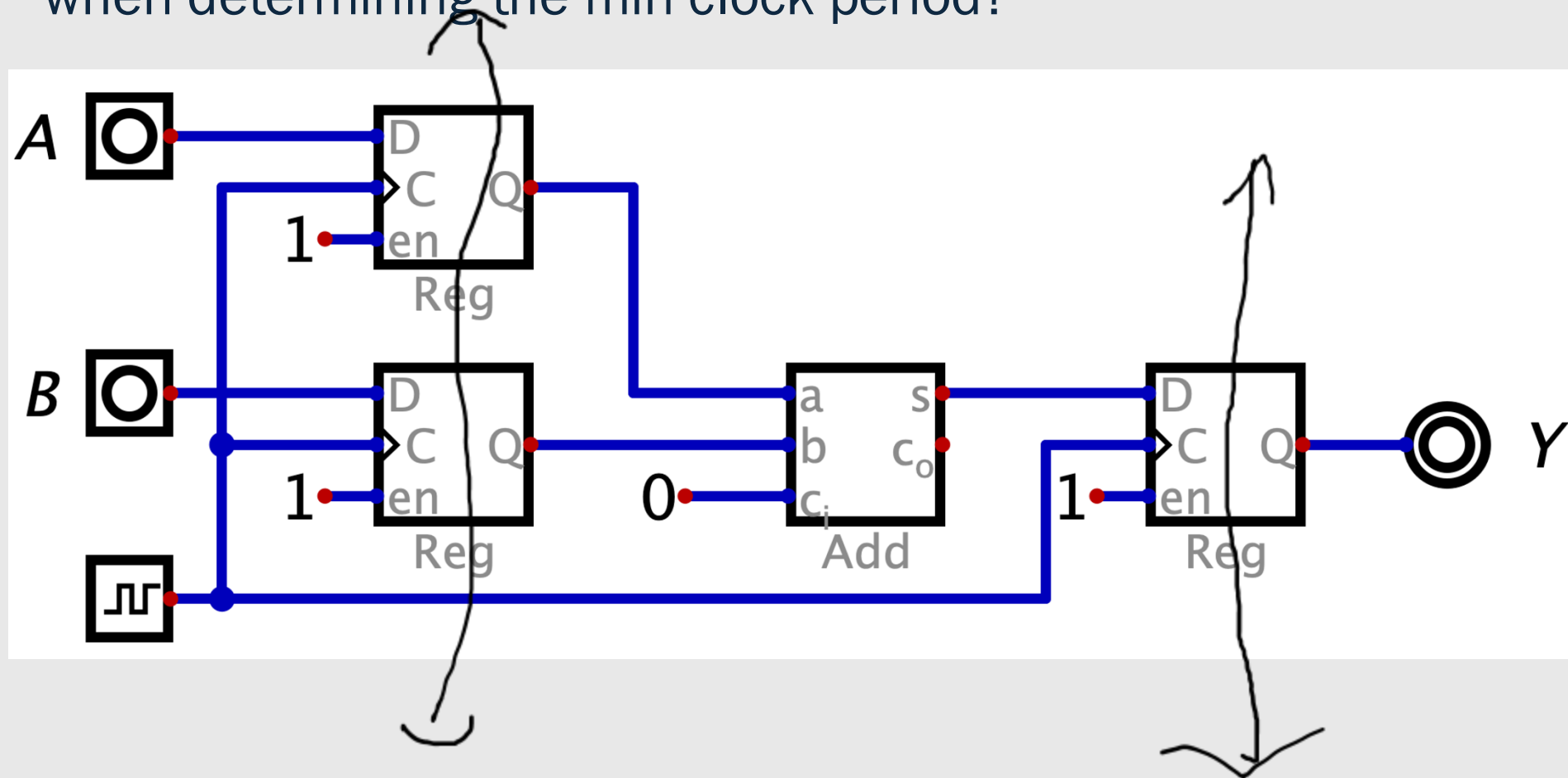- Why do we not include the clk-to-q delay of the output register when determining the min clock period?



Min Clock Period

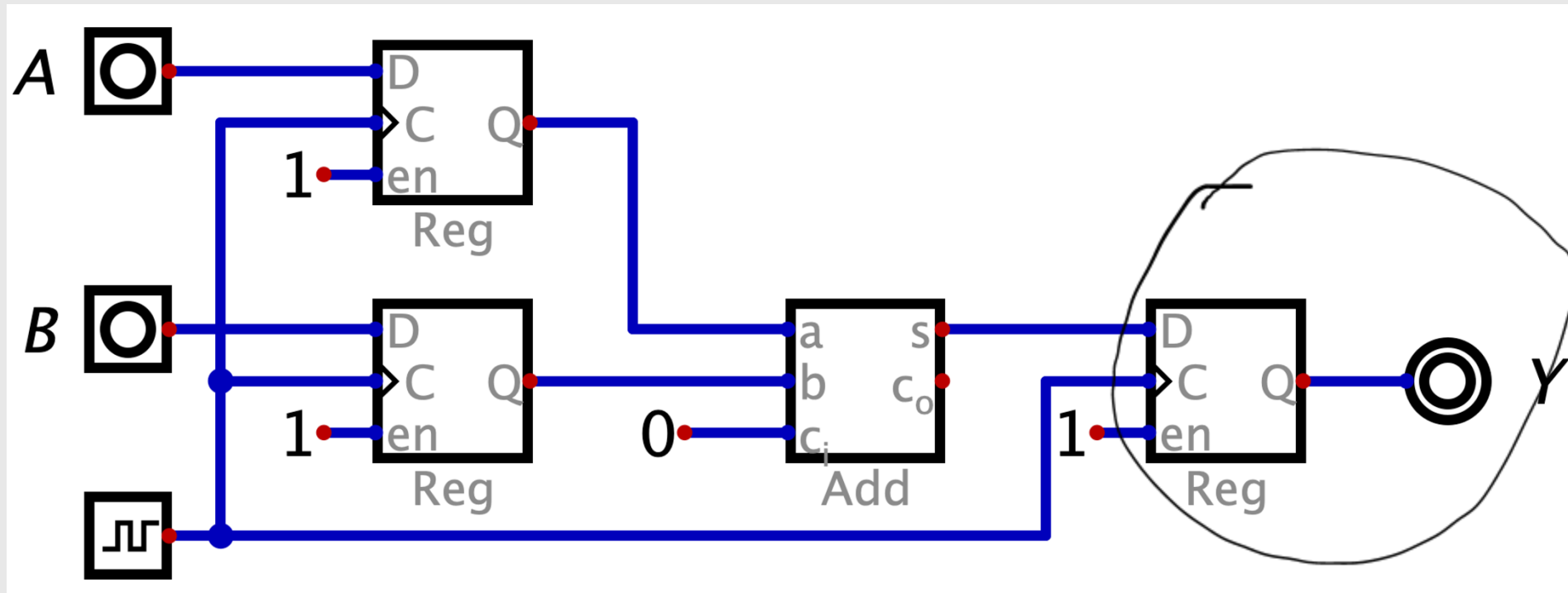
- Why do we not include the clk-to-q delay of the output register when determining the min clock period?



In one clock cycle, we need to read the input registers, compute their sum, and ensure the value is ready for the output register before the next rising edge of the clock. The value will not pass through the output register until the next rising edge of the clock.

COMPUTER PERFORMANCE

He said, we need to squeeze the clock

 

$2 + 2$
 $3 << 512$

Why study performance?

- Helps us to make intelligent choices
- Helps us see through marketing hype
- Affects computer organization (pipelining, caches, etc.)
- Why is some hardware faster than others?
- What factors of system performance are hardware related?
 - *Do we need a new machine,*
 - *more memory*
 - *a better compiler*
 - *or a new OS?*
- How does a machine's instruction set affect its performance?

Performance Metrics

- **Latency:** time from an input to its corresponding output
 - *How long does it take for my program to run?*
 - *How long must I wait after typing `return` for the result?*
- **Throughput:** The rate at which new outputs are generated
 - *How many calculations per second?*
 - *What is the average execution rate of my program?*
 - *How much work is getting done?*

By running a program on 20 different input files on the fastest available processor, what performance metric do we improve?

latency

By running our program simultaneously on 20 CPU's, each assigned an input file, what performance metric do we improve?

throughput

What airplane has the best performance?

Aircraft	Passengers	Range (miles)	Speed (mph)
Boeing 737-100	132	630	598
Boeing 747	470	4150	610
BAC/Sud Concorde	101	4000	1350
Douglas DC-8-50	146	8720	544



How much faster is the Concorde than the 747?

2.213 X

How much larger is the 747's capacity than the Concorde?

4.65 X

It is roughly 4000 miles from Raleigh to Paris. What is the throughput of the 747 in passengers/hr? The Concorde?

$470(610)/4000 = 71.65$ pass/hr


What is the latency of the 747?

$4000/610 = 6.56$ hr/pass


The Concorde?

$4000/1350 = 2.96$ hr/pass


Performance Tradeoffs

 

 Maximum Performance: measured by the “number of instructions executed per second”



 Minimum Cost: determined by the size-of-the-circuit/number-of-components-used plus power/cooling costs



Best Price/Performance: measured by the ratio of CPU-cost to number of instructions executed per sec.

Performance/Watt instructions per second per watt

→ Execution Time

Elapsed Time/Wall Clock Time

counts everything (disk and memory accesses, I/O , etc.)

a useful number, but often not good for comparison purposes

→ CPU time

Doesn't include I/O or time spent running other

*Programs can be broken up into **system** time,*

*and **user** time*



Our focus: user CPU time

Time spent executing actual instructions of “our” program

Definition of Performance

For some program running on machine X,

$$\text{Performance}_X = \text{Program Executions} / \text{Time}_X \text{ (executions/sec)}$$

"X is N times faster than Y"

$$\text{Performance}_X / \text{Performance}_Y = N$$



Problem:

Machine A runs a program in 20 seconds

Machine B runs the same program in 25 seconds

$$\text{Performance}_A = 1/20$$

$$\text{Performance}_B = 1/25$$

Machine A is $(1/20)/(1/25) = 1.25$ times faster than Machine B

Program Clock Cycles

Instead of reporting execution time in seconds, we can also use cycle counts

$$(\text{sec/program}) * (\text{clocks/sec}) = \text{clocks/program}$$

Clocks are when machine-state changes (synchronous abstraction):



cycle time = time between rising edges of the clock = seconds per clock

clock rate (frequency) = clocks per second (1 Hz. = 1 clock/sec)

A 200 Mhz. clock has a $1/(200 * 10^6) = 5.0 * 10^{-9} = 5 \text{ nS}$ cycle time

Overclocking: improves performance (seconds/program) by decreasing the cycle time (seconds/cycle), while hoping that the functional blocks continue to operate as specified.

Standard Computer Performance Measures

Millions of Instructions per Second

Frequency in Hz

$$\text{MIPS} = \frac{1}{10^6} \frac{\text{clocks / second}}{\text{clocks / instruction}}$$


CPI (Average Clocks Per Instruction)

How to improve performance?

$$(\text{sec/program}) (\text{clocks/sec}) = \text{clocks/program}$$

$$\text{MIPS} = \frac{1}{10^6} \frac{\text{clocks / second}}{\text{clocks / instruction}}$$

 So, to improve performance (everything else being equal) you can either



the # of required clocks for a program, or

the clock cycle time or, ~~or~~ said another way,

the clock rate.

the CPI (average clocks per instruction)

"clocks" == clock cycles

How to improve performance?

$$(\text{sec/program}) (\text{clocks/sec}) = \text{clocks/program}$$

$$\text{MIPS} = \frac{1}{10^6} \frac{\text{clocks / second}}{\text{clocks / instruction}}$$

So, to improve performance (everything else being equal) you can either

Decrease

(improve ISA)

the # of required clocks for a program, or

Decrease

the clock cycle time or, said another way,

Increase

the clock rate.

Decrease

the CPI (average clocks per instruction)



PIPELINING



Recall: Min Clock Pd + Max Frequency

Min Clock Period


clk-to-q delay + longest combinational delay

Max Clock Frequency

$1 / \text{min period}$


The longest combinational path is the **critical path** or sequence of gates between two registers that has the **maximum propagation delay**

Single-Cycle: Longest Combinational Path

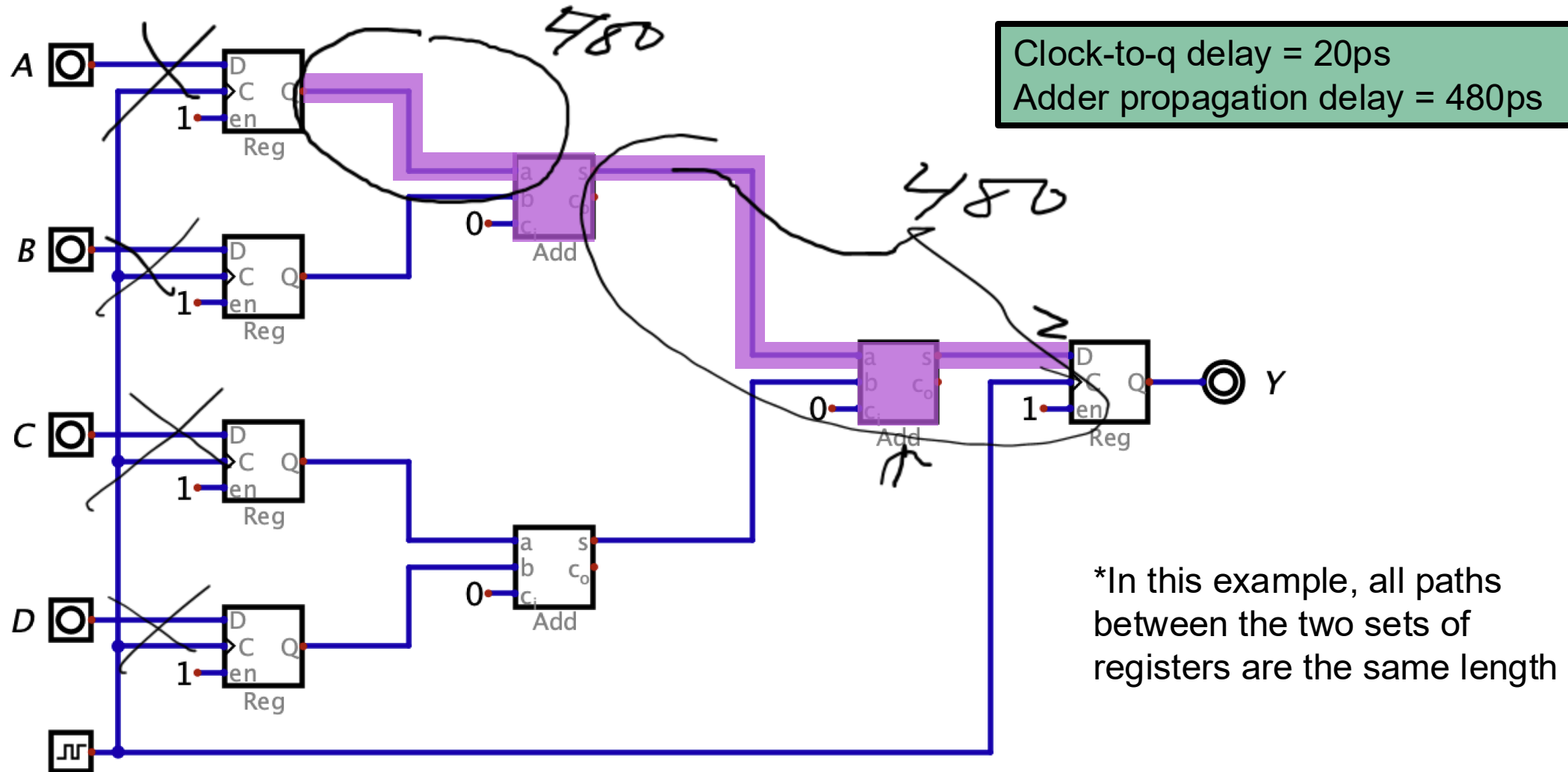


Longest comb path = 480ps + 480ps = 960ps

Single-Cycle: Longest Combinational Path

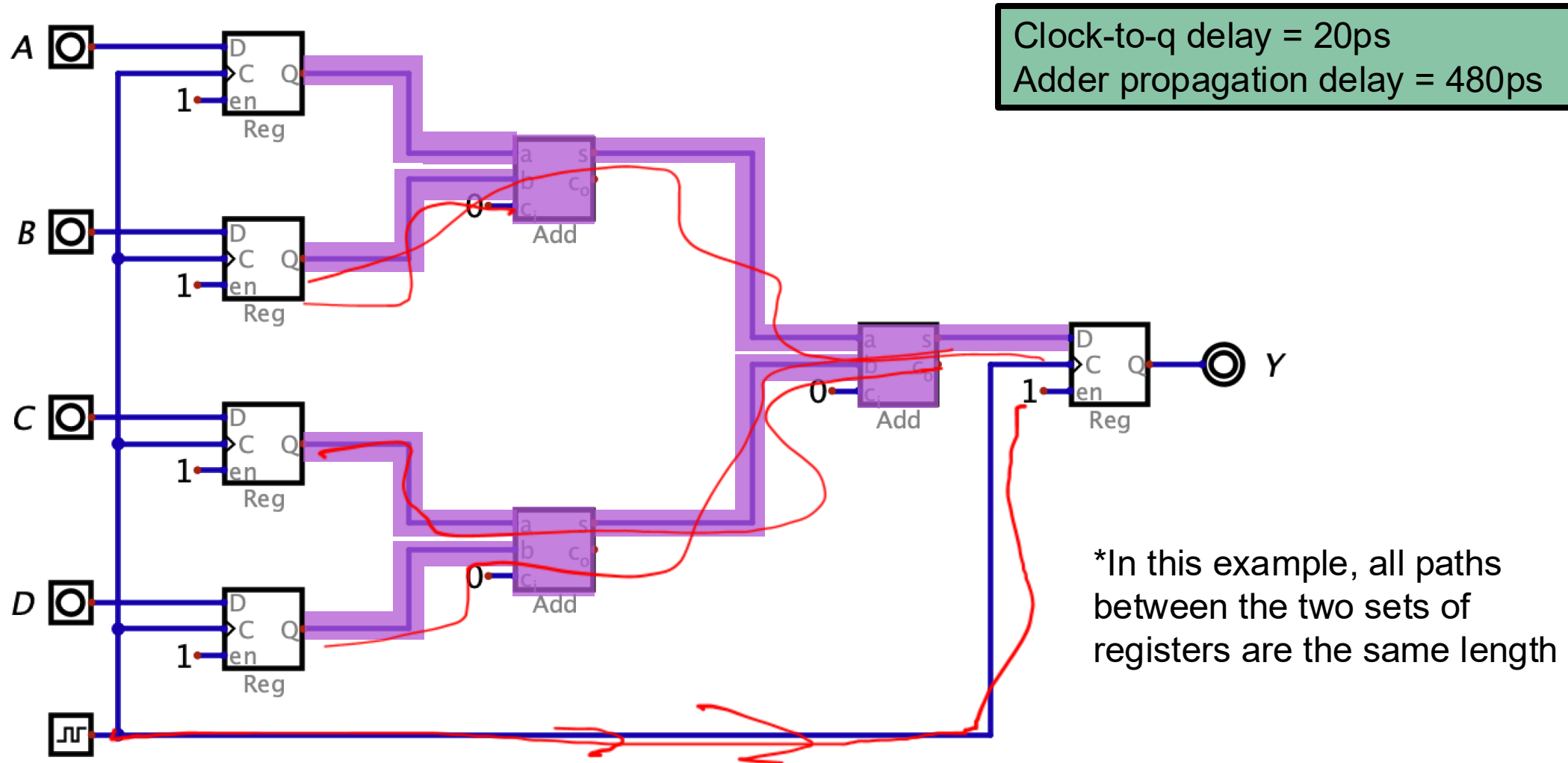

Longest comb path = 480ps + 480ps = 960ps

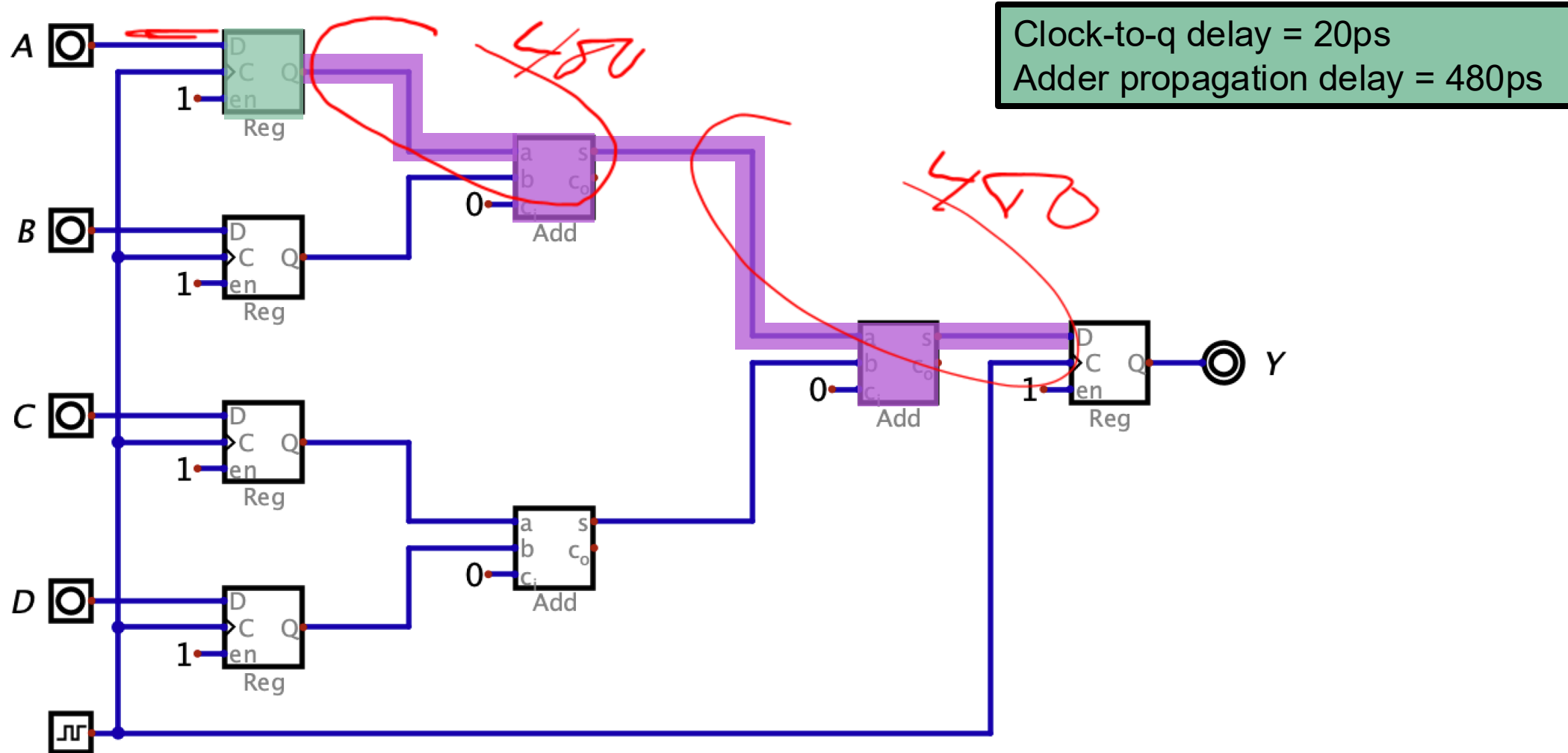Single-Cycle: Min Clock Period = Critical Path



Min clock period = clk-to-q delay + longest comb path = 20ps + 960ps = 980ps

Clock Period

- At which of the following clock periods will the previous circuit work properly?

- 1000ps

- 960ps

- 2000ps

- 4000ps

Clock Period

- At which of the following clock periods will the previous circuit work properly?
 - *1000ps*
 - *960ps*
 - *2000ps*
 - *4000ps*

Any clock period greater than or equal to the min clock period

Pipelining

- The previous circuit is referred to as a **single-cycle** implementation because it completes one operation within a single clock cycle.
- We'll improve the performance of our implementation by using a technique called pipelining
- We'll break down our circuit into **two stages** that can operate simultaneously
- This will make more efficient use of our hardware

Pipelining

