

10/7/26



COMP 311: *Computer Organization!*

Lecture 13: Some Basic Gate Minimization Algos/Processes



The University
of North Carolina
at Chapel Hill

<https://tinyurl.com/comp311-fa26>

Logistics Update



- Lab 2 Released
 - Due 10/22



**Sit in your seats from
last quiz!**



A definition: Logical Equivalence

- What does logically equivalent mean?
 - For any input, they will produce the same output
 - In other words, their truth tables are equivalent!

Plan for Class Today



- 4:20-4:50: Gate Optimization via Transformation

Guiding Question ☺

How do optimize our circuits with universal gates (NANDS, NORs)?



Gate Minimization (cont.)

Optimizing our circuits...



- Fewer transistors means....
 - Smaller area!
 - Lower power consumption!
 - Shorter time from input to output!
 - Lower cost!
- How will we do this?
 - Visual inspection
 - Boolean algebra simplification
 - In practice, → advanced synthesis algorithms to create **logically equivalent**, more efficient circuits! 😊




Strategies for Minimizing Circuits




- Deriving a **logically equivalent circuit** that uses **fewer transistors**
- What does logically equivalent mean?
 - For any input, they will produce the same output
 - In other words, their truth tables are equivalent!

Inverters

 


Any even number of inverters chained together is logically equivalent to having no inverters

Inverters

 


Any odd number of inverters chained together is logically equivalent to having one inverter

 A Bubble is Logically Equivalent to Inverter




4 transistors

 

8 transistors

NAND == Inverted OR

 


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


→

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NAND == Inverted OR

 


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0



NOR == Inverted AND

 

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

NOR == Inverted AND

  


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0



Ex1: Minimizing Transistor Count



 Minimize the number of transistors in this circuit by redesigning it to use only NAND gates and inverters.




NAND gates:

  


Ex1: Minimizing Transistor Count



 Step 1: Start with the right-most gate. Turn it into a NAND gate. Then add bubbles to make the circuit logically equivalent.




NAND gates:

 



Ex1: Minimizing Transistor Count



 Step 2: Now make the top left gate a NAND gate. Then add a bubble to make the circuit logically equivalent.




NAND gates:

 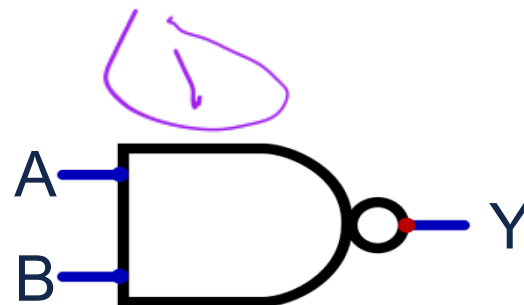

Ex1: Minimizing Transistor Count




Step 3: Cancel out the free bubbles. (Pairs of inverters/bubbles cancel!)

 

Ex1: Minimizing Transistor Count



 Step 4: Draw the gates in their conventional form.




Original Transistor Count: 14

Final Transistor Count: 8



Minimizing Transistor Count



 Minimize the number of transistors in this circuit by redesigning it to use only **NAND** gates and inverters. Compare the number of transistors in the original circuit and the new circuit.




NAND gates:

  


Minimizing Transistor Count



 Step 1: Transform the OR gate into a NAND gate. Add bubbles to make the circuit logically equivalent.




NAND gates:

 

Minimizing Transistor Count



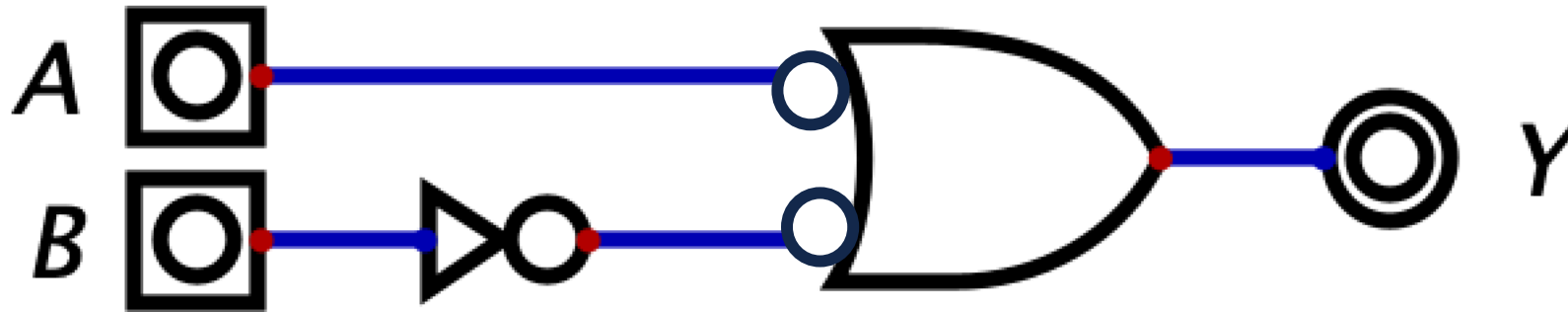
Step 2: Cancel out extra bubbles and inverters.



Minimizing Transistor Count



 Step 3: Draw the gates in their conventional form.




Original Transistor Count: 12

Final Transistor Count: 6



Ex2: Minimizing Transistor Count



 Minimize the number of transistors in this circuit by redesigning it to use only **NOR** gates and inverters.




NOR gates:

  



Ex2: Minimizing Transistor Count



 Step 1: Start with the right-most gate that is not an inverter. Turn it into a NOR gate. Then add bubbles to make the circuit logically equivalent.




NOR gates:

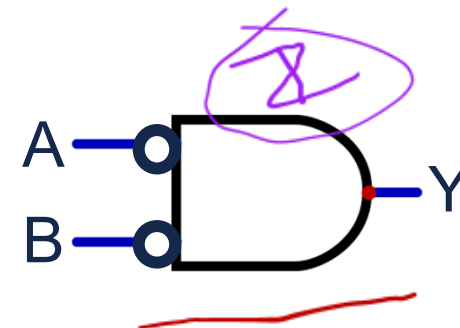 


Ex2: Minimizing Transistor Count



 Step 2: Move to the next gate on the left. Transform this into a NOR gate. Add a bubble to make the circuit logically equivalent.




NOR gates:

 

Ex2: Minimizing Transistor Count




Step 3: Cancel out the extra bubbles and inverters.

 

Ex2: Minimizing Transistor Count



 Step 4: Draw the gates in their conventional form.




Original Transistor Count: 18

Final Transistor Count: 8


Minimizing Transistor Count



 Minimize the number of transistors in this circuit by redesigning it to use only NOR gates and inverters. Compare the number of transistors in the original circuit and the new circuit.




NOR gates:

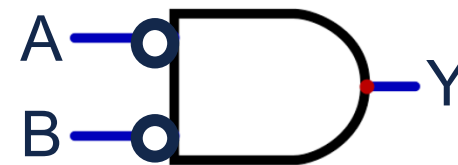


Minimizing Transistor Count



 Step 1: Start with the right-most gate. Turn it into a NOR gate. Then add bubbles to make the circuit logically equivalent.




NOR gates:

 


Minimizing Transistor Count



 Step 2: Move to the next gate on the left. Transform this into a NOR gate. Add a bubble to make the circuit logically equivalent.




NOR gates:

 

Minimizing Transistor Count



 
Step 3: Cancel out the extra bubbles and inverters.



Minimizing Transistor Count



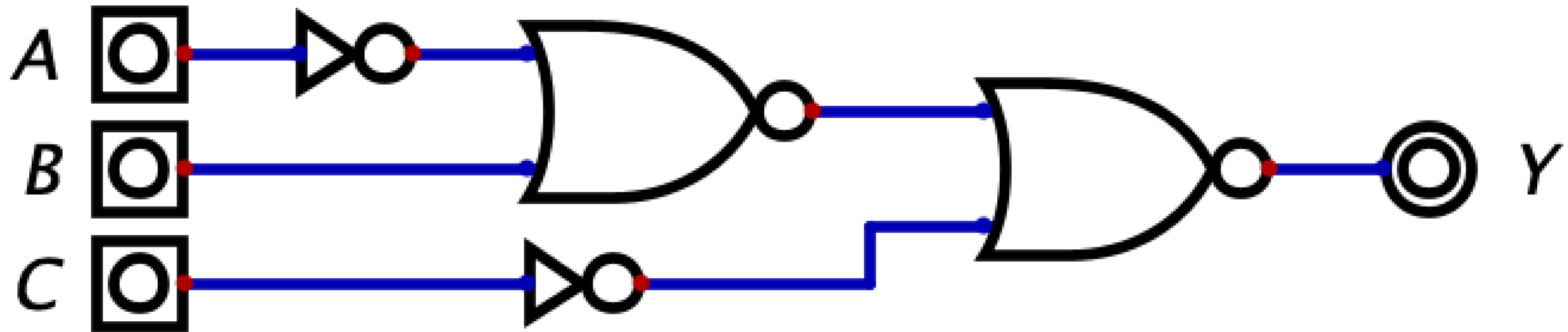Step 4: Draw the gates in their conventional form.




Original Transistor Count: 18

Final Transistor Count: 12



Minimizing Transistor Count



 Minimize the number of transistors in this circuit by redesigning it to use only **NAND** gates and **inverters**. Compare the number of transistors in the original circuit and the new circuit.




NAND gates:

 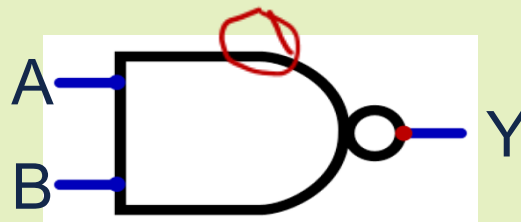


Minimizing Transistor Count



 Minimize the number of transistors in this circuit by redesigning it to use only NAND gates and inverters. Compare the number of transistors in the original circuit and the new circuit.




NAND gates:

 

Minimizing Transistor Count



 
Minimize the number of transistors in this circuit by redesigning it to use only NAND gates and inverters. Compare the number of transistors in the original circuit and the new circuit.




Minimizing Transistor Count



 Minimize the number of transistors in this circuit by redesigning it to use only NAND gates and inverters. Compare the number of transistors in the original circuit and the new circuit.




NAND gates:

 

Minimizing Transistor Count



 Minimize the number of transistors in this circuit by redesigning it to use only NAND gates and inverters. Compare the number of transistors in the original circuit and the new circuit.




Original Transistor Count: 32

Final Transistor Count: 24

Minimizing Transistor Count



 
Minimize the number of transistors in this circuit by redesigning it to use only NAND gates and inverters. Compare the number of transistors in the original circuit and the new circuit.



Minimizing Transistor Count



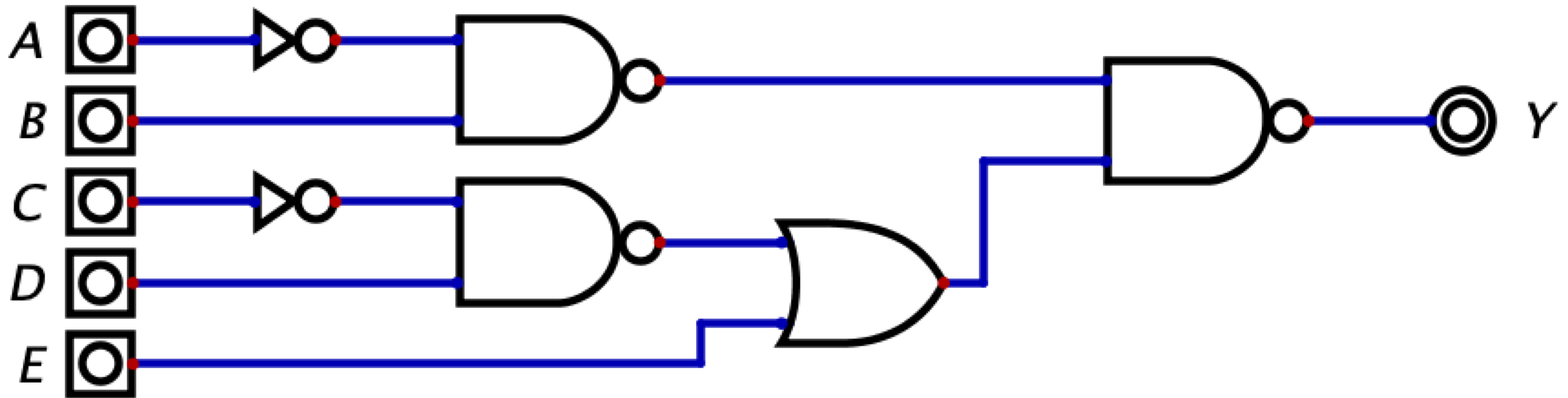Minimize the number of transistors in this circuit by redesigning it to use only NAND gates and inverters. Compare the number of transistors in the original circuit and the new circuit.



Original Transistor Count: 32

Final Transistor Count: 22