

**Question 1: Boolean Algebra** Simplify the following Boolean expression, and express the result in terms of SOP form.

1.1.  $\overline{AB} \oplus C + A + CB$

1.2.  $\overline{A + B} + \overline{AB}(C + \overline{C}(D + \overline{D + E}))$

**Question 2: Reducing Transistors** Explain in a couple sentence why we need to care about transistor counts when designing circuits? What strategies can we use to reduce transistor counts?

**Question 3: Problem 1: Two-Bit Comparator** (*Very similar to the comparator example from class slides.*)

Let  $A = A_1A_0$  and  $B = B_1B_0$  be two-bit unsigned numbers.

Define an output  $Y$  such that:

$$Y = 1 \iff A > B + 1$$

3.1. Construct the truth table for  $Y$ .

--

3.2. Write the Sum-of-Products (SOP) expression for  $Y$ .

--

3.3. Derive the simplest Boolean expression for  $Y$ .

--

**Question 4: Problem 2: Transistor Count Optimization (NOR-only)** Assume CMOS gates with the following transistor counts:

Gate	Transistors
NOT	2
NAND (2-input)	4
NOR (2-input)	4
AND (2-input)	6
OR (2-input)	6

Given the Boolean function:

$$F = (A + B)(\bar{C} + D)$$

4.1. Implement  $F$  using AND, OR, and NOT gates. Count the total number of transistors.

4.2. Rewrite  $F$  using **only NOR gates and inverters**.

4.3. Compute the new transistor count and determine which implementation is cheaper.

**Question 5: Problem 3: Boolean Reduction** Simplify the following Boolean expression as much as possible:

$$F = A\bar{B} + AB + A\bar{B}C$$

Show each step and clearly state the Boolean laws used.

**Question 6: Problem 4: Universal Gates** 6.1. Which two logic gates are universal?

6.2. Explain why a gate being universal is useful.

6.3. Give one advantage and one disadvantage of using only universal gates in a circuit.


Question 7: Problem 1 Simplify:

$$\overline{(A + \overline{AB} + \overline{AB})} + \overline{(A + \overline{B})}$$




Question 8: Problem 2 Simplify:


$$\overline{AB} + \overline{ABC} + \overline{(A + \overline{C})}$$

 


**Question 9: 8:1 Mux Design** Design an 8:1 mux using only 2:1 muxes

 

**Question 10: XOR Gate Design** Implement a two input XOR gate using a 4:1 mux

 

**Question 11: 4:1 Mux Design** Design a 4:1 mux using logic gates

 

**Question 12: Transistor Minimization** Minimize the transistor count for your 4:1 mux

