

COMP311: *COMPUTER ORGANIZATION!*

Lecture 5: Logic Gates

tinyurl.com/comp311-sp26

Logistics Updates

- WA1 due tonight!
 - *WA2 to follow shortly*
- Quiz schedule will be updated. I will announce via Canvas




BUILDING LOGIC GATES WITH TRANSISTORS





Abstraction ☺

CMOS Gates

Physical Transistors

 

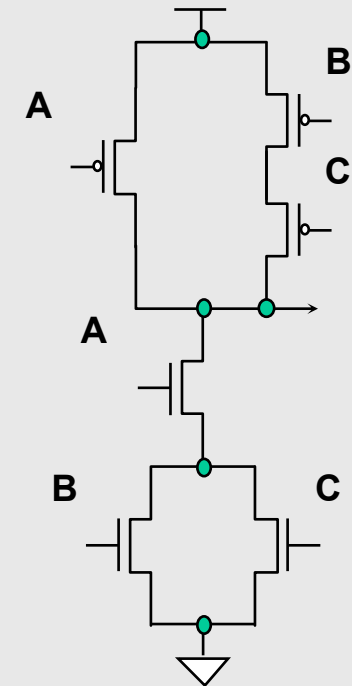 CMOS gates abstract away individual transistors, letting us design reliable logic at a higher level.



CMOS gates are the abstraction that lets many transistors behave like a single logical unit.

CMOS Gates


- CMOS = Complementary MOS
 - *The pMOS and nMOS transistors complement each other to form the logic gate*
- Common confusion
 - *CMOS is not a type of transistor!*
 - *It is a technology that combines both nMOS and pMOS transistors*

MOS: Metal Oxide
Semiconductor 😊

You might also see **MOSFET:**
Metal Oxide Semiconductor
Field-Effect Transistor


Pull-up and Pull-down Networks

 - Only one network will be on at a time
- The pull-up network drives the output when the output is 1
- The pull-down network drives the output when the output is 0



CMOS Inverter

In	Out
0	1
1	0

 




General CMOS Gate Recipe

Step 1. Figure out pulldown network that does what you want (i.e the set of conditions where the output is '0')

$$\text{e.g., } F = A*(B+C)$$

Step 2. Build the "opposite" version of that network to figure out when the output should be 1.

  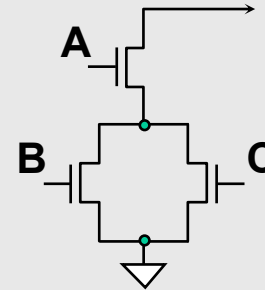Step 3. Combine the two so you have a circuit that always pulls the output either up to 1 or down to 0.



Recall:
Series = AND
Parallel = OR


This comes from DeMorgan's Laws! In practice, we swap series + parallel connections, use pMOS instead of nMOS

But isn't it hard to wire it all up? \



Yes it is!
This does not scale...

What function does this gate compute?

 

NOR

A	B	C
0	0	
0	1	
1	0	
1	1	

Designing hardware at the transistor level...

- Does not scale!
- What should we do?
 - *Abstract again!*
 - Logic gates are next!
- But before we jump to the next level of abstraction, let's cover some ***standard, easy-to-wire*** primitives
 - *NAND and NOR*
 - These functions are universal, meaning any Boolean function or digital logic can be built from them



CMOS NOR




CMOS NOR



A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


CMOS NOR

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

 

CMOS NOR

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

 


pull-up network

pull-down network

CMOS NOR

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


both pMOS on,
output pulled up

 

CMOS NOR

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


B's nMOS on,
pulls down

 

CMOS NOR

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0


A's nMOS on,
pulls down

 

CMOS NOR

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

both nMOS on,
strong pull down

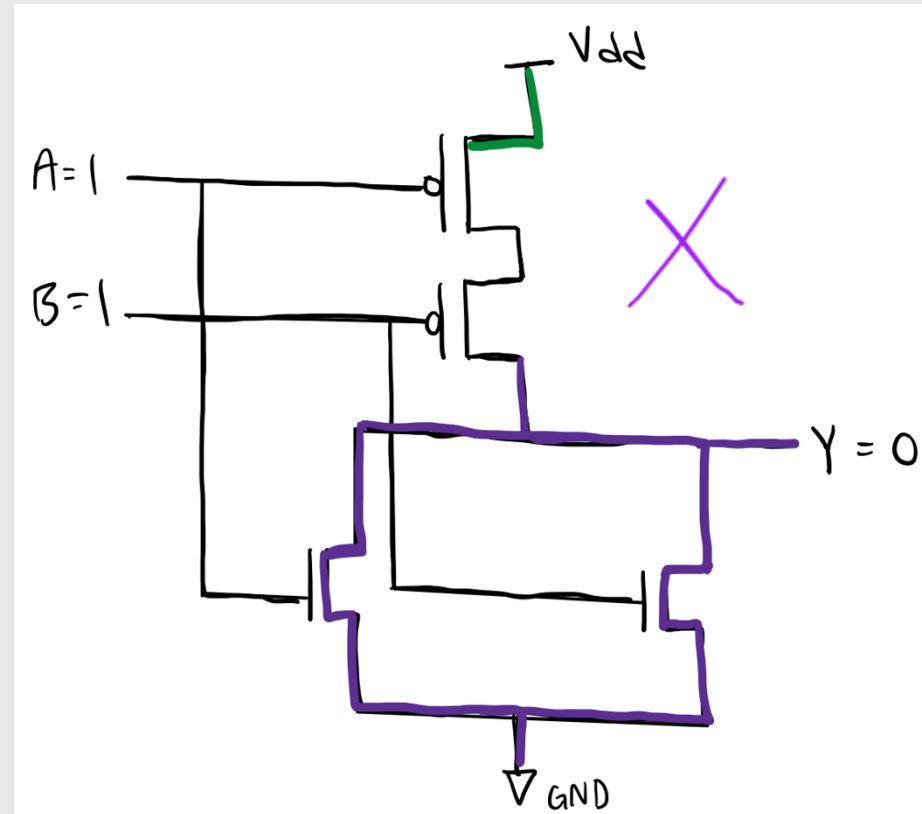



CMOS NAND




CMOS NAND

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

CMOS NAND


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 

CMOS NAND

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


both pMOS on,
pull-up works

 

CMOS NAND

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


A's pMOS still
on, output
pulled high

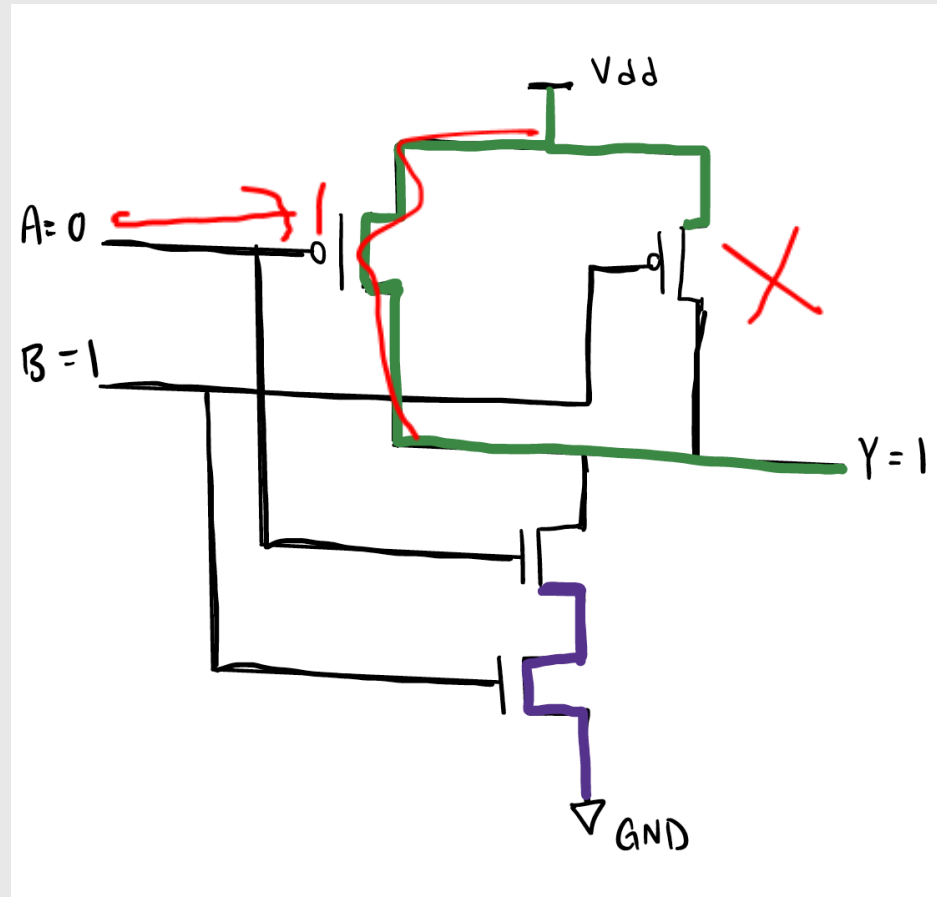

CMOS NAND

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


B's pMOS still
on, output
pulled high

 

CMOS NAND


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 both pMOS off,
both nMOS on
→ path to
ground



CMOS NAND

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

 

pull-up network

pull-down network



CMOS AND


CMOS AND

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

CMOS AND

AND $\equiv$ *NAND*

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 


NAND

INVERTER


CMOS AND

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

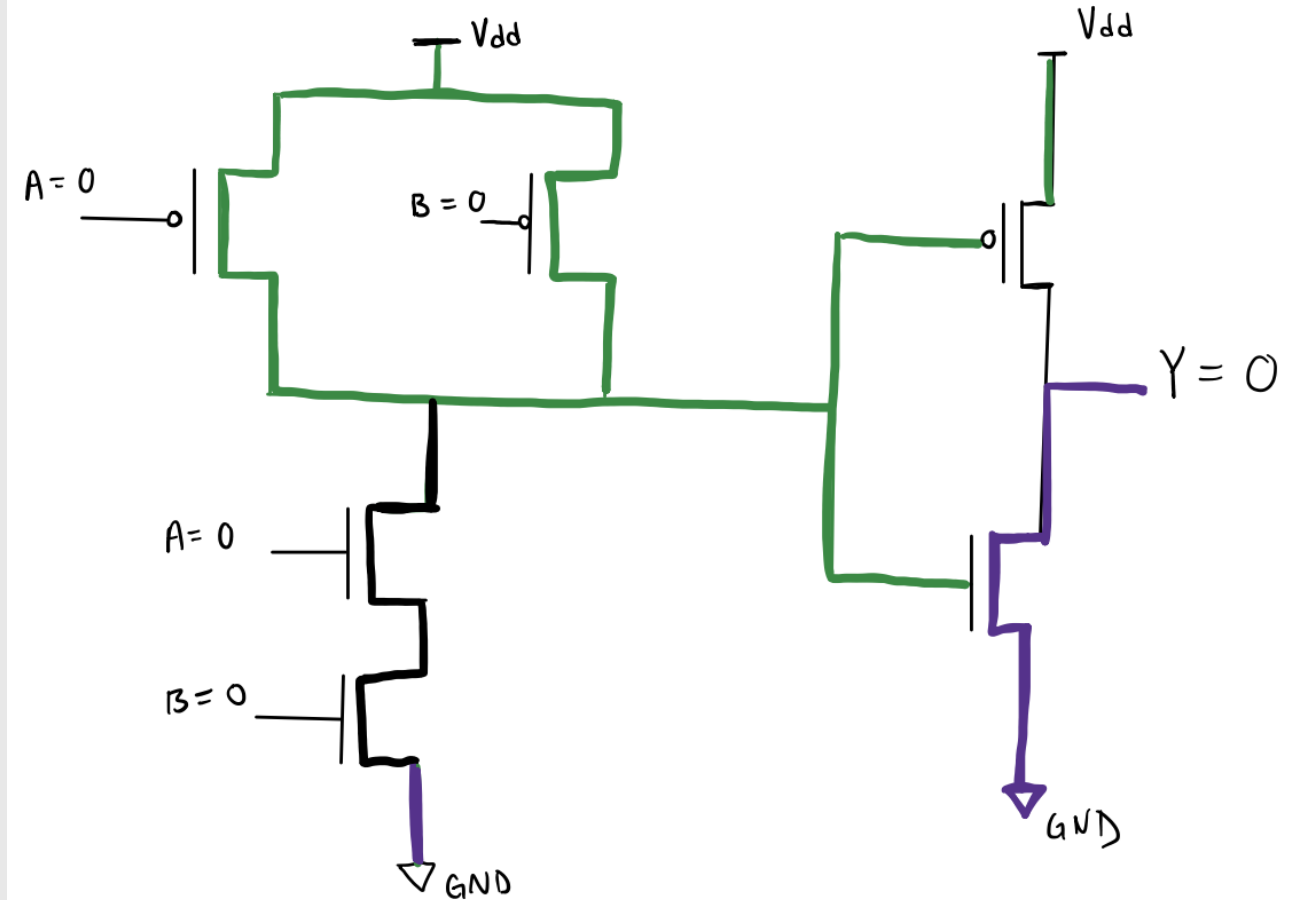


CMOS AND

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 


CMOS AND


A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 

CMOS AND

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 

 


CMOS OR

CMOS OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


CMOS OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 


CMOS OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

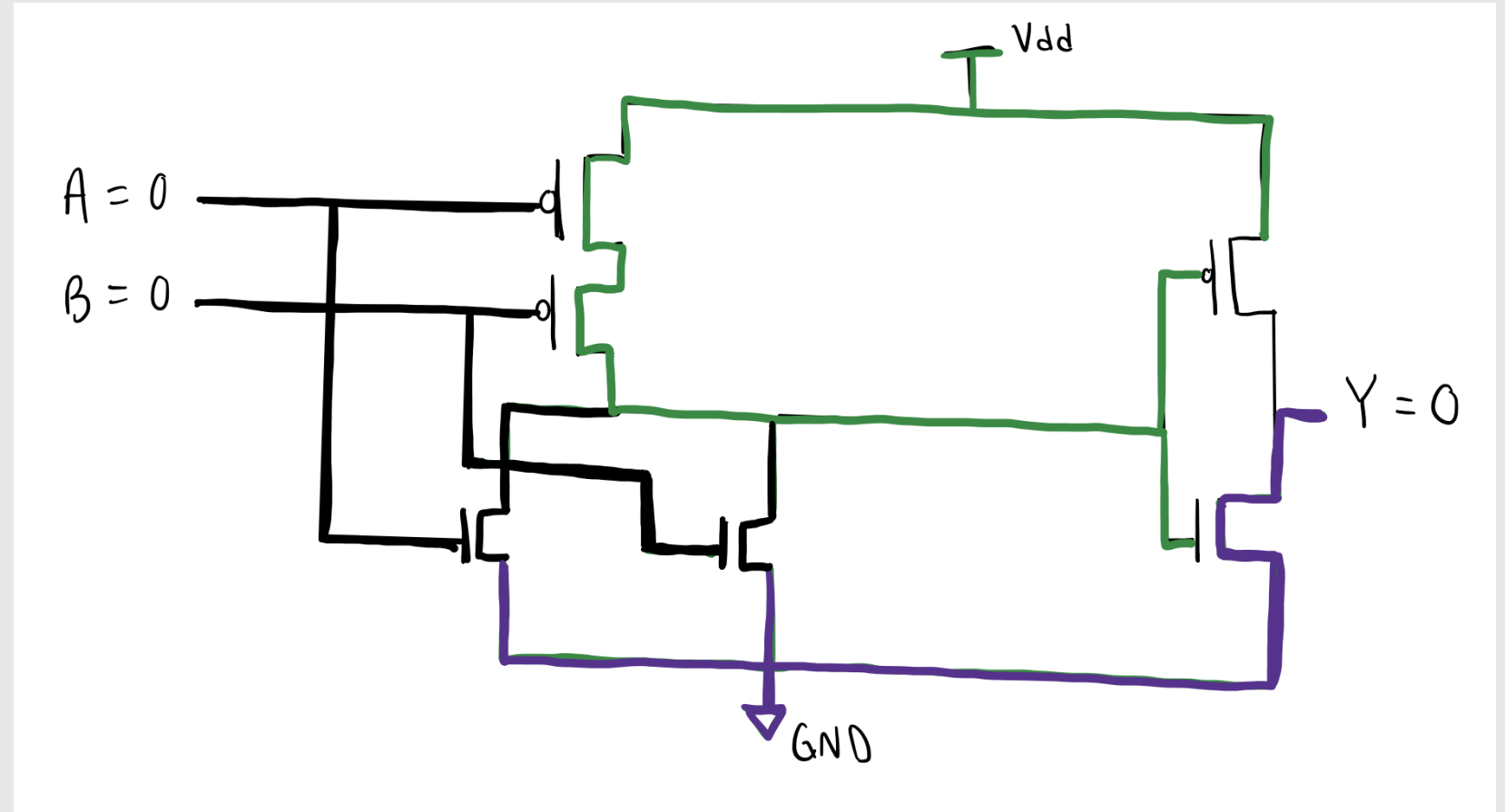


CMOS OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 


CMOS OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 

CMOS OR

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 

Transistor Count


Gate	Number of Transistors
NOT	2
AND	6
OR	6
 NAND	4
 NOR	4
XOR	12
XNOR	12

Popping up a level of
abstraction! 😊

LOGIC GATES

Now can we design larger systems!

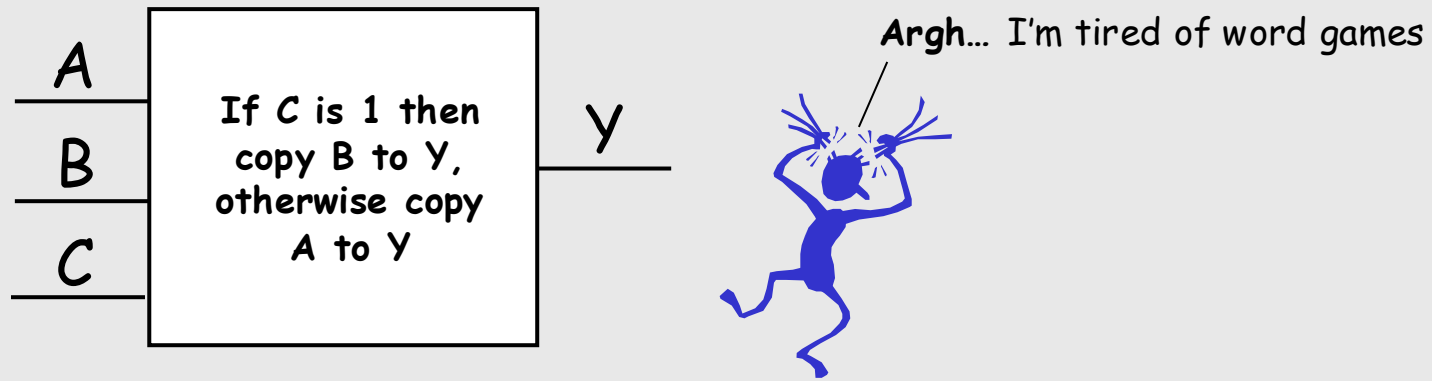We need to start somewhere – usually with a functional specification




Every combinational function can be expressed as a table!

“Truth tables” are a concise description of the combinational system’s function, where an output is specified for **every** input combination.

Inverter/Not Gate

Symbol

 

Circuit

Truth Table

A	Y
0	1
1	0

Equation

$$Y = \bar{A}$$

What logic gates can we build?

Recall, we need to design our gates using a pull-up network of pMOS transistors and a pull-down network of nMOS transistors

What gates can we
- build?
- define?

Let's start by
considering only
2-input gates.

AND		OR		NAND		NOR	
AB	Y	AB	Y	AB	Y	AB	Y
00	0	00	0	00	1	00	1
01	0	01	1	01	1	01	0
10	0	10	1	10	1	10	0
11	1	11	1	11	0	11	0

How many possible 2-input gates are there?

KEY IDEA: As many as there are 2-input truth tables.

All the gates!

There are only 16 possible 2-input gates... Let's examine all of them. Some we already know, others are just silly.

I N P U T AB															
	Z	A	A		B		X			X	N	A	N	B	N
	E	N	>		>		O	O		O	O	<=	O	<=	O
	R	D	B	A	A	B	R	R	R	R	'B'	B	'A'	A	D
00	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1

How many of these gates can be implemented using a single CMOS gate?





Do we really need all of these gates?

Nope! Once we realize that we can describe all of them using just AND, OR, and NOT

Composing gates: AND and OR

Each can be constructed using a pair of CMOS gates

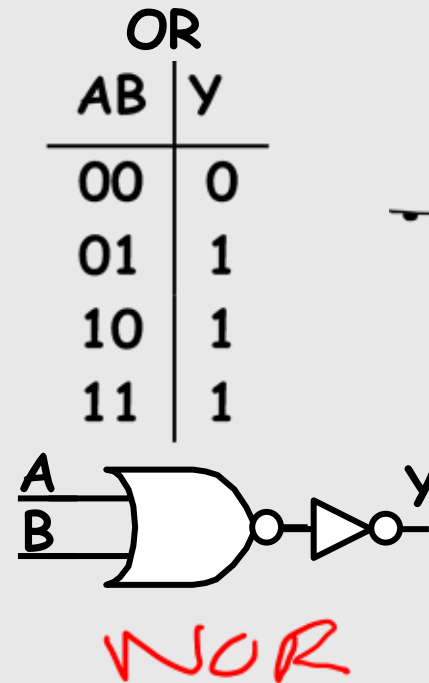 AND is just NAND with an inverter, and OR is just NOR with an inverted output.






These two gates are particularly important. Using them will allow us to develop a systematic approach for constructing any combinational function.

Composing gates

B > A		
AB	Y	
00	0	
01	1	
10	0	
11	0	

XOR		
AB	Y	
00	0	
01	1	
10	1	
11	0	

   

AND, OR, NOT

How many different gates do we really need?

We can always do it with 3 different types of gates (AND, OR, INVERT), and sometimes with 2, but, can we use fewer?

Implementing XOR with AND, OR, NOT!

Truth Table


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Challenge question: convert this use ONLY NAND gates. How many NAND gates did you use?

One gate will do!


NANDs and NORs are UNIVERSAL!

 A UNIVERSAL gate is one that can be used to implement
ANY COMBINATIONAL FUNCTION. There are many
UNIVERSAL gates, but not all gates are UNIVERSAL.



AND Gate

Symbol

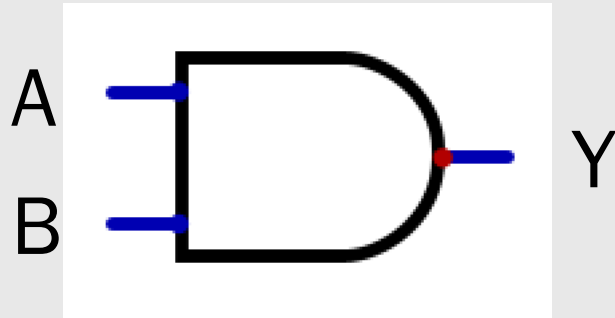

Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Equation

$$Y = A \times B$$


or
$$Y = AB$$

$$Y = A \cdot B$$

$$A * B$$

OR Gate

Symbol

 

Truth Table


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

Equation

$$Y = A + B$$

XOR Gate

Symbol

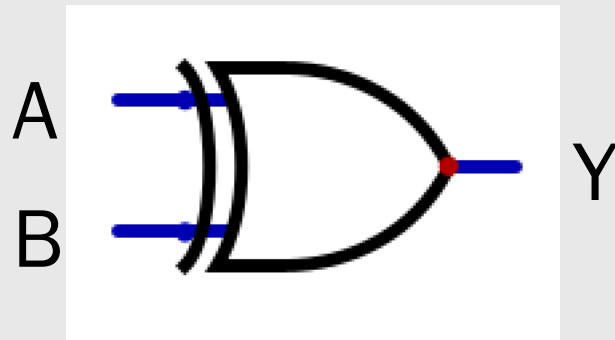

Truth Table


A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Equation

$$Y = A \oplus B$$

NAND

Symbol

 

Truth Table

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

Equation

$$Y = \overline{A \times B}$$


or

$$Y = \overline{AB}$$

$$Y = \overline{A \times B}$$

NOR

Symbol

 

Truth Table


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Equation

$$Y = \overline{A + B}$$

XNOR Gate

Symbol

 

Truth Table

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1


Equation

$$Y = \overline{A \oplus B}$$




FORMING EQUATIONS FROM LOGIC DIAGRAMS

Ex1: Forming Equations from Logic Diagrams

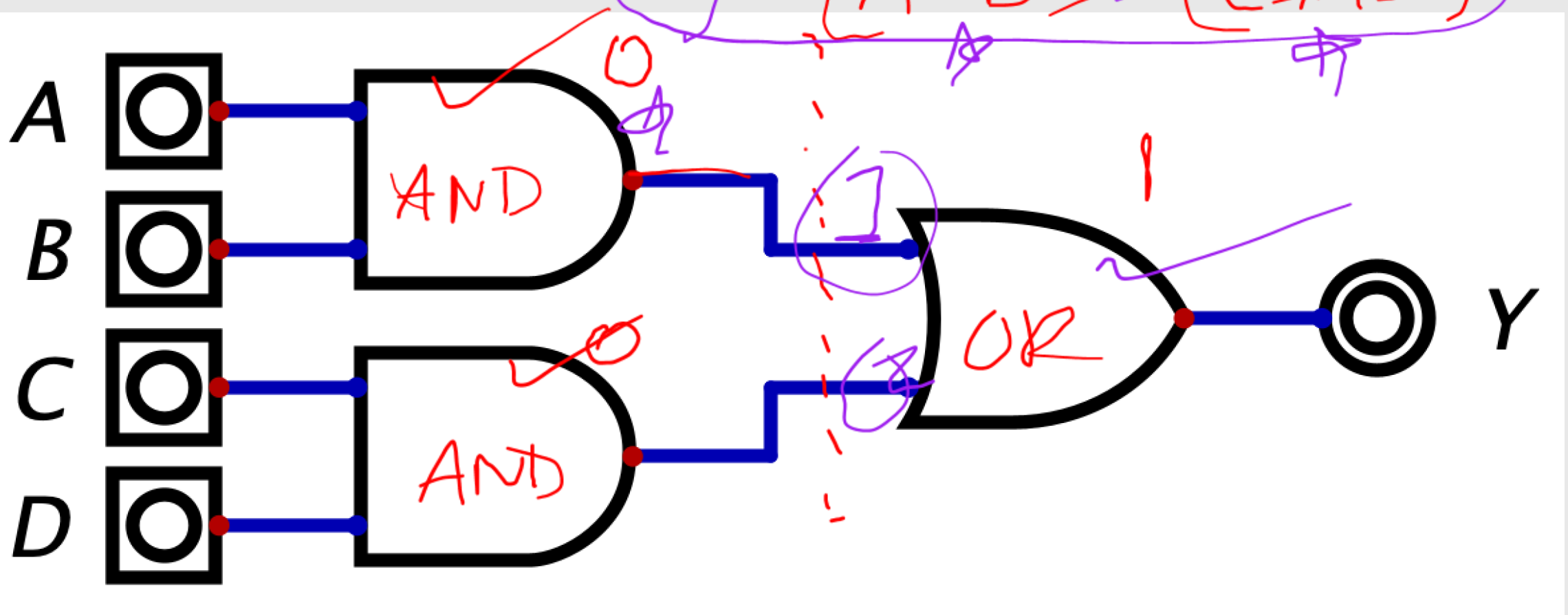


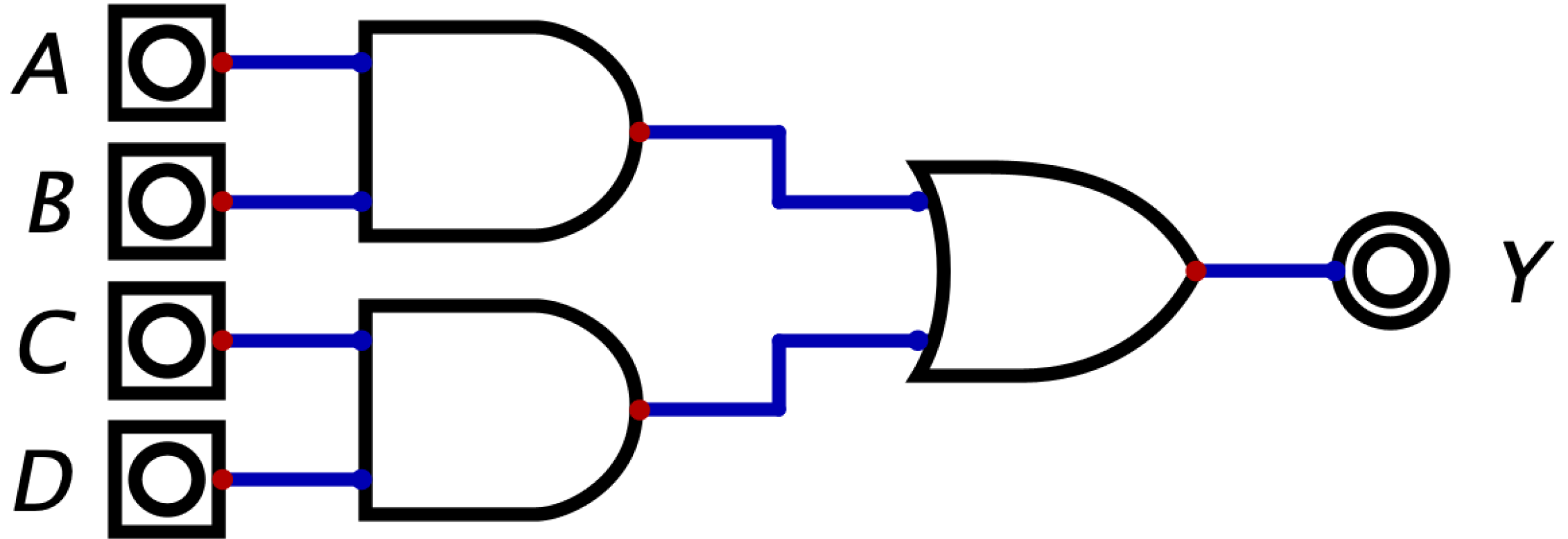Ex1: Forming Equations from Logic Diagrams




$$Y = AB + CD$$

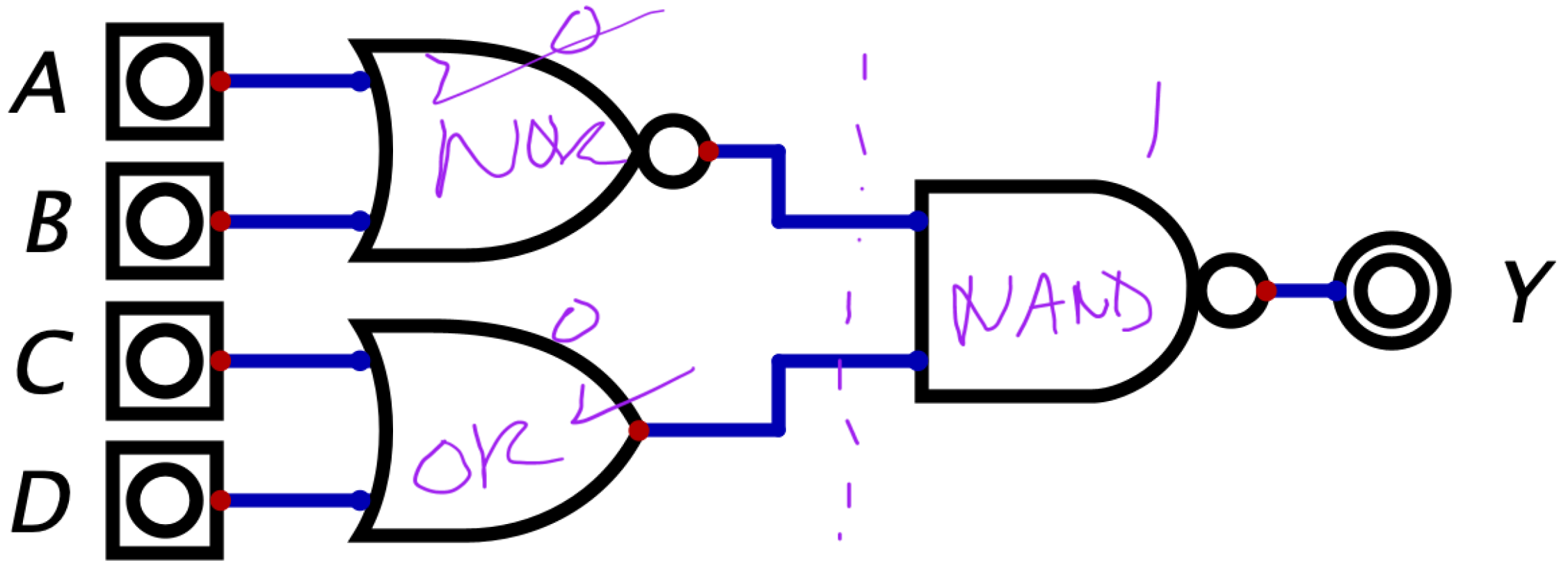Ex2: Forming Equations from Logic Diagrams




$$Y = (A + B) * (C + D)$$

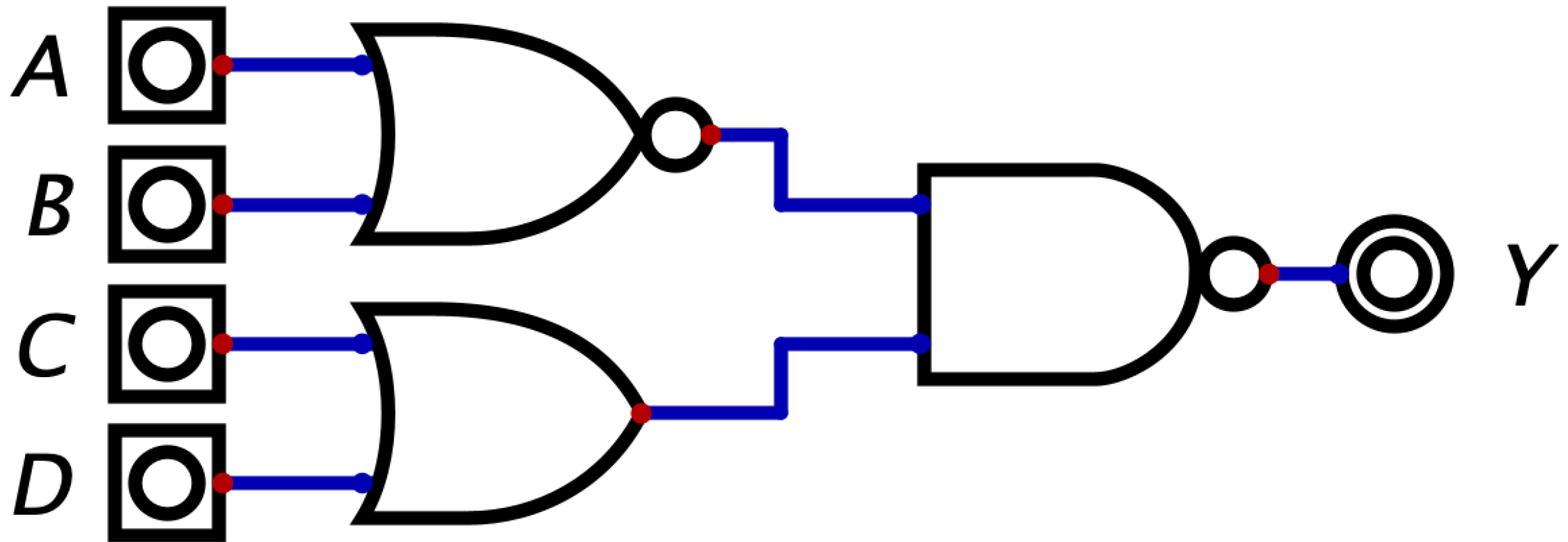Ex2: Forming Equations from Logic Diagrams




$$Y = \overline{(A + B)}(C + D)$$

Ex3: Forming Equations from Logic

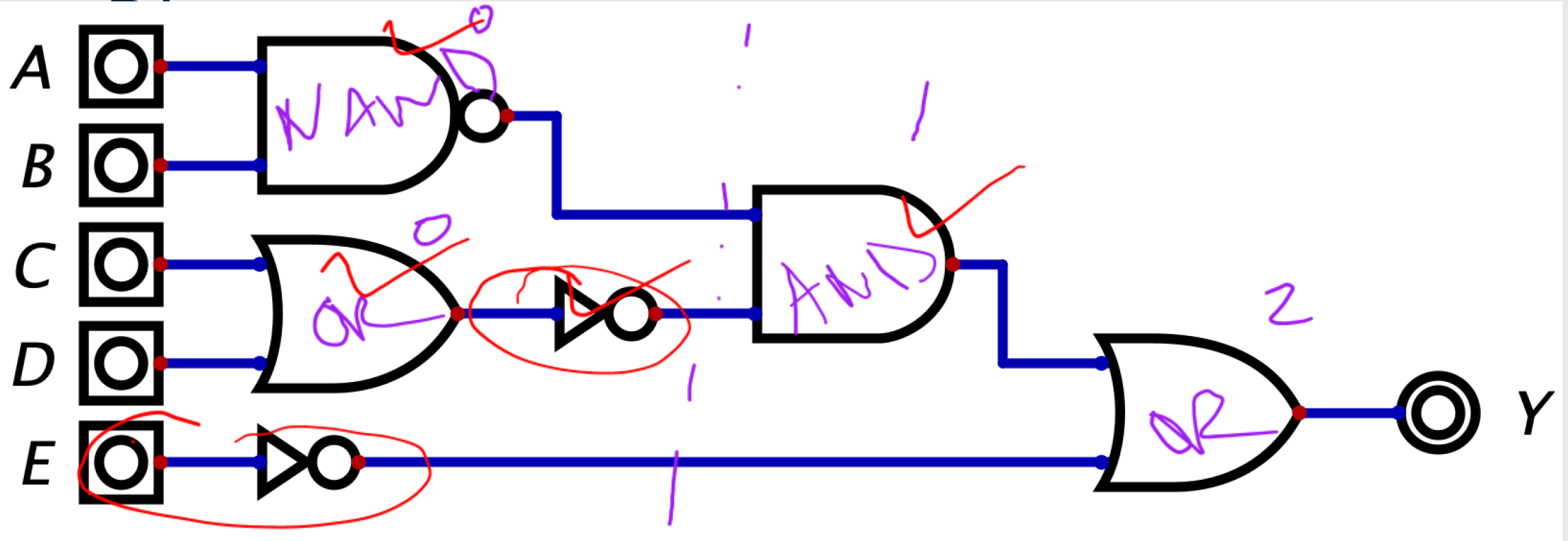


$$Y = \overline{(A \times B) \times (C + D)} + \overline{E}$$

 Ex3: Forming Equations from Logic Diagrams



$$Y = (\overline{AB})(\overline{C + D}) + \overline{E}$$

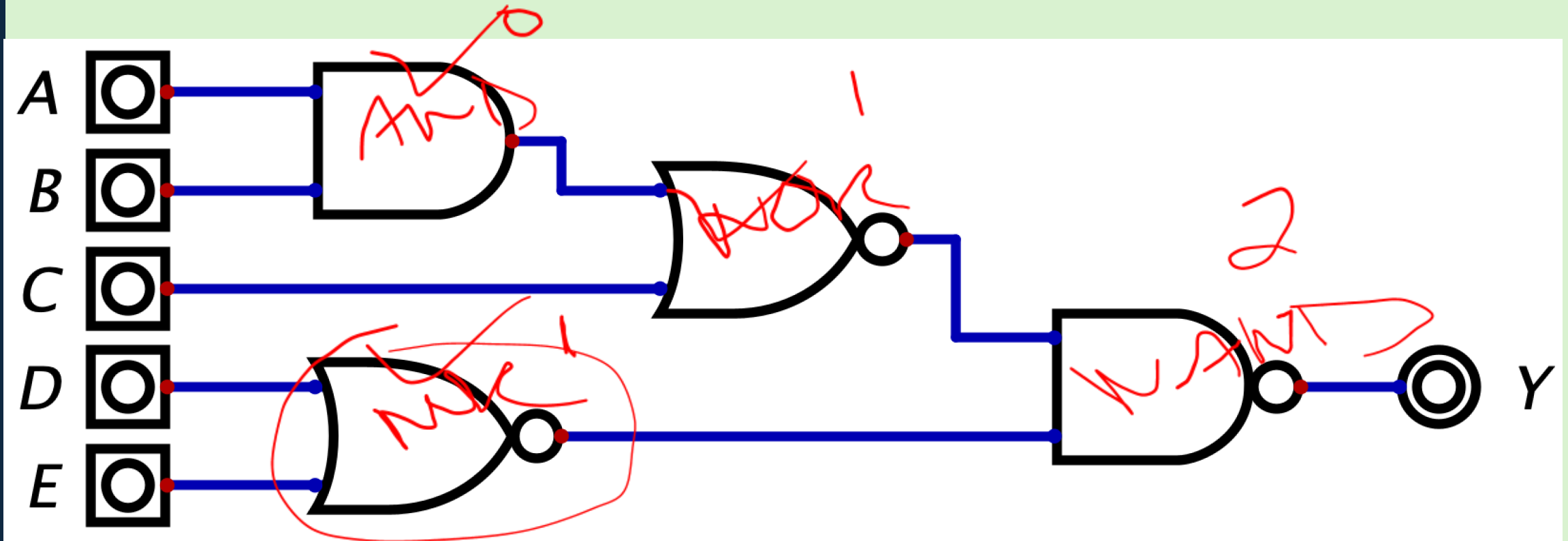
EX4: Forming Equations from Logic Diagrams



$$(\overline{AB + C}) \times \overline{(D + E)} = Y$$




FORMING LOGIC DIAGRAMS FROM EQUATIONS

 


Ex1: Forming Logic Diagrams from Equations

$$Y = (A + B)C$$

 


Ex1: Forming Logic Diagrams from Equations

$$Y = \overline{(A + B)C}$$

 


Ex2: Forming Logic Diagrams from Equations

$$Y = \overline{(A + B)}CD$$

 


Ex2: Forming Logic Diagrams from Equations

$$Y = \overline{(A + B)}CD$$

 


Ex3: Forming Logic Diagrams from Equations $Y = \underline{(\overline{A + B})}(\overline{CD}) + \underline{E}$

 


Ex3: Forming Logic Diagrams from Equations
 
$$Y = (\overline{A + B})(\overline{CD}) + E$$



Forming Logic Diagrams from Equations

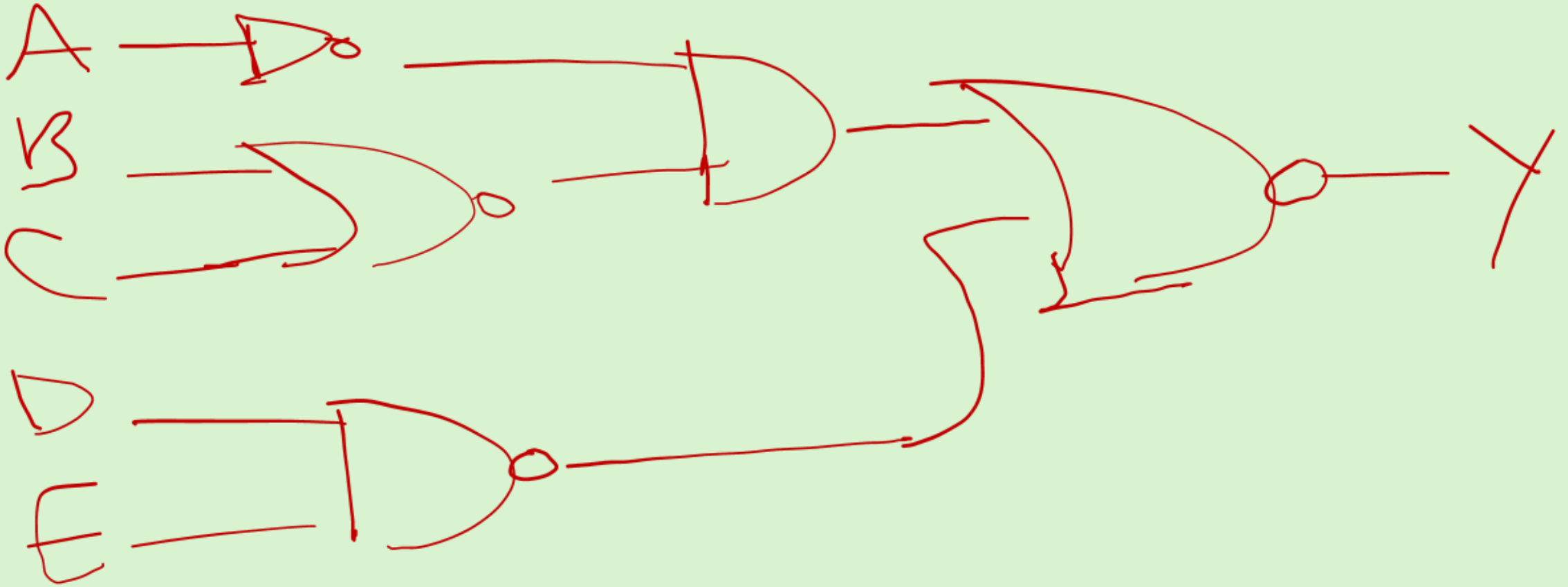
$$Y = (\bar{A})(\overline{B + C}) + \overline{DE}$$





Forming Logic Diagrams from Equations
 
$$Y = \overline{(\bar{A})(\overline{B + C}) + \overline{DE}}$$





FORMING TRUTH TABLES FROM EQUATIONS

Ex1: Forming Truth Tables from Equations

$$Y = A + \bar{B}$$



A	B	Y
0	0	1
0	1	0
1	0	1
1	1	1

Ex1: Forming Truth Tables from Equations

$$Y = A + \bar{B}$$

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	1

Ex2: Forming Truth Tables from Equations

$$Y = AB + \bar{C}$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Ex2: Forming Truth Tables from Equations

$$Y = AB + \bar{C}$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Forming Truth Tables from Equations

$$Y = \bar{A}\bar{B} + \overline{AB}$$

A	B	Y
0	0	1
0	1	0
1	0	1
1	1	0



FORMING EQUATIONS FROM TRUTH TABLES

Sum of Products Form

When two or more products (AND) are summed (OR) together

Sum of Products

$$Y = \underline{AB} + \underline{AC}$$

~~Not Sum of Products~~

$$Y = (A + B)(C + A)$$

Approach: write down a boolean expression for every '1' in the output

Ex: Forming Equations from Truth Tables

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Ex: Forming Equations from Truth Tables

A	B	C	Y	
<u>0</u>	<u>0</u>	<u>0</u>	<u>1</u>	<u>$\bar{A}\bar{B}\bar{C}$</u>
0	0	1	0	
<u>0</u>	<u>1</u>	<u>0</u>	<u>1</u>	<u>$\bar{A}B\bar{C}$</u>
0	1	1	0	
1	0	0	0	
<u>1</u>	<u>0</u>	<u>1</u>	<u>1</u>	<u>$A\bar{B}C$</u>
1	1	0	0	
1	1	1	0	

minterms

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}C$$

Forming Equations from Truth Tables

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

A Systematic Design Approach

Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- it's systematic!
- it works!
- it's easy!
- we are done! (?)



- 1) Write the functional spec as a truth table
- 2) Write down a Boolean expression for every '1' in the output

$$Y = (!C \&\& !B \&\& A) \mid\mid (!C \&\& B \&\& A) \mid\mid (C \&\& B \&\& !A) \mid\mid (C \&\& B \&\& A)$$

- 3) Wire up the ideal gates, replace them with equivalent realizable gates, call it a day, and go home!

This approach will **always** give us logic expressions in a particular form:

SUM-OF-PRODUCTS

Straightforward Synthesis

We can implement sum-of-products with just 3 levels of logic, using...

INVERTERS/AND/OR!

