

COMP311: *COMPUTER ORGANIZATION!*

Lecture 6: Multiplexers, Gate Minimization Pt. 1

tinyurl.com/comp311-sp26

Logistics Updates

- Quiz schedule updated
 - *Quiz 2 & 3 shifted by one week.*
- Quiz 2 is next class! Next Wednesday.
- Quiz 1 grades posted
 - *Mean: 90*
 - *Median: 91*



Quiz Topics

Review Tues Spm


■ Topics:

- *Tracing CMOS gates*
- *Going between circuit diagrams, boolean equations, and truth tables*
- *Be able to draw basic circuit diagrams made of logic gates!*
- *Multiplexers*
- *Counting the number of transistors*
- *Boolean algebra simplification*
- *Whatever we get through today*




LOGIC GATES WITH 2+ INPUTS

3-input AND

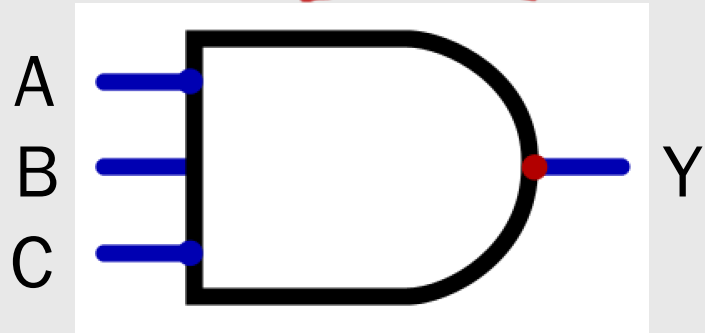

logically
equivalent
circuits

 


A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1


$A \cdot B \cdot C$



3-input OR

 


logically
equivalent
circuits

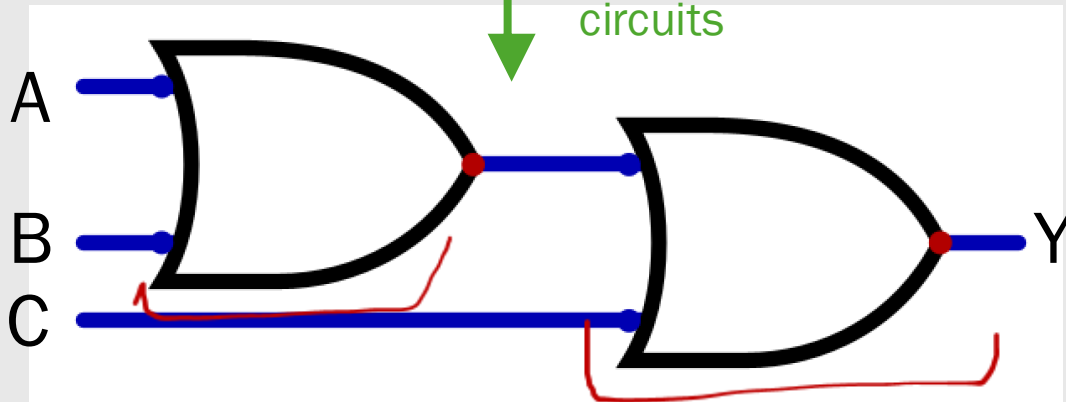


$$A + B + C$$

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

3-input NAND

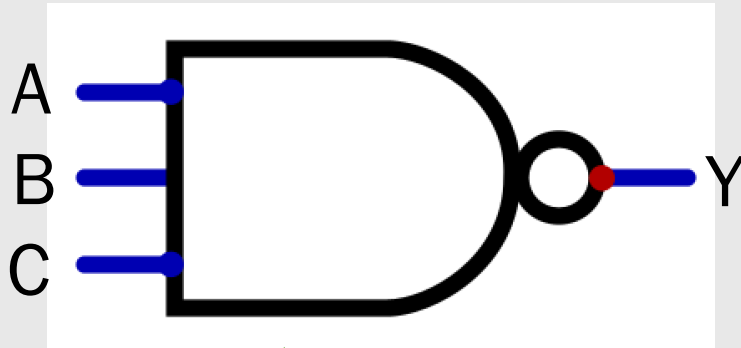


logically
equivalent
circuits

 


A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

3-input NOR

 


logically
equivalent
circuits

 


$$(A + B) + C$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

3-input XOR

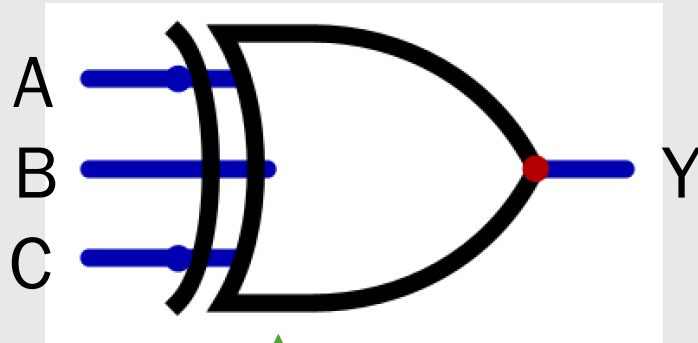


logically
equivalent
circuits

 


A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

For any number of inputs, the output is 1 when an odd number of inputs is 1

3-input XNOR

 


logically
equivalent
circuits

 

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Recall: Transistor Count

Gate	Number of Transistors
NOT	2
AND	6
OR	6
NAND	4
NOR	4
XOR	12
XNOR	12

 A hand-drawn purple bracket groups the rows for NAND, NOR, XOR, and XNOR gates. To the right of the bracket, there is a purple star-like symbol.

Transistor Count

Gate	# of Transistors
NOT	2
n-input AND	<u>$2n + 2$</u>
n-input OR	<u>$2n + 2$</u>
n-input NAND	$2n$
n-input NOR	$2n$
2-input XOR	12
3-input XOR	28
2-input XNOR	12
3-input XNOR	28




MULTIPLEXERS



An interesting 3-input gate....!

 
Based on C, select the A or B input to be copied to Y.




Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

2-input Multiplexer

 

schematic

 

Gate
symbol

NANDS

select

A Circuit for If-Statements! 😊

C
if (S == 0)
 Y = A
elseif (S == 1)
 Y = B



In Assembly...

$X/10 = S$

$\Rightarrow$ `beq x10, x0, S_is_zero` $\downarrow$ `# if S == 0, jump`
 $\swarrow$ `addi x14, x0, 1` $X/4 \leftarrow 0 + 1$
 $\Rightarrow$ `beq x10, x14, S_is_one` `# if S == 1, jump`

`S_is_zero:` *# label 1*
 $\rightarrow$ `add x13, x11, x0` `# Y = A`

`S_is_one:` *# label 1*
`add x13, x12, x0` `# Y = B`

New instruction:
beq: branch if equal

Multiplexers

Truth Table

S	A	B	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Equation

Diagram

Multiplexers

Truth Table

S	A	B	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1
S	A	B	Y
0	0	1	0
0	1	1	1
1	0	0	0
1	1	1	1

2:1 Mux

Equation

$$Y = A\bar{S} + BS$$

Diagram

Multiplexers

Truth Table


S	A	B	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

S	A	B	Y
0	0	X	0
0	1	X	1
1	X	0	0
1	X	1	1

Equation

$$Y = \overset{(1)}{A}\bar{\underset{(2)}{S}} + \underset{(2)}{B}S$$

Diagram

 

Multiplexers

Truth Table

S	A	B	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

S	A	B	Y
0	0	X	0
0	1	X	1
1	X	0	0
1	X	1	1

Equation

Diagram


Don't-cares can be used to simplify logic!

For input combinations that never occur, the designer may assume either 1 or 0, whichever is more useful to achieving a minimum-cost implementation.


Y

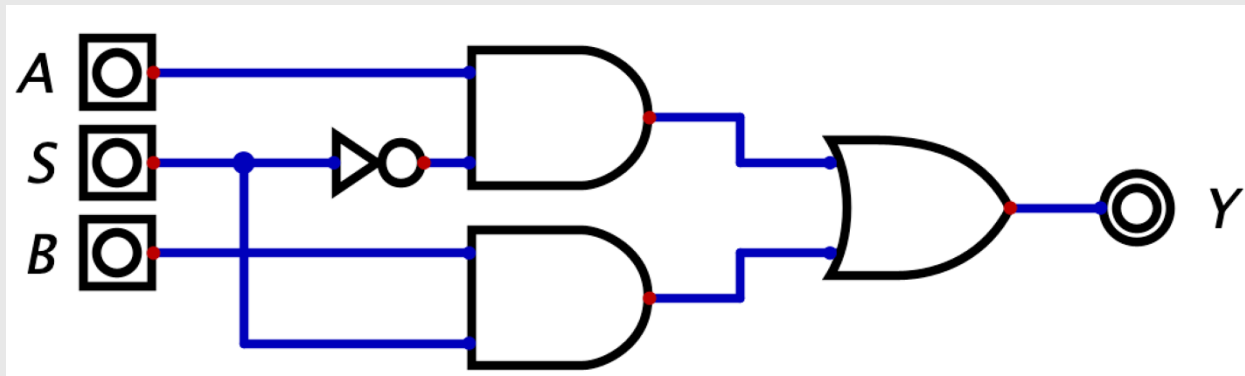2:1 Multiplexer (2:1 mux)

- A circuit that chooses an output from among two inputs based on the value of a select signal




2:1 Multiplexer Schematic
(Gate Diagram)

 

2:1 Multiplexer Symbol

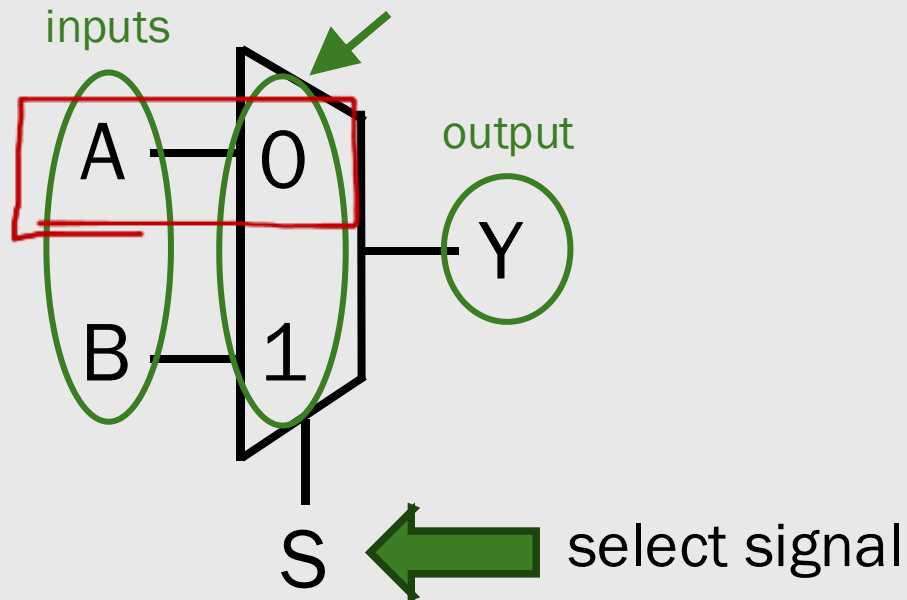
2:1 Multiplexer (2:1 mux)

These labels tell us how the multiplexer chooses the output based on the value of the select signal




→ When $S = 0$, $Y = A$
→ When $S = 1$, $Y = B$

2:1 Multiplexer (2:1 mux)

 


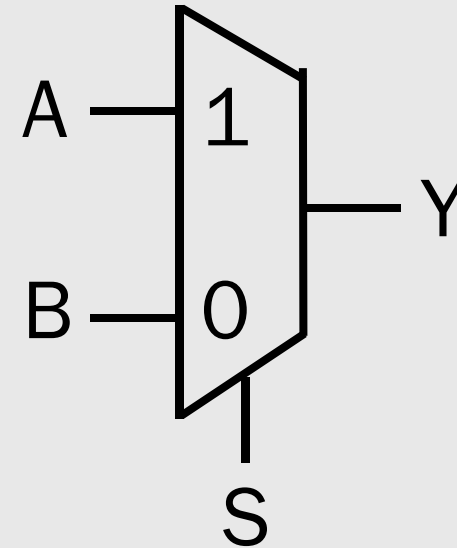
When $S = 0$, $Y = A$
When $S = 1$, $Y = B$





When $S = 0$, $Y = B$
When $S = 1$, $Y = A$

MUX Compositions and Shortcuts

A 4-input Mux
(implemented as a tree)

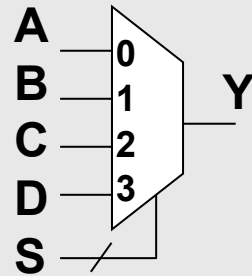 

A 4-bit wide 2-input Mux

 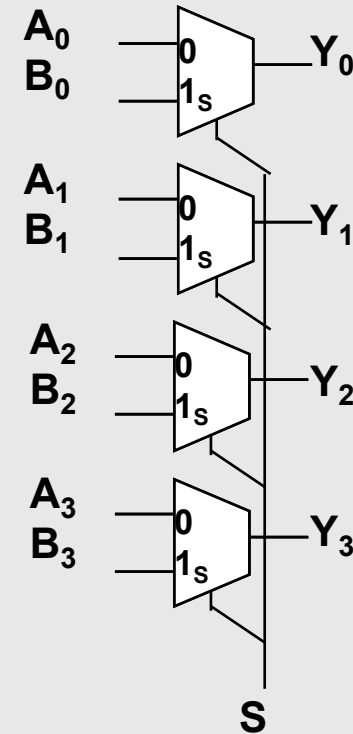


MUX Function Synthesis

A mux plus constants is enough to implement *any* Boolean function

Consider implementation of some arbitrary Combinational function, $F(A,B,C)$... using a MULTIPLEXER as the only circuit element:

 Mux: An example “configurable” logic element



8:1
MUX


MUX Logic Tricks

We can apply certain optimizations to MUX Function synthesis

Desired Logic Function

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

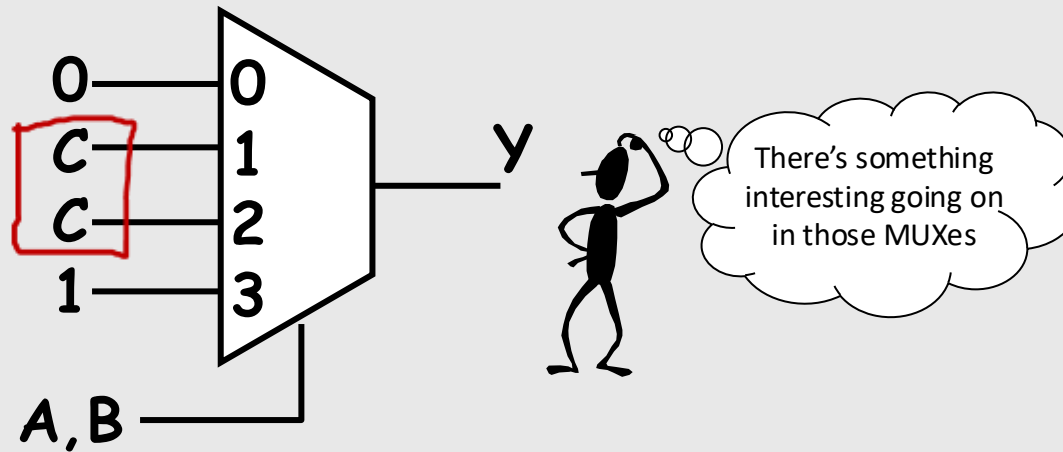- Largely by inspection or exhaustive search



- N-input function == N-1 input MUX & 1 inverter

If adjacent truth-table rows differ by just one bit, that bit can become a mux input



FORMING EQUATIONS FROM TRUTH TABLES

From Last Time: Sum of Products Form

When two or more products (AND) are summed (OR) together

Sum of Products

$$Y = AB + AC$$

Not Sum of Products

$$Y = (A + B)(C + A)$$

Approach: write down a boolean expression for every '1' in the output

Ex: Forming Equations from Truth Tables

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Ex: Forming Equations from Truth Tables

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

$$\underline{\bar{A}\bar{B}\bar{C}}$$

$$\underline{\bar{A}B\bar{C}}$$

$$\underline{\underline{A\bar{B}C}}$$

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}C$$

Forming Equations from Truth Tables

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Forming Equations from Truth Tables



A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

$\bar{A}\bar{B}C$

$A\bar{B}\bar{C}$

$AB\bar{C}$

ABC

$$Y = \bar{A}\bar{B}C + A\bar{B}\bar{C} + AB\bar{C} + ABC$$

A Systematic Design Approach

Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

-it's systematic!
-it works!
-it's easy!
-we are done! (?)



- 1) Write the functional spec as a truth table
- 2) Write down a Boolean expression for every '1' in the output

$$Y = (!C \&\& !B \&\& A) \mid\mid (!C \&\& B \&\& A) \mid\mid (C \&\& B \&\& !A) \mid\mid (C \&\& B \&\& A)$$

- 3) Wire up the ideal gates, replace them with equivalent realizable gates, call it a day, and go home!


This approach will **always** give us logic expressions in a particular form:

SUM-OF-PRODUCTS

Straightforward Synthesis

We can implement sum-of-products with just 3 levels of logic, using...

INVERTERS/AND/OR!

 

Let's Try it Out

A_1	A_0	B_1	B_0	Y
0	0	0	0	0
0	0	1	0	0
0	0	0	1	0
0	0	1	1	0
1	0	0	0	1
1	0	1	0	0
1	0	0	1	1
1	0	1	1	0
0	1	0	0	1
0	1	1	0	1
0	1	0	1	0
0	1	1	1	0
1	1	0	0	1
1	1	1	0	1
1	1	0	1	1
1	1	1	1	0

I want to build a circuit that will output 1 if $A > B$, and 0 if $A \leq B$. A and B are both two-bit unsigned numbers.

Additionally, define A_1 and B_1 as the left bits of A and B, and A_0 and B_0 as the right bits.

Y =

Let's Try it Out

A_1	A_0	B_1	B_0	Y
0	0	0	0	0
0	0	1	0	0
0	0	0	1	0
0	0	1	1	0
1	0	0	0	1
1	0	1	0	0
1	0	0	1	1
1	0	1	1	0
0	1	0	0	1
0	1	1	0	0
0	1	0	1	0
0	1	1	1	0
1	1	0	0	1
1	1	1	0	1
1	1	0	1	1
1	1	1	1	0

I want to build a circuit that will output 1 if $A > B$, and 0 if $A \leq B$. A and B are both two-bit unsigned numbers.

Additionally, define A_1 and B_1 as the left bits of A and B, and A_0 and B_0 as the right bits.

y =

$$\bar{A}_1 A_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{A}_0 \bar{B}_1 B_0 + A_1 A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_1 B_0 + A_1 A_0 B_1 \bar{B}_0$$

Is the simplest possible form?? 🤖



GATE MINIMIZATION



Optimizing our circuits...

- Fewer transistors means....

- *Smaller area!*
- *Lower power consumption!*
- *Shorter time from input to output!*
- *Lower cost!*

- How will we do this?

- *Visual inspection*

 – *Boolean algebra simplification*

- *In practice, → advanced synthesis algorithms to create **logically equivalent**, more efficient circuits! 😊*

Recall: Transistor Count

Gate	Number of Transistors
NOT	2
AND	6
OR	6
NAND	4
NOR	4
XOR	12
XNOR	12

Boolean Algebra Laws

Name	OR Form	AND Form
Identity	$A + 0 = A$	$A \cdot 1 = A$
Null	$A + 1 = 1$	$A \cdot 0 = 0$
→ Idempotent	$A + A = A$	$A \cdot A = A$
Complement	$A + \overline{A} = 1$	$A \cdot \overline{A} = 0$
Commutative	$A + B = B + A$	$A \cdot B = B \cdot A$
Associative	$(A + B) + C = A + (B + C)$	$(A \cdot B) \cdot C = A \cdot (B \cdot C)$
Distributive	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$	$A + (B \cdot C) = (A + B) \cdot (A + \overline{C})$
★ De Morgan's	$\overline{A + B} = \overline{A} \cdot \overline{B}$	$\overline{A \cdot B} = \overline{A} + \overline{B}$

Boolean Algebra Practice

Using the laws that you have just learned, simplify the following Boolean expression:

$$A \cdot (A + B)$$

$$AA + AB$$

$$A + AB$$

$$A(1 + B)$$

$$A(1) \rightarrow A$$

Boolean Algebra Practice

$$A \cdot (A + B)$$

$$AA + AB$$

$$A + AB$$

$$A(1 + B)$$

$$A(1)$$


$$A$$

Name	OR Form	AND Form
Identity	$A + 0 = A$	$A \cdot 1 = A$
Null	$A + 1 = 1$	$A \cdot 0 = 0$
Idempotent	$A + A = A$	$A \cdot A = A$
Complement	$A + \overline{A} = 1$	$A \cdot \overline{A} = 0$
Commutative	$A + B = B + A$	$A \cdot B = B \cdot A$
Associative	$(A + B) + C = A + (B + C)$	$(A \cdot B) \cdot C = A \cdot (B \cdot C)$
Distributive	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$	$A + (B \cdot C) = (A + B) \cdot (A + C)$
De Morgan's	$\overline{A + B} = \overline{A} \cdot \overline{B}$	$\overline{A \cdot B} = \overline{A} + \overline{B}$

$$\text{Absorption Law: } A \cdot (A + B) = A$$

Comparing Number of Transistors Used

Original Circuit

 

$$Y = A \cdot (A + B)$$

Number of Transistors = 12

Simplified Circuit



$$Y = A$$

Number of Transistors = 0

Boolean Algebra Practice

Simplify the following Boolean expression: $B + \bar{B}C$

Name	OR Form	AND Form
Identity	$A + 0 = A$	$A \cdot 1 = A$
Null	$A + 1 = 1$	$A \cdot 0 = 0$
Idempotent	$A + A = A$	$A \cdot A = A$
Complement	$A + \bar{A} = 1$	$A \cdot \bar{A} = 0$
Commutative	$A + B = B + A$	$A \cdot B = B \cdot A$
Associative	$(A + B) + C = A + (B + C)$	$(A \cdot B) \cdot C = A \cdot (B \cdot C)$
Distributive	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$	$A + (B \cdot C) = (A + B) \cdot (A + C)$
De Morgan's	$\overline{A + B} = \bar{A} \cdot \bar{B}$	$\overline{A \cdot B} = \bar{A} + \bar{B}$
Absorption	$A \cdot (A + B) = A$	$A + (A \cdot B) = A$

Boolean Algebra Practice

$$B + \bar{B}C$$

$$\begin{aligned} &(B + \bar{B})(B + C) \\ &(1)(B + C) \\ &B + C \end{aligned}$$

Name	OR Form	AND Form
Identity	$A + 0 = A$	$A \cdot 1 = A$
Null	$A + 1 = 1$	$A \cdot 0 = 0$
Idempotent	$A + A = A$	$A \cdot A = A$
Complement	$A + \bar{A} = 1$	$A \cdot \bar{A} = 0$
Commutative	$A + B = B + A$	$A \cdot B = B \cdot A$
Associative	$(A + B) + C = A + (B + C)$	$(A \cdot B) \cdot C = A \cdot (B \cdot C)$
Distributive	$A \cdot (B + C) = (A \cdot B) + (A \cdot C)$	$A + (B \cdot C) = (A + B) \cdot (A + C)$
De Morgan's	$\overline{A + B} = \bar{A} \cdot \bar{B}$	$\overline{A \cdot B} = \bar{A} + \bar{B}$

Recall: De Morgan's Theorem

De Morgan's Theorem:
express conjunctions &
disjunctions (ANDS, ORS)
solely in terms of negation!

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

$$\overline{AB} = \bar{A} + \bar{B}$$

Applying DeMorgan's

$$\overline{AB + CD}$$

- How would you apply DeMorgan's to this expression?
 - We group our terms based on the lowest operator precedence under the bar
 - The order of operations for Boolean Algebra is **NOT**, then **AND**, then **OR**. Expressions inside brackets are always evaluated first.
 - In this case, the operator with the lowest precedence is OR

(1)

$$(\overline{AB})(\overline{CD})$$

(2)

$$(\overline{A} + \overline{B})(\overline{C} + \overline{D})$$

DeMorgan's Practice

$$\overline{\overline{A}B + \overline{C}}$$

- How would you apply DeMorgan's to this expression?

$$\rightarrow (A + \overline{B})C$$

$$\overline{\overline{A}B + \overline{C}}$$



$$(A + \overline{B})C$$

DeMorgan's Practice

$$\overline{\bar{A}B + \bar{C}}$$

- How would you apply DeMorgan's to this expression?

$$\overline{\bar{A}BC}$$

$$(A + \bar{B})C$$

DeMorgan's Practice

- How would you apply DeMorgan's to this expression?

$$\overline{(\bar{A} + B)(C + D)\overline{(E + F)} + G}$$

$$\overline{X + Y} = \overline{X} \cdot \overline{Y}$$
$$\overline{XY} = \overline{X} + \overline{Y}$$

DeMorgan's Practice

- How would you apply DeMorgan's to this expression?

X + Y $\overline{(\bar{A} + B)(C + D)(E + F) + G}$

$$\overline{(\bar{A} + B)(C + D)(E + F)} \cdot \bar{G}$$

$$(\overline{\bar{A} + B} + \overline{C + D} + E + F) \cdot \bar{G}$$


$$(A\bar{B} + \bar{C}\bar{D} + E + F) \cdot \bar{G}$$

DM #1

DM #2

simplify

Can we optimize this?

 


Simplify the following Boolean expression

$$ABC + AB\bar{C} + \overline{AC}B + ACB + \overline{\overline{A}\overline{B}\overline{C}\overline{D}} + \overline{\overline{A}B + \bar{C}}$$

Solution

$$\begin{aligned} & ABC + AB\bar{C} + \overline{AC}B + ACB + \overline{\overline{AB}\overline{C}\overline{D}} + \overline{\overline{AB} + \bar{C}} \\ & AB(C + \bar{C}) + B(\overline{AC} + AC) + AB + C + D + (\overline{\overline{AB}})C \\ & AB(1) + B(1) + AB + C + D + (A + \bar{B})C \\ & AB + B + AB + C + D + AC + \bar{B}C \\ & AB + B + C + D + AC + \bar{B}C \\ & B(A + 1) + C(1 + A) + \bar{B}C + D \\ & B(1) + C(1) + \bar{B}C + D \\ & B + C + \bar{B}C + D \\ & B + C(1 + \bar{B}) + D \\ & B + C(1) + D \\ & \underline{B + C + D} \end{aligned}$$

Optimizing Our Gates

 

Yay! We did it!

Recall: Our Problem from Earlier

A_1	A_0	B_1	B_0	Y
0	0	0	0	0
0	0	1	0	0
0	0	0	1	0
0	0	1	1	0
1	0	0	0	1
1	0	1	0	0
1	0	0	1	1
1	0	1	1	0
0	1	0	0	1
0	1	1	0	0
0	1	0	1	0
0	1	1	1	0
1	1	0	0	1
1	1	1	0	1
1	1	0	1	1
1	1	1	1	0

I want to build a circuit that will output 1 if $A > B$, and 0 if $A \leq B$. A and B are both two-bit unsigned numbers.

Additionally, define A_1 and B_1 as the left bits of A and B, and A_0 and B_0 as the right bits.

$$\bar{A}_1 A_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{A}_0 \bar{B}_1 B_0 + A_1 A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_1 B_0 + A_1 A_0 B_1 \bar{B}_0$$

Is the simplest possible form?? 🤔

Simplify?

$$\bar{A}_1 A_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + A_1 \bar{A}_0 \bar{B}_1 B_0 + A_1 A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_1 B_0 + A_1 A_0 B_1 \bar{B}_0$$

Our Problem from Earlier

A_1	A_0	B_1	B_0	Y
0	0	0	0	0
0	0	1	0	0
0	0	0	1	0
0	0	1	1	0
1	0	0	0	1
1	0	1	0	0
1	0	0	1	1
1	0	1	1	0
0	1	0	0	1
0	1	1	0	1
0	1	0	1	0
0	1	1	1	0
1	1	0	0	1
1	1	1	0	1
1	1	0	1	1
1	1	1	1	0

I want to build a circuit that will output 1 if $A > B$, and 0 if $A \leq B$. A and B are both two-bit unsigned numbers.

Additionally, define A_1 and B_1 as the left bits of A and B, and A_0 and B_0 as the right bits.

$$A_1\bar{B}_1 + A_0\bar{B}_1\bar{B}_0 + A_1A_0\bar{B}_0$$