

COMP311: *COMPUTER ORGANIZATION!*

Lecture 10: Adders/Subtractors, Shifters

tinyurl.com/comp311-sp26

Logistics

- Quiz next class! Review tomorrow 5pm in SN014. Topics:

- *K-Maps: Reading them, filling them in, using them to find simplified Boolean equations*
- *“Don’t Cares” (in relation to K-Maps, Truth Table Minimization)*
- *Transistor Minimization (review lecture where we converted things into NAND/NOR gates)*
- *Multiplexers: conceptually + circuit design w/ them*
- *Reading + writing basic assembly. Instructions we have covered: ADD, ADDI, SUB, BEQ. Understanding how labels work.*
- *Adder + subtractor circuits*
- *Circuit design generally. Given an English specification, can you write down the truth table/draw the circuit*

- WA3 due Thurs

- Lab due Monday!

ADD, ADDI,
SUB

ADDER CIRCUITS!

Full Adder

- We need to build a circuit that can add together three one-bit values


$$\begin{array}{r} 111 \\ + 101 \\ + 111 \\ \hline 100 \end{array}$$

Full Adder

- This circuit will be able to add together the three bits in column 1

Output: C_o
 
$$\begin{array}{r} \text{Input: } C_i \rightarrow 111 \\ \text{Input: } A \rightarrow 101 \\ + \text{Input: } B \rightarrow 111 \\ \hline \text{Output: } S \rightarrow 100 \end{array}$$



Full Adder

1. Fill in truth table
2. Find the equations

3. Draw the schematic

1. Count the transistors in your design

$$S = A \oplus B \oplus C$$

A	B	C _i	C _o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

BC _i		00	01	11	10
A	0			1	
1					1

Hint: Maybe a K-Map would help for C_o



Full Adder


A	B	C _i	C _o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_i$$


A	BC _i			
	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$C_o = AC_i + AB + BC_i$$

Recall: 3-input XOR

 

logically
equivalent
circuits

 

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$\equiv S$

For any number of inputs, the output is 1 when an odd number of inputs is 1

Transistor Count


Gate	# of Transistors
NOT	2
n-input AND	$2n + 2$
n-input OR	$2n + 2$
n-input NAND	$2n$
n-input NOR	$2n$
2-input XOR	12
3-input XOR	28
2-input XNOR	12
3-input XNOR	28

Full Adder



$$S = A \oplus B \oplus C_i$$
 
$$C_o = \underbrace{AC_i}_1 + \underbrace{AB}_2 + \underbrace{BC_i}_3$$




Full Adder: transistor minimization



$$S = A \oplus B \oplus C_i$$

$$C_o = AC_i + AB + BC_i$$

 


Full Adder: transistor minimization



$$S = A \oplus B \oplus C_i$$

$$C_o = AC_i + AB + BC_i$$

 

Transistor count = 42



Full Adder: Alternate implementation

A	B	C _i	C _o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C$$

$$C_o =$$



Full Adder: Alternate Implementation

A	B	C _i	C _o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C$$

Canonical SOP

$$C_o = \bar{A}BC_i + A\bar{B}C_i + AB\bar{C}_i + ABC_i$$

$$C_o = \bar{A}BC_i + A\bar{B}C_i + AB(\bar{C}_i + C_i)$$

$$C_o = \bar{A}BC_i + A\bar{B}C_i + AB$$

$$C_o = C_i(\bar{A}B + A\bar{B}) + AB$$


$$C_o = C_i(A \oplus B) + AB$$



Full Adder: Alternate Implementation

$$S = A \oplus B \oplus C_i$$

$$C_o = C_i(A \oplus B) + AB$$

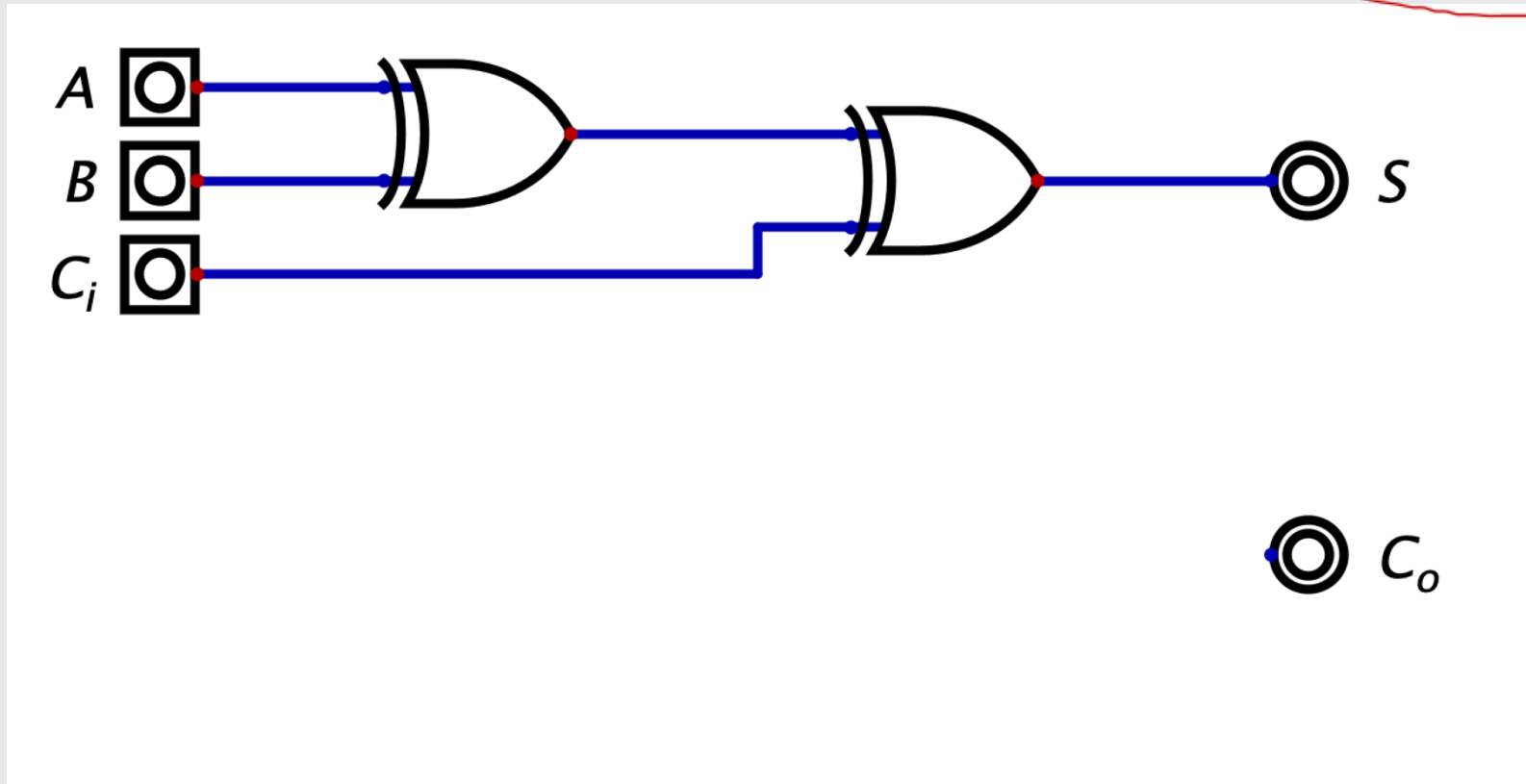




Full Adder: Alternate Implementation

$$S = A \oplus B \oplus C_i$$

$$C_o = C_i(A \oplus B) + AB$$

 




Full Adder: Reducing Transistor Count


$$S = A \oplus B \oplus C_i$$

$$C_o = C_i(A \oplus B) + AB$$

 


Transistor Count: 36

Full Adder Abstraction

 


4-bit Adder

 

4-bit Adder


- How would you use 4 full-adders to add together A and B?

 
$$\begin{array}{cccc} C_{o,3} & C_{o,2} & C_{o,1} & C_{o,0} \\ + & A_3 & A_2 & A_1 & A_0 \\ & B_3 & B_2 & B_1 & B_0 \\ \hline S_3 & S_2 & S_1 & S_0 \end{array}$$



4-bit Adder
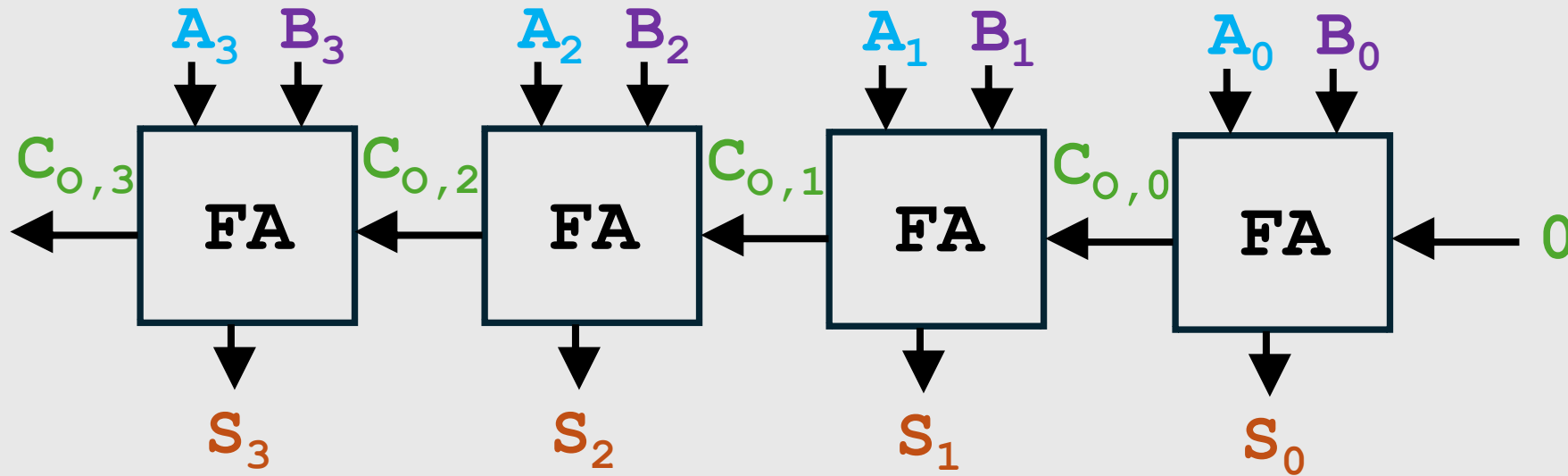
$$\begin{array}{rcccc} C_{0,3} & C_{0,2} & C_{0,1} & C_{0,0} \\ + & A_3 & A_2 & A_1 & A_0 \\ & B_3 & B_2 & B_1 & B_0 \\ \hline S_3 & S_2 & S_1 & S_0 \end{array}$$



 

ADDER-SUBTRACTOR CIRCUIT

Recall: Two's Complement

Ex: Represent -15 in two's complement with 7 bits

- To represent a negative number, take the positive representation of the number, flip the bits, and add 1

Unsigned: 0b 000 1111

Flip bits: 0b 111 0000

Add one: 0b 111 0001



15

Recall Two's Complement Subtraction

$$\begin{array}{r} -10 \\ - \quad 4 \\ \hline -14 \end{array}$$

$$\begin{array}{r} 10110_2 \\ - \quad 00100_2 \\ \hline \end{array}$$

$$A - B == A + (-B)$$



Equivalent
Operations

$$\begin{array}{r} -10 \\ + \quad -4 \\ \hline -14 \end{array}$$

$$\begin{array}{r} 10110_2 \\ + \quad 11100_2 \\ \hline 10010_2 \end{array}$$

Subtraction

- Instead of building a separate circuit for subtraction, we will modify the ripple carry adder such that it can perform addition and subtraction
- When we want to perform $A - B$
 - We will actually perform $A + \underline{-}B$
 - We need to modify our circuit such that it can negate B

Subtraction

- Let's say that we want to perform the operation A - B where $A = 5$ and $B = 1$.
- We will modify the circuit such that it can flip each bit of B and add 1.

$$\begin{array}{r} 0101_2 \\ - 0001_2 \\ \hline \end{array}$$

$$\begin{array}{r} \rightarrow + 0101_2 \\ + 1110_2 \\ + 1_2 \\ \hline 0100_2 \end{array}$$


Keep A the same

Flip the bits of B

Add 1



Subtractor

 

Subtractor


X inverter . . .

A_3 B_3

A_2 B_2


A_1 B_1

A_0 B_0

 

How would you wire up this circuit to have it correctly perform subtraction?

Subtractor

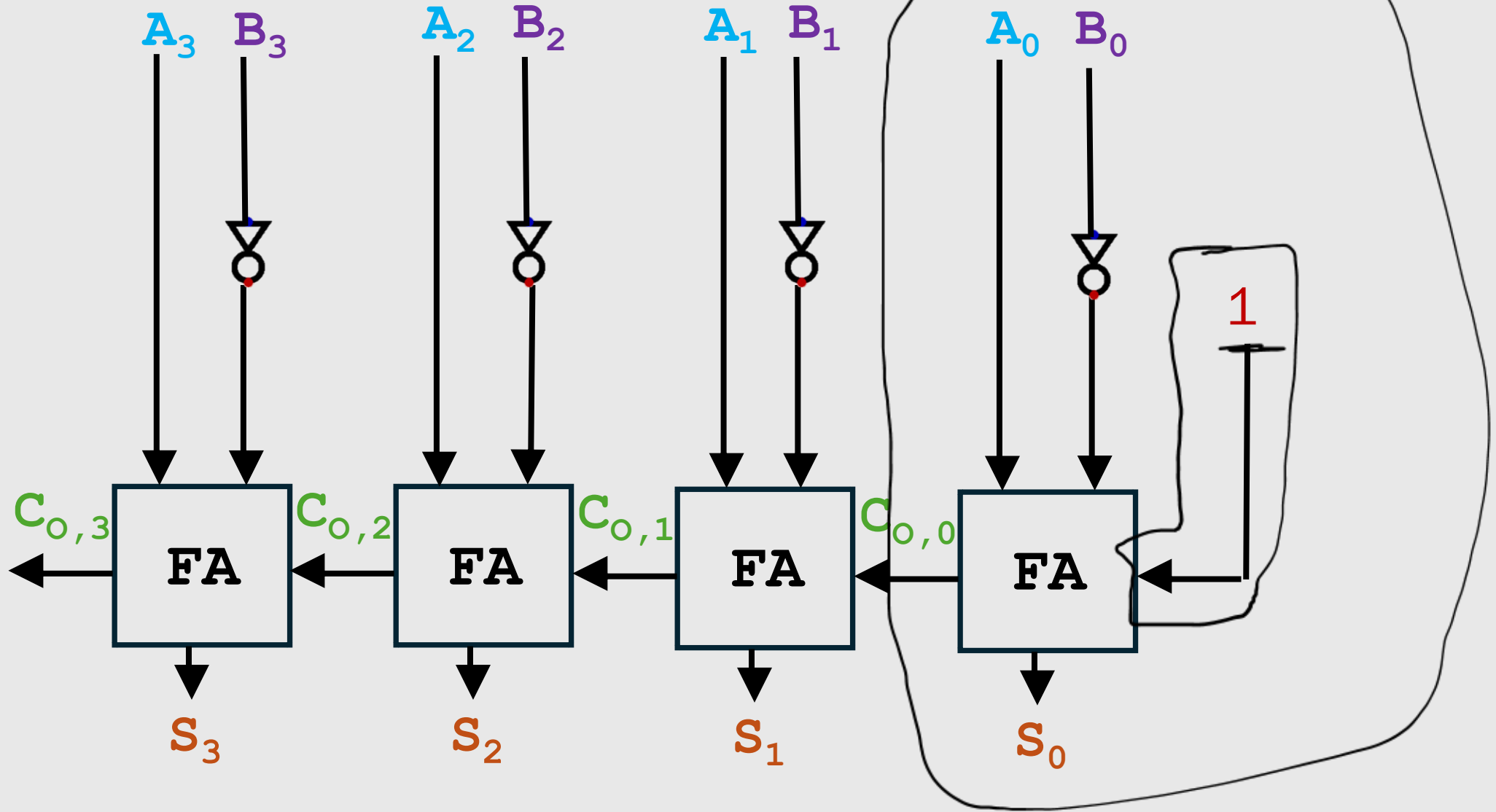


Adder/subtractor

A_3 B_3

A_2 B_2

A_1 B_1


A_0 B_0

 

K If $K == 0$, $A + B$
If $K == 1$, $A - B$

MUX

Adder/Subtractor Implementation 1

 

XOR

$$N \oplus 1 = \bar{N}$$


$$N \oplus 0 = N$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

If we XOR B_i with K

- When $K = 0$, $B_i \oplus K = B_i$
- When $K = 1$, $B_i \oplus K = \bar{B}_i$

Adder/Subtractor Implementation 2

 



SHIFTER CIRCUITS

Reminder: Types of Shifts

■ $A \ll B$

- logical shift left
- Fill right side with 0s

✓ 1011 ←
 10110 larger

■ $A \ggg B$

- arithmetic shift right
- Fill left side with the sign bit

→ 1011
1101 smaller ✓

■ $A \gg B$

- logical shift right
- Fill left side with 0s

1011
0101


Left Shifting

- Let's say my input, A, is a 4-bit number: 0b1101

Shift Amount	Result
0	
1	
2	
3	
4	
5	
6	
7	
8	

Left Shifting

- Let's say my input, A, is a 4-bit number: 0b1101

 Shift Amount	Result
 0	0b1101
1	0b1010
2	0b0100
3	0b1000
4	0b0000
5	0b0000
6	0b0000
7	0b0000
8	0b0000

Shift Amount

- Let's say my input, A, is a 4-bit number: 0b1101

Shift Amount	Result
0	0b1101
1	0b1010
2	0b0100
3	0b1000
4	0b0000
5	0b0000
6	0b0000
7	0b0000
8	0b0000

If we shift A by more than 3 bits, the result will always be 0. We want to make our shifter circuit as simple as possible, so we will only support a shift amount range of 0-3.

Shift Amount

Shift Amount	Result
0	0b1101
1	0b1010
2	0b0100
3	0b1000
4	0b0000
5	0b0000
6	0b0000
7	0b0000
8	0b0000

We need to be able to shift by up to 3 bits.

To represent the numbers 0-3, we need 2 bits.

Shift Amount

Shift Amount	Result
0	0b10101
1	0b01010
2	0b10100
3	0b01000
4	0b10000
5	0b00000
6	0b00000
7	0b00000
8	0b00000


We need to be able to shift by up to 4 bits.

To represent the numbers 0-4, we need 3 bits.

For an n-bit number, need
 $\text{ceil}(\log_2 n)$ bits for the shift
amount

Left Shift

 - Design a circuit that can perform a left shift operation on a 4-bit number.



Left Shift


Output Value

Shift
Amount

	Y_3	Y_2	Y_1	Y_0
0	A_3	A_2	A_1	A_0
1	A_2	A_1	A_0	0
2	A_1	A_0	0	0
3	A_0	0	0	0

Left Shift

 
- Design a circuit that can perform a variable left shift on a 4-bit number.
 - *shamt* is a 2-bit input
 - *you may use ground for 0*



Left Shift

- Design a circuit that can perform a variable left shift on a 4-bit number.

1011

 



R-TYPE & I-TYPE INSTRUCTIONS

What is the course about?

High-level programming
languages

```
// High-level (C)
int add3(int a, int b)
{
    return a + b + 3;
}
```

Easy for humans to
read/write

Assembly
Low-level languages

```
# Matching RISC-V assembly
# a0 = a, a1 = b; return in a0

add    a0, a0, a1    # a0 = a0 + a1
addi   a0, a0, 3     # a0 = a0 + 3
ret                               # return
```

Human readable

Machine code

```
00000000 01011 01010
000 01010 0110011

0000000000011 01010
000 01010 0010011

0000000000000 00001
000 00000 1100111
```

Machine-readable

Square in different assembly languages

MIPS

x86

ARM

RISC-V

square(int):

```
    addi    sp, sp, -16      # make stack frame
    sw      ra, 12(sp)      # save return address
    sw      s0, 8(sp)       # save frame pointer
    addi    s0, sp, 16      # set up new frame pointer
    sw      a0, -4(s0)      # save argument x

    lw      t0, -4(s0)      # t0 = x
    mul     t0, t0, t0      # t0 = x * x
    mv      a0, t0          # move result to a0

    lw      ra, 12(sp)      # restore return address
    lw      s0, 8(sp)       # restore frame pointer
    addi    sp, sp, 16      # pop stack frame
    jr      ra              # return
```

square(int):

```
    push    {r7}
    sub     sp, sp, #12
    add     r7, sp, #0
    str     r0, [r7, #4]
    ldr     r3, [r7, #4]
    mul     r3, r3, r3
    mov     r0, r3
    adds    r7, r7, #12
    mov     sp, r7
    ldr     r7, [sp], #4
    bx      lr
```

Square in different assembly languages

MIPS

```
1 square(int):
2     addiu    $sp,$sp,-8
3     sw       $fp,4($sp)
4     move     $fp,$sp
5     sw       $4,8($fp)
6     lw       $2,8($fp)
7     nop
8     mult     $2,$2
9     mflo     $2
10    move     $sp,$fp
11    lw       $fp,4($sp)
12    addiu    $sp,$sp,8
13    jr       $31
14    nop
```

x86

```
1 square(int):
2     push     rbp
3     mov      rbp, rsp
4     mov      DWORD PTR [rbp-4], edi
5     mov      eax, DWORD PTR [rbp-4]
6     imul     eax, eax
7     pop      rbp
8     ret
```

ARM


```
1 square(int):
2     push     {r7}
3     sub      sp, sp, #12
4     add      r7, sp, #0
5     str      r0, [r7, #4]
6     ldr      r3, [r7, #4]
7     mul      r3, r3, r3
8     mov      r0, r3
9     adds     r7, r7, #12
10    mov      sp, r7
11    ldr      r7, [sp], #4
12    bx       lr
```


Instruction Set Architecture (ISA)

- A set of rules that define the interface between the hardware and software.

Anatomy of an Instruction

 - Computers execute a set of primitive operations called **instructions**
- Instructions specify an **operation** and its **operands** (arguments of the operation)
- Types of operands: **destination**, **source**, and **immediate**



Instruction Set Architecture (ISA)

Encoding of instructions raises some interesting choices...

- Trade Offs: performance, compactness, programmability
- Uniformity. Should different instructions
 - *Be the same size (number of bits)?*
 - *Take the same amount of time to execute?*
 - *Trend: Uniformity. Affords simplicity, speed, pipelining.*
- Complexity. How many different instructions? What level operations?
 - *Level of support for particular software operations: array indexing, procedure calls, “polynomial evaluate”, etc*
 - **“Reduced Instruction Set Computer”**
(RISC) philosophy: simple instructions, optimized for speed
- Mix of Engineering & Art...

RISC-V 32

RISC-V Register Details

- There are 32 named registers [x0, x1, x31]
- x0 is special. It always contains "0" and, when used as a destination, the result is ignored
- The operands of most instructions are registers
- This means to operate on a variables in memory you must:
 - *Load the value/values from memory into a register*
 - *Perform the instruction*
 - *Store the result back into memory*
- Going to and from memory can be expensive (4x to 20x slower than operating on a register)
- Net effect: Keep variables in registers as much as possible!
- By convention, most registers are dedicated to specific tasks

**A.K.A a
"Load-Store
Architecture"**

Basic RISC-V Instructions


ADD, SUB → R-type

ADDI → I-type


- Instructions include various “fields” that encode combinations of OPCODES and arguments
- special fields enable extended functions
- several 5-bit OPERAND fields, for specifying the sources and destination of the operation, usually one of the 32 registers
- Embedded constants (“immediate” values) of various sizes,

The basic data-processing instruction formats:

R-type:

 

I-type:

 

Reading Binary

0b 1110 0001 0011 1011

Reading Binary

0b 1110 0001 0011 1011

Bit 15

Most Significant Bit (msb)

Bit 0

Least Significant Bit (lsb)

$r1 = r2 + r3;$ add x1, x3, x2

funct7								source register 2								source register 1								funct3								destination register								opcode															
31								25 24								20 19								15 14								12 11								7 6								0							

$r1 = r2 + r3$; add ~~x3, x2, x1~~

add x1, x3, x2

funct7	source register 2	source register 1	funct3	destination register	opcode
0000000	00011	00010	000	00001	0110011

31 25 24 3 20 19 2 15 14 12 11 7 6 0

0000000000011000100000000010110011

3 2 1

Opcode is always 0110011 for integer R-type ALU instructions
funct3 is always the primary operation code group (e.g. 000 = add/sub. 100 = xor, 111 = and)
funct7 is used to further specify the operation (e.g. distinguishes add vs. sub. srl vs. sra)