


COMP311 In-Class Practice 10/26/26 Name: _____

Question 1: Waveform Practice Fill in the waveform diagram, for the intermediate points and the result Y.

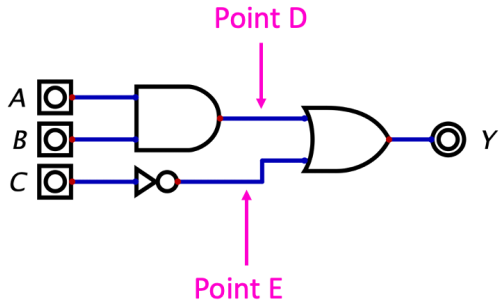


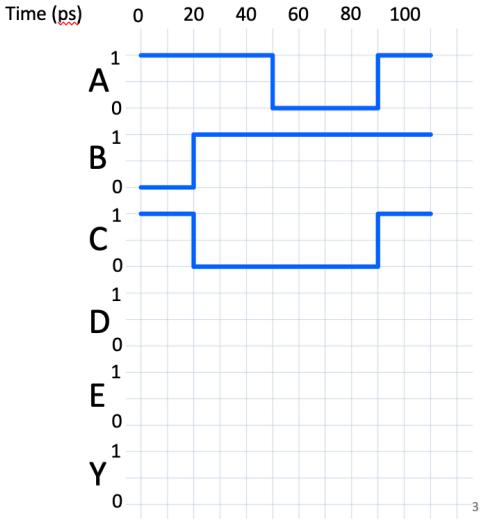

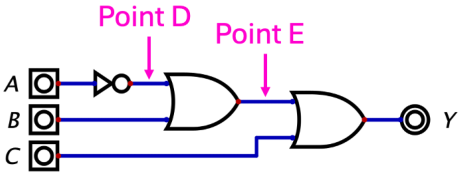Question 2: Propagation Delay Practice Fill in the waveform diagram, for the intermediate points and the result Y.



Gate	t_{pd} (ps)
NOT	10
OR	30

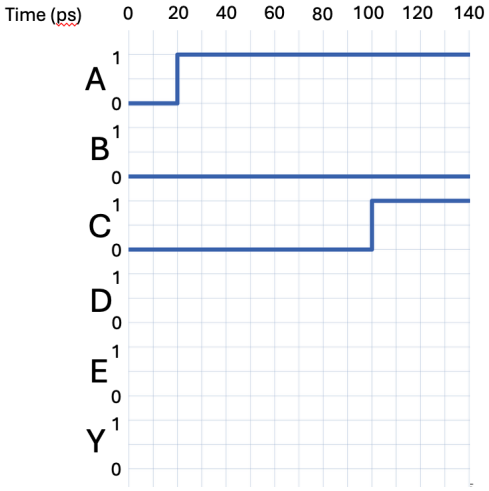

Question 3: Flip Flop Practice Fill in the waveform diagram for the D Flip-Flop Q. Assume Q starts at 0.

